

# Electronic Power Conversion

Review of Basic Electrical and Magnetic Circuit  
Concepts

# 3. Review of Basic Electrical and Magnetic Circuit Concepts

- Notation
- Electric circuits
  - Steady state – sinusoidal, non-sinusoidal
  - Power – apparent, real, reactive
  - Power factor, THD, harmonics
- Magnetic circuits
  - Ampere's law, Faraday's law
  - Magnetic reluctance and magnetic circuits
  - Inductor
  - Transformer

# Notation

- Notation:
  - Lowercase – instantaneous value e.g.  $v_o (=v_o(t))$
  - Uppercase – average or rms value e.g.  $V_o$
  - Bold – phasor, vector
- Steady state:
  - State of operation where waveforms repeat with a period  $T$  that is specific for the system.

# Instantaneous, Average Power and RMS current

- Instantaneous power


$$p = vi$$

- Average power

$$P_{av} = \frac{1}{T} \int_0^T p dt = \frac{1}{T} \int_0^T vi dt$$

- Power to resistive load
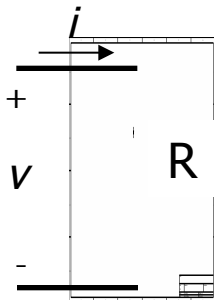
$$P_{av,R} = R \frac{1}{T} \int_0^T i^2 dt \quad \text{or} \quad P_{av,R} = R I^2$$
$$P_{av,R} = \frac{V^2}{R}$$



- I – RMS (Root-mean-square)

$$I = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

- Example


$$v = 10V + 5V \sin(2 \cdot \pi \cdot 10kHz \cdot t)$$

$$V_{av} = 10V$$

$$V_{rms} = 10.607V$$

$$R = 10\Omega$$

$$P_{av} = 11.25W$$

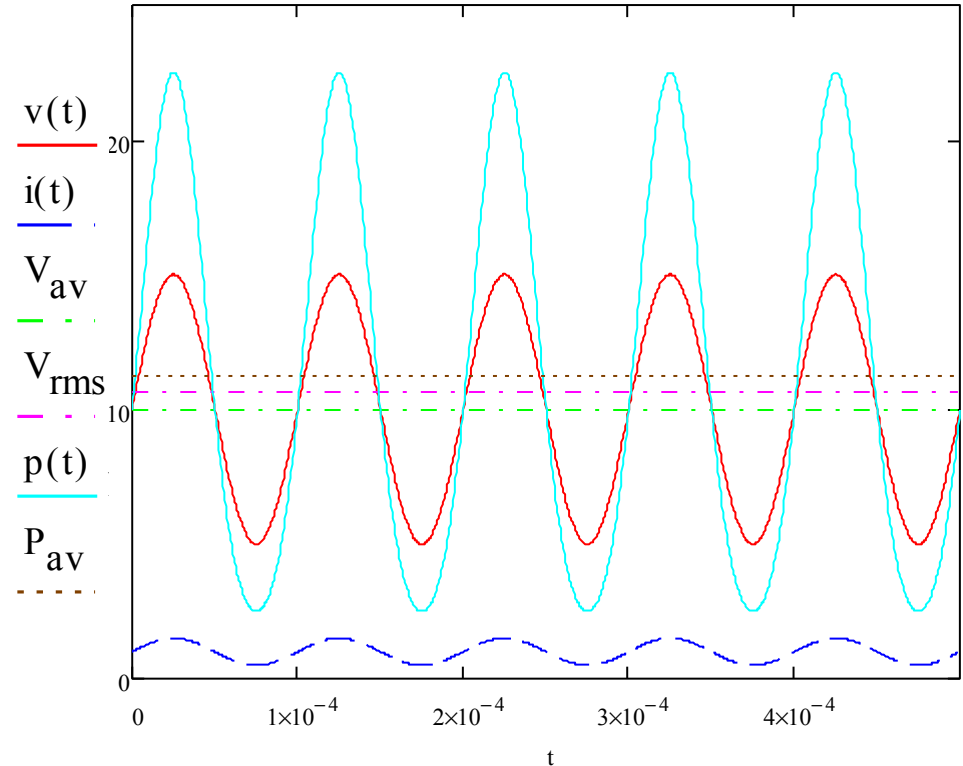

# Steady-State ac Sinusoidal Waveforms

- Resistive/inductive load

$$v(t) = \sqrt{2} V \cos \omega t \quad i(t) = \sqrt{2} I \cos (\omega t - \phi)$$

- Phasor representation

$$\mathbf{V} = V e^{j0} \quad \mathbf{I} = I e^{-j\phi}$$

Complex impedance

$$\mathbf{Z} = R + j\omega L = Z e^{j\phi}$$

$$\mathbf{V} = \mathbf{I} \cdot \mathbf{Z}$$



$$i(t) = i_p(t) + i_q(t)$$

$$i_p(t) = \sqrt{2} I_p \cos \omega t$$

$$= (\sqrt{2} I \cos \phi) \cos \omega t$$

$$i_q(t) = \sqrt{2} I_q \sin \omega t$$
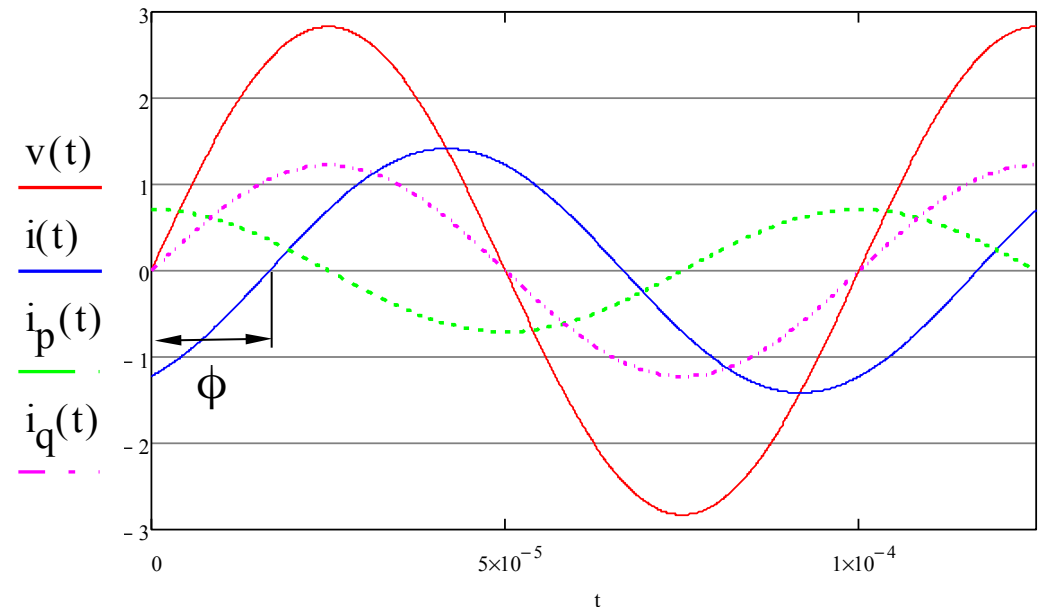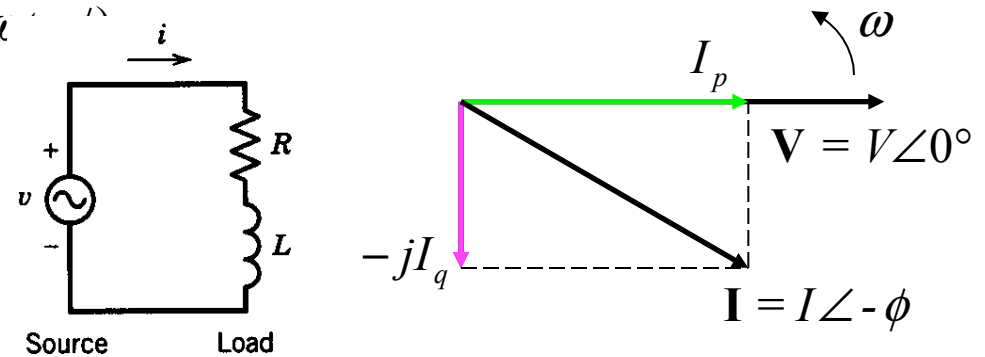
$$= (\sqrt{2} I \sin \phi) \sin \omega t$$



# Complex, Real and Reactive Power

- Complex power [VA]

$$\mathbf{S} = \mathbf{V} \mathbf{I}^* = S e^{j\phi}$$

- Apparent power


$$S = V I$$

- Real average power [W]

$$P = \text{Re}[\mathbf{S}] = VI \cos \phi$$

- Reactive power [VAr]
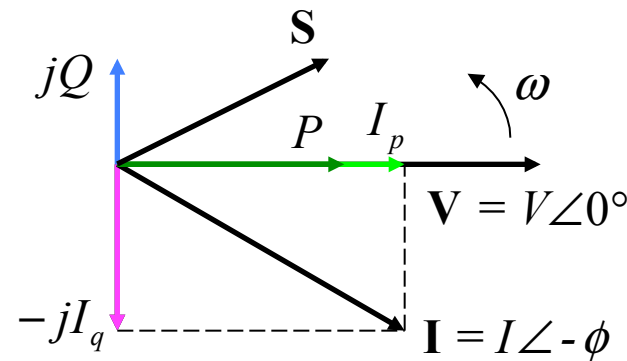
$$Q = \text{Im}[\mathbf{S}] = VI \sin \phi$$



$$\mathbf{S} = P + jQ$$

- Only  $I_p$  is responsible for power transfer from source to load!

# Complex, Real and Reactive Power

- Physical meaning
  - Apparent power  $S$  influences cost and size:
    - Insulation level and magnetic core size depend on  $V$
    - Conductor size depends on  $I$
  - Real power  $P$  – useful work and losses;
  - Reactive power  $Q$  – preferably zero.



# Power Factor (*arbeidsfactor*)

- Power factor
  - How effectively is energy transferred between source and load


$$PF @ \frac{P}{S}$$

- For **sinusoidal** systems:

$$PF = \frac{P}{S} = \frac{V \cdot I \cdot \cos \phi}{V \cdot I} = \cos \phi$$
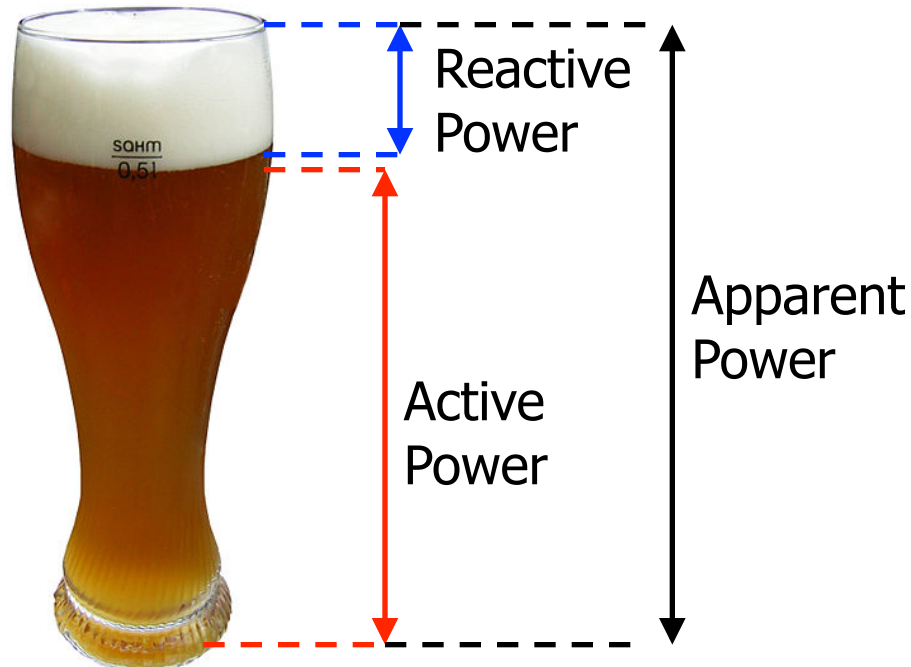
# Power Factor – Beer Mug Analogy

- Glass (over)sized to hold beer *and* foam
- Power wires (over)sized for Watts *and* VARs



Source: Wikimedia Commons CC-BY-SA

# Three Phase Circuits

$$V_{LL} = \sqrt{3}V$$




$$P_{ph} = VI \cos \phi$$

$$S_{ph} = VI$$

$$S_{3ph} = 3VI = \sqrt{3}V_{LL}I$$



$$P_{3ph} = 3VI \cos \phi = \sqrt{3}V_{LL}I \cos \phi$$

$$PF = \cos \phi$$

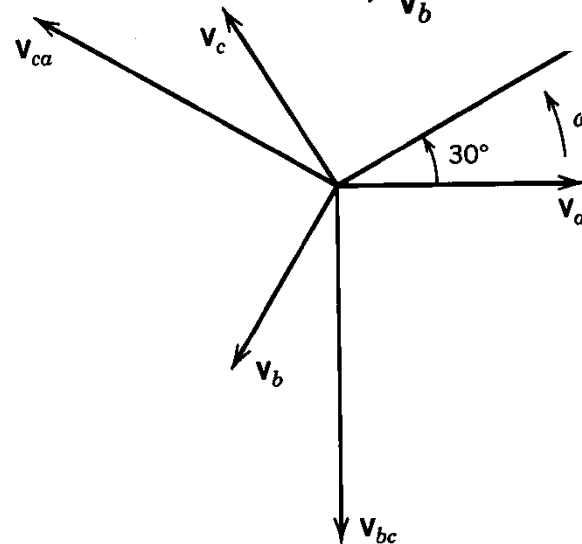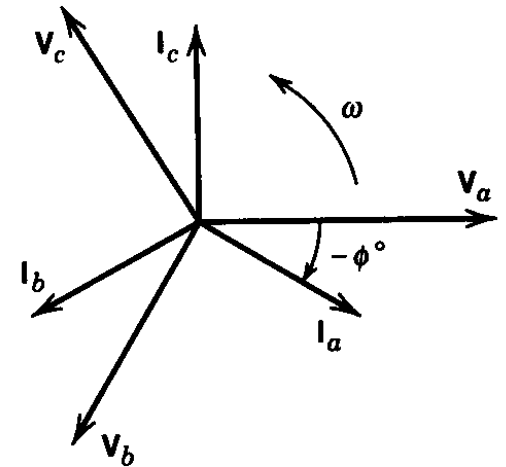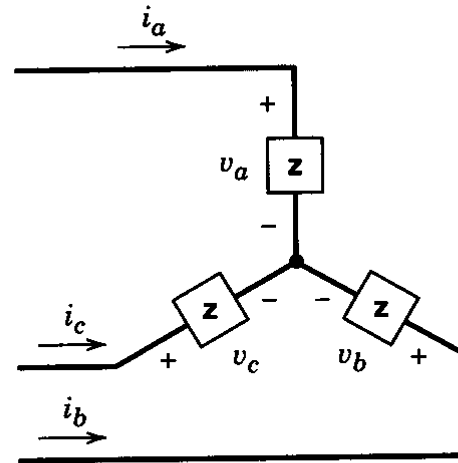
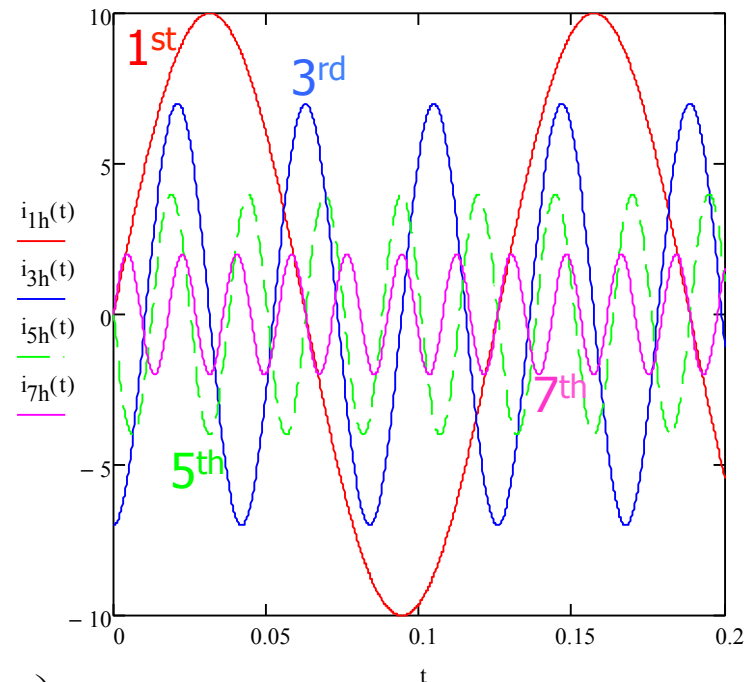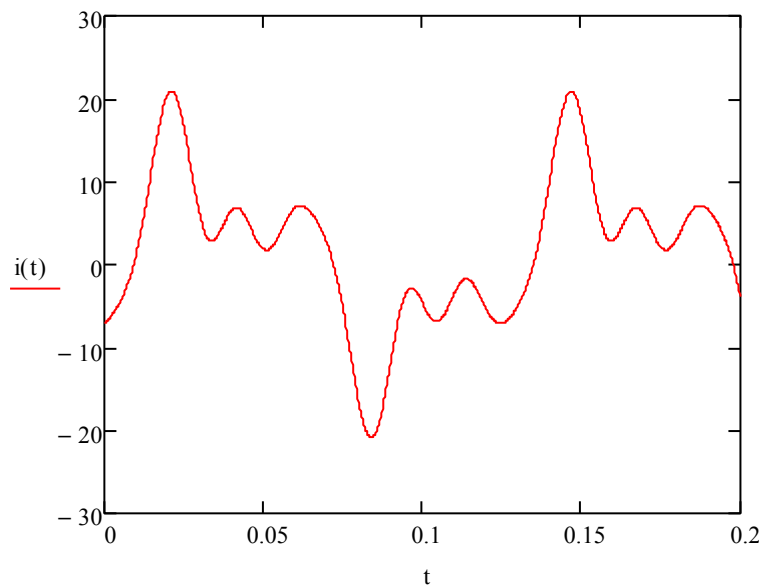
# Steady-State Non-Sinusoidal Waveforms

- Periodic non-sinusoidal waveform
  - Represented as sum of its harmonics



$$i(t) := 10A \sin(\omega_1 \cdot t) + 7 \cdot A \cdot \sin\left(3\omega_1 \cdot t - \frac{\pi}{2}\right) - 4 \cdot A \cdot \sin(5\omega_1 \cdot t) + 2 \cdot A \sin(7\omega_1 \cdot t)$$

# Fourier Analysis of Non-Sinusoidal Waveforms

- Non-sinusoidal periodic waveform  $f(t)$

$$\text{where } f(t) = F_0 + \sum_{h=1}^{\infty} f_h(t) = \frac{1}{2} \cdot a_0 + \sum_{h=1}^{\infty} \{a_h \cdot \cos(h\omega t) + b_h \cdot \sin(h\omega t)\}$$


$$F_0 = \frac{1}{2} a_0 = \frac{1}{2\pi} \int_0^{2\pi} f(t) d(\omega t) = \frac{1}{T} \int_0^T f(t) d(t)$$

$$a_h = \frac{1}{\pi} \int_0^{2\pi} f(t) \cos(h\omega t) d(\omega t) \quad h = 1, \dots, \infty$$

$$b_h = \frac{1}{\pi} \int_0^{2\pi} f(t) \sin(h\omega t) d(\omega t) \quad h = 1, \dots, \infty$$
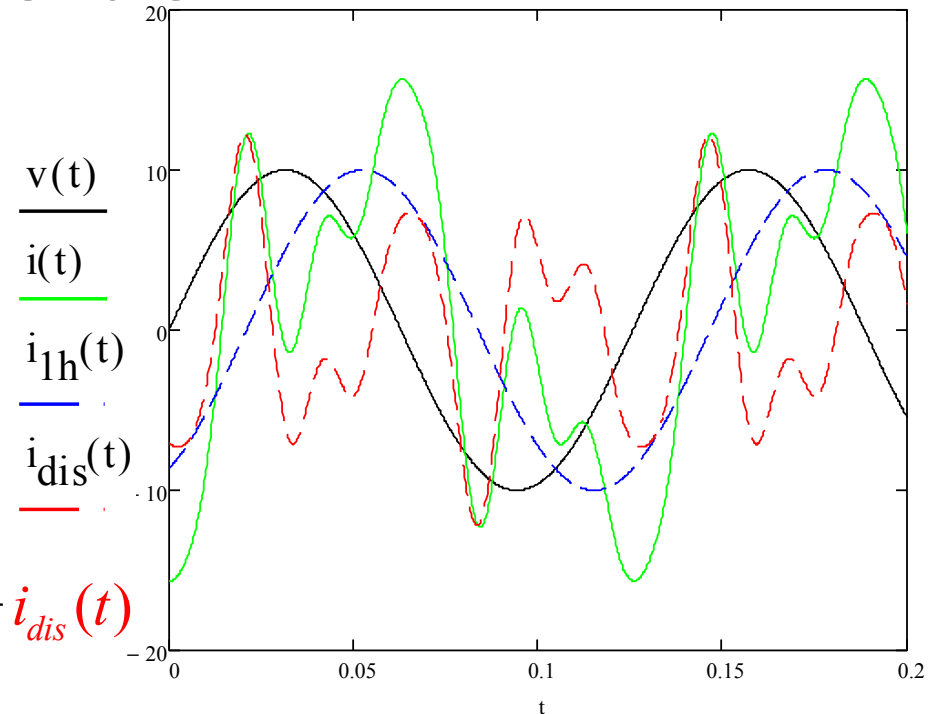
# Line Current Distortion

$$v_s(t) = \sqrt{2} V_s \sin \omega_1 t$$



$$i_s(t) = i_{s1}(t) + \sum_{h=2}^{\infty} i_{sh}(t) = i_{s1}(t) + i_{dis}(t)$$

$$i_s(t) = \sqrt{2} I_{s1} \sin(\omega_1 t - \phi_1) + \sum_{h=2}^{\infty} \sqrt{2} I_{sh} \sin(\omega_h t - \phi_h)$$

current  $i$  = fundamental harmonic  $i_{s1}$  + distortion current  $i_{dis}$

# Total Harmonic Distortion (THD)

- A measure of how much a composite current deviates from an ideal sine wave
- Caused by the way that electronic loads draw current

$$i_s(t) = \sqrt{2} I_{s1} \sin(\omega_1 t - \phi_1) + \sum_{h=2}^{\infty} \sqrt{2} I_{sh} \sin(\omega_h t - \phi_h)$$

$$I_s = \sqrt{\frac{1}{T_1} \int_0^{T_1} i_s^2(t) dt} \quad \text{or} \quad I_s = \sqrt{I_{s1}^2 + \sum_{h=2}^{\infty} I_{sh}^2}$$

$$\text{and:} \quad I_{dis} = \sqrt{I_s^2 - I_{s1}^2} = \sqrt{\sum_{h=2}^{\infty} I_{sh}^2}$$

$$\text{Total harmonic distortion:} \quad THD = \sqrt{\sum_{h=2}^{\infty} \left( \frac{I_{sh}}{I_{s1}} \right)^2}$$

# Harmonics

- Negative effects of harmonics
  - Conductor overheating
  - Capacitors can be affected by heat rise increases due to power loss and reduced life time
  - Distorted voltage waveform
  - Increased losses (e.g. transformers overheating)
  - Fuses and circuit breakers fault operation
- Harmonic standards
  - International Electrotechnical Commission Standard IEC-555
  - IEEE/ANSI Standard 519



# Power Factor

$$PF @ \frac{P}{S}$$

with  $P = \frac{1}{T_1} \int_0^{T_1} p(t) dt = \frac{1}{T_1} \int_0^{T_1} v_s(t) i_s(t) dt$  Real power (*vermogen*)

and  $S = V_s I_s$  Apparent power (*schijnbaar vermogen*)





$$P = \frac{1}{T_1} \int_0^{T_1} \underbrace{\sqrt{2} V_s \sin(\omega_1 t)}_{v_s(t)} \cdot \underbrace{\sum_{h=1}^{\infty} \sqrt{2} I_{sh} \sin(\omega_h t - \phi_h)}_{i_s(t)} dt$$

$$P = \frac{1}{T_1} \int_0^{T_1} \sqrt{2} V_s \sin(\omega_1 t) \cdot \sqrt{2} I_{s1} \sin(\omega_1 t - \phi_1) dt = V_s I_{s1} \cos \phi_1$$

$$PF = \frac{V_s I_1 \cos \phi_1}{V_s I_s} = \frac{I_{s1}}{I_s} \cos \phi_1 \quad \text{DPF}$$
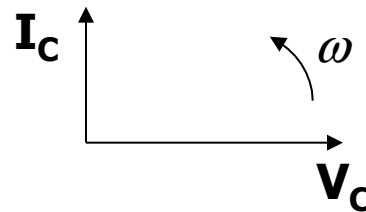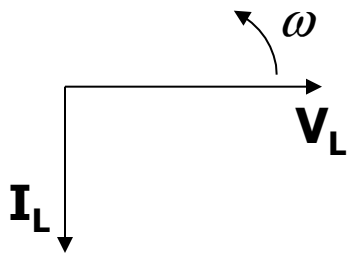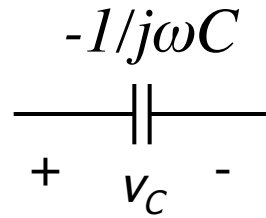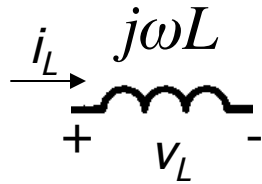
# Inductor and Capacitor Phasor Diagrams

- Phasors are only applicable to sinusoidal steady state waveforms.



# Inductor and Capacitor Response





- Time domain:

$$v_L(t) = L \cdot \frac{di_L}{dt}$$


$$i_C(t) = C \cdot \frac{dv_C}{dt}$$

$$i_L(t) = i_L(t_1) + \frac{1}{L} \int_{t_1}^t v_L(t) dt$$
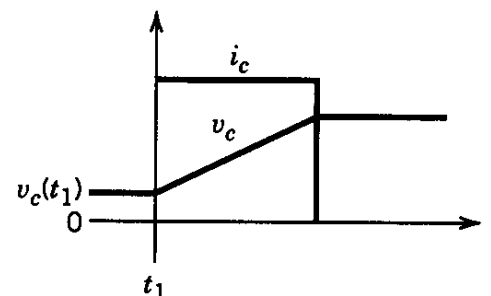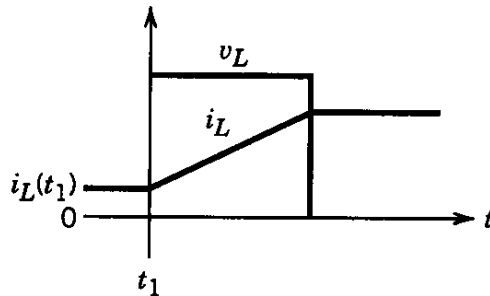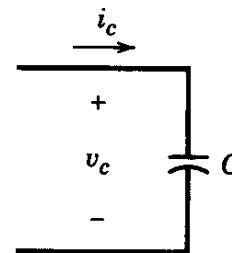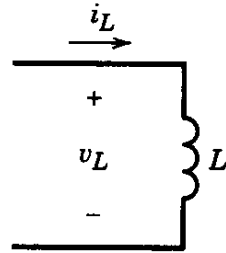
$$v_C(t) = v_C(t_1) + \frac{1}{C} \int_{t_1}^t i_C(t) dt$$



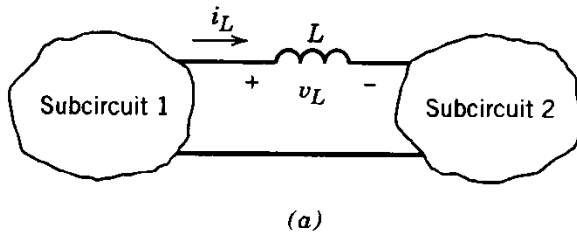
# Inductor in Steady State Volt-second Balance



Steady state implies:

$$v(t + T) = v(t)$$

$$i(t + T) = i(t)$$

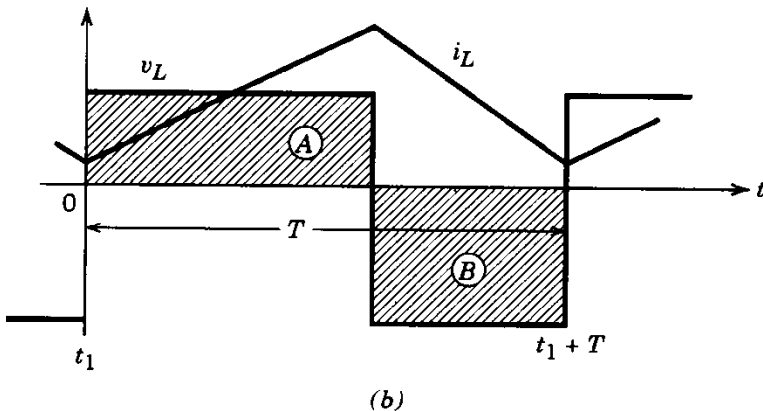


$$i_L(t) = i_L(t_1) + \frac{1}{L} \int_{t_1}^t v_L(t) dt \quad \longrightarrow \quad \int_{t_1}^{t_1+T} v_L(t) dt = 0 \quad \boxed{v_{L,av} = 0}$$

Net change in flux is zero

# Capacitor in Steady State

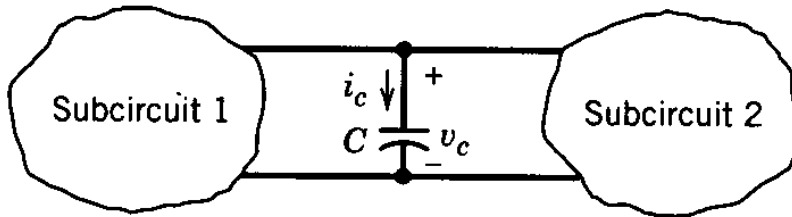
## Amp-second balance

$$v_c(t) = v_c(t_1) + \frac{1}{C} \int_{t_1}^t i_c(t) dt$$



$$\int_{t_1}^{t_1+T} i_c(t) dt = 0 \quad \boxed{i_{C,av} = 0}$$

Net change in charge is zero

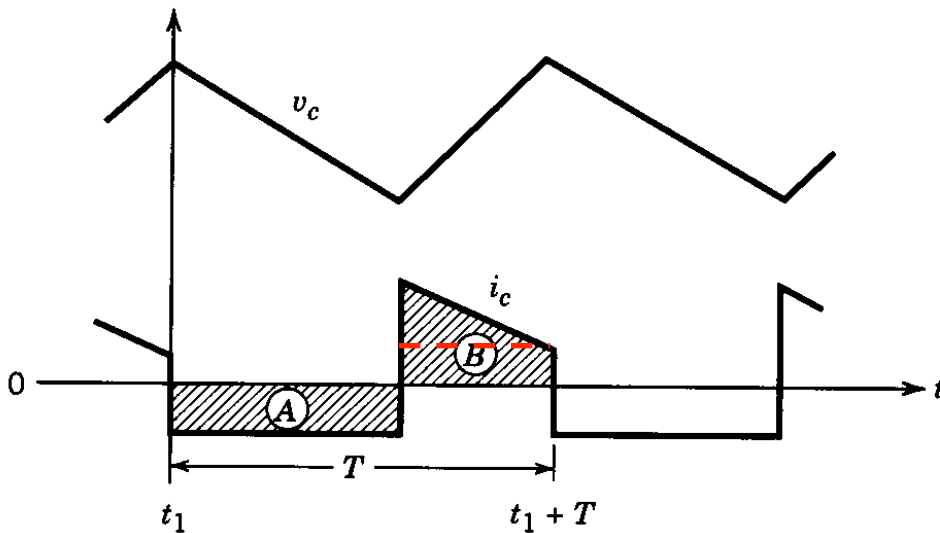


**Fig. 3-9**

**Note:** error in fig 3-9 from textbook  
 $i_c$  in the second interval should be constant,


-----  
 because  $v_c$  has a constant derivative in that interval
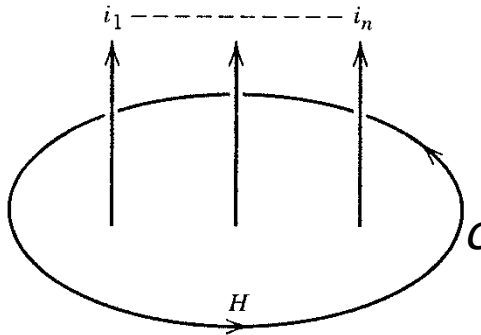
# Basic Magnetics Theory

Ampere's law  
(4<sup>th</sup> Maxwell's equation)




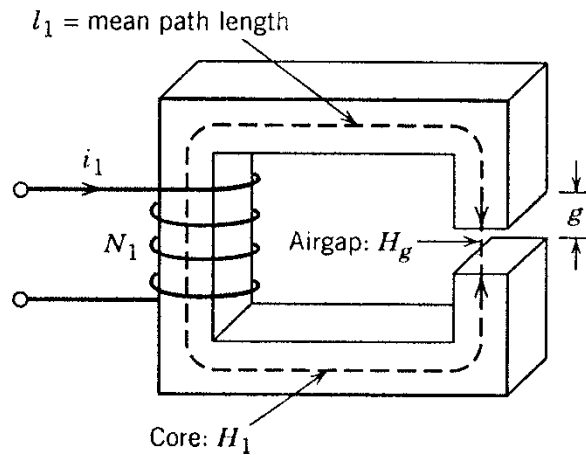
$$\oint_C \mathbf{H} \cdot d\mathbf{l} = \sum i$$



$$\sum_{K \text{ core sections}} H_k l_k = \sum_{M \text{ windings}} N_m I_m$$

$$H_i l + H_g l_g = N_1 i$$

Right-hand rule:

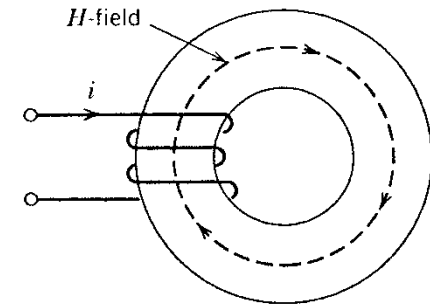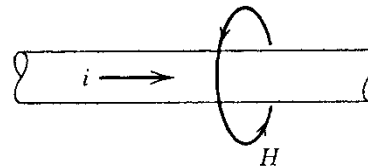


# H-field, B-field and Material Properties

- Relationship between  $\mathbf{B}$  and  $\mathbf{H}$  given by:
  - material properties
  - often approximated by:

$$\mathbf{B} = \mu \mathbf{H}$$


- Continuity of flux

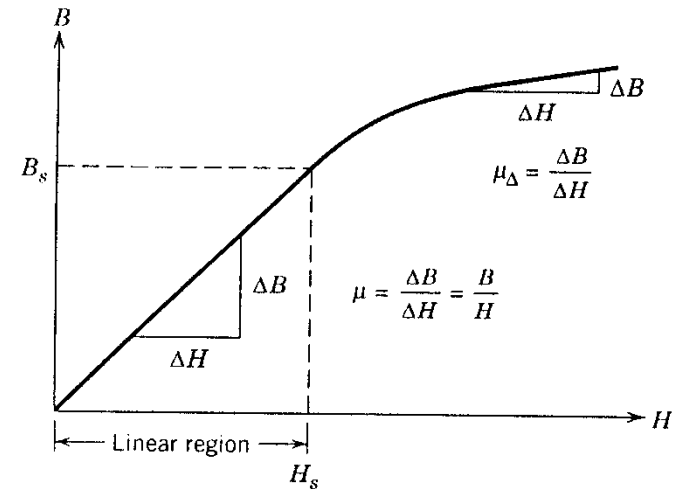

Flux (by def.): 
$$\phi = \iint_A \mathbf{B} \cdot d\mathbf{A}$$

$$\oint_{closedArea} \mathbf{B} \cdot d\mathbf{A} = 0$$

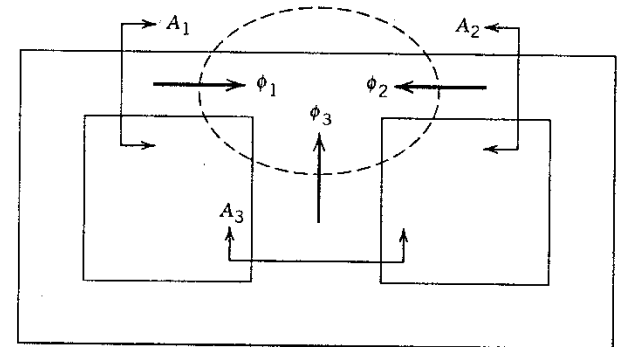Continuity of flux:  
Gauss's law of magnetism  
(2<sup>nd</sup> Maxwell's equation)




# Magnetic Reluctance

Ampere's law:

$$\sum_m N_m I_m = \sum_k H_k l_k = \sum_k (B_k A_k) \frac{l_k}{\mu_k A_k} = \sum_k \phi_k \frac{l_k}{\mu_k A_k} = \phi \sum_k \frac{l_k}{\mu_k A_k} = \phi \cdot \mathfrak{R}_k$$

$\mathbf{B} = \mu \mathbf{H}$

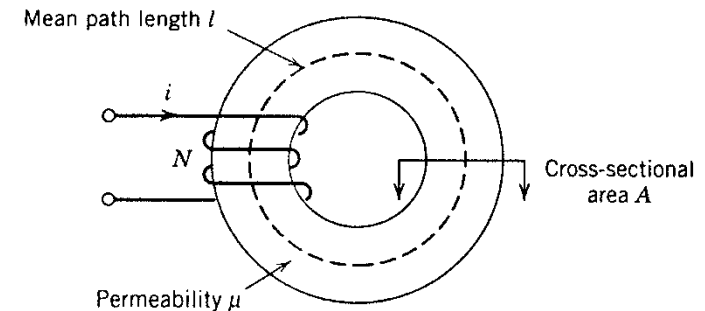Magnetic reluctance:  $\mathfrak{R}_k = \frac{l_k}{\mu_k A_k}$



Magnetic	Electrical
$\mathfrak{R}_k$	$R$
$\phi$	$i$
$Ni$	$v$



# Magnetic Circuit Analysis

Magnetic

Electrical

$$Ni = \phi \cdot \mathfrak{R}_k$$

$$v = i \cdot R$$

Ohm's law:

$$\sum_m N_m I_m = \phi \sum_k \mathfrak{R}_k$$




$$\sum_m v_m = i \sum_k R_k$$

Kirchhoff's voltage law

$$\sum_k \phi_k = 0$$


$$\sum_k i_k = 0$$

Kirchhoff's current law

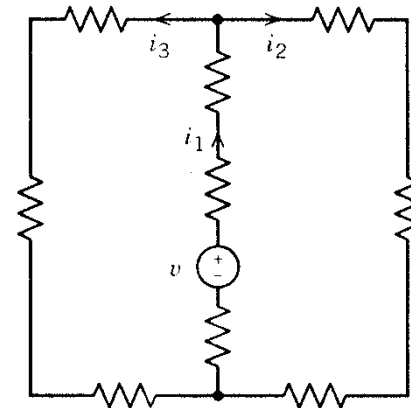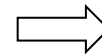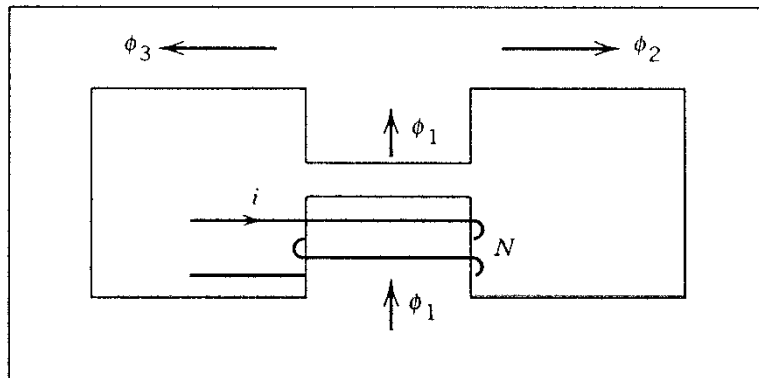

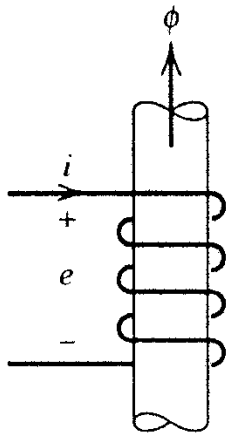
# Faraday's law

$$e = \frac{d\Psi}{dt} = \frac{d(N\phi)}{dt} = NA \frac{dB}{dt}$$



(a)


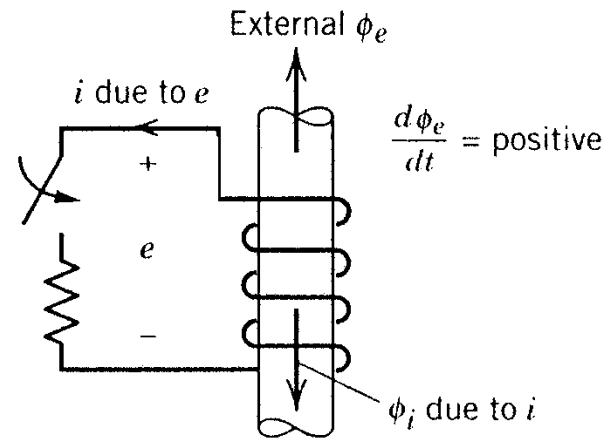


(b)
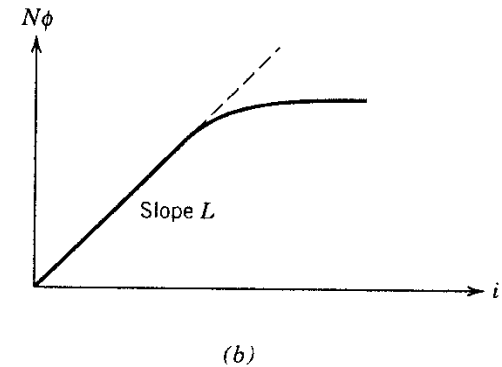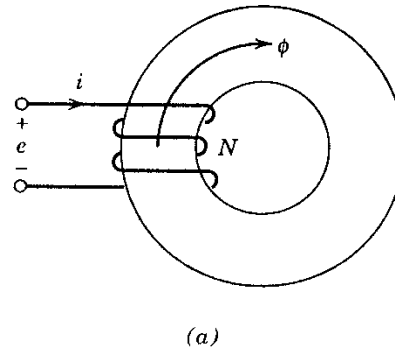
# Inductor

- Coil self-inductance

$$\left. \begin{array}{l} L @ \frac{N\phi}{i} \\ e = \frac{d(N\phi)}{dt} \end{array} \right\} \rightarrow e = L \frac{di}{dt}$$



$$\left. \begin{array}{l} L = \frac{N\phi}{i} \\ \phi \mathfrak{R} = Ni \end{array} \right\} \rightarrow L = \frac{N^2}{\mathfrak{R}} = \frac{\mu N^2 A}{l}$$

$$\mathfrak{R} = \frac{l}{\mu A}$$

# Transformer

- Ideal transformer

*Faraday's law*



$$v_1 = N_1 \cdot \frac{d\phi}{dt} \quad v_2 = N_2 \cdot \frac{d\phi}{dt}$$

$$\frac{v_1}{N_1} = \frac{v_2}{N_2}$$

*Ampere's law*

$$\sum_{i=1,2} N_i i_i = \phi \cdot \mathcal{R} \quad N_1 i_1 - N_2 i_2 = \phi \cdot \mathcal{R}$$

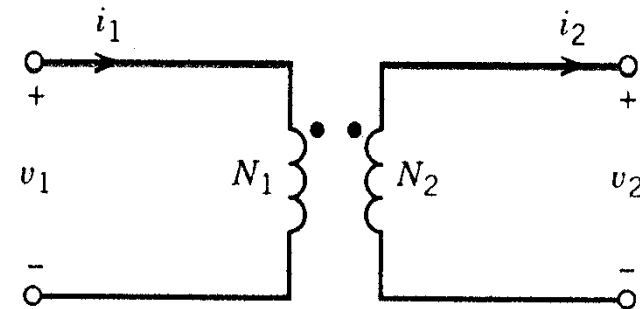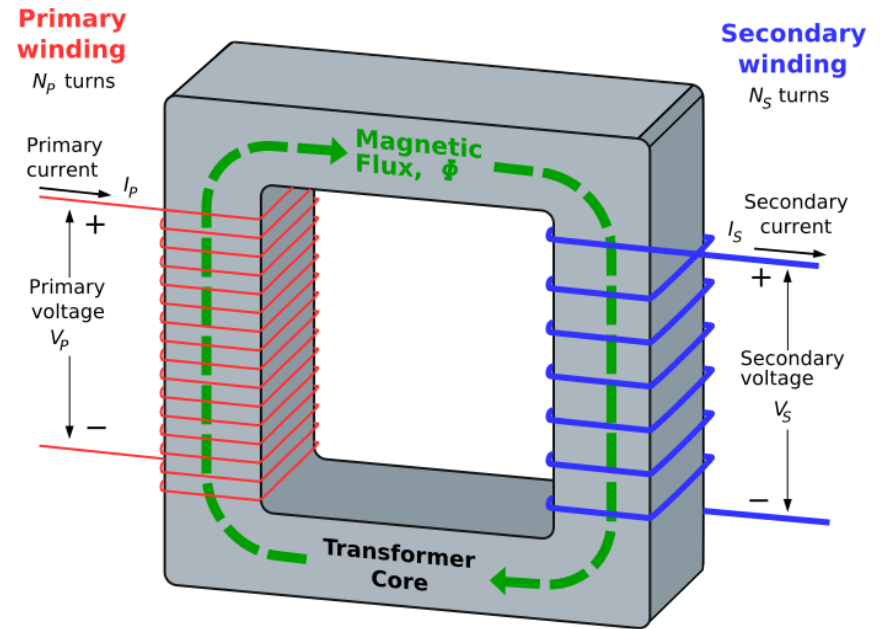Core reluctance  $\mathcal{R} = \frac{l}{\mu A} \approx 0$




$$i_1 N_1 = i_2 N_2$$
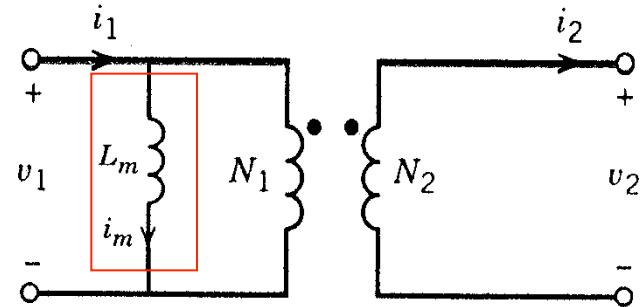
# Transformer

- Magnetising inductance

$$\mathfrak{R} = \frac{l}{\mu A} \neq 0 \quad \text{Non-zero core reluctance}$$



$$\left. \begin{aligned} N_1 i_1 - N_2 i_2 &= \phi \cdot \mathfrak{R} \\ v_1 &= N_1 \cdot \frac{d\phi}{dt} \end{aligned} \right\} v_1 = \frac{N_1}{\mathfrak{R}} \cdot \frac{d}{dt} \left( i_1 - \frac{N_2}{N_1} i_2 \right) = L_m \cdot \frac{d}{dt} i_m$$

$$L_m = \frac{N_1^2}{\mathfrak{R}}$$

$$i_m = i_1 - \frac{N_2}{N_1} i_2$$

# Transformer

- Leakage flux

$\phi_{l1,2}$  – leakage flux


$$\phi_1 = \phi + \phi_{l1}$$

$$\phi_2 = -\phi + \phi_{l2}$$

$R_{1,2}$  – ohmic resistances of the windings

$$v_1 = R_1 i_1 + N_1 \frac{d\phi_1}{dt} = R_1 i_1 + N_1 \left( \frac{d\phi_{l1}}{dt} + \frac{d\phi}{dt} \right)$$
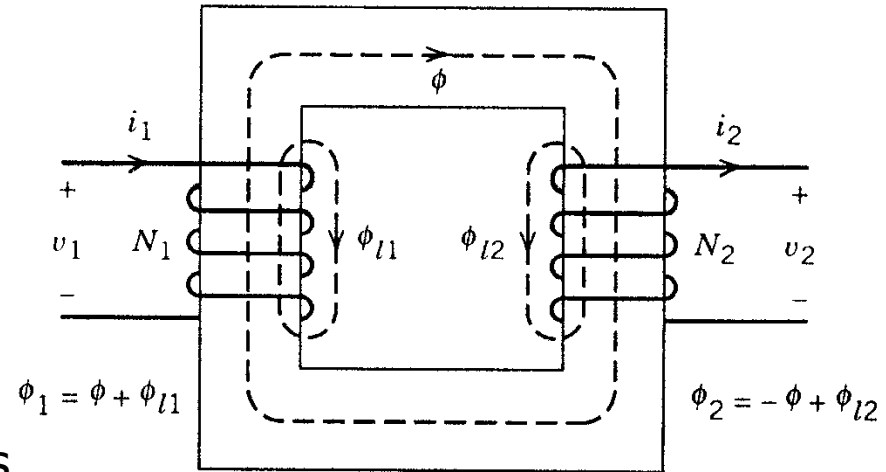
$$v_2 = -R_2 i_2 - N_2 \frac{d\phi_2}{dt} = -R_2 i_2 - N_2 \left( \frac{d\phi_{l2}}{dt} - \frac{d\phi}{dt} \right)$$




# Equivalent Transformer Circuit

$$v_1 = R_1 i_1 + N_1 \frac{d\phi_1}{dt} = R_1 i_1 + N_1 \left( \frac{d\phi_{l1}}{dt} + \frac{d\phi}{dt} \right) \quad L = N \cdot \phi / i \quad v_1 = R_1 i_1 + L_{l1} \frac{di_1}{dt} + L_m \frac{di_m}{dt}$$

$$v_2 = -R_2 i_2 - N_2 \frac{d\phi_2}{dt} = -R_2 i_2 - N_2 \left( \frac{d\phi_{l2}}{dt} - \frac{d\phi}{dt} \right) \quad \Rightarrow \quad v_2 = -R_2 i_2 - L_{l2} \frac{di_2}{dt} + \frac{N_2}{N_1} L_m \frac{di_m}{dt}$$
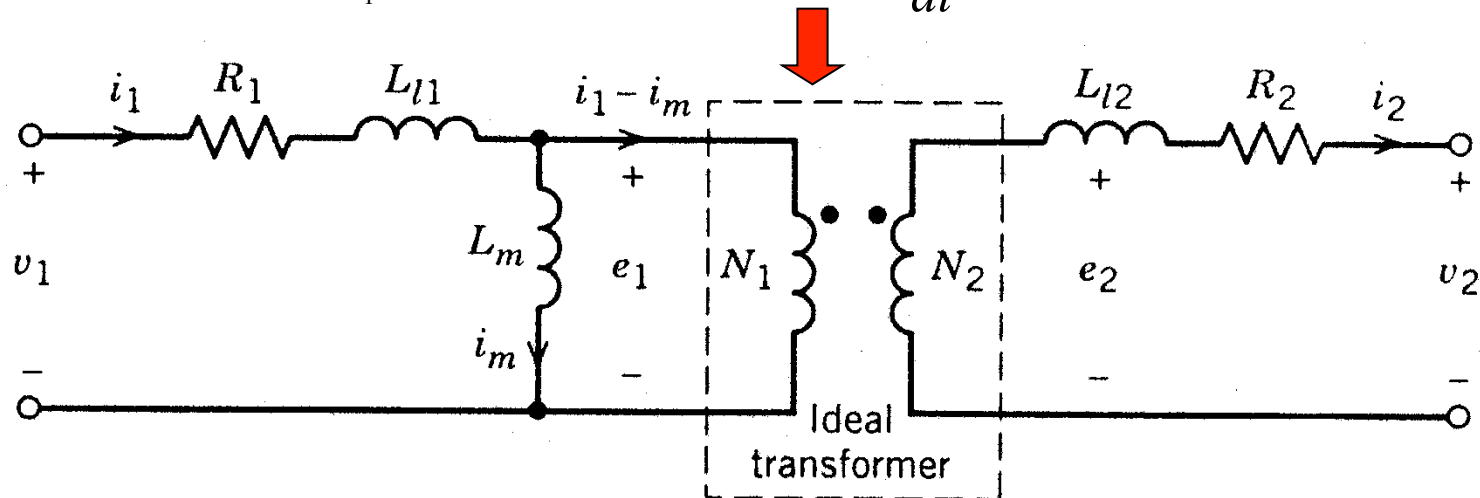
$$\Rightarrow \quad \begin{aligned} v_1 &= R_1 i_1 + L_{l1} \frac{di_1}{dt} + e_1 \\ i_1 &= i_m + \frac{N_2}{N_1} i_2 \\ v_2 &= -R_2 i_2 - L_{l2} \frac{di_2}{dt} + e_2 \end{aligned}$$



# Image credits

- All uncredited diagrams are from the book "Power Electronics: Converters, Applications, and Design" by N. Mohan, T.M. Undeland and W.P. Robbins.
- All other uncredited images are from research done at the EWI faculty.