

# Electronic Power Conversion

## Line-Frequency Diode Rectifiers


# 5. Line-frequency diode rectifiers

- Conversion: line frequency ac  $\rightarrow$  uncontrolled dc (control often in next converter stage)
- Applications: power supplies, ac/dc/ac drives, dc servo drives, ...

☺ Low cost, popular


☹ Large capacitor needed for ripple-free dc voltage  $\rightarrow$  distorted line current

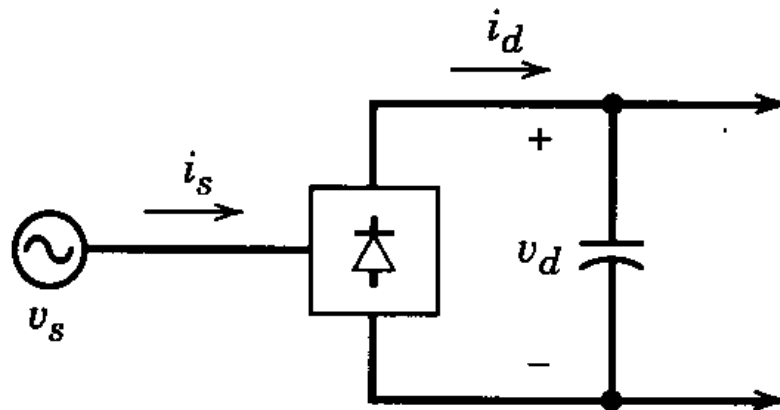☹ Filters required to comply with standards on allowable line-current harmonic



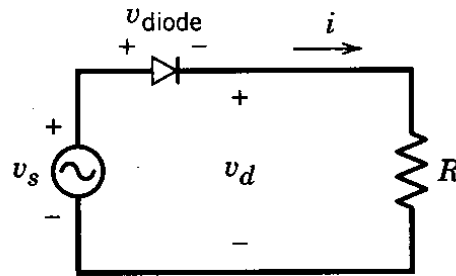
# Single-phase diode rectifiers

- Basic rectifier, single diode, purely resistive load
- Large ripple in  $v_d$




(a)

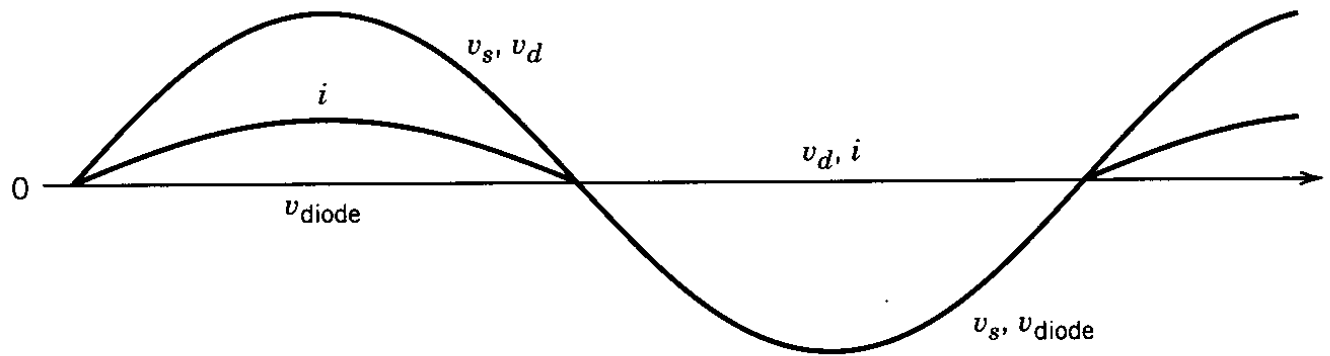

(b)

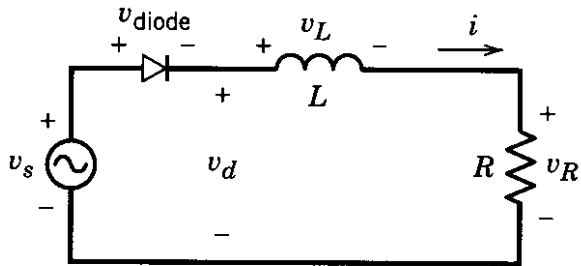
# Single-phase diode rectifiers

- Basic rectifier, single diode, inductive load




$$v_L = L \cdot \frac{di}{dt} = v_s - Ri$$

$$V_{L,av} = \int_0^{t_3} v_L dt = 0$$

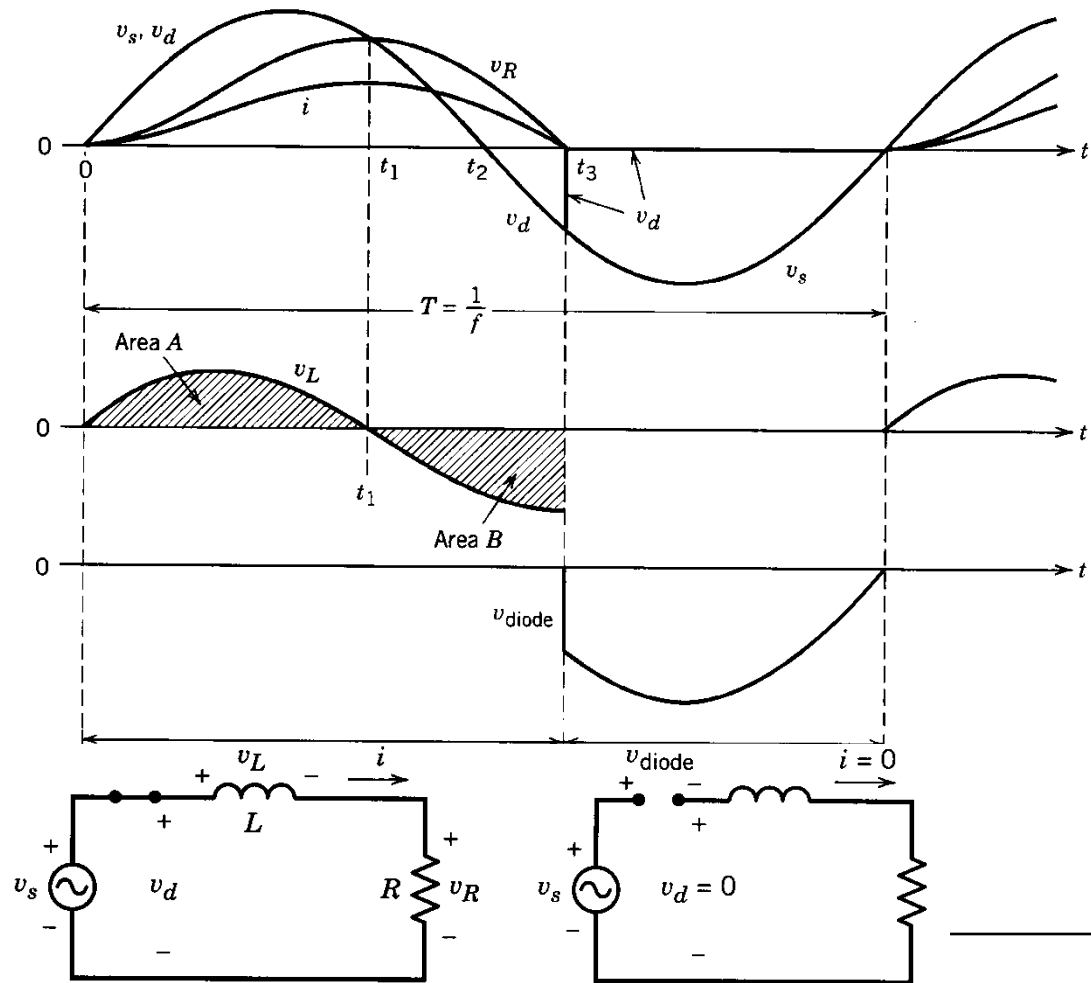

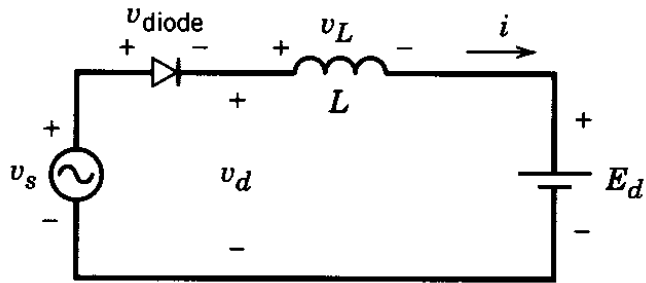
# Single-phase diode rectifiers



- Single diode, load with internal dc voltage, load with large C


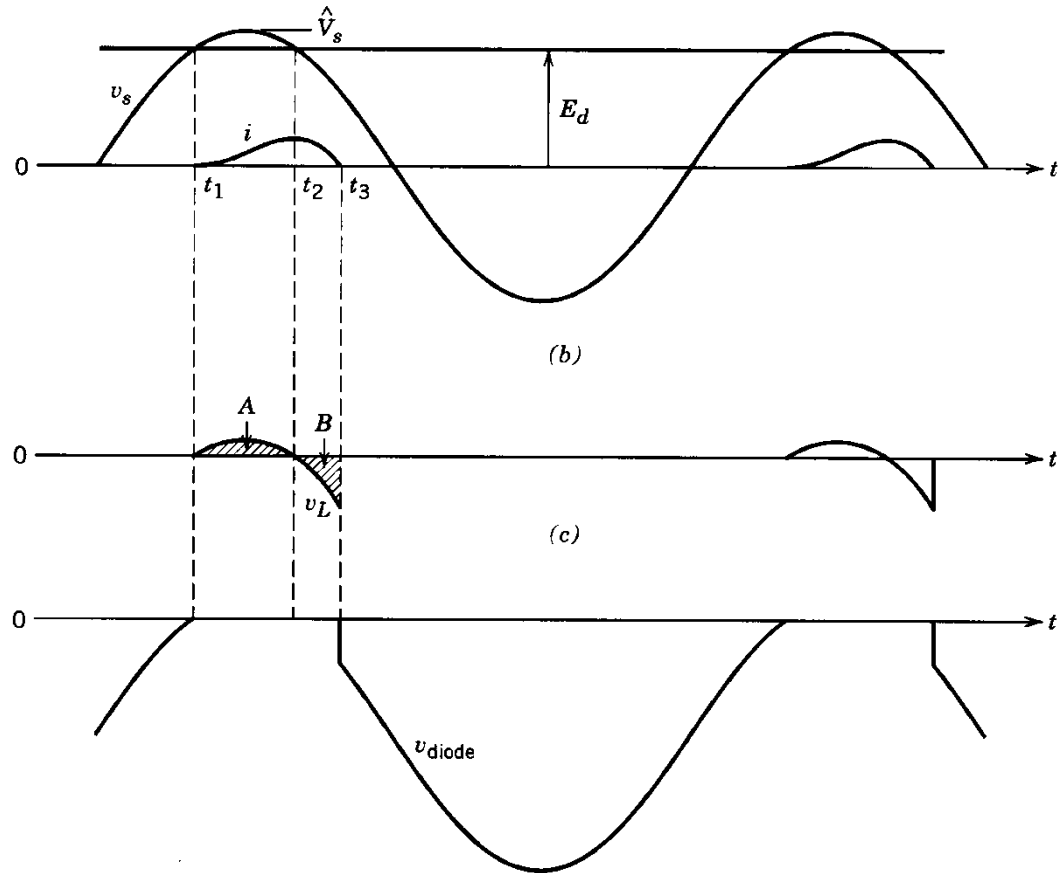
$$V_{L,av} = \int_{t_1}^{t_3} v_L dt = 0$$



# Single-phase bridge rectifier

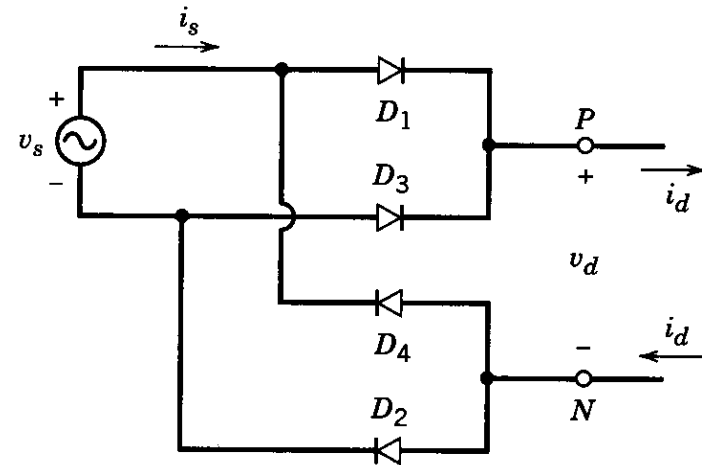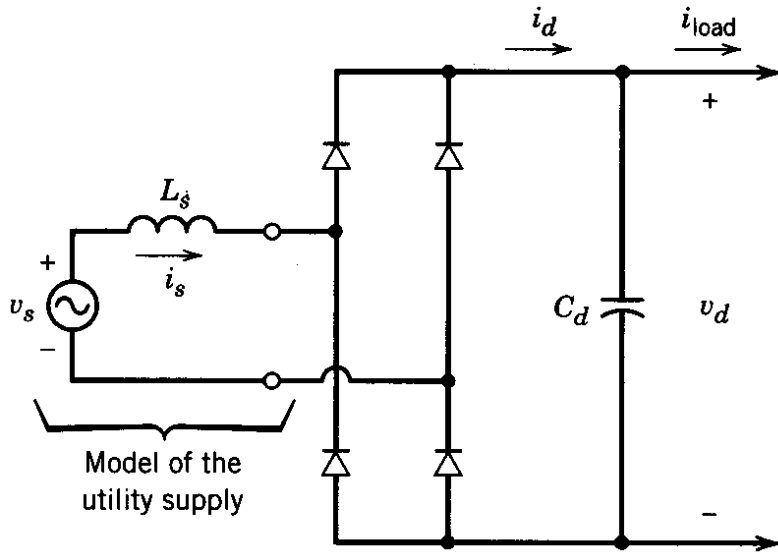

+ rail:



Diode with highest anode potential is conducting)

- rail:

Diode with lowest cathode potential is conducting



# Single-phase bridge rectifier

- Resistive load

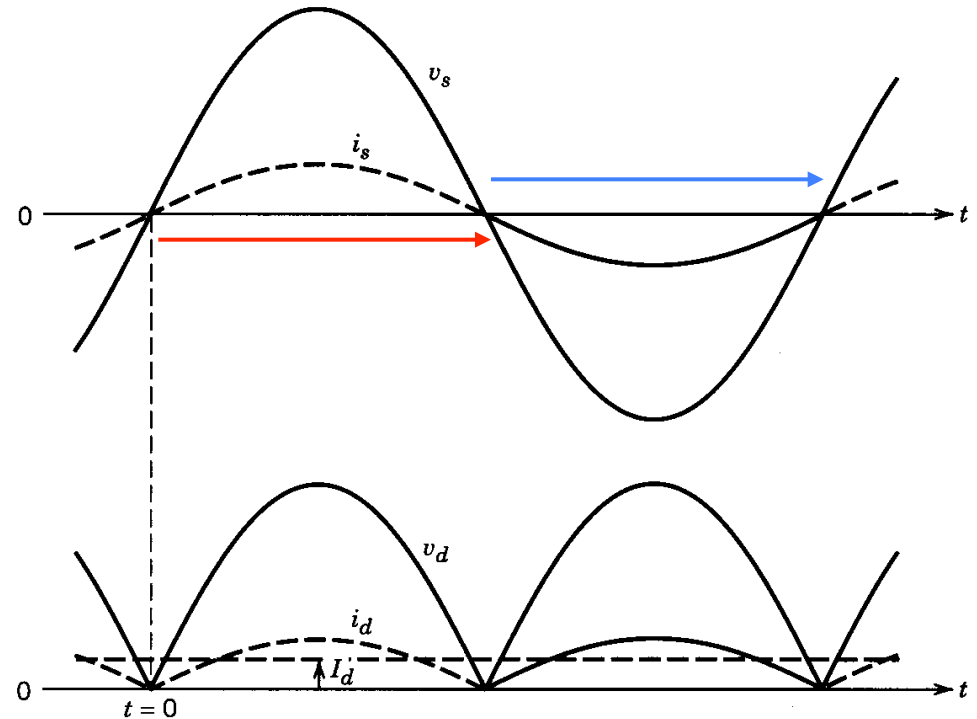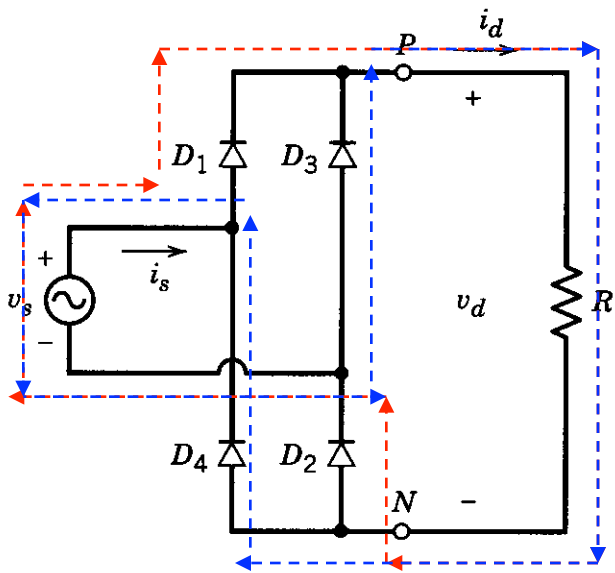

# Single-phase bridge rectifier

- Resistive load

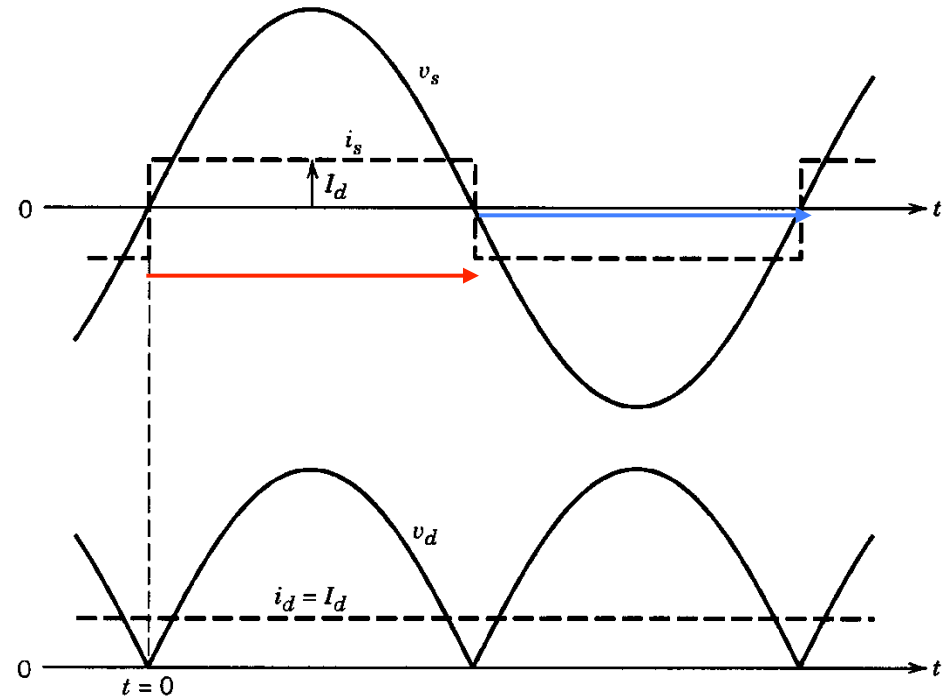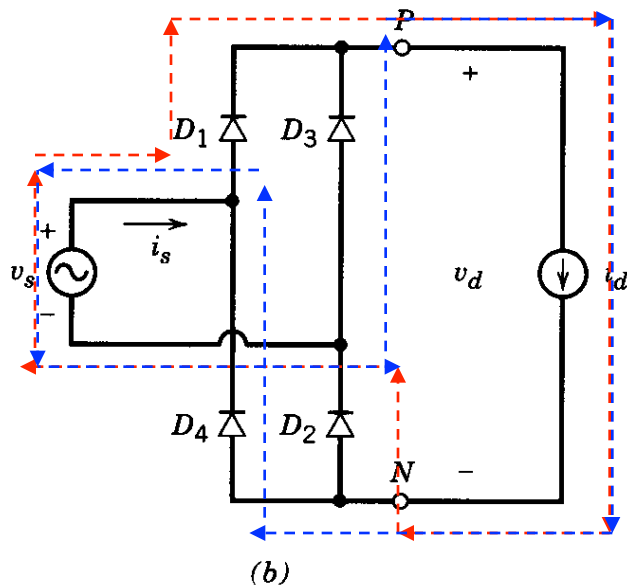




- Output voltage

$$V_{d0} = \frac{1}{T/2} \int_0^{T/2} \sqrt{2}V_s \sin \omega t dt = \frac{2}{\pi} \sqrt{2}V_s = 0.9V_s$$

- For inductive load

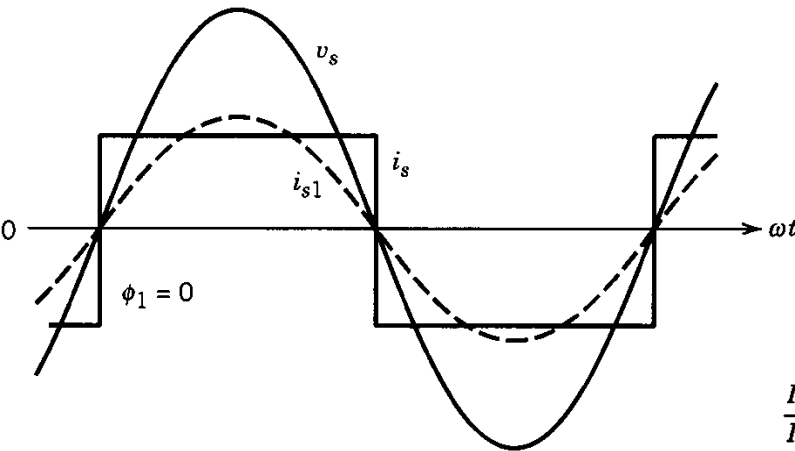


Fourier analysis of  $i_s$ :

$$I_{s1} = \frac{2}{\pi} \sqrt{2}I_d = 0.9I_d \quad I_{sh} = I_{s1} / h$$



$$DF = I_{s1} / I_d = 0.9$$





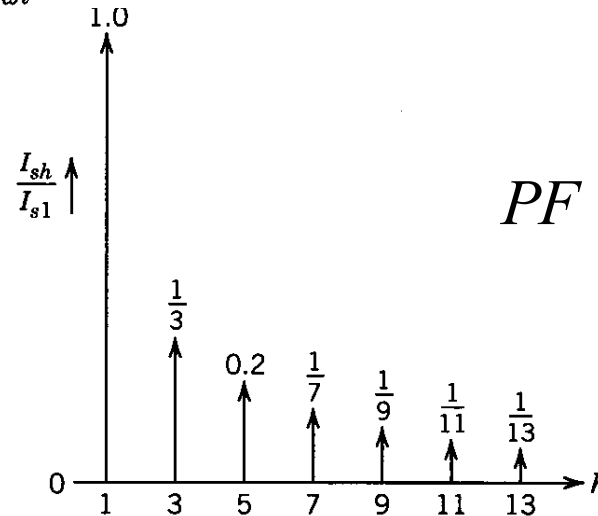
$$PF = (I_{s1} / I_d) \cdot \cos \varphi = 0.9$$


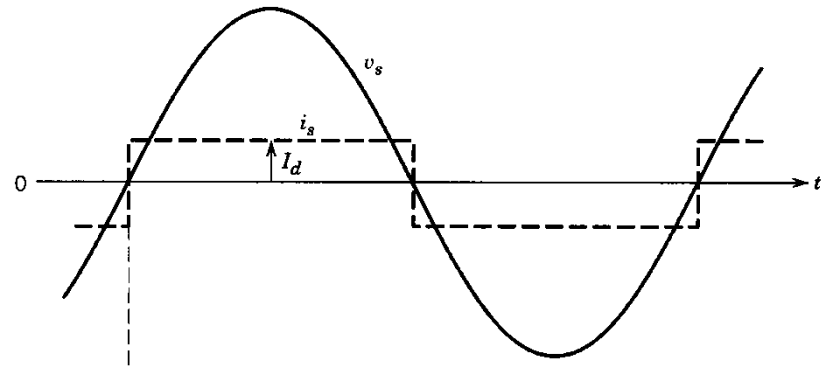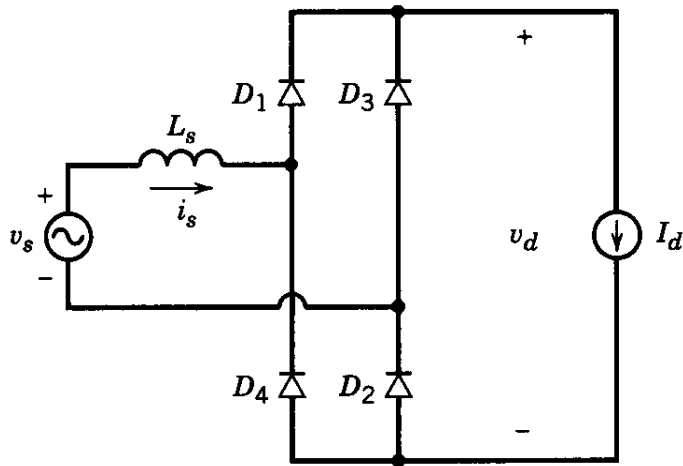
# Single-phase bridge rectifier

- Large inductive load - Effect of  $L_s$  on current commutation
- $i_s$  (inductor current) can not change from  $I_d$  to  $-I_d$  instantaneously



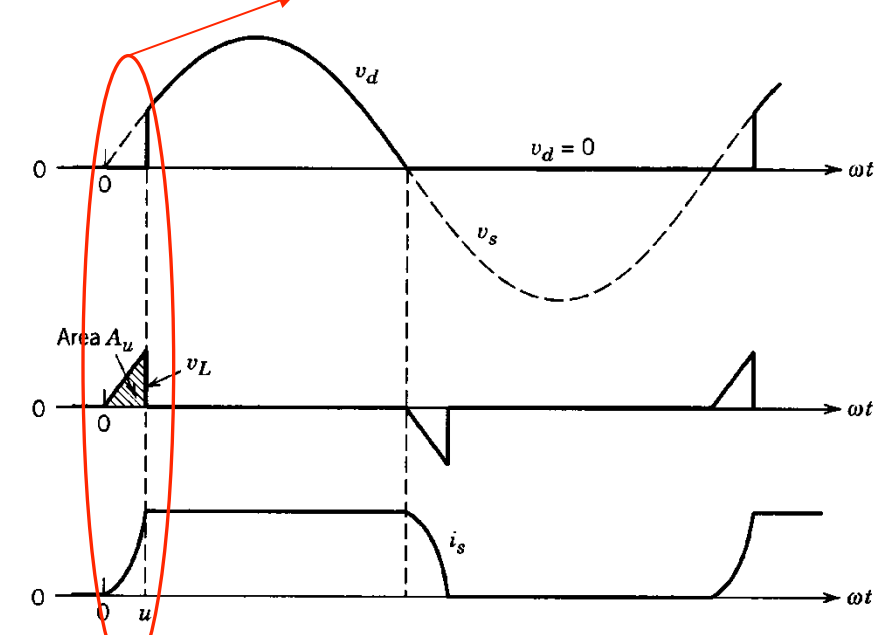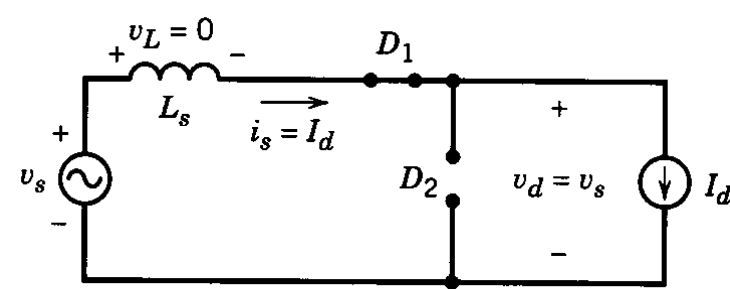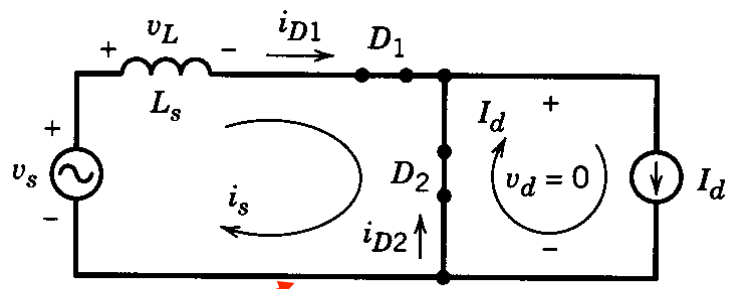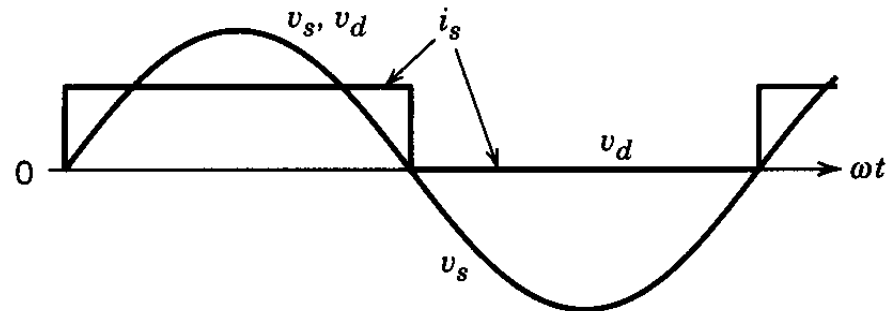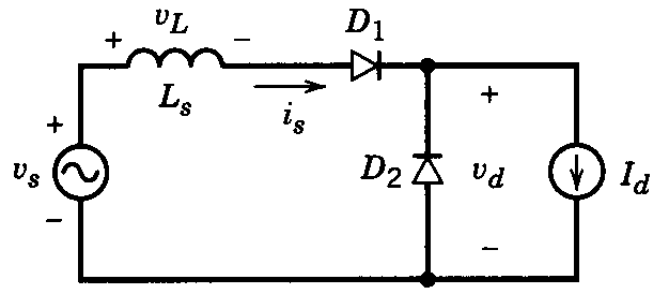

$$v_L = \sqrt{2} V_s \sin \omega t = L_s \frac{di_s}{dt} \quad 0 < \omega t < u$$

$$i_s(t) = i_s(0) + \frac{1}{L_s} \int_0^t \sqrt{2} V_s \sin \omega t d(t)$$

$$i_s(0) = 0 \quad i_s(u/\omega) = I_d$$

$$\omega L_s I_d = \sqrt{2} V_s (1 - \cos u)$$

$$\cos u = 1 - \frac{\omega L_s I_d}{\sqrt{2} V_s} \quad A_u = \int_0^u \sqrt{2} V_s \sin \omega t d(\omega t)$$

$u$  - commutation angle


# Voltage drop due to current commutation

For  $L_s = 0$ :  $V_d = \frac{1}{2\pi} \int_0^\pi \sqrt{2} V_s \sin \omega t d(\omega t) = \frac{2\sqrt{2} V_s}{2\pi} = 0.45 V_s$

For  $L_s \neq 0$ :  $V_d = \frac{1}{2\pi} \int_u^\pi \sqrt{2} V_s \sin \omega t d(\omega t)$

$$V_d = 0.45 V_s - \frac{1}{2\pi} \int_0^u \sqrt{2} V_s \sin \omega t d(\omega t)$$

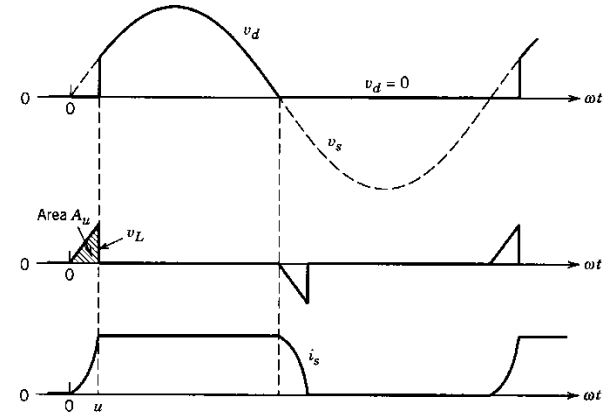
$$= 0.45 V_s - \frac{\text{area } A_u}{2\pi} = 0.45 V_s - \frac{\omega L_s}{2\pi} I_d$$




Every cycle the area  $A_u$  is lost once



$$\Delta V_d = \frac{\text{area } A_u}{2\pi} = \frac{\omega L_s}{2\pi} I_d$$

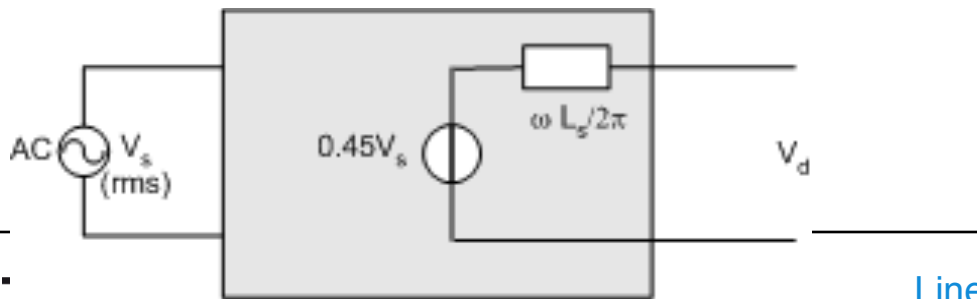= apparent resistor (no losses)  
Static model of dc-side of rectifier



Line

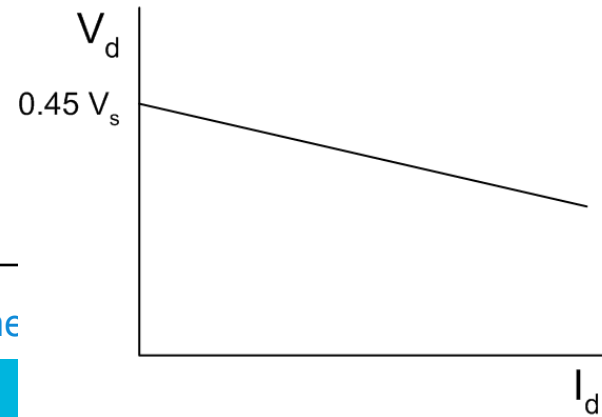

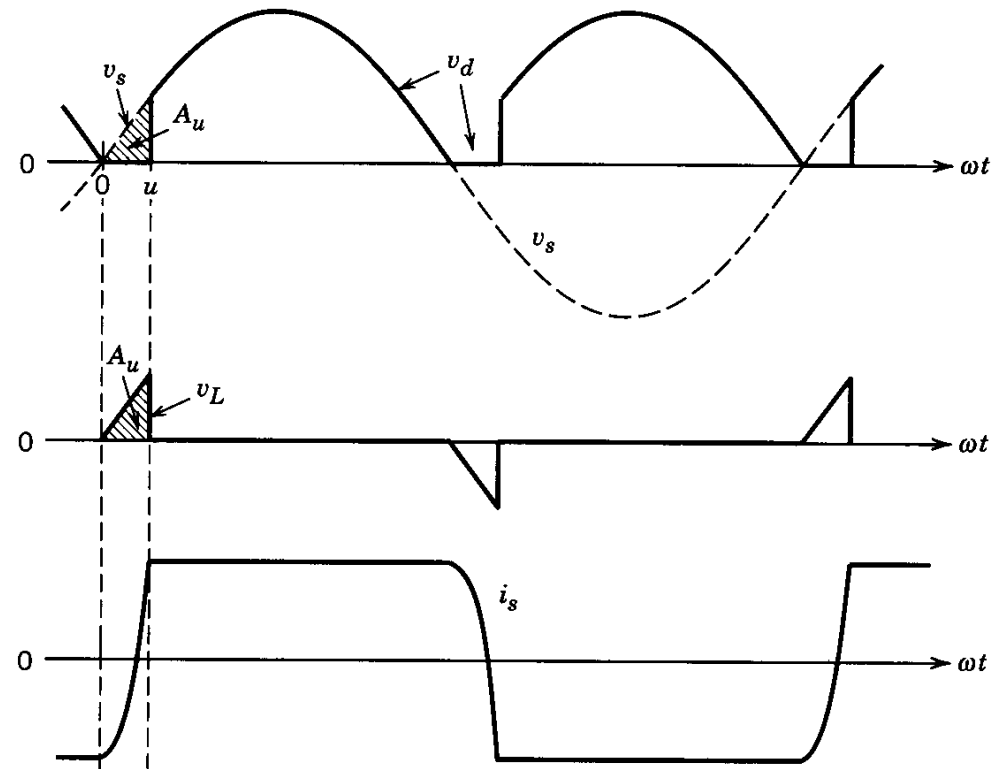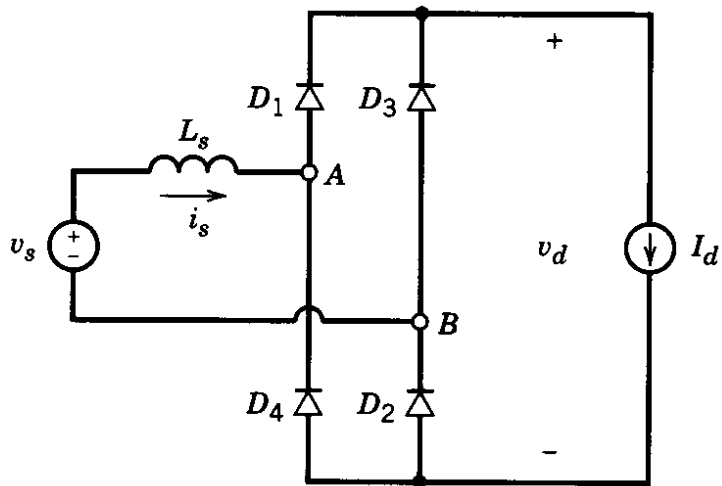


commutation:  $3+4 \implies 1+2$

1. describe problem as superposition of  $I_d$  and commutation current  $i_u$
2. identify commutation meshes and driving voltages
3. note that  $I_d$  is constant

Current  $i_s(t)$  goes from  $-I_d$  to  $I_d$  in interval  $(0, u)$

$$i_s(\omega t) = i_s(0) + \frac{I}{\omega L_s} \int_0^{\omega t} \sqrt{2} V_s \sin \omega t d(\omega t)$$
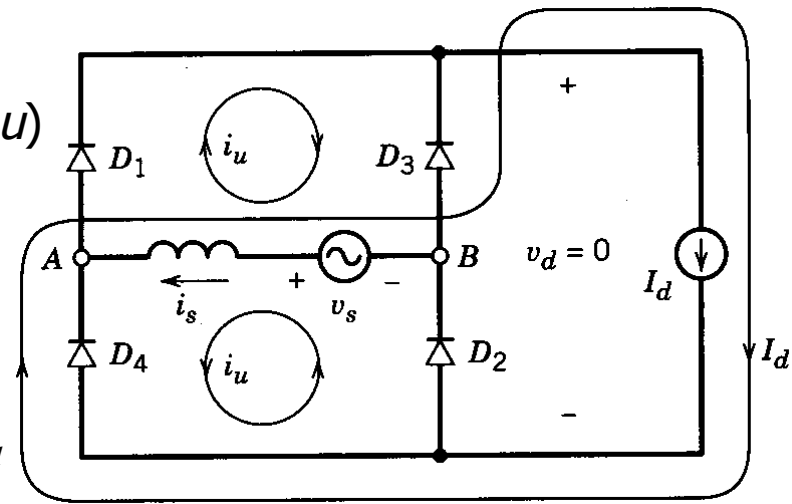
$$\omega L_s \Delta i_s = \int_0^u \sqrt{2} V_s \sin \omega t d(\omega t) \quad \text{with} \quad \Delta i_s = 2 I_d$$



$$\text{or} \quad 2\omega L_s I_d = \sqrt{2} V_s (1 - \cos u) \quad \rightarrow \quad \cos u = 1 - \frac{2\omega L_s I_d}{\sqrt{2} V_s}$$


Shaded area forces the current from  $-I_d$  to  $I_d$  :

$$A_u = \int_0^u \sqrt{2} V_s \sin \omega t d(\omega t)$$

$$2\omega L_s I_d = \int_0^u \sqrt{2} V_s \sin \omega t d(\omega t)$$



Output voltage: 
$$V_d = 0.9 V_s - \frac{2 \text{Area } A_u}{2\pi} = 0.9 V_s - \frac{2\omega L_s I_d}{\pi}$$

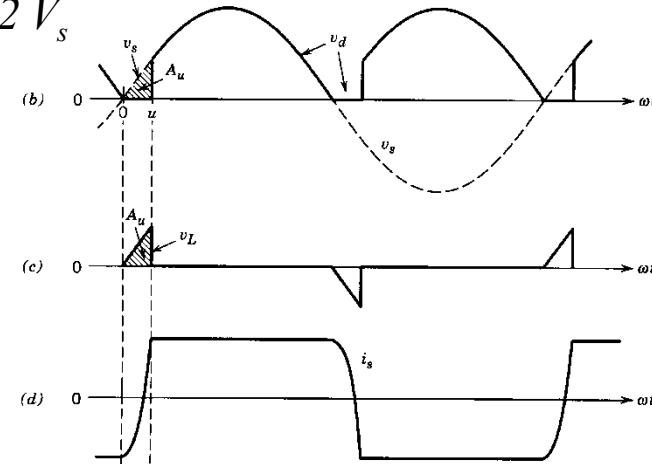Every cycle the area  $A_u$  is lost **twice**


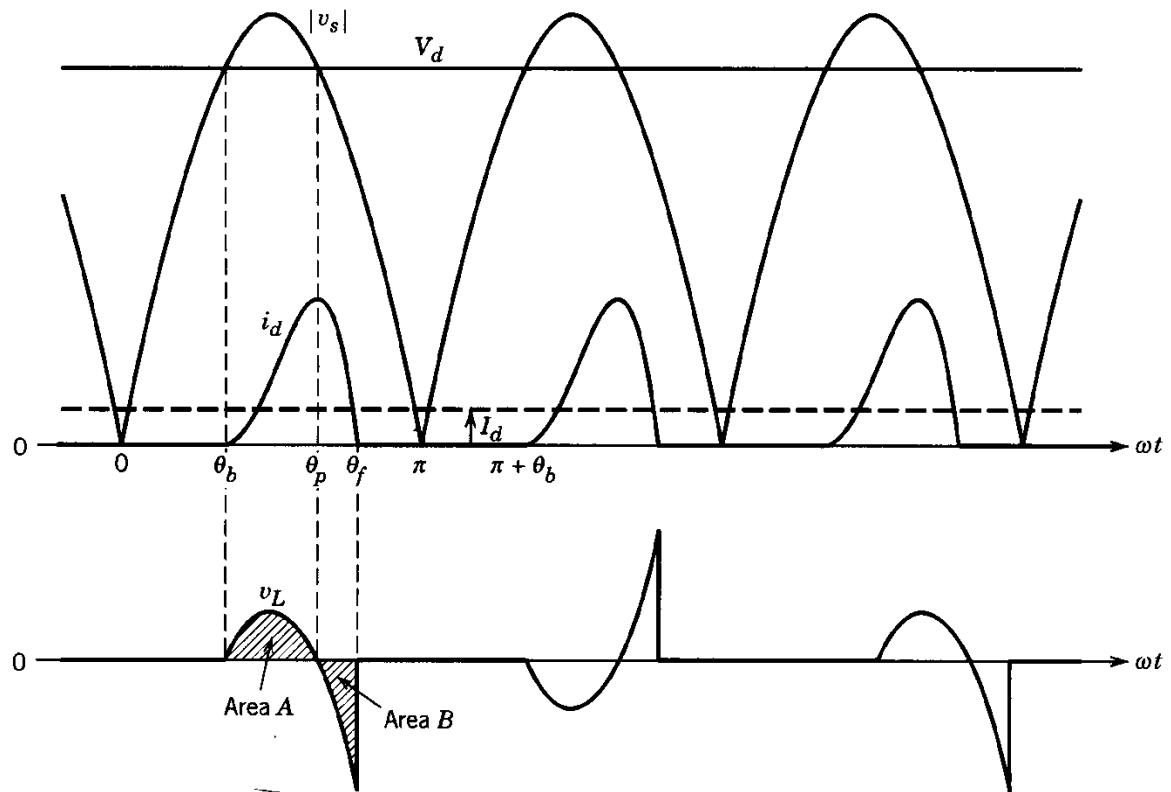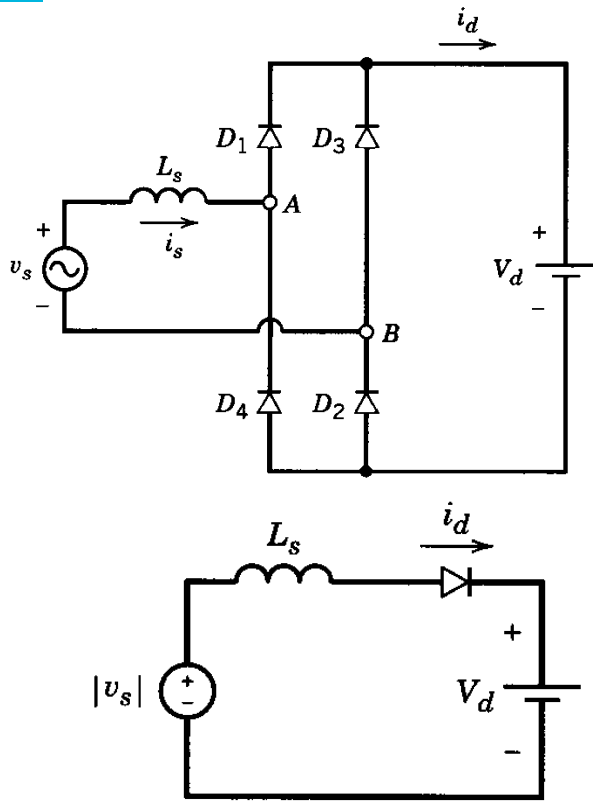
# Single-phase bridge rectifier

- Constant dc-side voltage  
(Approximation of RC-load with  $RC \gg 10 \text{ ms}$ )



$$V_d = \sqrt{2} V_s \sin \theta_b$$


- $i_d$  has maximum when  $v_s$  crosses  $V_d$  again ↓

$$i_d(\theta) = \frac{1}{\omega L_s} \int_{\theta_b}^{\theta} (\sqrt{2} V_s \sin \omega t - V_d) d(\omega t)$$

- $\theta_f$  follows from:

$$0 = \frac{1}{\omega L_s} \int_{\theta_b}^{\theta_f} (\sqrt{2} V_s \sin \omega t - V_d) d(\omega t)$$


- high peak line current

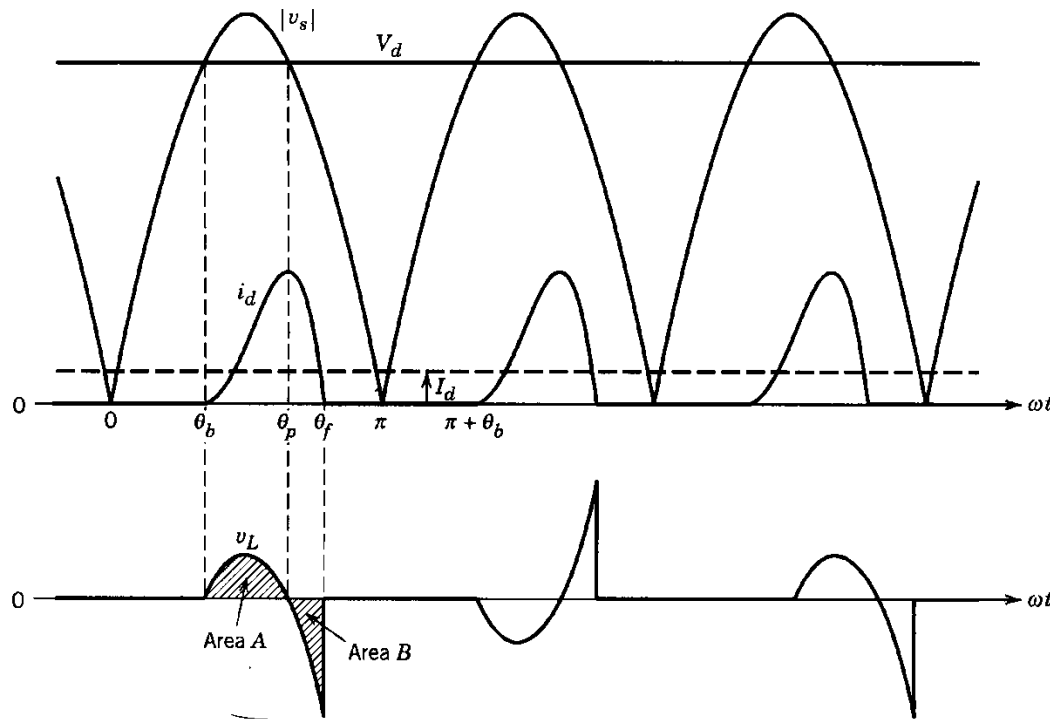



# Practical bridge rectifier


$$L_s = 0$$

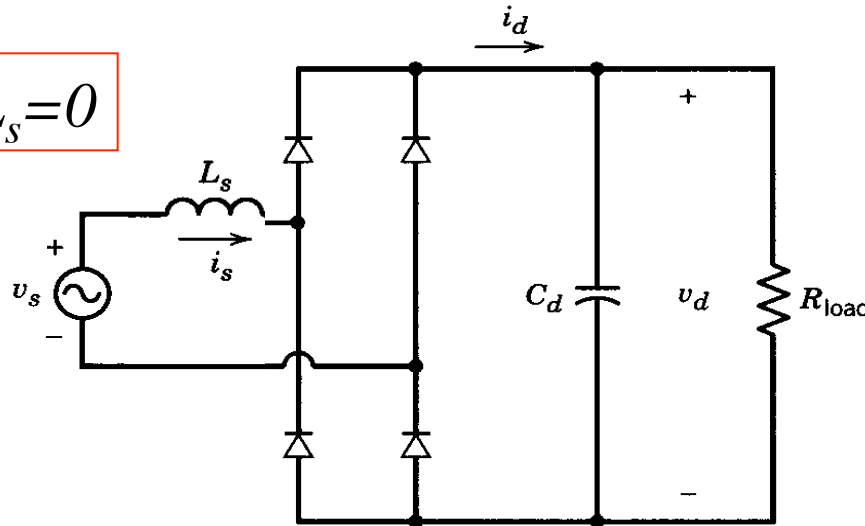

$$t_1 < t < t_2$$


$v_d < v_s \rightarrow$  diodes conducting

$$t_2 < t < t_3$$

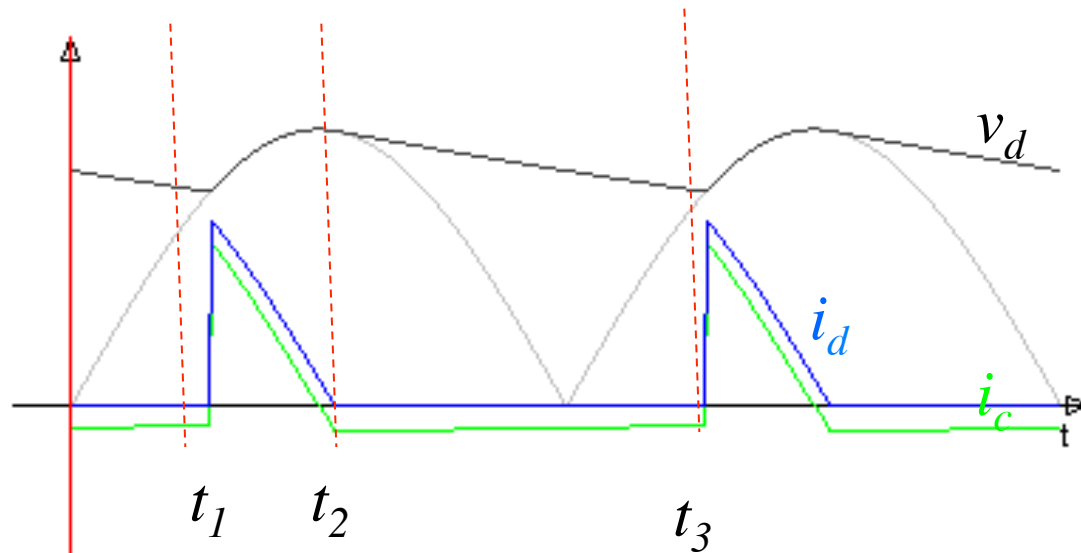



# Practical bridge rectifier

$$L_s > 0$$

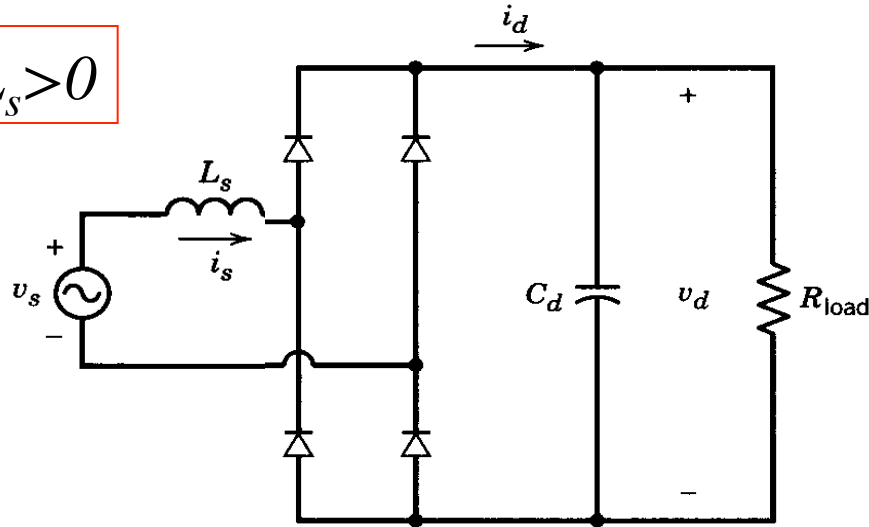

$v_d < v_s \rightarrow$  diodes conducting

# Line voltage distortion

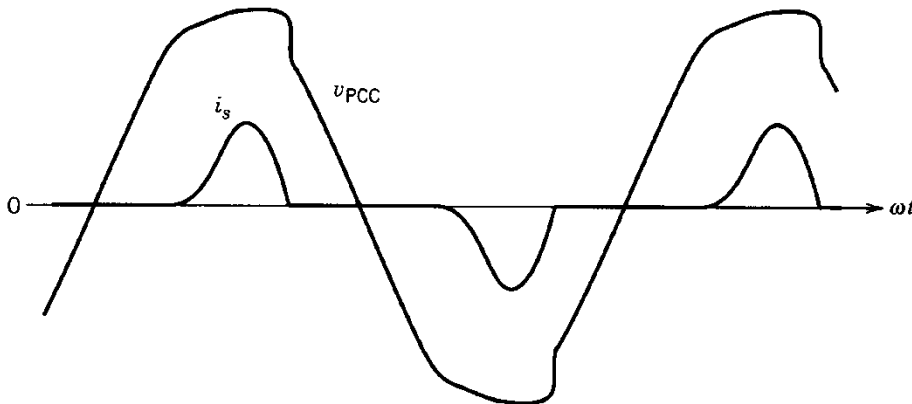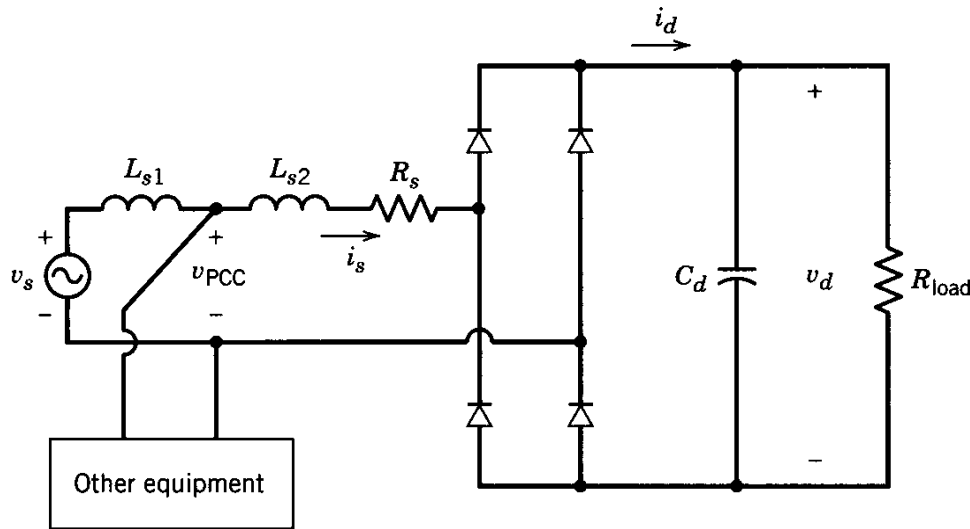

$$v_{pcc} = v_s - L_{s1} \frac{di_s}{dt}$$

$i_s$  contains harmonics:

$$i_s = i_{s1} + \sum_{h=2}^{\infty} i_{sh}$$

$$v_{pcc} = v_s - L_{s1} \frac{di_1}{dt} - L_{s1} \sum_{h=2}^{\infty} \frac{di_{sh}}{dt}$$


Fundamental component of  $v_{pcc}$

$$v_{pcc,1} = v_s - L_{s1} \frac{di_{s1}}{dt}$$

Voltage distortion component

$$v_{pcc,dis} = -L_{s1} \sum_{h=2}^{\infty} \frac{di_{sh}}{dt}$$

# Three phase full-bridge rectifiers

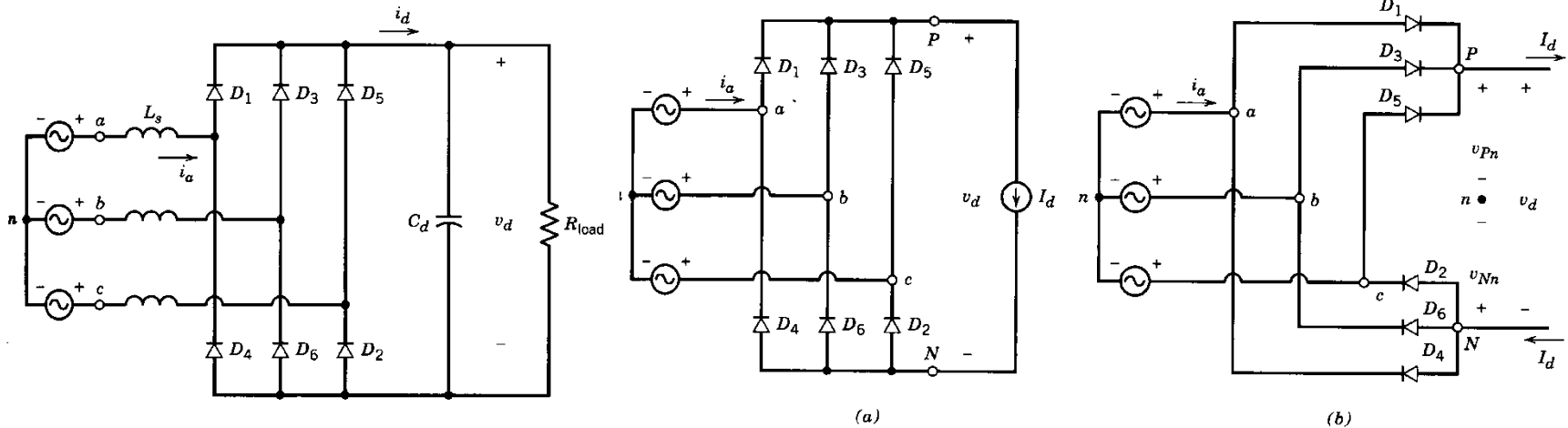

Assume:  $i_d$  constant and equal to  $I_d$  and  $L_s = 0$

How many diodes are conducting?

Which diodes are conducting?

Diode with highest anode potential is conducting (+rail)




Diode with lowest cathode potential is conducting (-rail)

Fig. (b):  $v_d = v_{Pn} - v_{Nn}$

$i_a = +I_d$  when diode 1 is conducting

$= -I_d$  when diode 4 is conducting

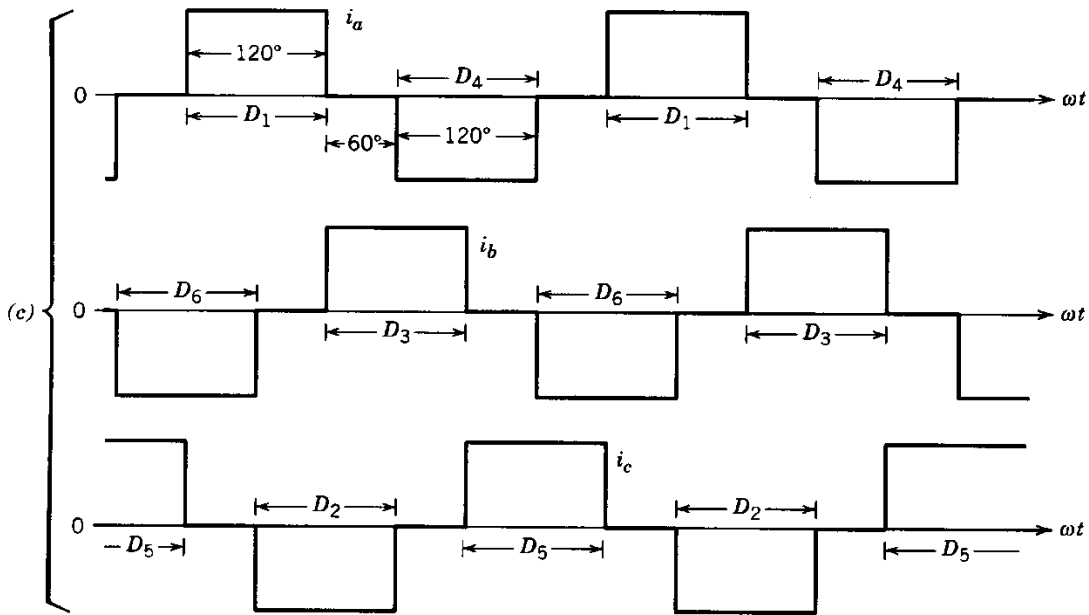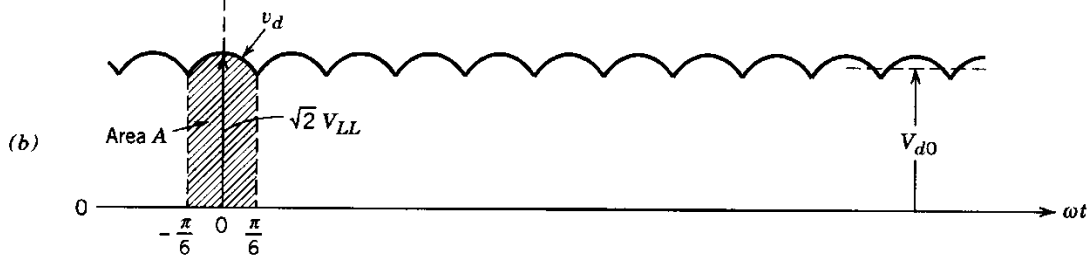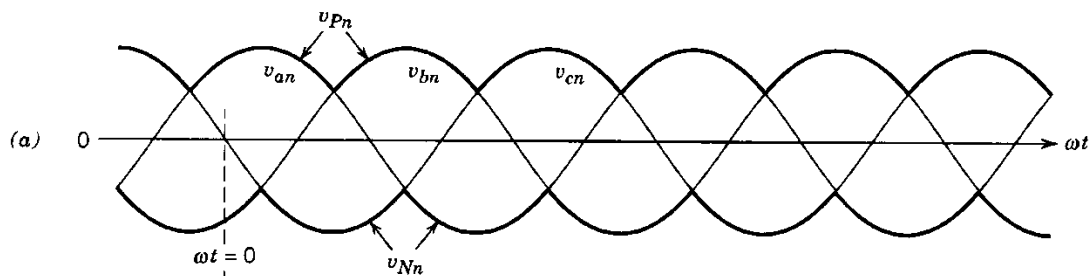$= 0$  when neither diode 1 or 4 is conducting




For:  $-\frac{1}{6}\pi < \omega t < \frac{1}{6}\pi$


$$v_d(t) = v_{ab}(t) = \sqrt{2} V_{LL} \cos \omega t$$

$$V_{do} = \frac{1}{\pi/3} \int_{-\pi/6}^{\pi/6} \sqrt{2} V_{LL} \cos \omega t$$
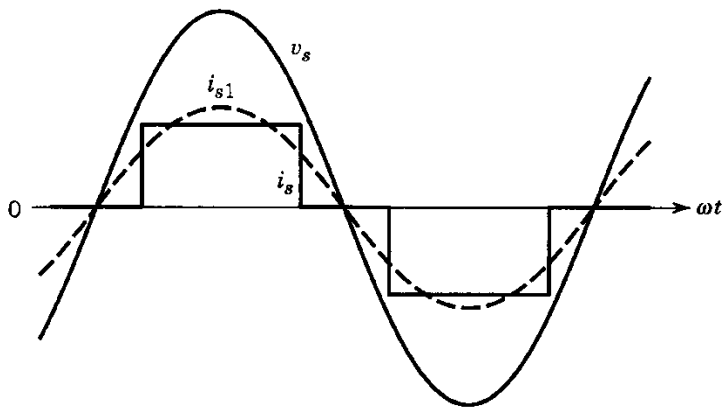
$$= \frac{3}{\pi} \sqrt{2} V_{LL} = 1.35 V_{LL}$$



(a)

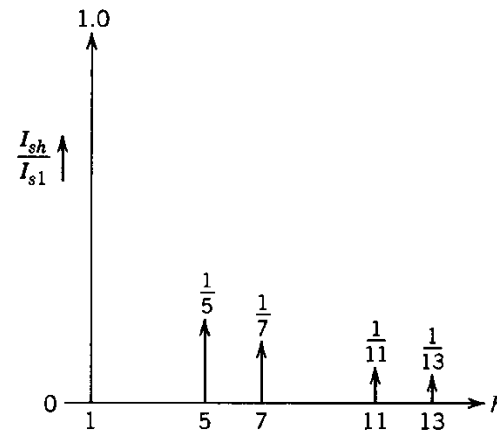

(b)

$h = 5, 7, 11, 13, 17, \dots$

$$I_s = \sqrt{\frac{2}{3}} I_d = 0.816 I_d$$





From Fourier analysis:  $I_{sh} = \frac{I_{s1}}{h}$  with  $I_{s1} = \frac{\sqrt{6}}{\pi} I_d = 0.78 I_d$

$$DF = \frac{I_{s1}}{I_s} = \frac{3}{\pi} = 0.955 \quad \text{and} \quad DPF = \cos \alpha$$

$$PF = DF \cdot DPF = \frac{I_{s1}}{I_s} \cdot 1 = \frac{3}{\pi} = 0.955$$

# Three phase full-bridge rectifiers

## Commutation

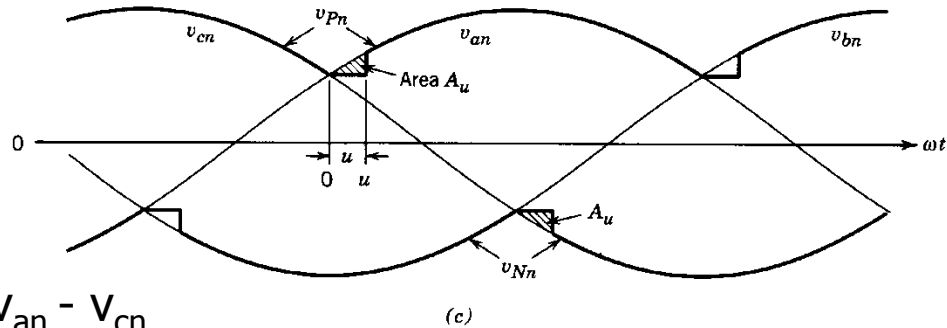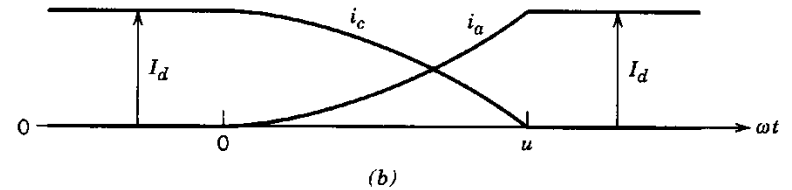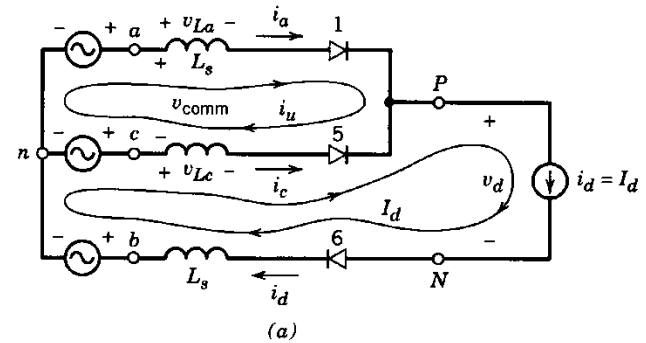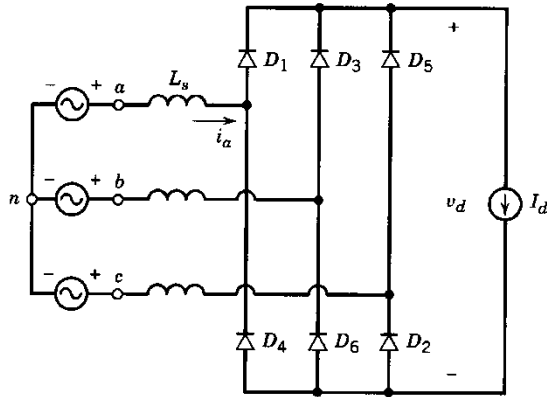

Commutation starts when  $v_{ac} = v_{cn}$

Driving voltage in a mesh:  $v_{comm} = v_{an} - v_{cn}$

$$v_{comm} = v_{an} - v_{cn} = v_{La} - v_{Lc} \quad \text{SO:} \quad v_{comm} = 2L_s \frac{di_u}{dt}$$

$$i_u(t) = i_u(0) + \frac{1}{L_s} \int_0^t \frac{v_{an} - v_{cn}}{2} d(t) \quad \rightarrow \quad \omega L_s \Delta i_d = \int_0^u \frac{\sqrt{2} V_{LL} \sin \omega t}{2} dt$$

$$\omega 2L_s I_d = \sqrt{2} V_{LL} (1 - \cos u) \quad \rightarrow \quad \cos u = 1 - \frac{2\omega L_s I_d}{\sqrt{2} V_s}$$

During commutation:  $v_{Pn} = v_{an} - L_s \frac{di_u}{dt} = \frac{v_{an} + v_{cn}}{2}$

Shaded area forces the current from 0 to  $I_d$  in **one** inductor:

$$A_u = \frac{1}{2} \int_0^u \sqrt{2} V_{LL} \sin \omega t d(\omega t) \quad \text{or:} \quad A_u = \omega L_s I_d$$

Every period the area  $A_u$  is lost six times

$$\text{Voltage drop: } \Delta V_{do} = \frac{6 \cdot \text{area } A_u}{2\pi} = \frac{3\omega L_s}{\pi} I_d \quad V_d = V_{do} - \Delta V_d = 1.35V_{LL} - \frac{3\omega L_s}{\pi} I_d$$



# Image credits

- All uncredited diagrams are from the book "Power Electronics: Converters, Applications, and Design" by N. Mohan, T.M. Undeland and W.P. Robbins.
- All other uncredited images are from research done at the EWI faculty.