

ET4119 Electronic Power Conversion 2011/2012  
**Exam 20 April 2012**

Remarks:

In front of every question the maximum rating that can be obtained is indicated.

First solve the problems on draft paper and make a neat version subsequently.

Start each problem on a separate piece of paper.

Always show the formulas that you used to make the calculations.

You can give your answers in Dutch or in English.

It is allowed to use a (self-made) single sided piece of paper (1xA4) with formulas and figures from the textbook.

1. Figure 1a shows a single-phase rectifier that is connected to a supply voltage  $v_s$  and a battery. The battery is represented by a DC load voltage  $V_d$ . The voltage  $v_s$  has a block-like shape (Figure 1b) that is produced by some HF inverter (not shown). The rectifier is intended to charge the battery. Depending on the charging state of the battery the voltage  $V_d$  may vary. The circuit specifications are as follows:

- $V_{d,nom}=160V$  (nominal voltage of  $V_d$ )
- $V_s=300V$  (amplitude of  $v_s$  as shown in Figure 1b)
- $T_s=30\mu s$  (period of voltage  $v_s$ )
- $f_s=1/T_s=33.3\text{ kHz}$  (frequency of  $v_s$ )
- $L_s=20\ \mu H$

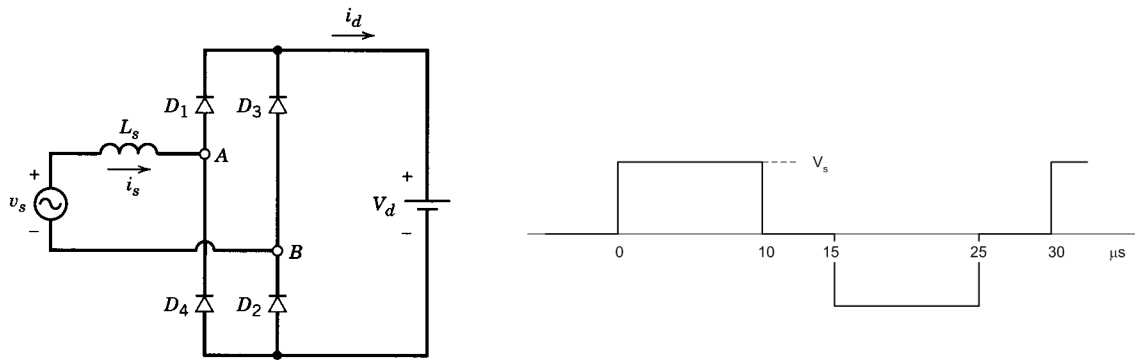


Figure 1 a. rectifier circuit b. input voltage waveform

- 1.1 (10) Sketch  $v_L$  and  $i_s$  as a function of time and indicate relevant values for  $V_d = V_{d,nom}$ .
- 1.2 (10) Calculate the peak value of  $i_s$ , the average current  $I_d$  and the average output power  $P_d$  for  $V_d = V_{d,nom}$ .
- 1.3 (5) What will happen if  $V_d$  is increased above 200V?

2. Figure 2 shows a boost converter used in the Toyota Prius hybrid electric vehicle for stepping up the battery voltage from 150-250 V to 500 V. The converter's switching frequency is  $f_s = 20\text{kHz}$ .

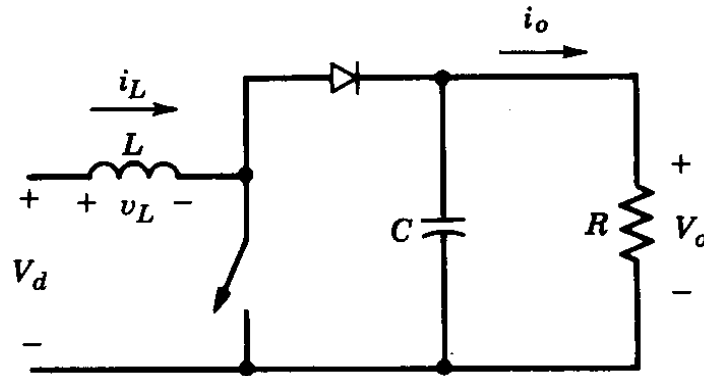


Figure 2 Boost converter

- 2.1 (10) Calculate the critical (maximum) inductance value of the filter inductor to ensure that the converter operates in the discontinuous conduction mode for the given input voltage range and the load current up to  $I_o = 10\text{A}$ . Show the derivation of the expression for the inductance (do not use ready-made formulas).
- 2.2 (5) Given the inductance value obtained in 1.1 calculate the duty cycle range to keep the output voltage  $V_o$  constant (500V) for the given range of the input voltage and the nominal current of  $I_{nom} = 4\text{A}$ .
- 2.3 (10) Calculate the required capacitance value of the output filter capacitor to ensure that at the nominal input voltage ( $V_{d_{nom}} = 200\text{V}$ ) and the output current of 12A the output voltage ripple is less than 2% of the nominal output voltage ( $V_o$ ). Show the derivation of the expression for the inductance (do not use ready-made formulas).

3. A switch-mode power supply is to be designed with the following specifications:
- $V_d=48V\pm 10\%$
  - $V_o=5V$  (regulated)
  - $f_s=100kHz$
  - $P_{load}=15-50W$

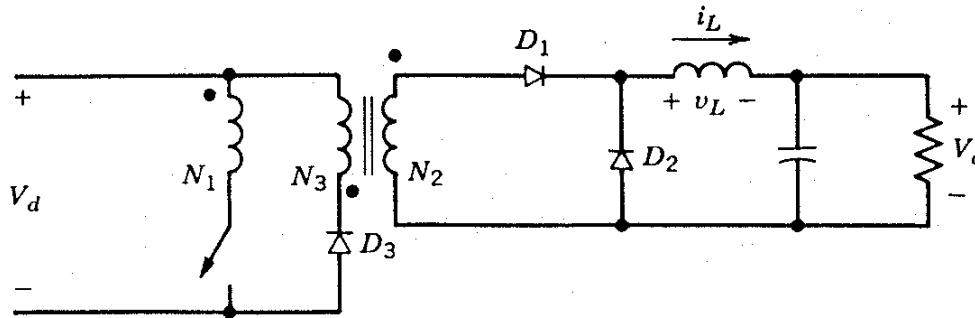


Figure 3 Forward converter

A forward converter topology shown in Figure 3 operating in a continuous conduction mode with a demagnetising winding ( $N_3=N_1$ ) is chosen. Assume all components to be ideal except for the presence of transformer magnetising inductance.

- 3.1 (5) Sketch the operating waveforms of the converter.
- 3.2 (10) Calculate  $N_2/N_1$  if this turns ratio is desired to be as small as possible.
- 3.3 (10) Calculate the minimum value of the filter inductance.

4. Given is a single-phase full bridge dc/ac voltage source converter that is connected to a single phase induction motor with counter emf  $e_0$ , as shown in Figure 4. The output voltage  $v_0$  of the inverter is obtained by bipolar voltage switching. To obtain a low distortion linear modulation is applied.

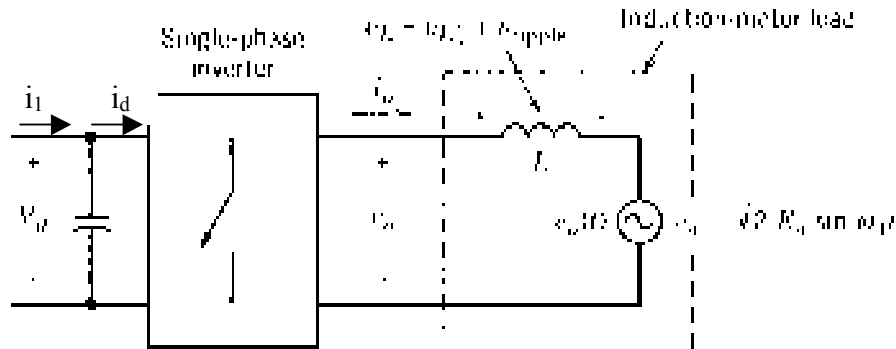


Figure 4 Full bridge inverter

Given is further:

- $V_d = 350\text{V}$  (DC link voltage)
- $\omega_{1,\text{nom}} = 2\pi 60 \text{ rad/s}$  (nominal value of  $\omega_1$ )
- $V_{01,\text{nom}} = 230 \text{ V}$  (nominal rms value of fundamental of  $v_0$ )
- $L = 30 \text{ mH}$  (inductance of machine)
- $f_s = 7.5 \text{ kHz}$  (frequency of triangular carrier  $v_{\text{tri}}$ )
- $C_d = 1 \text{ mF}$  (capacitance of input filter)
- At nominal speed and nominal voltage the input power of the loaded drive is 1 kW at  $\cos \phi_1 = 0.8$

- 4.1 (5) Calculate the rms value of the fundamental of  $i_0$  when the machine runs at rated speed and rated power. Sketch a phasor diagram with the phasors of  $e_0$ ,  $v_0$  and  $i_0$ .
- 4.2 (5) Define the modulation ratio  $m_a$  and give the relation between  $V_{01}$ ,  $m_a$  and  $V_d$ , where  $V_{01}$  is the rms value of the fundamental of the output voltage. Calculate the modulation ratio  $m_a$  such that the machine runs at nominal speed and nominal voltage.
- 4.3 (5) Calculate the expression for and sketch the instantaneous power  $p_0(t)$  that is transmitted by the fundamental current  $i_0$  and voltage  $v_0$
- 4.4 (10) Calculate the low-frequency ( $< 1 \text{ kHz}$ ) peak-to-peak voltage ripple  $\Delta V_d$  assuming that the current  $i_1$  is constant.