

ET4119 Electronic Power Conversion 2011/2012  
**Solutions 20 April 2012**

1. Figure 1a shows a single-phase rectifier that is connected to a supply voltage  $v_s$  and a battery. The battery is represented by a DC load voltage  $V_d$ . The voltage  $v_s$  has a block-like shape (Figure 1b) that is produced by some HF inverter (not shown). The rectifier is intended to charge the battery. Depending on the charging state of the battery the voltage  $V_d$  may vary. The circuit specifications are as follows:

- $V_{d,nom}=160\text{V}$  (nominal voltage of  $V_d$ )
- $V_s=300\text{V}$  (amplitude of  $v_s$  as shown in Figure 1b)
- $T_s=30\mu\text{s}$  (period of voltage  $v_s$ )
- $f_s=1/T_s=33.3\text{ kHz}$  (frequency of  $v_s$ )
- $L_s=20\mu\text{H}$

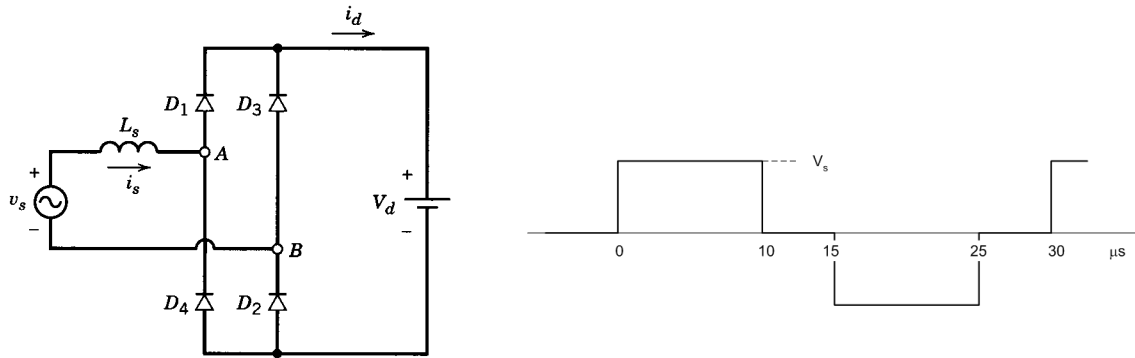


Figure 1 a. rectifier circuit b. input voltage waveform

**No worked out solutions**

2. Figure 2 shows a boost converter used in the Toyota Prius hybrid electric vehicle for stepping up the battery voltage from 150-250 V to 500 V. The converter's switching frequency is  $f_s = 20\text{kHz}$ .

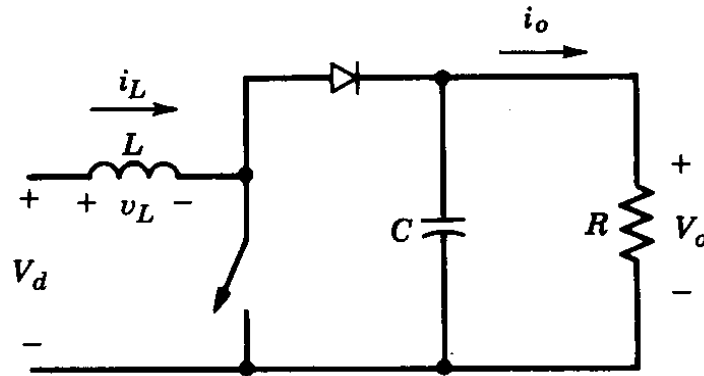


Figure 2 Boost converter

2.1.

$$I_o := 10\text{A}$$

$$L_{\text{crit}}(V_{\text{in}}) := \frac{V_o \cdot \left(1 - \frac{V_{\text{in}}}{V_o}\right) \cdot \left(\frac{V_{\text{in}}}{V_o}\right)^2}{2 \cdot I_o} \cdot T_s$$

$$L_{\text{crit}}(V_{\text{inmin}}) = 78.75\mu\text{H}$$

$$L_{\text{crit}}(V_{\text{inmax}}) = 156.25\mu\text{H}$$

2.2

$$L_o := L_{\text{crit}}(V_{\text{inmin}})$$

$$I_{\text{onom}} := 4\text{A}$$

$$D(V_{\text{in}}) := \sqrt{\frac{2 \cdot I_{\text{onom}}}{1 + \left(\frac{T_s}{L_o}\right) \cdot \frac{V_{\text{in}}^2}{V_o - V_{\text{in}}}}$$

$$D(V_{\text{inmin}}) = 0.443$$


$$D(V_{\text{inmax}}) = 0.224$$

### 2.3

$$\Delta(V_{in}) := \frac{I_{onom} \cdot 2 \cdot L_o}{T_s \cdot D(V_{in}) \cdot V_{in}}$$

$$V_{in} := 200V$$
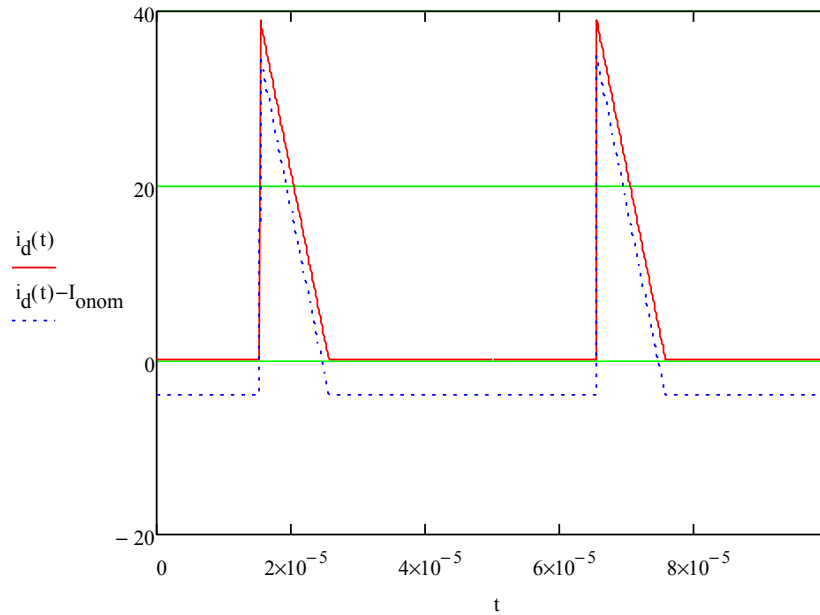
$$D_1 := D(V_{in}) \quad \Delta_1 := \Delta(V_{in}) \quad D_1 = 0.307 \quad \Delta_1 = 0.205$$



$$t_1 := D_1 \cdot T_s$$

$$t_2 := \frac{\frac{V_{in}}{L_o} \cdot D_1 \cdot T_s - I_{onom} + \frac{V_o - V_{in}}{L_o} \cdot D_1 \cdot T_s}{\left( \frac{V_o - V_{in}}{L_o} \right)}$$

$$t_1 = 15.37\mu s$$

$$t_2 = 24.567\mu s$$

$$Q := \left[ \int_{t_1}^{t_2} (i_d(t) - I_{onom}) dt \right]$$

$$Q = 1.611 \times 10^{-4} C$$

$$C_{req} := \frac{Q}{2\% \cdot V_o}$$

$$C_{req} = 16.111\mu F$$

3. A switch-mode power supply is to be designed with the following specifications:
- $V_d=48V\pm 10\%$
  - $V_o=5V$  (regulated)
  - $f_s=100kHz$
  - $P_{load}=15-50W$

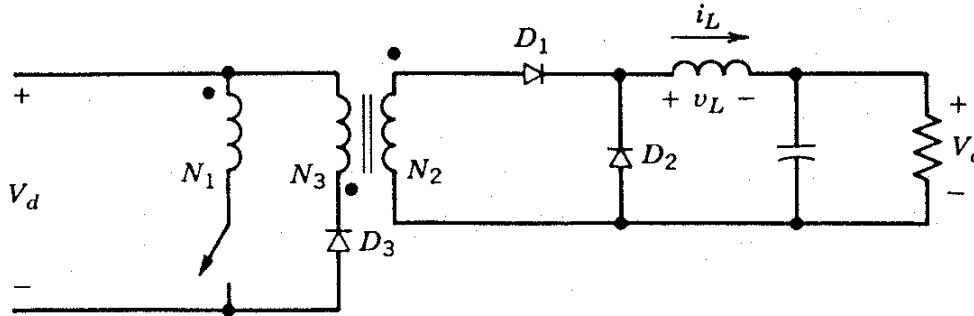


Figure 3 Forward converter

A forward converter topology shown in Figure 3 operating in a continuous conduction mode with a demagnetising winding ( $N_3=N_1$ ) is chosen. Assume all components to be ideal except for the presence of transformer magnetising inductance.

3.1 See book, especially the chapter titled Forward Converter

3.2

Since  $N_3 = N_1$ ,  $D_{max} = 0.5$ ,  $V_d = 43.2 V$  to  $52.8 V$ .

$$\frac{V_o}{V_d} = \frac{N_2}{N_1} D \quad (\text{continuous conduction})$$

$$\text{or, } \frac{N_2}{N_1} = V_o \frac{1}{(V_d)_{min} \cdot D_{max}} = \frac{5}{43.2 \times 0.5} = 0.232$$

The reason for using  $(V_d)_{min}$  at the maximum allowable duty ratio is that at higher values of  $V_d$ , this converter can operate at lower values of  $D$  ( $D < D_{max}$  of 0.5). For example, at  $(V_d)_{max} = 52.8 V$  with the above choice of  $\frac{N_2}{N_1}$ ,

$$D = \left( \frac{5}{52.8} \right) / 0.232 = 0.408.$$

3.3

At the boundary of cont./discont. conduction,

$$\frac{1}{2} \frac{(V_d \frac{N_2}{N_1} - V_o)}{L_{\min}} t_{\text{on}} = I_{o,\min}$$

or,

$$L_{\min} = \frac{(V_d \cdot \frac{N_2}{N_1} - V_o) D}{2f_s I_{o,\min}}$$

at  $(V_d)_{\min} = 43.2 \text{ V}$ ,  $D = 0.5 \therefore L_{\min 1} = 4.18 \mu\text{H}$

at  $(V_d)_{\max} = 52.8 \text{ V}$ ,  $D = 0.408 \therefore L_{\min 2} = 4.93 \mu\text{H}$

Therefore,  $L_{\min} = 4.93$  should be used.

4. Given is a single-phase full bridge dc/ac voltage source converter that is connected to a single phase induction motor with counter emf  $e_0$ , as shown in Figure 4. The output voltage  $v_0$  of the inverter is obtained by bipolar voltage switching. To obtain a low distortion linear modulation is applied.

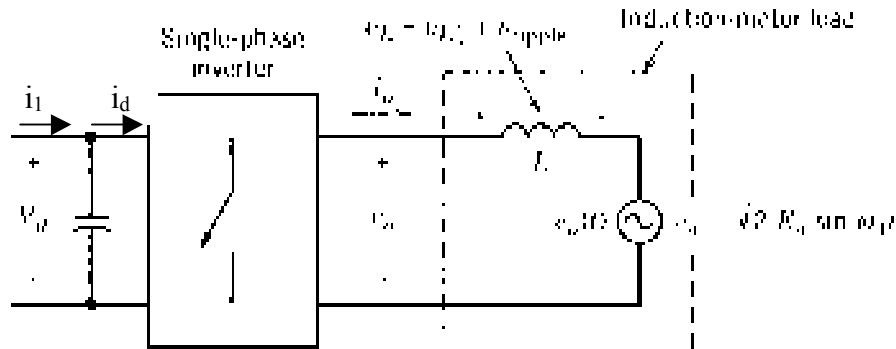



Figure 4 Full bridge inverter

Given is further:

- $V_d = 350\text{V}$  (DC link voltage)
- $\omega_{1,\text{nom}} = 2\pi 60 \text{ rad/s}$  (nominal value of  $\omega_1$ )
- $V_{01,\text{nom}} = 230 \text{ V}$  (nominal rms value of fundamental of  $v_0$ )
- $L = 30 \text{ mH}$  (inductance of machine)
- $f_s = 7.5 \text{ kHz}$  (frequency of triangular carrier  $v_{\text{tri}}$ )
- $C_d = 1 \text{ mF}$  (capacitance of input filter)
- At nominal speed and nominal voltage the input power of the loaded drive is 1 kW at  $\cos \phi_1 = 0.8$

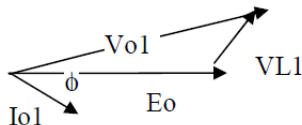4.1

$\therefore P_0 = V_0 I_0 \cos \phi_1$  or  $I_0 = 5.43 \text{ A}$ . (so  $\omega L_s I_0 = 61.4\text{V}$ ). Note that  $\phi$  is the angle between  $V_0$  and  $I_0$ . The phasor diagram is like fig 8-18d.



4.2

$$m_a = \frac{\hat{V}_{\text{control}}}{\hat{V}_{\text{tri}}}; \quad V_0 \sqrt{2} = m_a \cdot V_d \quad \text{or} \quad m_a = 0.929.$$

4.3

$$p_0(t) = \sqrt{2} V_0 \sin \omega_1 t \cdot \sqrt{2} I_0 \sin(\omega_1 t - \phi) = V_0 I_0 \cos \phi - V_0 I_0 \cos(2\omega_1 t - \phi).$$

#### 4.4

For low frequencies:  $p_d(t) = p_0(t)$  with  $p_d(t) = V_d \cdot i_d$  (See Mohan fig 8-13) so

$$i_d(t) = \frac{V_0 I_0}{V_d} \cos \phi - \frac{V_0 I_0}{V_d} \cos(2\omega_1 t - \phi) = 2.85 - 3.57 \cos(\omega_1 t - 36.9^\circ)$$

Amplitude of (sinusoidal) low frequency (120 Hz) current ripple:

$$\hat{i}_{ripple} = \frac{V_0 I_0}{V_d} = \frac{230 \cdot 5.43}{350} = 3.57 A; \quad \rightarrow$$

$$\hat{V}_{d,ripple} = \frac{\hat{i}_{ripple}}{2\omega_1 C_d} = \frac{3.57}{2 \cdot 120\pi \cdot 10^{-3}} = 4.73 V; \quad \text{Peak-to-peak}$$

$$\text{value: } \Delta V_d = 2\hat{V}_{d,ripple} = 9.46 V$$