

DC reference sources

Arie van Staveren
Wouter A. Serdijn




Overview

- Voltage sources (Main part) → Basics and Implementations
- Current sources → Basics and Implementations


Ideal voltage source

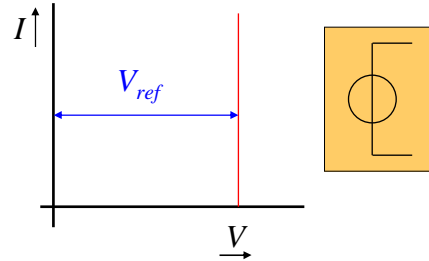- Output voltage *independent* of I , T ,




Ideal current source

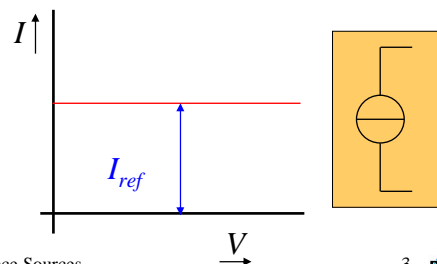- Output current *independent* of V , T ,




Practical voltage source

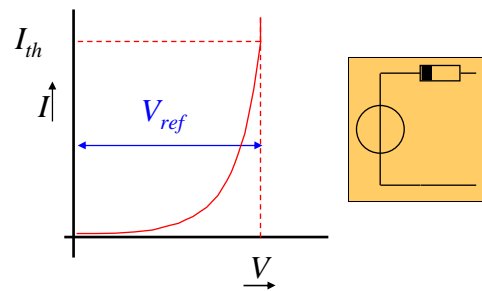- Beyond I_{th} a voltage source
- Output voltage *depends on* external parameters



Practical current source

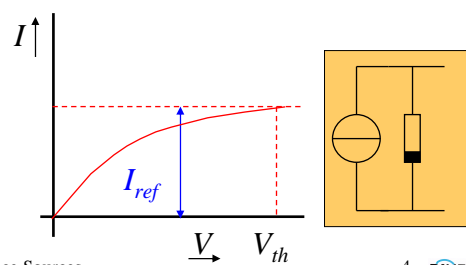- Beyond V_{th} a current source
- Output current *depends on* external parameters



Quality Aspects V,I Source

- Output impedance
 - Noise level
- Power
- Temperature dependency
- Circuit design

Power Supply Rejection Ratio

- V,I source powered by a *power source*

PSRR is a measure for the *sensitivity* of the output quantity (V,I) for *power supply variations*

$$PSRR = 20 \cdot 10 \log \left(\frac{dV_{\text{supply}}}{dV_{\text{ref}}} \frac{V_{\text{ref}}}{V_{\text{supply}}} \right)$$

unit: dB


$$PSRR = 20 \cdot 10 \log \left(\frac{dV_{\text{supply}}}{dI_{\text{ref}}} \frac{I_{\text{ref}}}{V_{\text{supply}}} \right)$$

unit: dB

- The larger the better

Voltage sources


Simple

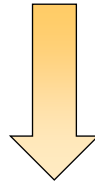

Complicated

Quality


Most simple voltage source

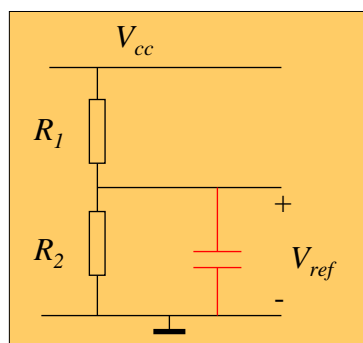

- Accuracy depends on V_{cc} and matching of R_1 and R_2
- Low output impedance and low noise costs *power* or a *capacitor*
- $PSRR = 1$
Can also be improved by *capacitor*


$$V_{ref} = V_{cc} \frac{R_2}{R_1 + R_2}$$

Non-linear voltage divider


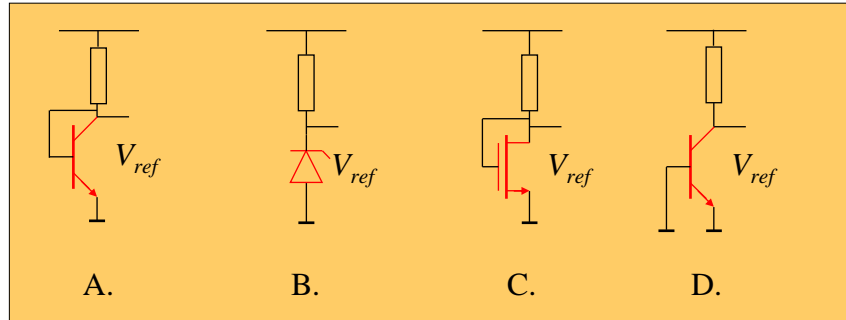


- A. Diode-connected transistor
- B. Zener diode \longrightarrow Zener and Avalanche breakdown
- C. Normally-off FET (NMOS)
- D. Bipolar transistor at punch-through

Zener breakdown

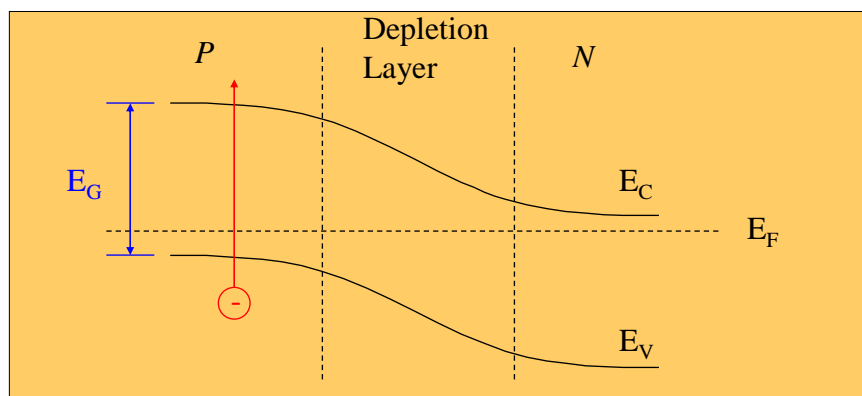


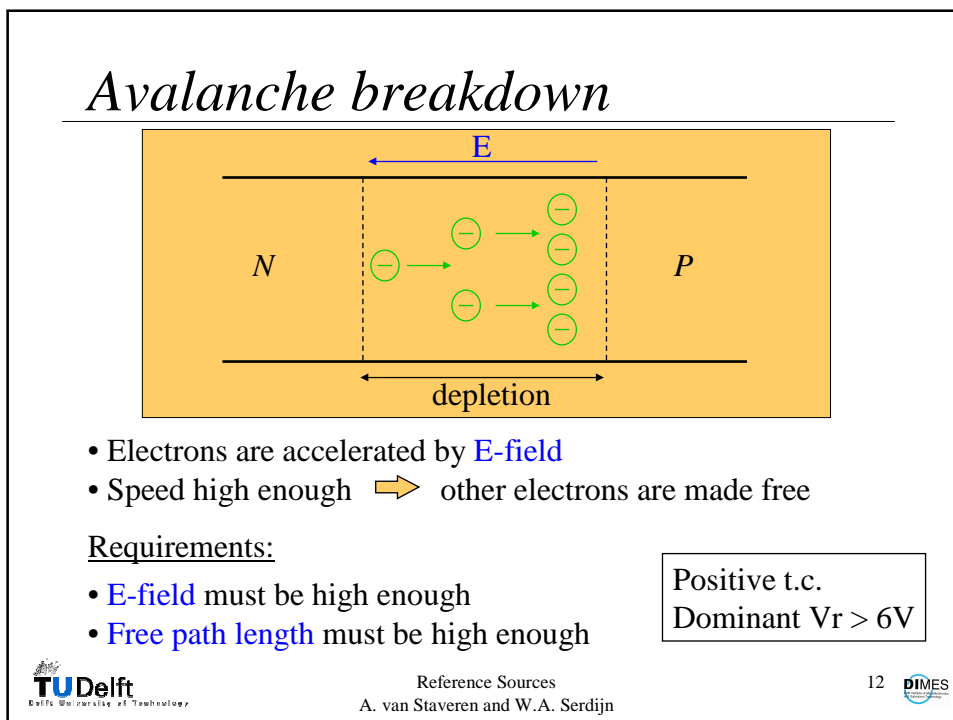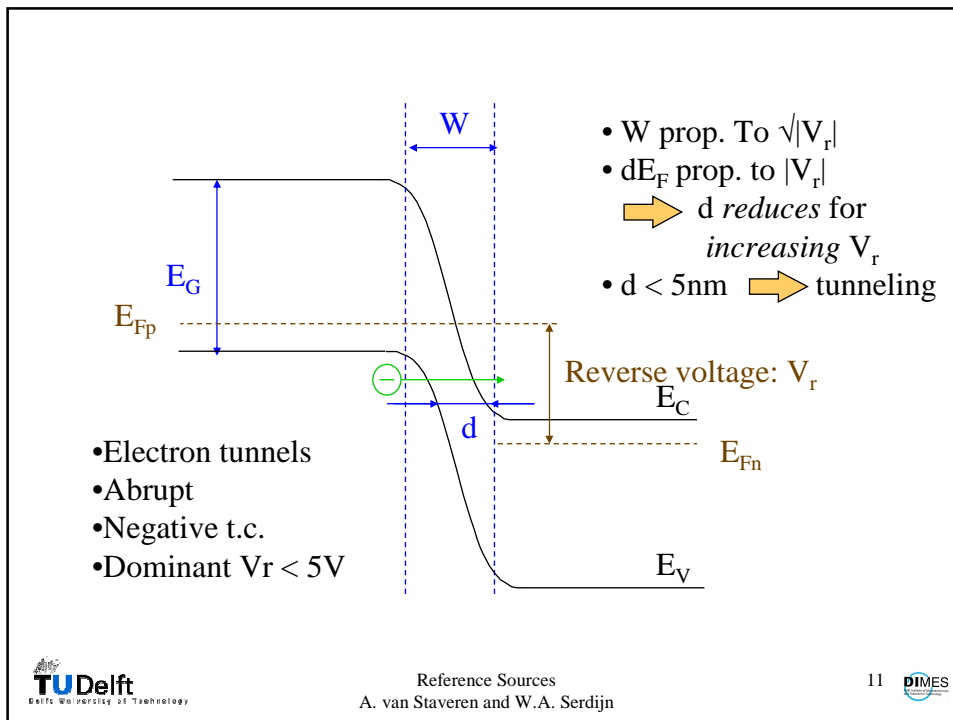Electron must gain energy equal to E_G for a transition from valence band to conduction band




Temperature compensation Zener diode

- Use a Zener diode with $V_{br} = 5 \dots 6V$ (5.6V)
 - ➔ Both Avalanche and Zener breakdown occur
 - ➔ Temperature behavior reduced
- Zener diode with avalanche in series with a forward biased junction

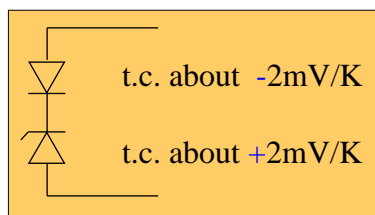


Requires 6..7V

Buried Zener diode

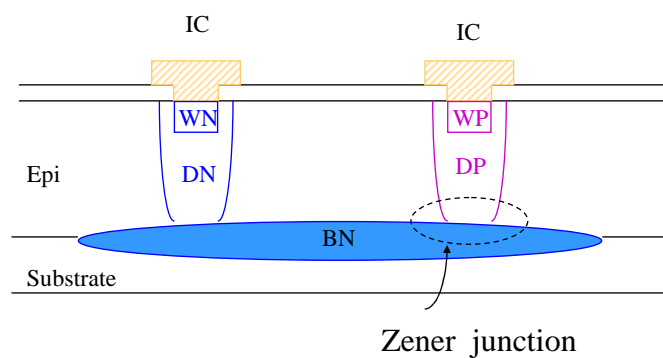

- No degradation due to surface effects
 - ➔ less 1/f - noise
 - ➔ less sensitive to stress

Forward biased junction

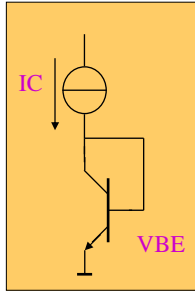

$$I_C = I_S \exp(qV_{BE} / kT)$$

$$I_C = \frac{qAn_i^2 \bar{D}}{N_B} CT^3 \exp[-E_G(T) / kT] \frac{kT}{q} \cdot \mu \rightarrow BT^n$$

($\eta = XTI = 4-n$)

$$I_{C0}(T/T_0)^\theta = C'(T/T_0)^\eta \exp\left[\frac{qV_{BE} - E_G(T)}{kT}\right]$$

$$V_{BE}(T) = \frac{E_G(T)}{q} - \left[\frac{E_G(T_0)}{q} - V_{BE}(T_0) \right] \frac{T}{T_0} + (\theta - \eta) \cdot \frac{kT}{q} \ln\left(\frac{T}{T_0}\right)$$


First-order approximation around T_0

$$V_{BE}(T) = \frac{E_G(T)}{q} - \left[\frac{E_G(T_0)}{q} - V_{BE}(T_0) \right] \frac{T}{T_0} + (\theta - \eta) \cdot \frac{kT}{q} \ln\left(\frac{T}{T_0}\right)$$

$$V_{BE}(T)_1 = \frac{E_G(T)}{q} - \left[\frac{E_G(T_0)}{q} - V_{BE}(T_0) \right] \frac{T}{T_0} + (\eta - \theta) \cdot \frac{kT}{q} \frac{T_0 - T}{T_0}$$

$$V_{BE}(T)_1 = V_{Geff} - \left[V_{Geff} - V_{BE}(T_0) \right] \frac{T}{T_0}$$

Taylor

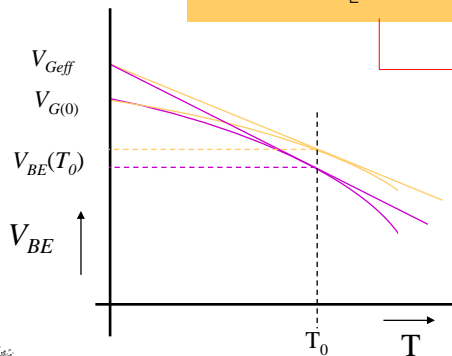

$$V_{Geff} = V_{G(0)} + (\eta - \theta)kT_0 / q$$

- V_{BE} has negative t.c.
- $V_{BE} \downarrow$ |t.c.| \uparrow
- V_{Geff} independent of V_{BE}

Example

Assume a transistor is biased at a **constant** current of $1 \mu\text{A}$.
 For the transistor the following parameters apply: $I_S = 18 \text{ aA}$,
 $X_{TI} = 3$ and $V_{G(0)} = 1.2\text{V}$.

What is the first-order temperature coefficient at $T_0 = 300\text{K}$?

$$V_{BE}(300\text{K}) = 640 \text{ mV}$$

$$V_{Geff} = 1.2\text{V} + (3-0) \cdot 25.8\text{mV} = 1.28\text{V} \quad (V_{Geff} = V_{G(0)} + (\eta-0)kT/q)$$



$$\text{t.c.} = -2.1 \text{ mV/K}$$

$$(\text{t.c.} = -[V_{Geff} - V_{BE}(T_0)]/T_0)$$

Biassing a BE-junction


- Bias current far below high-level injection ($I_C \ll I_{KF}$)
- Bulk resistances (made) negligible
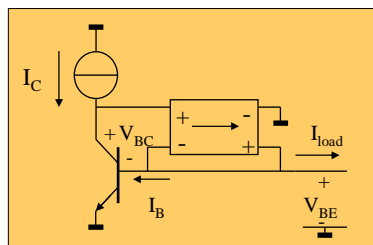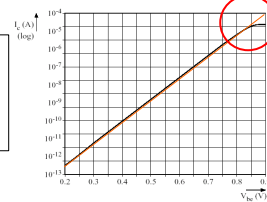
$$I_C = I_S \left[\exp(V_{BE} / V_T) - 1 \right] \left[1 - \frac{V_{BC}}{V_{AF}} - \frac{V_{BE}}{V_{AR}} \right]$$




- Nullor makes $V_{BC} = 0 \Rightarrow V_{AF}$
- Nullor supplies I_B and I_{load}
 - \Rightarrow Low beta no problem
 - $\Rightarrow V_{BE}$ is buffered
- VAR remains

Simplest implementation nullor ?

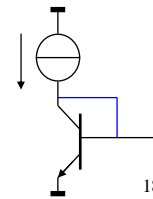

Noise of a BE junction

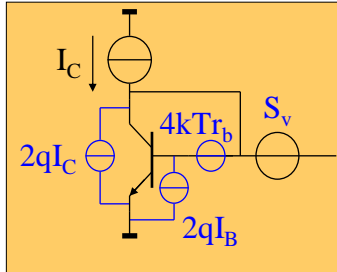

- S_v noise-power density spectrum [V^2/Hz]

$$S_v = 4kT \left(r_b + \frac{1}{2g_m} \right)$$


- Collector shot noise and thermal noise of the base resistance dominate

Assume $r_b = 150$, $I_C = 100 \mu A$ and $V_{BE} = 600 \text{ mV}$

$$\frac{1}{2g_m} = 130$$

$$S_v = 4kT \cdot 280 \Omega$$

Comparison

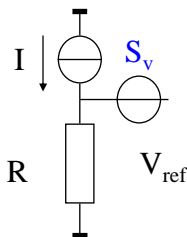


$$R = \frac{600 \text{ mV}}{100 \mu A} = 6000 \Omega$$

$$\Rightarrow S_v = 4kT \cdot 6000 \Omega$$

- Noise of a BE-junction is 20 times lower
- Output impedance is 25 times lower

Proportional To Absolute Temperature

- Difference of two junction voltages

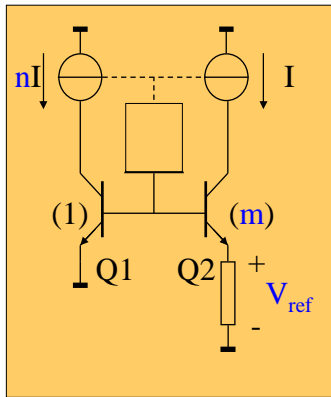

$$V_{\text{ref}} = V_{\text{BE1}} - V_{\text{BE2}}$$

$$= \frac{kT}{q} \ln(n m)$$

Example:


$$n=10 \Rightarrow V_{\text{ref}} = \frac{kT}{q} \ln(10)$$

$$m=1 \quad = T \cdot 198 \mu\text{V/K}$$

$$= 59.58 \text{ mV@300K}$$

Use as temperature sensor

Combination of a V_{BE} and V_{PTAT}

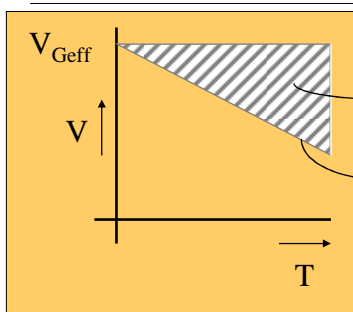

$$V_{\text{PTAT}} + V_{\text{BE}} \rightarrow V_{\text{Geff}}$$

V_{BE} has a *negative* t.c.

V_{PTAT} has a *positive* t.c. +

Sum can have *zero* t.c.




The Bandgap Reference

Question : What is a bandgap reference ?

**A VBE
plus a
VPTAT?!**



NO!

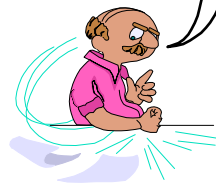

The bandgap reference

Relates output voltage to the bandgap voltage at 0K

$$V_{ref} = x \cdot \frac{E_G(0)}{q}$$

- Describe base-emitter voltage as:

$$V_{BE}(T) = V_{Geff} - \left[V_{Geff} - V_{BE}(T_0) \right] \frac{T}{T_0}$$


Use linear combination of base-emitter voltages

Linear combination of V_{BE} s


$$a_1 V_{BE1} = a_1 V_{Geff} - a_1 [V_{Geff} - V_{BE1}(T_0)] T / T_0$$

$$a_2 V_{BE2} = a_2 V_{Geff} - a_2 [V_{Geff} - V_{BE2}(T_0)] T / T_0 +$$
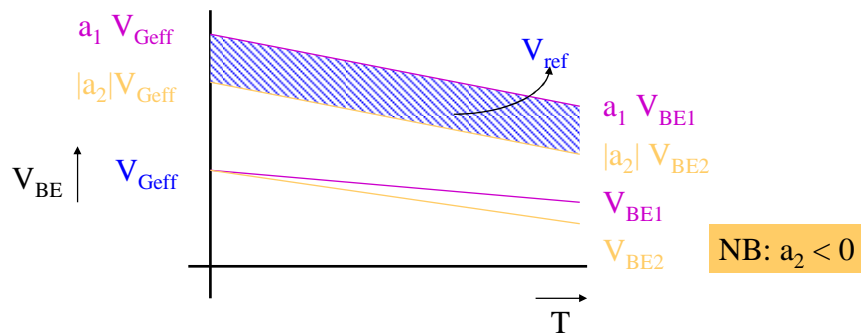
$$= (a_1 + a_2) V_{Geff} + 0 \cdot T / T_0$$



Bandgap Reference Example

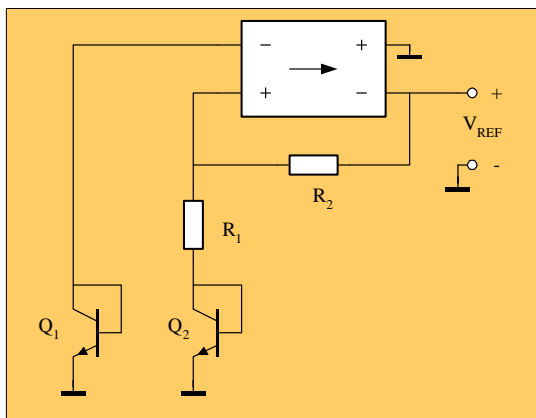

$$V_{REF} = a_1 V_{BE1} + a_2 V_{BE2}$$

$$\left. \begin{aligned} a_1 &= 1 + \frac{R_2}{R_1} \\ a_2 &= -\frac{R_2}{R_1} \end{aligned} \right\} a_1 + a_2 = 1$$

$$V_{REF} = (a_1 + a_2) V_{Geff} = V_{Geff}$$



But also: $V_{R1} = V_{BE2} - V_{BE1} = V_{PTAT}$ ➔

$$V_{REF} = V_{BE2} + A_U V_{PTAT}$$

Accuracy of V_{ref}

a_1, a_2 : rely on matching


V_{BE1}, V_{BE2} : several parameters are important

- I_{S1}, I_{S2} : matching and absolute accuracy
- I_{C1}, I_{C2} : use accurate bias techniques
- θ_1, θ_2
- E_G, η, V_{AR} : given by process, good characterization required

Key parameters of device : E_G, V_{AR}, I_S, η

For accurate design these should be well-known !


Noise performance of Bandgap Reference

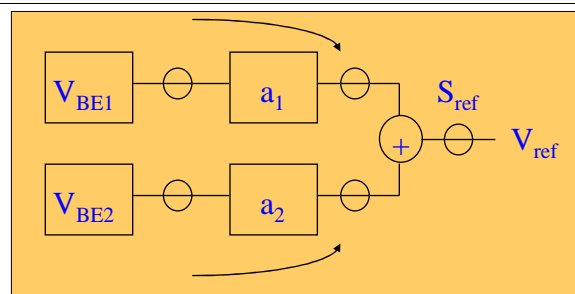


- Noise of the bandgap reference is a weighted sum of the noise contributions of the V_{BE} s

S_{ref} is inversely proportional to the current consumption

Power-Supply Rejection Ratio

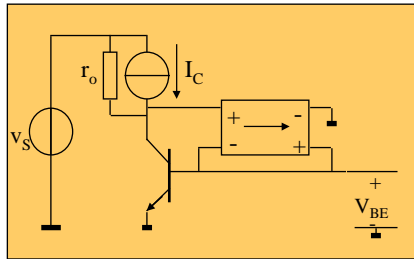

r_o due to Early effect

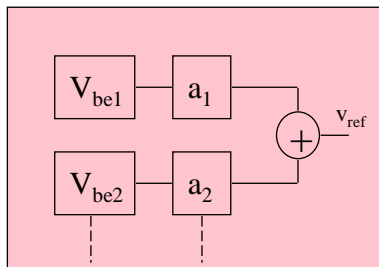

$$PSRR = 20 \cdot 10 \log \left(\frac{V_T V_{ref}}{V_{AF} V_S} \right)$$

unit: dB


Design example 1V, 100 μ A, BGR

(Second-order compensated)

- Describe V_{BE} s with a second-order polynomial


$$V_{BE}(T) = V_{BE}(T_0) + x_1 (T-T_0) + x_2 (T-T_0)^2$$

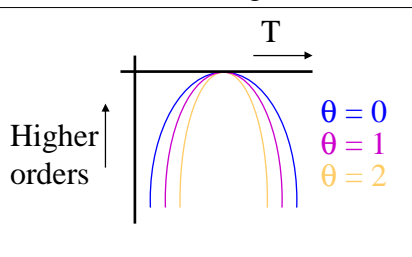- Second (higher) order terms can only be changed by θ



- Again use linear combination
- Two V_{BE} s for second-order compensation
- Different V_{BE} s (1 order)
- Different θ 's (1 order)


Block Schematic

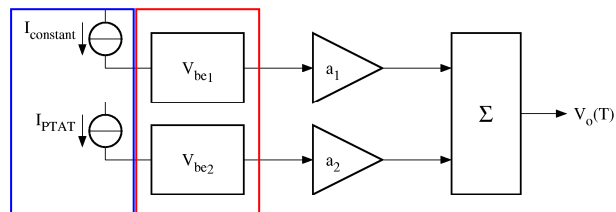

Different V_{BE} 's (1 order)
 Different θ 's (1 order)

$$V_{ref} = 200 \text{ mV}$$




First implementation step

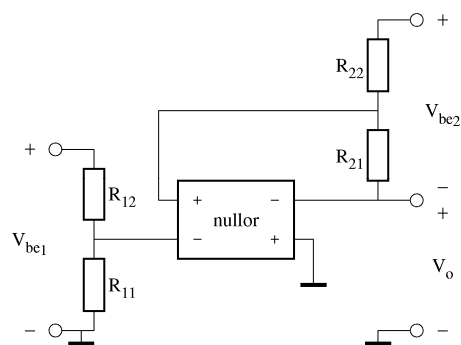

Both V_{BE} 's have negative t.c. \Rightarrow scale factors must have opposite sign

- a_1 positive
- a_2 negative



Implementation of VBE generators

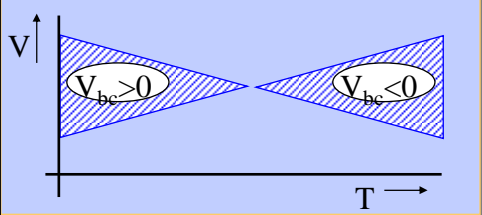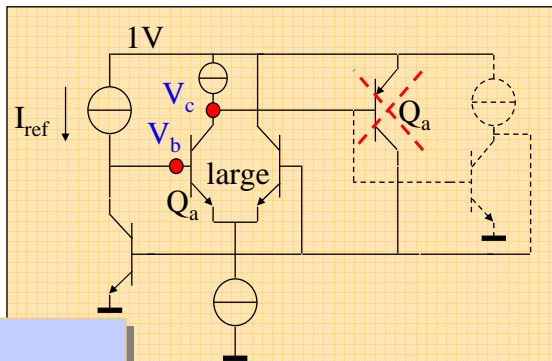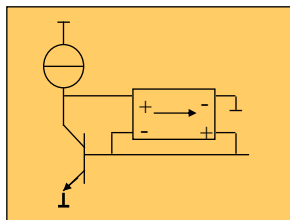

At low temperatures Q_a saturates $\Rightarrow I_B$ of Q_a degrades I_{ref}

\Rightarrow Use cascade of NPNs

Implementation of the adder

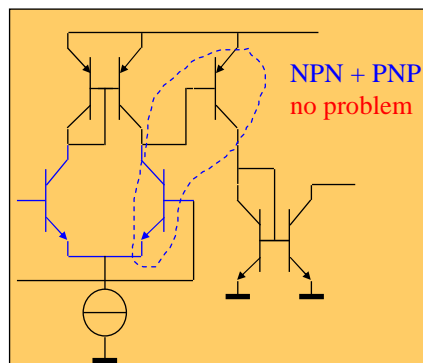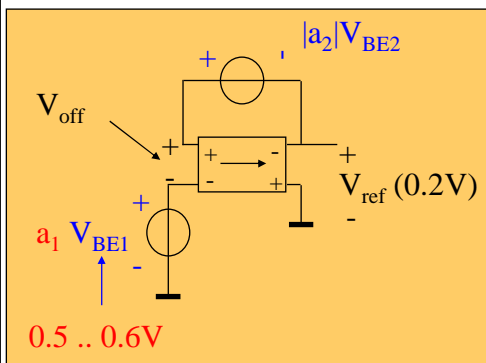

- V_{off} in series with V_{ref}
- Low voltage level at input



- Use differential input stage
- Use sized-emitter transistors



