

# *Sequential Logic Synthesis*

This presentation can be used for non-commercial purposes  
as long as this note and the copyright footers are not  
removed

© Giovanni De Micheli – All rights reserved

# Module 2

---



- Objective
  - Structural representation of sequential circuits
  - Retiming
  -

# Structural model for sequential circuits

---

- Synchronous logic network
  - Variables
  - Boolean equations
  - Synchronous delay annotation
- Synchronous network graph
  - Vertices  $\leftrightarrow$  equations  $\leftrightarrow$  I/O, gates
  - Edges  $\leftrightarrow$  dependencies  $\leftrightarrow$  nets
  - Weights  $\leftrightarrow$  synchronous delays  $\leftrightarrow$  registers

# Example

 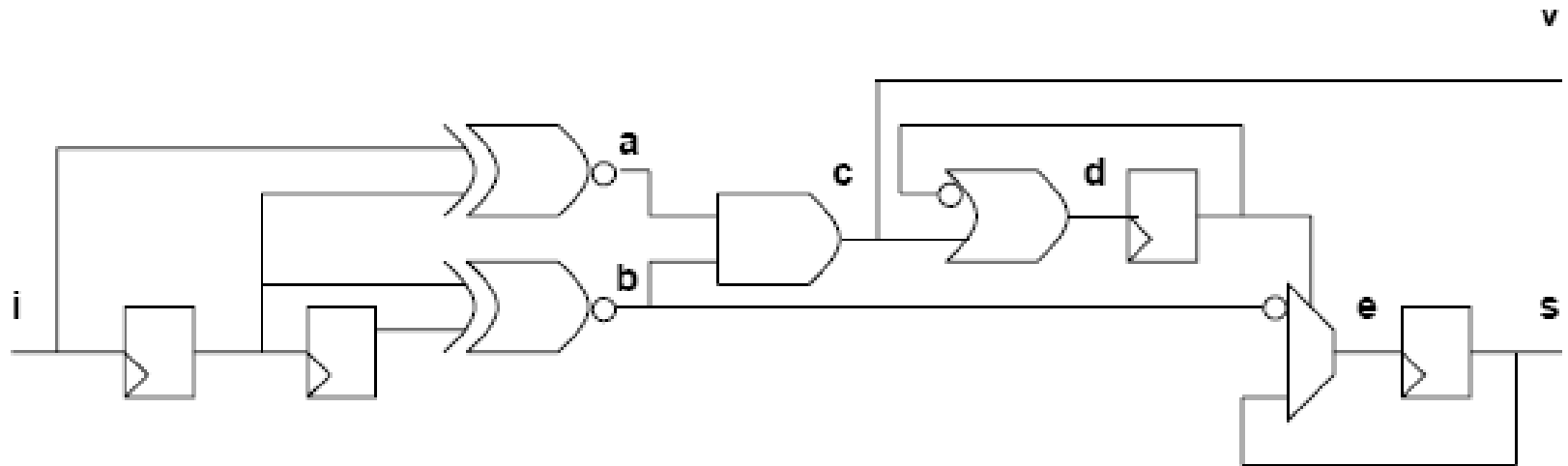


# Approaches to sequential synthesis


---

- Optimize combinational logic only
  - Freeze circuit at register boundary
  - Modify equation and network graph topology
- Retiming
  - Move register positions. Change weights on graph
  - Preserve network topology
- Synchronous transformations
  - Blend combinational transformations and retiming
  - Powerful, but complex to use


# Example of local retiming

 


(a)

 

(c)

 

(b)

 

(d)

# Retiming

---

- Global optimization technique
- Change register positions
  - Affects area:
    - Retiming changes register count
  - Affects cycle-time
    - Changes path delays between register pairs
- Retiming algorithms have polynomial-time complexity

# Retiming assumptions

---

- Delay is constant at each vertex
  - No fanout delay dependency
- Graph topology is invariant
  - No logic transformations
- Synchronous implementation
  - Cycles have positive weights
    - Each feedback loop has to be broken by at least one register
  - Edges have non-negative weights
    - Physical registers cannot anticipate time
- Consider topological paths
  - No false path analysis




# Retiming

---

- Retiming of a vertex  $v$ 
  - Integer  $r_v$
  - Registers moved from output to input –  $r_v$  positive
  - Registers moved from input to output –  $r_v$  negative
-


# Example 9.3.4

Original graph

 

Delay: 24


Retimed graph

 

Delay: 13
 
# Definitions and properties

- Definitions:
  - $(v_i, \dots, v_j)$  path from  $v_i$  to  $v_j$
  - $w(v_i, \dots, v_j)$  weight on path from  $v_i$  to  $v_j$
  - $d(v_i, \dots, v_j)$  combinational delay on path from  $v_i$  to  $v_j$
- Properties:
  - Retiming of an edge  $(v_i, v_j)$ 
    - $\hat{w}_{ij} = w_{ij} + r_j - r_i$
  - Retiming of a path  $(v_i, \dots, v_j)$ 
    - $\hat{w}(v_i, \dots, v_j) = w(v_i, \dots, v_j) + r_j - r_i$
  - Cycle weights are invariant



# Legal retiming


- Clock period  $\varphi$
- A retiming vector is legal if:
  - No edge weight is negative
    - $\hat{w}_{ij} (v_i, v_j) = w_{ij} (v_i, v_j) + r_j - r_i \geq 0$  for all  $i, j$
  - Each path  $(v_i, \dots, v_j)$  with  $d(v_i, \dots, v_j) > \varphi$  has at least one register:
    - $\hat{w}(v_i, \dots, v_j) = w(v_i, \dots, v_j) + r_j - r_i \geq 1$  for all  $i, j$
  - Equivalently, each combinational path delay is less than  $\varphi$

# Refined analysis

---

- Least-register path
  - $W(v_i, v_j) = \min w(v_i, \dots, v_j)$  over all paths between  $v_i$  and  $v_j$
- Critical delay:
  - $D(v_i, v_j) = \max d(v_i, \dots, v_j)$  over all paths between  $v_i$  and  $v_j$   
with weight  $W(v_i, v_j)$
- There exist a vertex pair  $(v_i, v_j)$  whose delay  $D(v_i, v_j)$  bounds the cycle time

# Example 9.3.9

 

•Vertices:  $v_a, v_e$

•Paths:  $(v_a, v_b, v_c, v_e)$  and  $(v_a, v_b, v_c, v_d, v_e)$

• $W(v_a, v_e) = 2$

• $D(v_a, v_e) = 16$

Maximum delay on path with minimum register count

# Other problems related to retiming

---

- Retiming pipelined circuits
  - Balance pipe stages by using retiming
  - Trade-off latency versus cycle time
- Peripheral retiming
  - Use retiming to move registers to periphery of a circuit
  - Restore registers after optimizing combinational logic
- Wire pipelining
  - Use retiming to pipeline interconnection wires
  - Model sequential and combinational macros
  - Consider wire delay and buffering

# Summary of retiming

---

- Sequential optimization technique for:
  - Cycle time or register area
- Applicable to
  - Synchronous logic networks
  - Architectural models of data paths
    - Vertices represent complex (arithmetic) operators
  - Exact algorithm in polynomial time
- Extension and issues
  - Delay modeling
  - Network granularity