

# Elektrische Aandrijvingen

WTB

Lokatie/evenement

P.BAUER

February 22, 2013



1

# Transformer

- AC circuits
- Isolate circuits
- Voltage or current higher/lower



# Concept

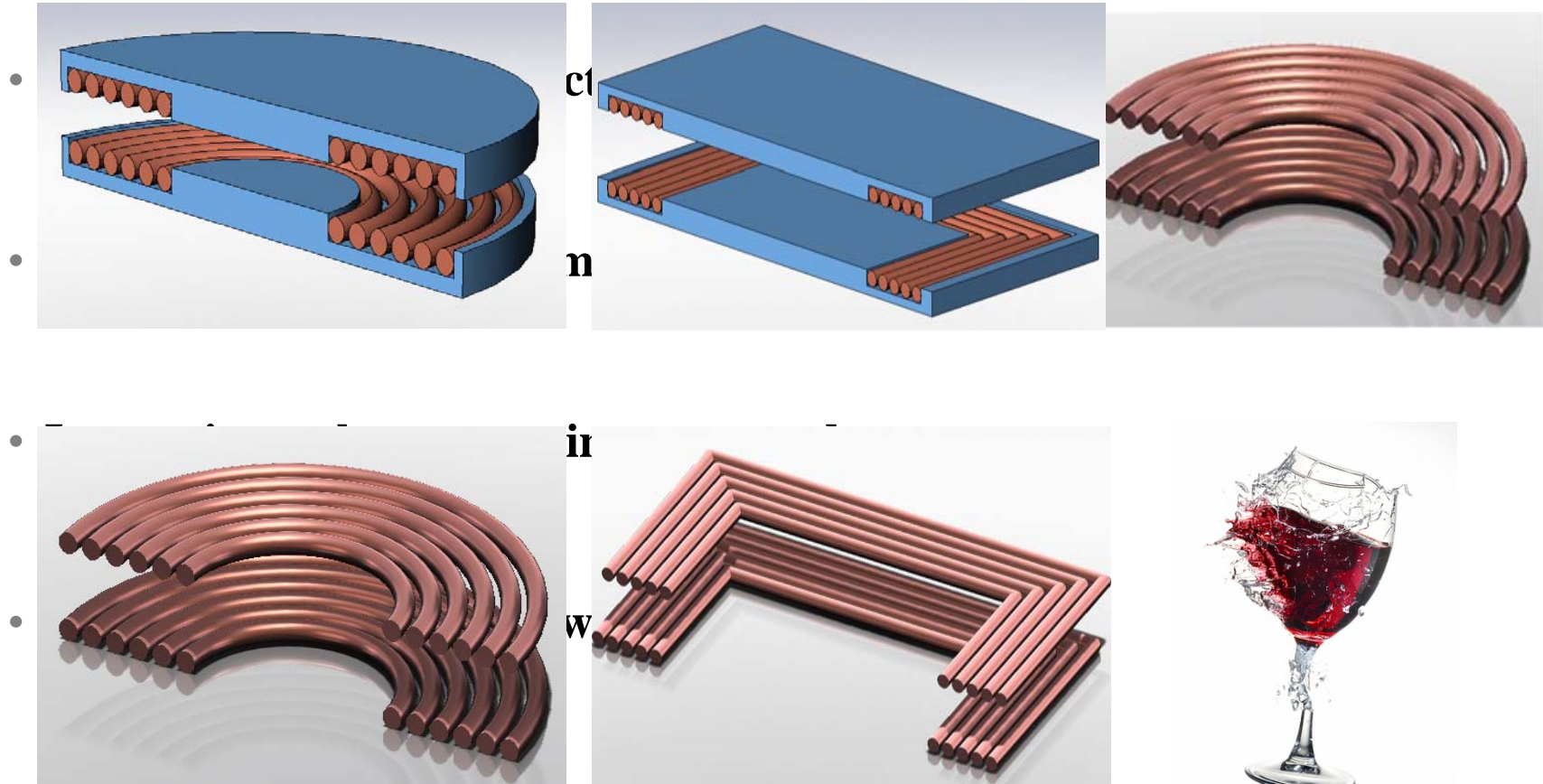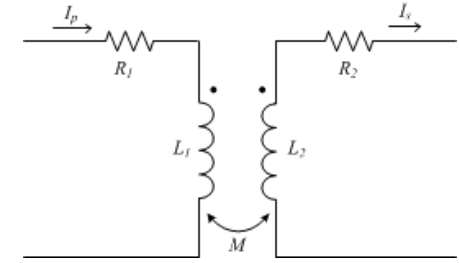

# Voltage induced in coil

- $E = 4.44 f N \Phi_{\max}$

- $I_m = E/X_m$

- $E_g = 4,44 f N \Phi$

FIGURE 9-1 a. A voltage is induced in a coil when it links a variable flux  
 . b. A sinusoidal flux induces a sinusoidal voltage.

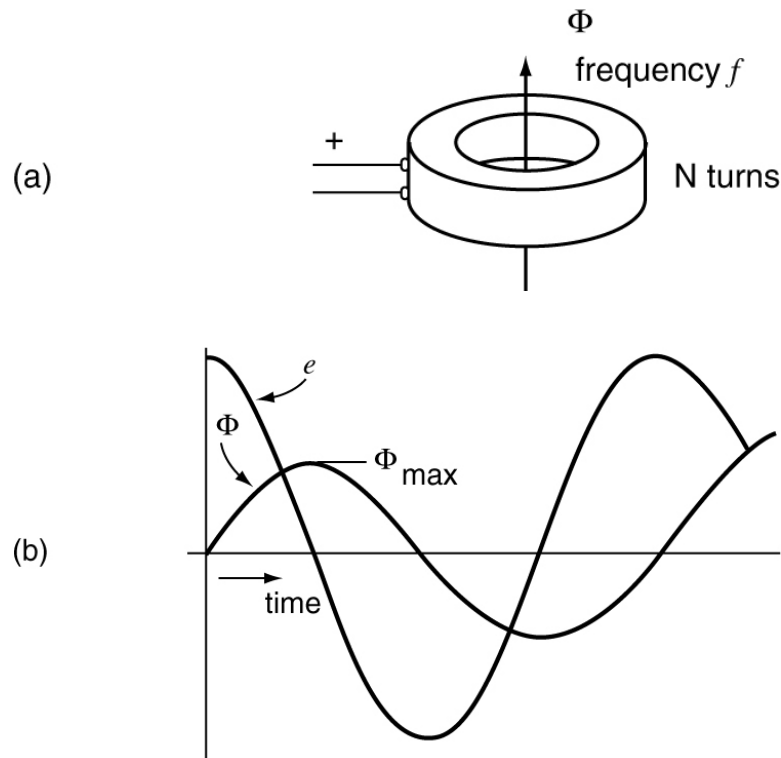


FIGURE 9-2 a. The voltage  $E$  induced in a coil is equal to the applied voltage  $E_g$ .  
 b. Phasor relationships among  $E_g$ ,  $E$ ,  $I_m$ , and  $\Phi$ .


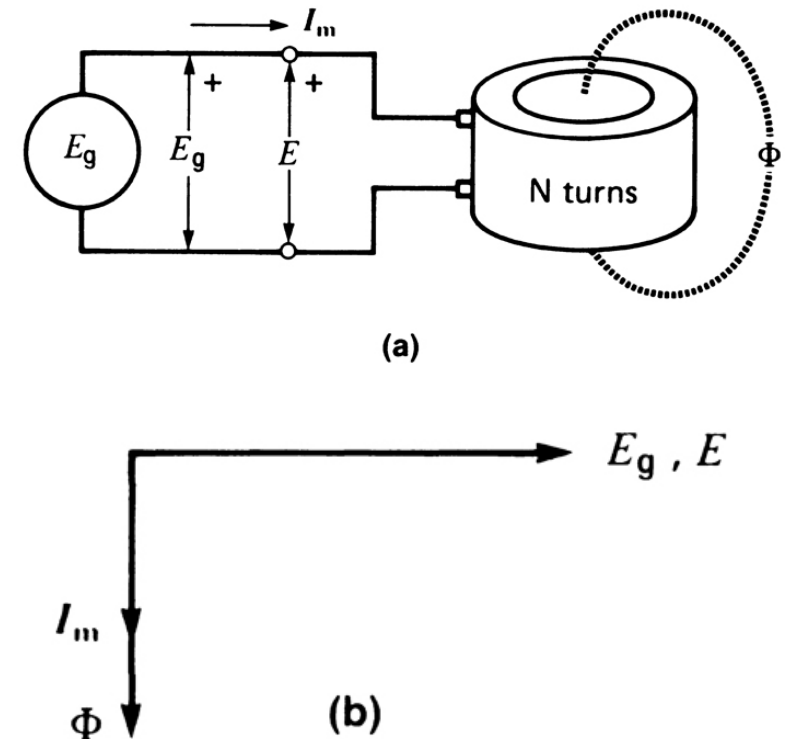
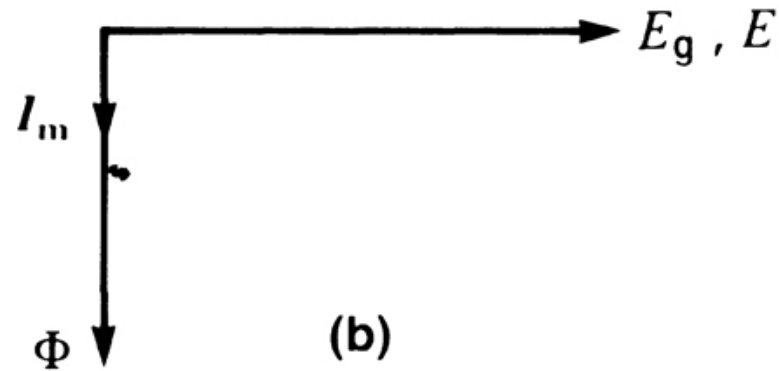


FIGURE 9-3 a. The flux in the coil remains constant so long as  $E_g$  is constant. b. Phasor relationships.

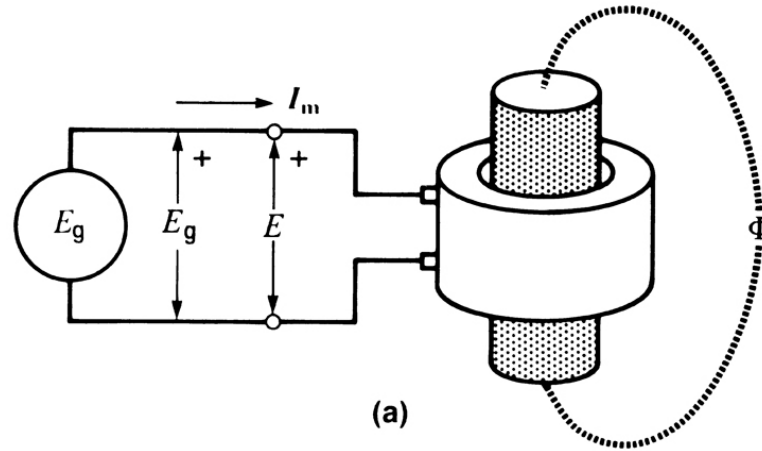

# Elementary transformer

FIGURE 9-4 Voltage induced in a secondary winding. Mutual flux is  $\Phi_{m1}$ ; leakage flux is  $\Phi_{f1}$ .


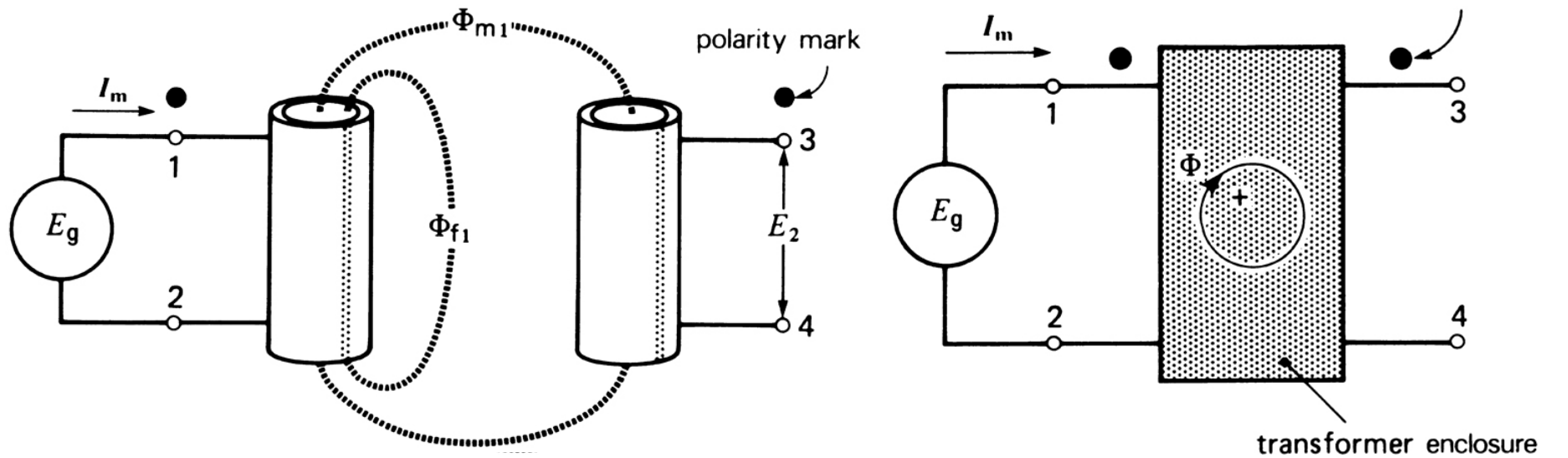


FIGURE 9-7 a. Instantaneous polarities when the magnetizing current is increasing. b. Phasor relationship.

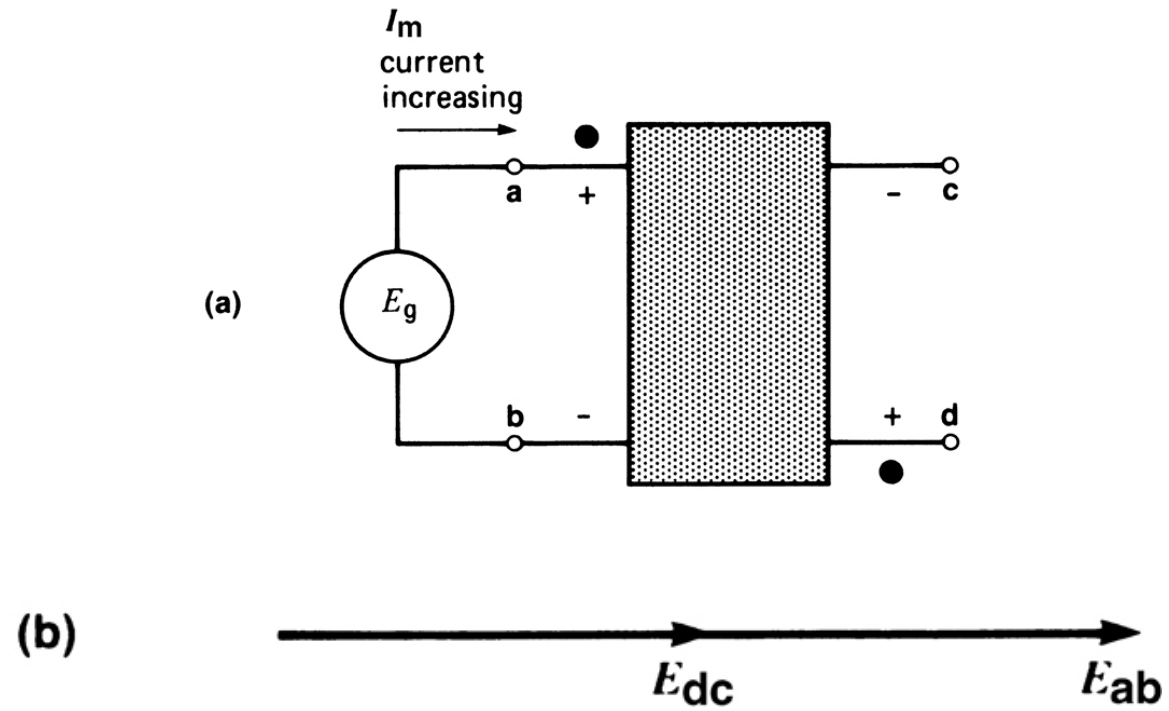

# Ideal Transformer

FIGURE 9-8 a. The ideal transformer at no-load. Primary and secondary are linked by a mutual flux  $\Phi_m$   
 b. Phasor relationships at no-load.



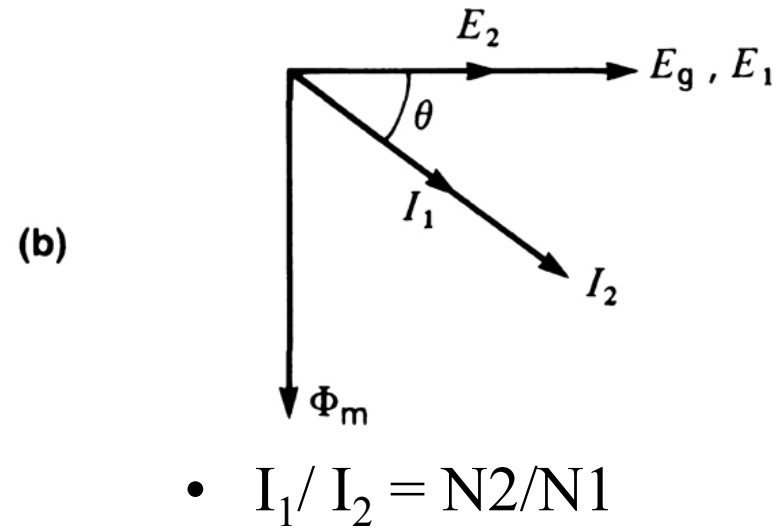
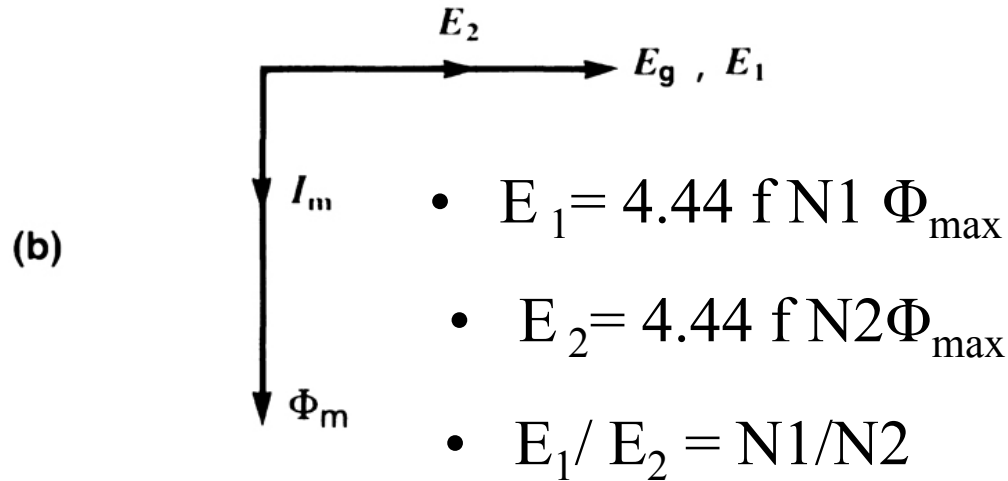
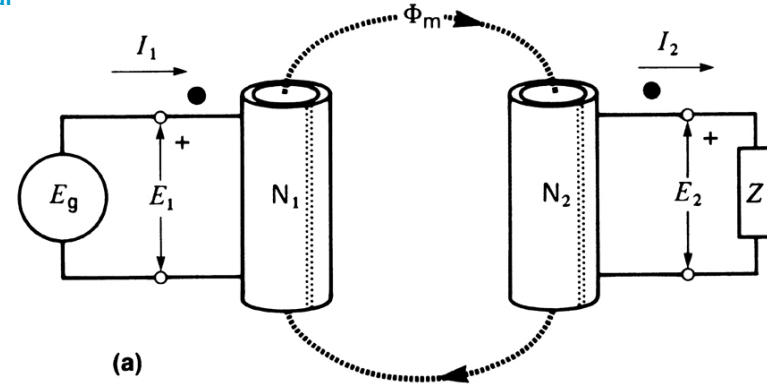


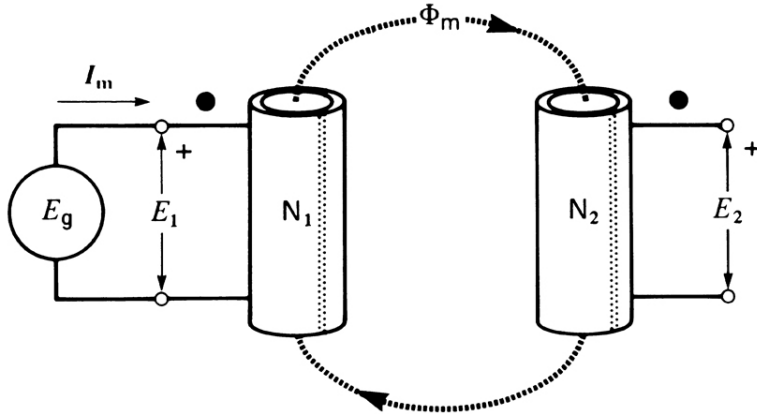

FIGURE 9-10 a. See Example 9-4. b. Phasor relationships.

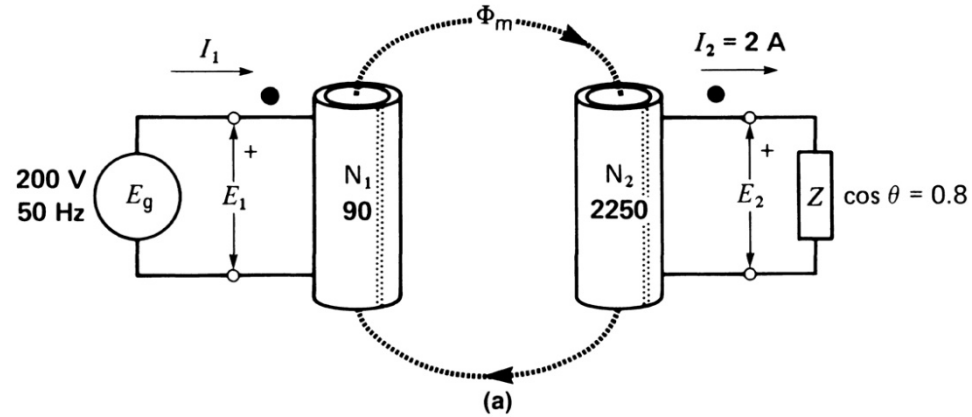- 90 turns, 2250 turns, 200 V , 50 Hz , load 2A



- $a = N_1/N_2 = 1/25$
- $I_1 = 25 \times 2 = 50 \text{ A}$

