

Elektrische Aandrijvingen

WTB

Lokatie/evenement

P.BAUER

March 5, 2009

1

Figure 16.1 Schematic diagram and cross-section view of a typical 500 MW synchronous generator and its 2400 kW dc exciter. The dc exciting current I_x (6000 A) flows through the commutator and two slip-rings. The dc control current I_c from the pilot exciter permits variable field control of the main exciter, which, in turn, controls I_x .



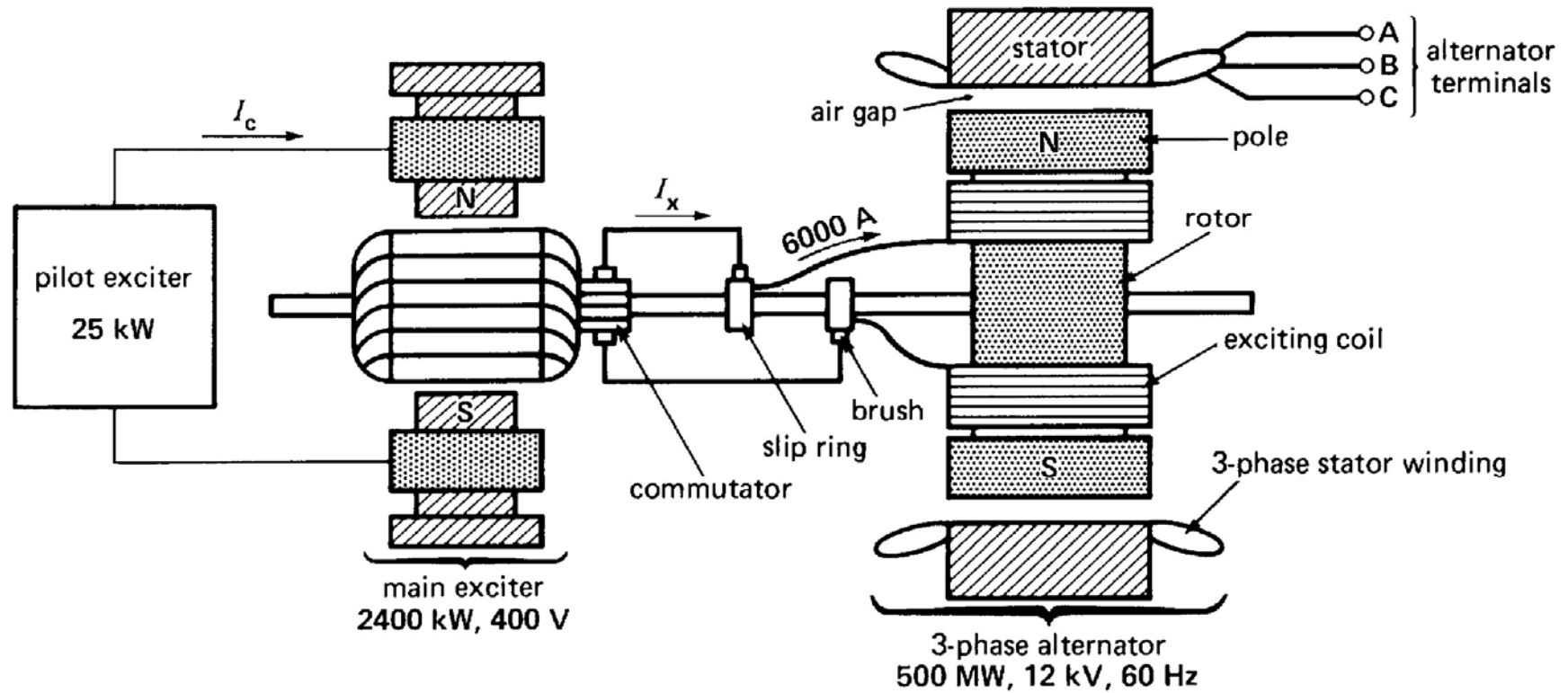
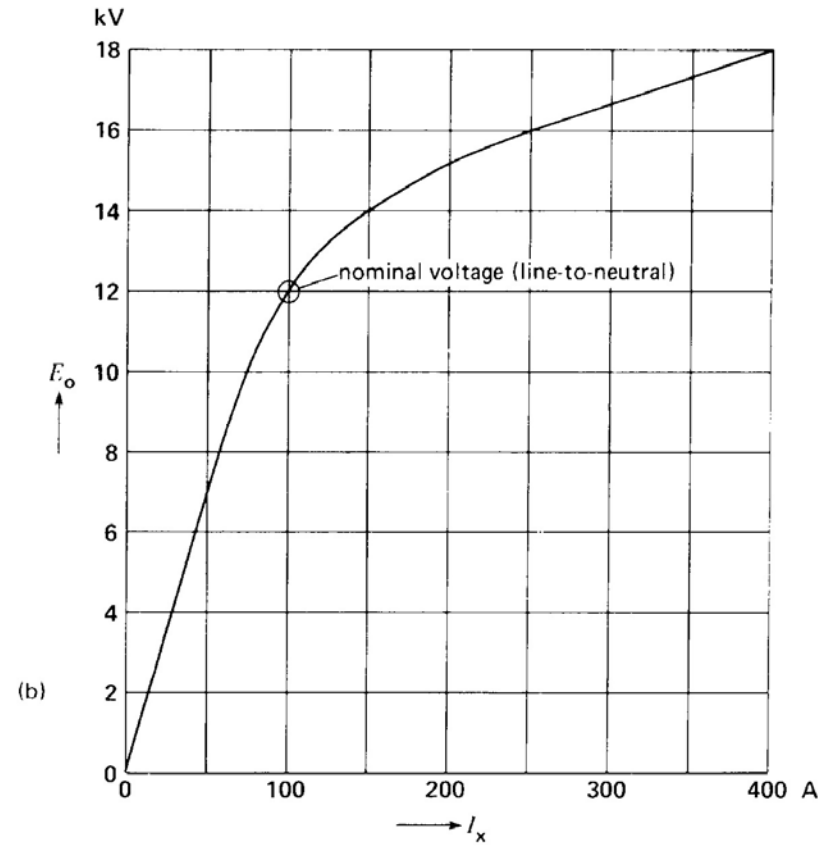



Figure 16.13a Generator operating at no-load.

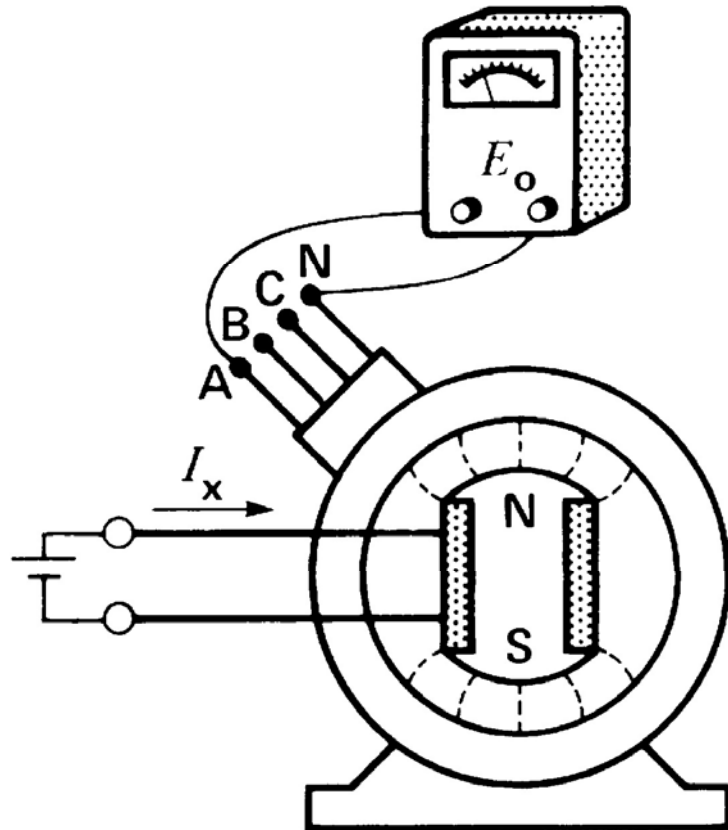

Synchronous generator

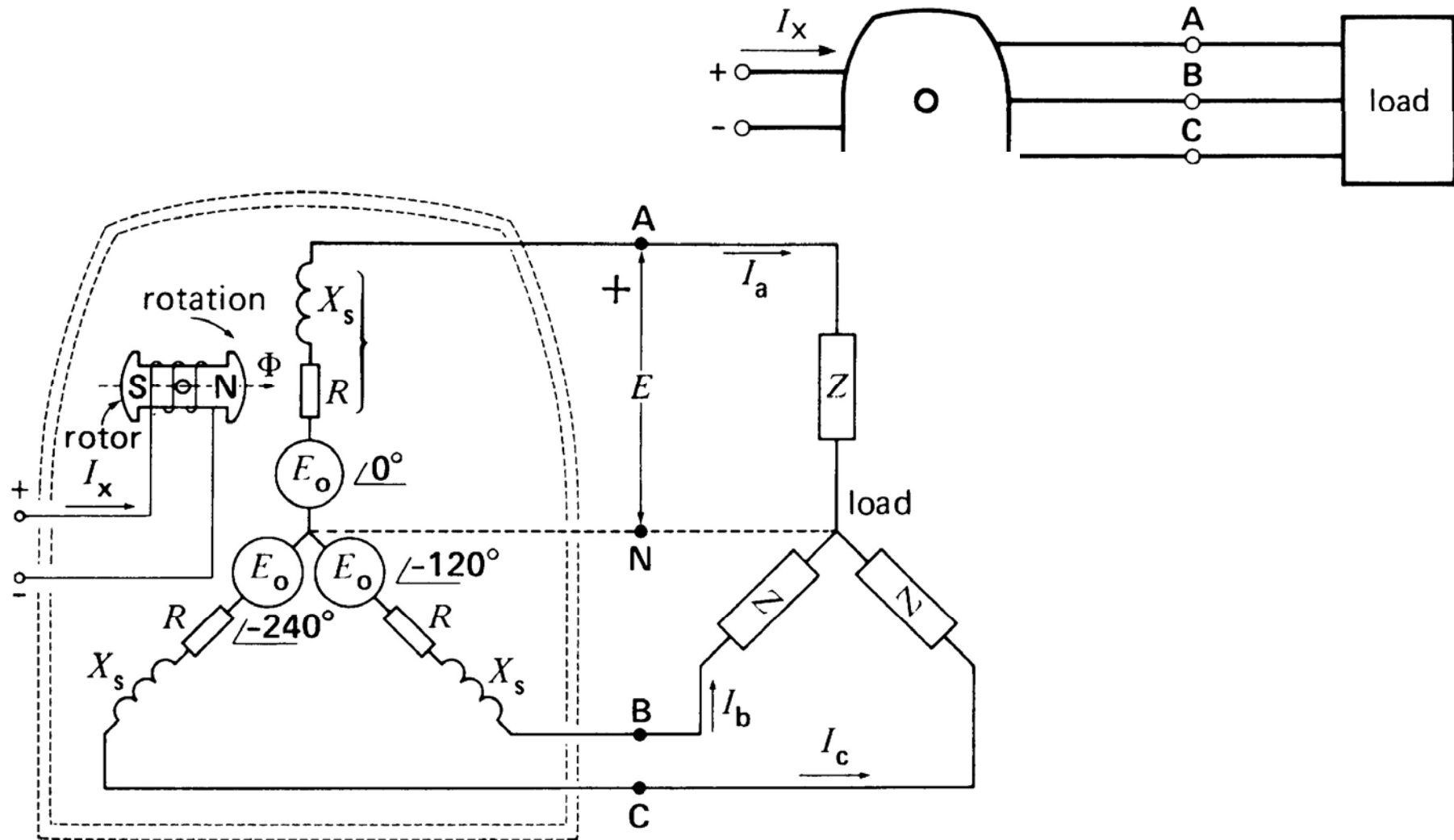


Determining the value of x_s

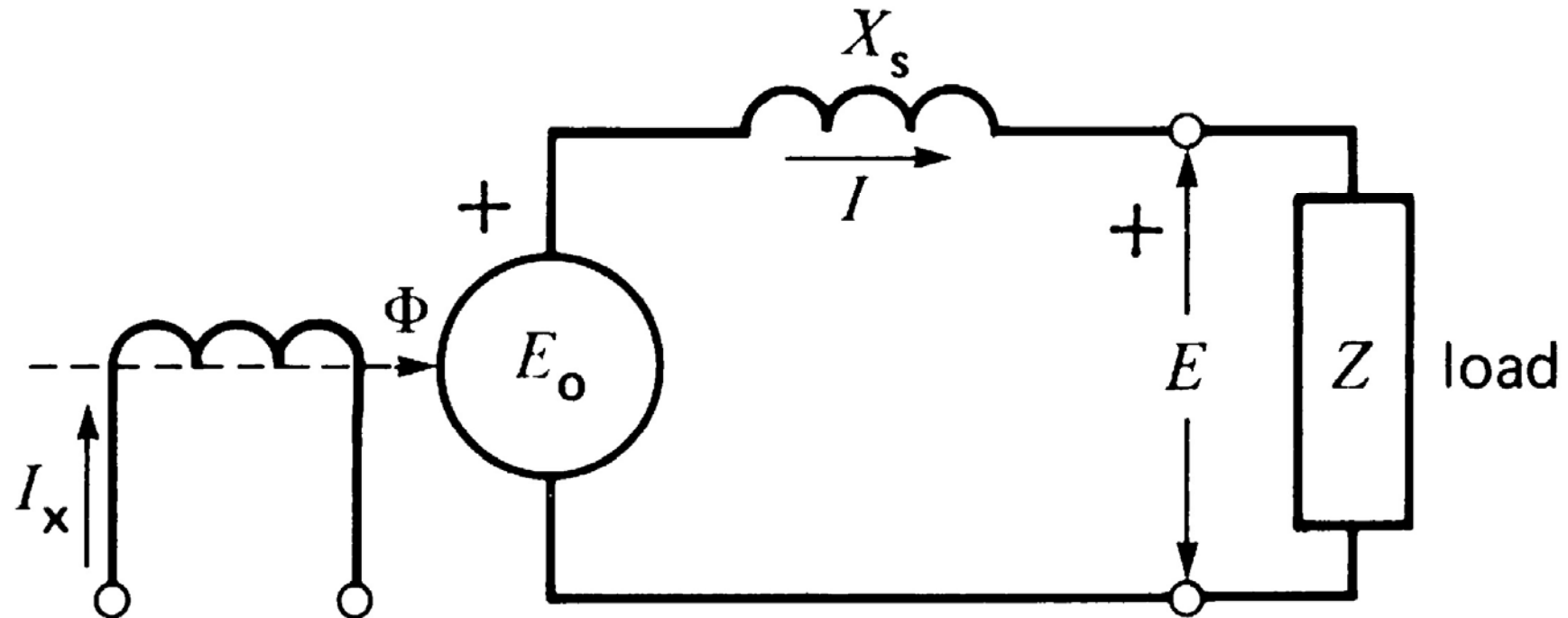


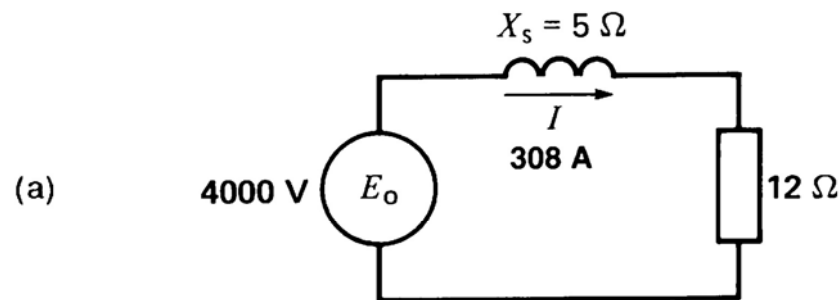Example 16.2



- 3 phase, SG produces an open circuit line voltage of 6928 V when the dc exc. current is 50 A. The AC terminals are short circuited and line currents are 800A.
- Calculate synchronous reactance
- Terminal voltage if three R 12 ohm are connected



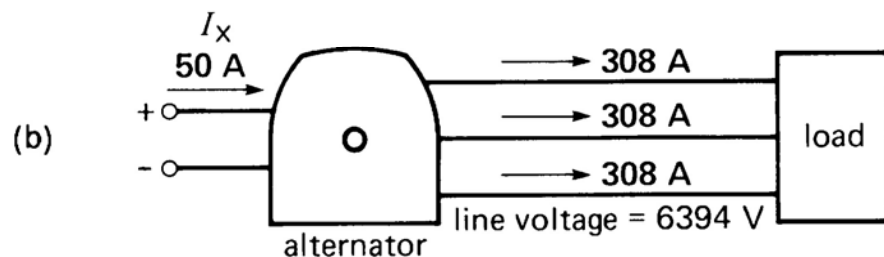- $E_o = E_L / \text{Sqrt}(3) = 4000 \text{ V}$
- $X_s = E_o / I = 4000/800$
- $Z = \text{Sqrt}(R^2 + X_s^2)$





SG under load

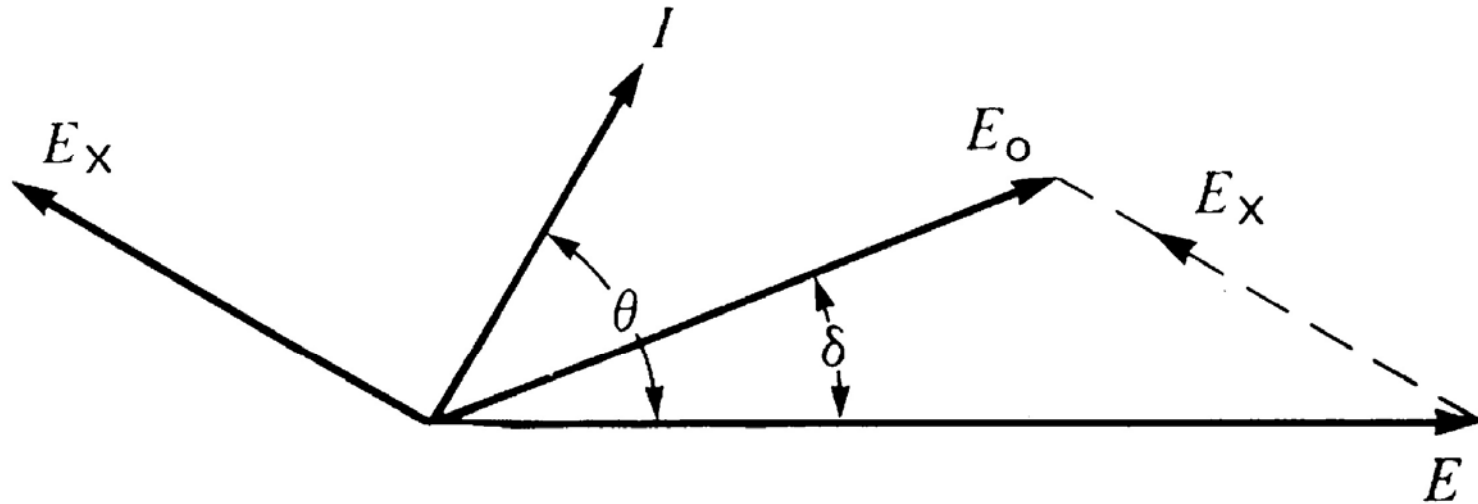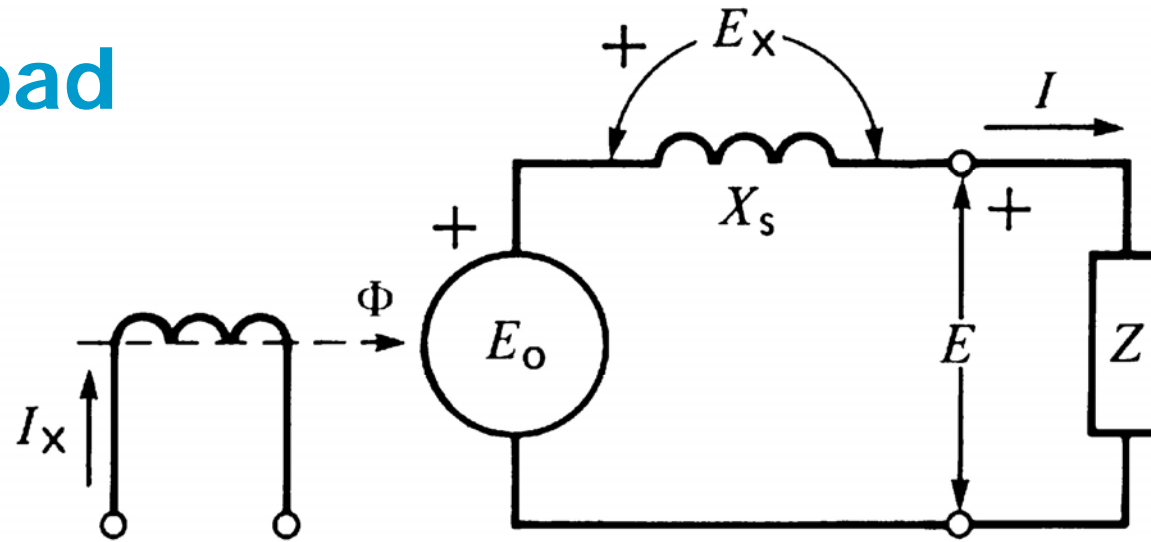

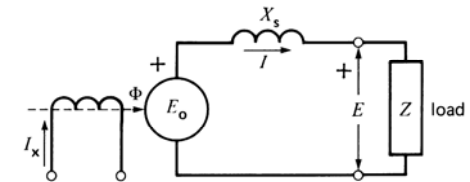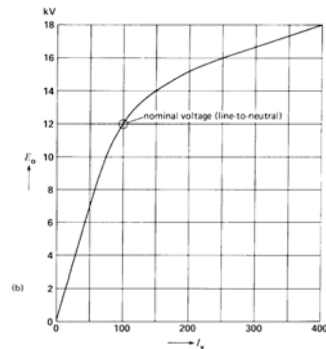Example 16.4

- 36 MVA, 20,8 kV 3phase, synchr. Reactance 9 ohm, the no load saturation curve is given. Terminal voltage remain 21kV., calculate the exciting current and draw the phasor diagram at:

- No load
- Resistive load of 36 MW
- Capacitive load of 12 MVar



- $E = 20,8 / \text{Sqrt}(3) = 12\text{kV}$

- $E_0 = E$



- $I_s = 100$

E, E_0
12 kV

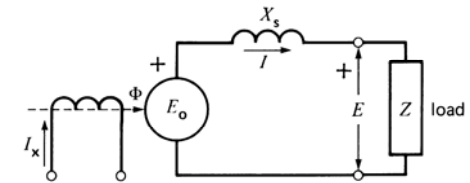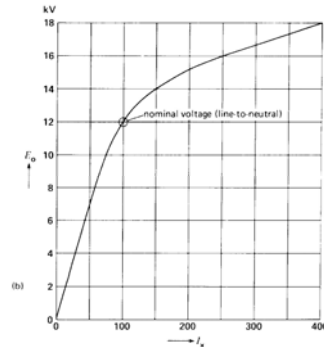
Example 16.4

- 36 MVA, 20,8 kV 3phase, synchr. Reactance 9 ohm, the no load saturation curve is given. Terminal voltage remain 21kV., calculate the exciting current and draw the phasor diagram at:

- No load
- **Resistive load of 36 MW**
- Capacitive load of 12 MVAR





- $P = 36 / 3 = 12\text{MW}$
- $I = P/E = 1000 \text{ A}$
- $E_x = j I X_s$
- $E_o =$
- $I_s = 100$

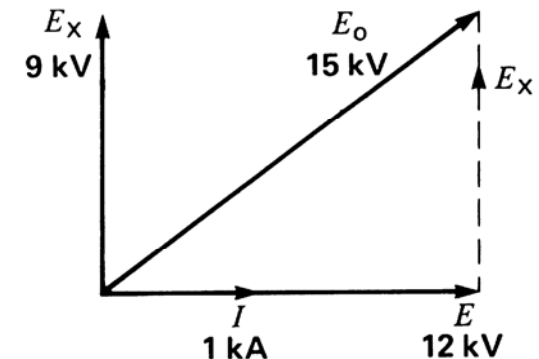

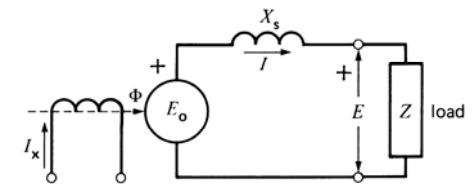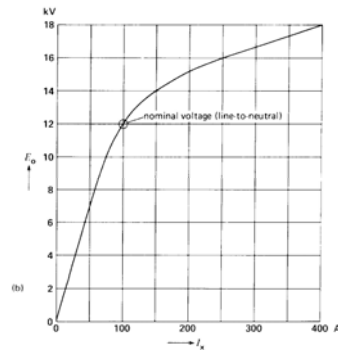Example 16.4

- 36 MVA, 20,8 kV 3phase, synchr. Reactance 9 ohm, the no load saturation curve is given. Terminal voltage remain 21kV., calculate the exciting current and draw the phasor diagram at:

- No load
- Resistive load of 36 MW
- **Capacitive load of 12 MVAr**



- $Q = 12 / 3 = 12\text{MVAr}$
- $E_x = j I X_s$
- $I_s = 70\text{A}$
- $I = Q/E = 333\text{A}$
- $E_o =$


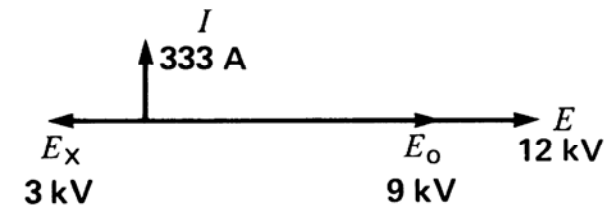


Figure 16.23 Regulation curves of a synchronous generator at three different load power factors.

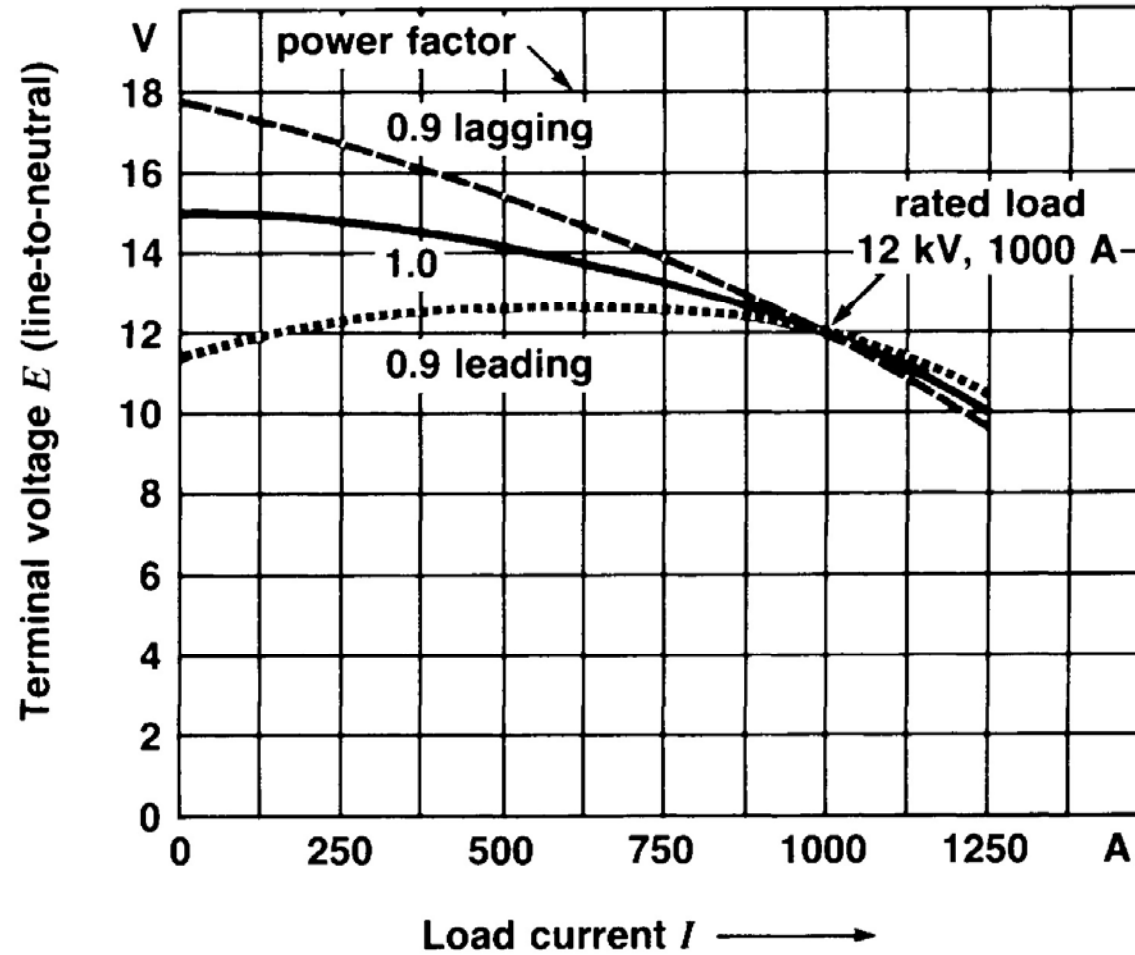


Synchronization

- The generator frequency is equal to system frequency
- Voltage equal
- Voltage in phase
- Phase sequence the same

Synchronous generator on an infinite bus

- Imposes voltage and frequency
- The exciting current
- Mechanical torque

Figure 16.26a Generator floating on an infinite bus.


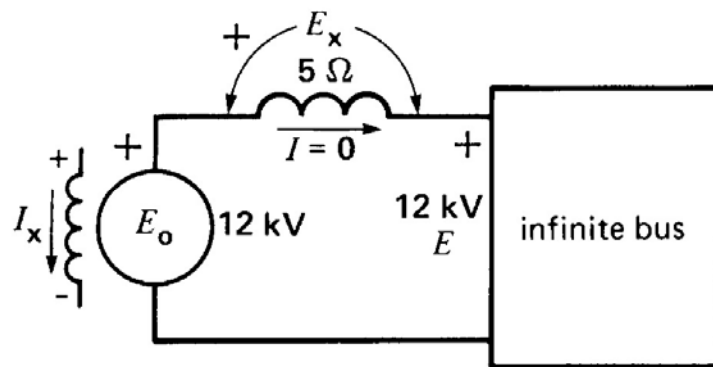


Synchronous generator on an infinite bus

- Increase the exciting current

- $E_x = E_0 - E$
- $I = (E_0 - E) / X_s$



Figure 16.26b Over-excited generator on an infinite bus.

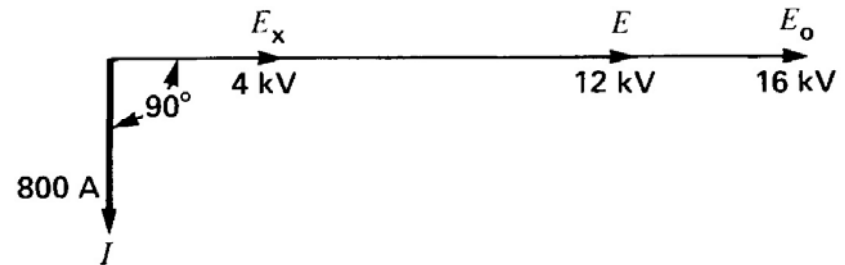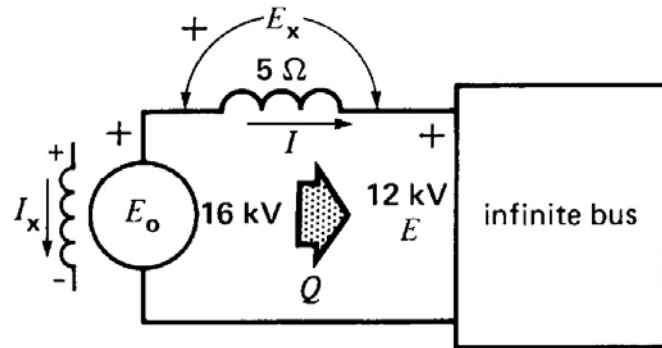

Synchronous generator on an infinite bus


- Decrease the exciting current

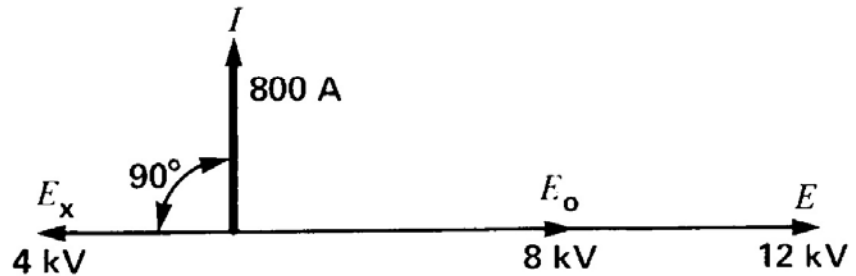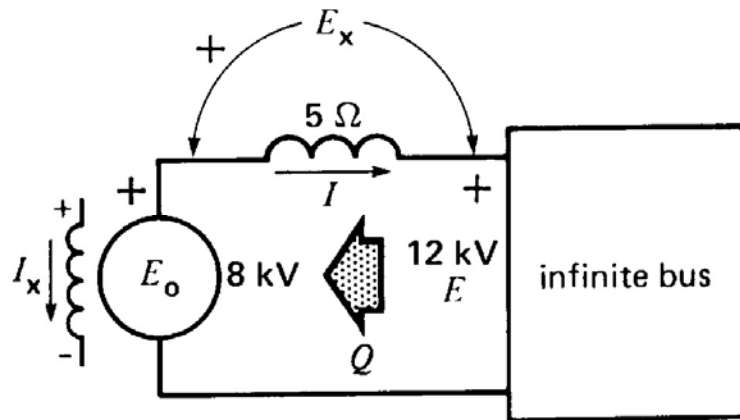- $E_x = E_0 - E$
- $I = (E_0 - E) / X_s$




Effect of varying the mechanical torque

- $E_x = E_0 - E$

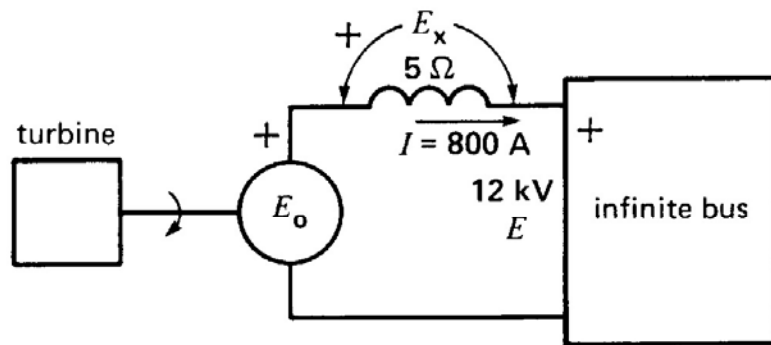

(a)

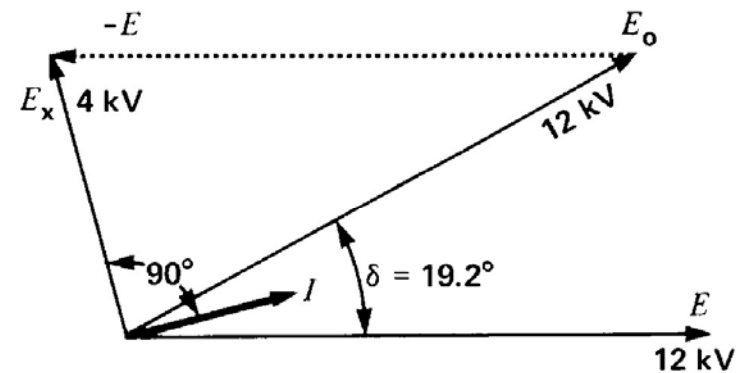


(b)


- Rotor accelerates, angle σ increases, electrical power too
- Electrical power = Mechanical power

Effect of varying the mechanical torque

- $E_x = E_0 - E$

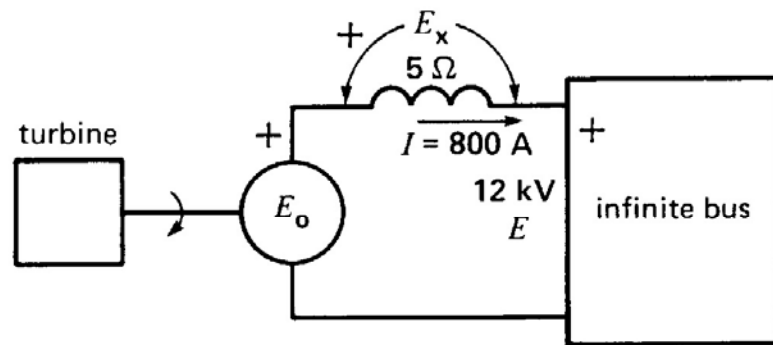

(a)

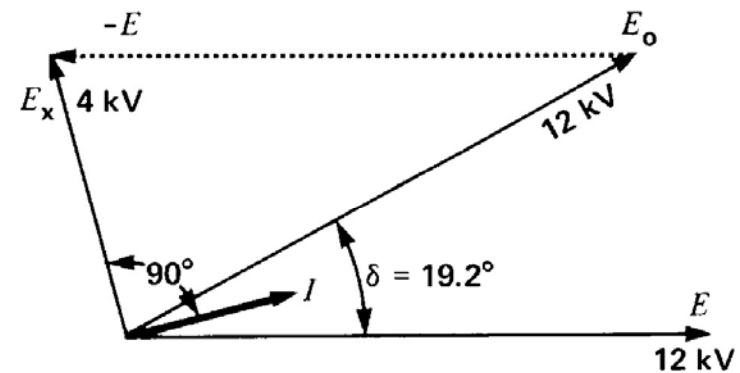



(b)

- Difference of potential is created when 2 equal voltages are out of the phase
- Increased phase angle = increased I = incr. active power

Figure 16.28a The N poles of the rotor are lined up with the S poles of the stator.

Physical interpretation

$$\delta = p \alpha / 2$$

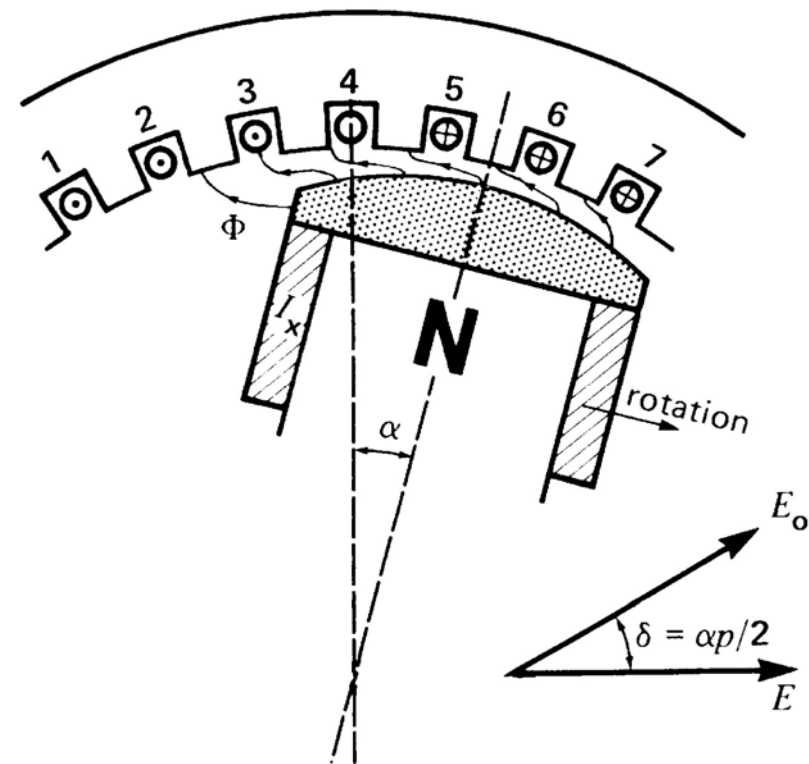
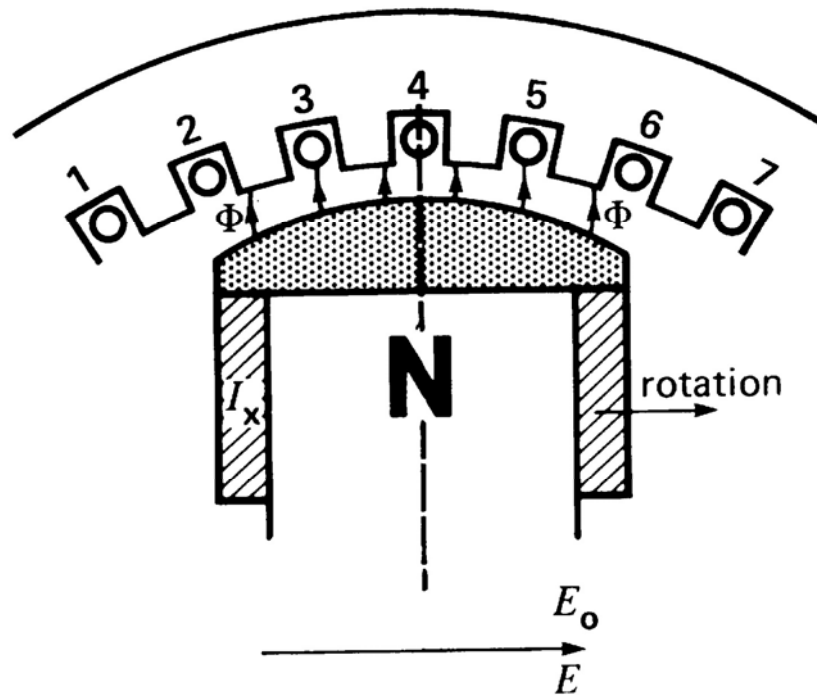


Example 16.6



- The rotor poles of an 8 pole SG shift by 10 mechanical degrees from no load full load
- Calculated the torque angle between E_o and E

$$\delta = p \alpha / 2 = 8 \cdot 10 / 2 = 40$$

- Which voltage E or E_o is leading ?

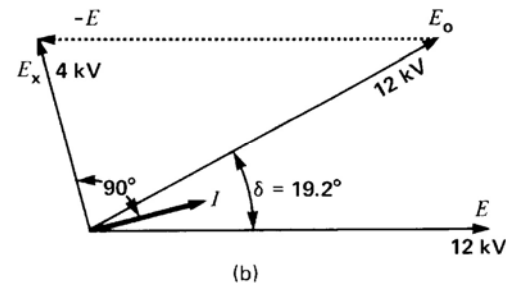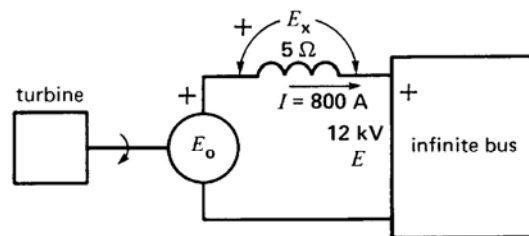


Active power

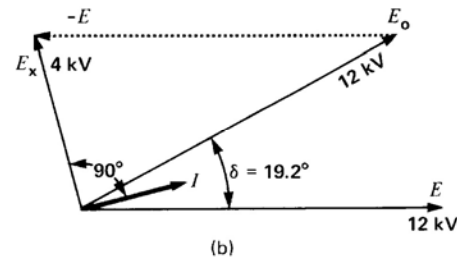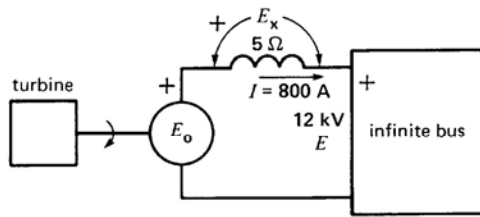

- $P = E_0 E \sin \delta / X_S$

is generator and the torque angle.

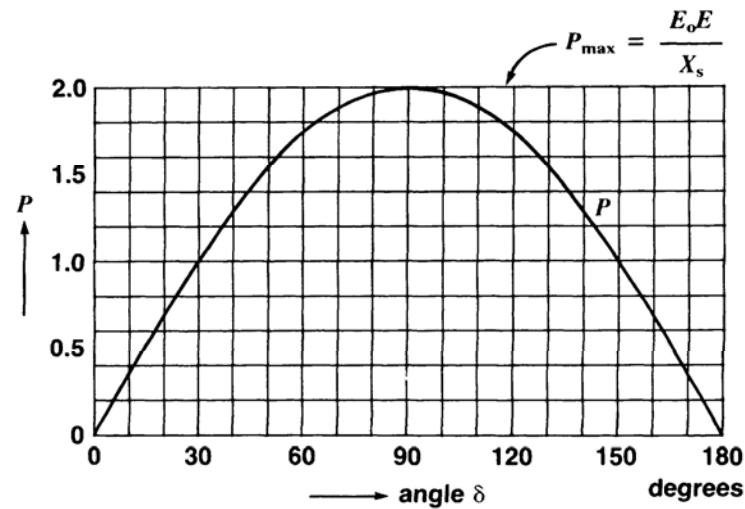

Example 16.7

- 36 MVA, 21 kV 1800 r/min 3 phase generator , $X_s = 9$ ohm per phase, $E_o = 12$ kV, $E = 17,3$ kV
- Calculated the active power when $\delta = 30$
 - $P = E_0 E \sin \delta / X_s$
- The peak power ?

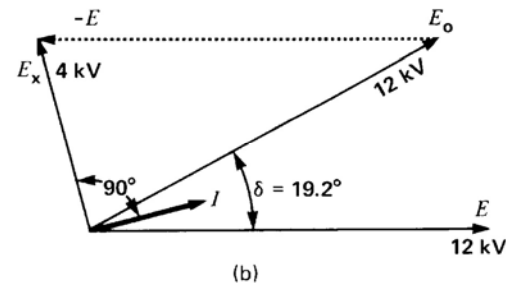
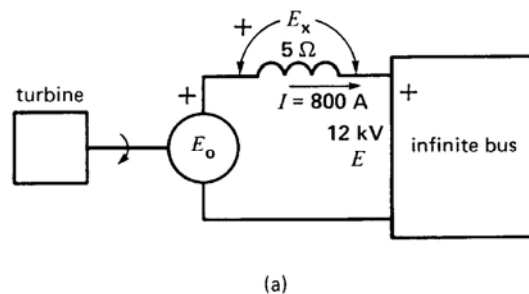


Figure 16.30 Variation of generator reactance following a short-circuit.

Transient reactance

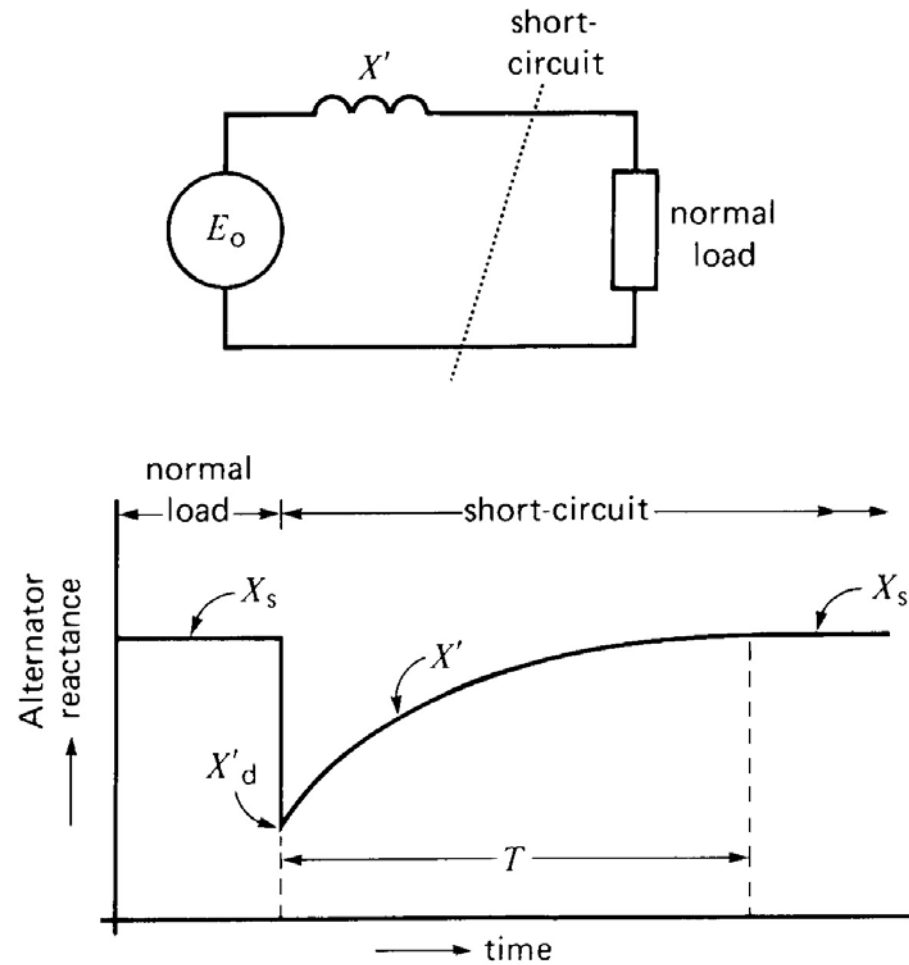


Figure 16.32 Change in current when a short-circuit occurs across the terminals of a generator. See Example 16-8.



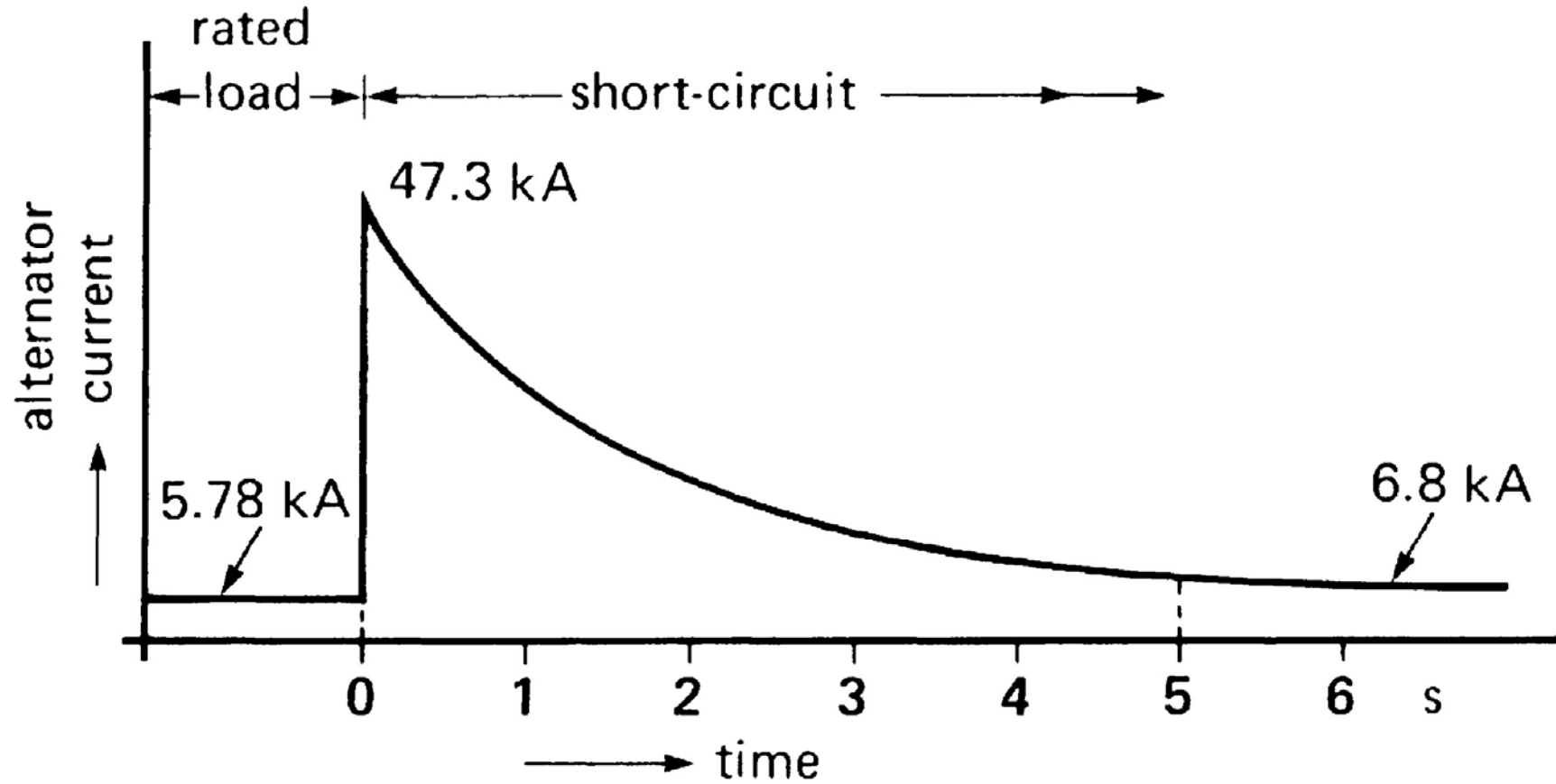


Figure 16.33 Power flow between two voltage sources.

Power transfer

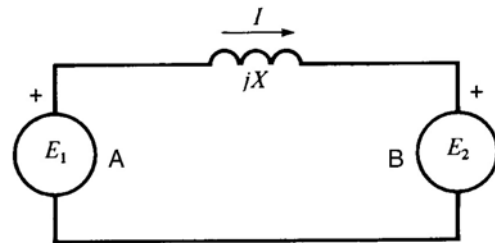

(a)

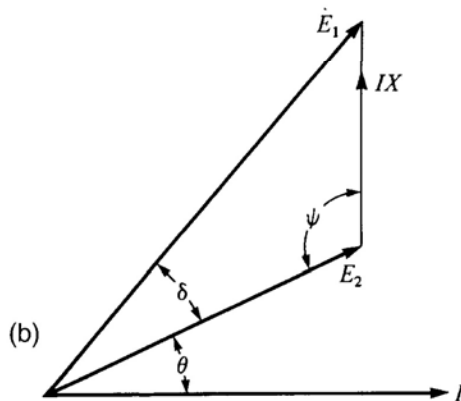

(b)

- $E_1 = E_2 + jIX$
- $P = E_2 I \cos \theta$
- $P = E_1 E_2 \sin \delta / X_S$