

<b>Opgave 1</b> 3-7 10 punten	<p>Oplossing:</p> $X_L = \omega L = 314.16 \times 16 \times 10^{-3} = 5.02 \Omega ; R = 6.8 \Omega$ $Z = R + jX_L = 8.44 \Omega \angle 36.4^\circ$ $\rho = 36.4^\circ$ $S = \frac{V^2}{Z} = \frac{230^2}{8.44} = 6297.6 \text{ VA}$ $P_R = S \cdot \cos \rho = 6297.6 \times 0.8 = 5038 \text{ W}$ $Q_L = S \cdot \sin \rho = 6297.6 \times 0.59 = 3716 \text{ VAR}$ $Q_C = -Q_L = -3716 \text{ VAR}$ $C = \frac{Q_C}{V^2 \cdot \omega} = \frac{3716}{230^2 \cdot 314} \approx 224 \mu\text{F}$
-------------------------------------	---


<b>Opgave 2a</b> 5-11 7 punten	<p>Oplossing:</p> <p>Reference phasor <math>\bar{V}_1 = 230\sqrt{2} \angle 0^\circ</math></p> $Z_L = R + jX_L = 1.9 + j1.1 = 2.2 \angle 30^\circ \Omega$ $Z_1 = \left( \frac{N_1}{N_2} \right)^2 Z_L$ $\bar{I}_2' = \frac{V_1}{Z_1} = \frac{230\sqrt{2}}{(3)^2 \times 2.2 \angle 30^\circ} = 16.43 \angle -30^\circ \text{ A}$ <p>Of:</p> $\bar{V}_2 = \bar{V}_1 / 3 \cdot \sqrt{2} = 230\sqrt{2} / 3 = 108.4 \angle 0^\circ \text{ V}$ $\bar{I}_2 = \frac{\bar{V}_2}{Z_L} = \frac{108.4 \angle 0^\circ}{2.2 \angle 30^\circ} = 49.27 \angle -30^\circ \text{ A}$ $\bar{I}_1 = \bar{I}_2 / 3 = 16.42 \angle -30^\circ \text{ A}$ $\bar{I}_m = -j\sqrt{2} \times 1.0 = 1.41 \angle 90^\circ \text{ A}$ $\bar{I}_1 = \bar{I}_2' + \bar{I}_m$ $= [16.43 \angle -30^\circ - 1.41 \angle 90^\circ]$ $= 14.23 - j8.22 - j1.41 = 14.23 - j9.63 = 17.18 \angle -34.01^\circ \text{ A}$
<b>Opgave 2b</b> 3 punten	<p>de amplitude en fase van <math>I_1</math>.</p> $\bar{I}_3' = \frac{V_3}{R} = \frac{230\sqrt{2}}{(3)^2 \times 2.2 \angle 0^\circ} = 16.43 \text{ A}$ $\bar{I}_1 = \bar{I}_2' + \bar{I}_m + \bar{I}_3'$ $= 14.23 - j8.22 - j1.41 + 16.43 = 30.66 - j9.63 = 31.37 \angle -17.45^\circ \text{ A}$

<p><b>Opgave 3a</b></p> <p>7-1</p> <p>3 punten</p>	<p>Oplossing 1: Voor 120V:</p> <p>Bij <math>T = 0 \text{ Nm} \Rightarrow I_a = 0 \text{ A}; \omega_m = \frac{E_a}{k_E} = \frac{120}{0.5} = 240 \text{ rad/sec}</math></p> <p>Bij <math>T = 4 \text{ Nm}: \Rightarrow I_a = \frac{T}{k_T} = \frac{4.0}{0.5} = 8.0 \text{ A}</math></p> $\omega_m = \frac{V_a - R_a \cdot I_a}{k_E} = \frac{120 - 0,35 \times 8}{0.5} = 234.4 \text{ rad/sec}$ <p>Voor 70V:</p> <p>Bij <math>T = 0 \text{ Nm} \Rightarrow I_a = 0 \text{ A}; \omega_m = \frac{E_a}{k_E} = \frac{70}{0.5} = 140 \text{ rad/sec}</math></p> <p>Bij <math>T = 4 \text{ Nm}: \Rightarrow I_a = \frac{T}{k_T} = \frac{4.0}{0.5} = 8.0 \text{ A}</math></p> $\omega_m = \frac{V_a - R_a \cdot I_a}{k_E} = \frac{70 - 0,35 \times 8}{0.5} = 134.4 \text{ rad/sec}$
<p><b>Opgave 3a</b></p> <p>7-7</p> <p>7 punten</p>	<p>Oplossing:</p> $\omega_{m1} = \frac{1500}{60} 2\pi = 157.08 \text{ rad/sec}$ $\omega_{m2} = \frac{750}{60} 2\pi = 78.54 \text{ rad/sec}$ $J_t = J_m + J_l = 0.02 + 0.04 = 0.06 \text{ kg.m}^2$ $\Delta E_{inertia} = \frac{1}{2} J_t [\omega_1^2 - \omega_2^2] = \frac{0.06 [157.08^2 - 78.54^2]}{2} = 555.17 \text{ J}$ $T_{em} = k_T  I_a  = 0.5 \times 10 = 5 \text{ Nm}$ $\Delta t = (\omega_{m1} - \omega_{m2}) \frac{J_t}{T_{em}} = 78.54 \times \frac{0.06}{5} = 0.942 \text{ sec}$ $E_{loss} = R_a I_a^2 \Delta t = 0.35 \times 10^2 \times 0.942 = 32.97 \text{ J}$ $E_{recovered} = \Delta E_{in} - E_{loss} = 555.7 - 32.97 = 522 \text{ J}$

**Vraag 1**

Zie pagina 4-17

2 punten

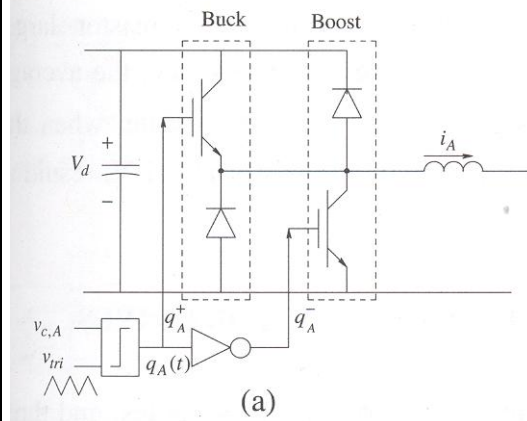

Twee kwadranten, 1 en 2.

**Vraag 2**

Zie pagina 16-28, pagina 16-28 / 16-31

3 punten

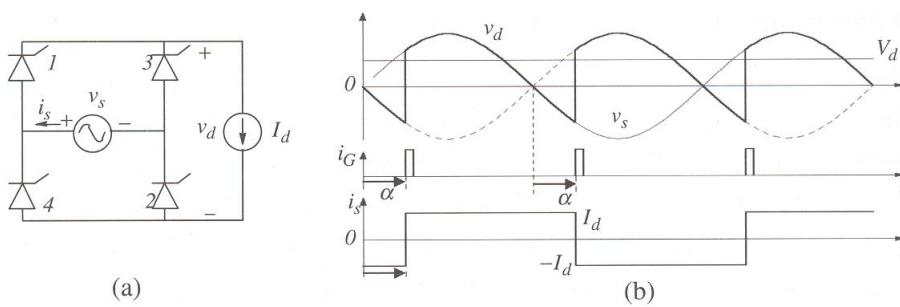


Figure 16-21 (a) Simplified circuit diagram of the converter; (b) waveforms.

$$v_d(t) = -v_s(t) \quad \text{and} \quad i_s(t) = -I_d \quad \alpha + \frac{\pi}{2} < \omega t \leq \alpha + \pi \quad (16-29)$$

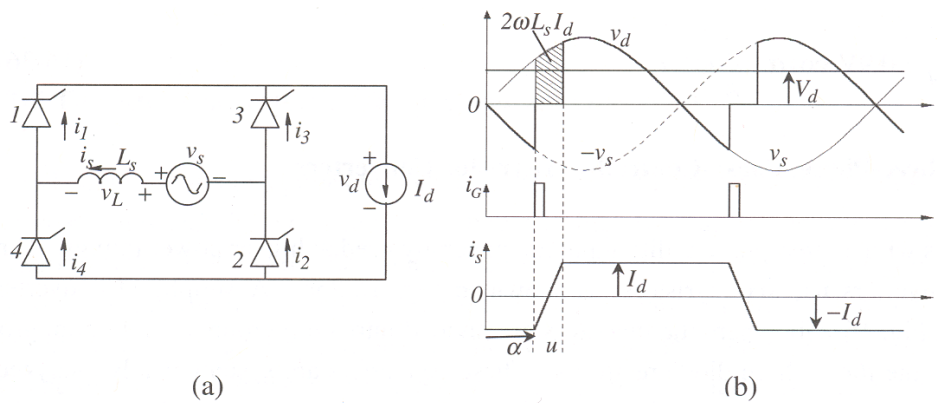
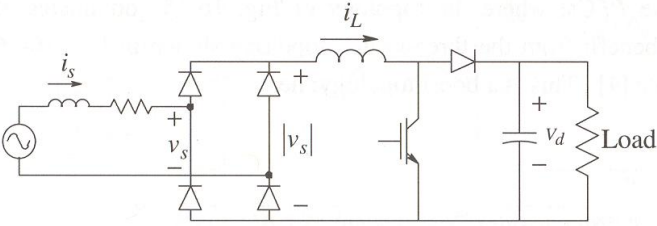
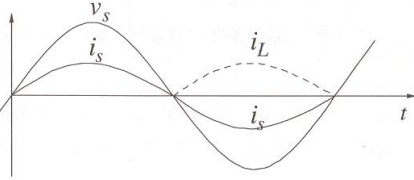
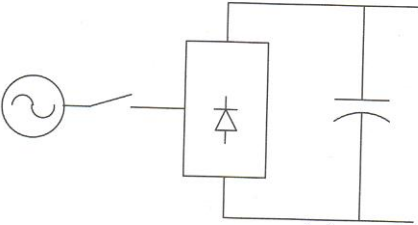
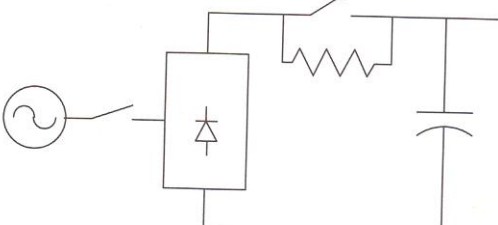


Figure 16-24 (a) Thyristor converter along with source inductance; (b) waveforms.

$$\frac{\omega L_s I_s}{T}$$

<p><b>Vraag 3</b> 2 punten</p>	<p>Beschrijving vanaf bladzijde 16-21  <math>V_d &gt; \hat{V}_s</math></p>  <p>(a)</p>  <p>(b)</p>
<p><b>Vraag 4</b> 1 punten</p>	<p>Zie pagina 16-23</p>  <p>(a)</p>  <p>(b)</p> <p>Figure 16-17 Means to avoid inrush current</p>
<p><b>Vraag 5</b> 2 punten</p>	<p>Twee fasen verwisselen</p> $\omega_r = \omega_s(1-s); \omega_s = \frac{60 \times f}{p/2}$