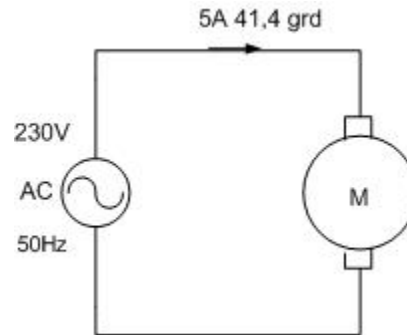


Problem 1

$$\cos \varphi = 0,75 \Rightarrow \varphi = 41,4^\circ$$

a) $Q = U \times I \times \sin 41,4 = 760,6 \text{ VAr}$

b) $P = U \times I \times \cos 41,4 = 862,6 \text{ W}$



c) new $\cos \varphi = 0,9$ $\cos \varphi = 0,9 \Rightarrow \varphi = 25,84^\circ$

New apparent power; $S_N = \frac{P}{\cos \varphi} = \frac{862,6}{0,9} = 958,44 \text{ VA}$

New reactive power: $Q_N = \sqrt{S_N^2 - P^2} = \sqrt{958,44^2 - 862,6^2} = 417,76 \text{ VAr}$


Reactive power supplied by capacitor: $Q_C = Q - Q_N = 760,6 - 417,76 = 342,84 \text{ VAr}$

$$X_C = \frac{U}{Q_C} = \frac{230}{342,84} = 154,3 \Omega$$

$$I_C = \frac{U}{X_C} = \frac{230}{154,3} = 1,49 \text{ A}$$

$$\frac{1}{C} = 2 \times \pi \times 50 \times 154,3 \Rightarrow C = 20,6 \mu\text{F}$$


d)

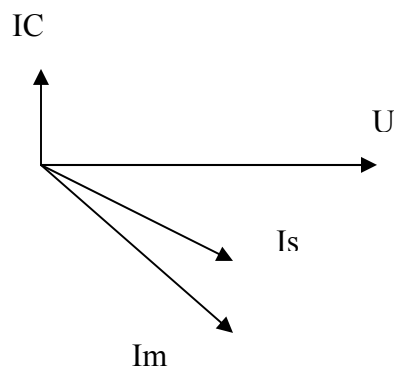

Problem 2

Example 16.2

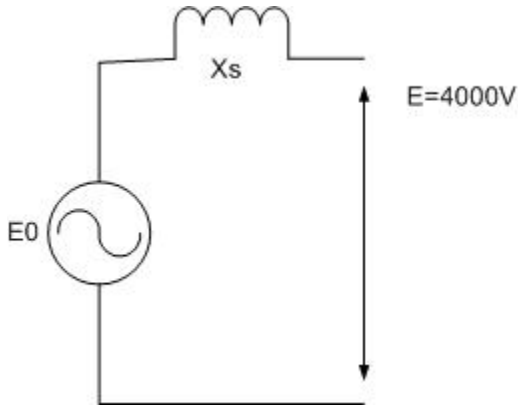a) Draw the per phase equivalent circuit in the open-circuit situation including the line-to-neutral voltage. (2 points)



$$U_{LIN} = \frac{6928}{\sqrt{3}} = 4000V$$

b) Calculate the synchronous reactance per phase. (3 points).


When the terminals are short-circuited, the only impedance limiting the current flow is that due to the synchronous reactance. Consequently,

$$\begin{aligned} X_s &= E_o/I = 4000/800 \\ &= 5 \Omega \end{aligned}$$

The synchronous reactance per phase is therefore 5 Ω.

c) Calculate the terminal voltage (line to neutral) if three 12Ω resistors are connected in wye across the terminals. (3 points)

Per phase equivalent.

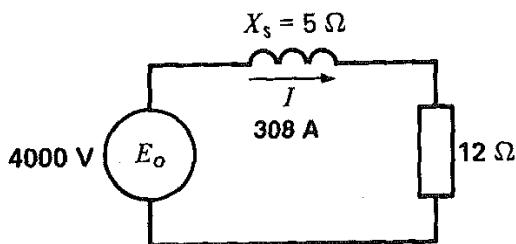

The impedance of the circuit is

$$\begin{aligned} Z &= \sqrt{R^2 + X_s^2} \\ &= \sqrt{12^2 + 5^2} \\ &= 13 \Omega \end{aligned}$$

The current is

$$I = E_o / Z = 4000 / 13 = 308 \text{ A}$$


The voltage across the load resistor is

$$E = IR = 308 \times 12 = 3696 \text{ V}$$

The line voltage under load is

$$\begin{aligned} E_L &= \sqrt{3} E \\ &= \sqrt{3} \times 3696 \\ &= 6402 \text{ V} \end{aligned}$$

d) Draw the fasor diagram with the voltages and the current of situation c). (2 points)

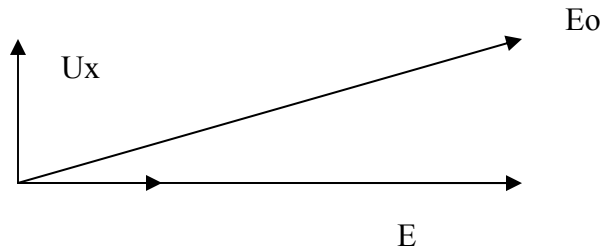

Problem 3

Example 21-11

a) The current drawn from the source. (2 points)

The power supplied to the battery is: $P = 120 \cdot 20 = 2400W$

The current from the source is: $I_s = \frac{P}{E_s} = \frac{2400}{600} = 4A$

b) The current in the diode. (2 points)

To calculate the average current in the diode, we refer to fig 21.61a. Current $I_o=20A$ and I_s was found to be $4A$. Applying Kirchoff's current law to the diode/inductor junction, the average diode current I_d is: $I_D = I_o - I_s = 20 - 4 = 16A$

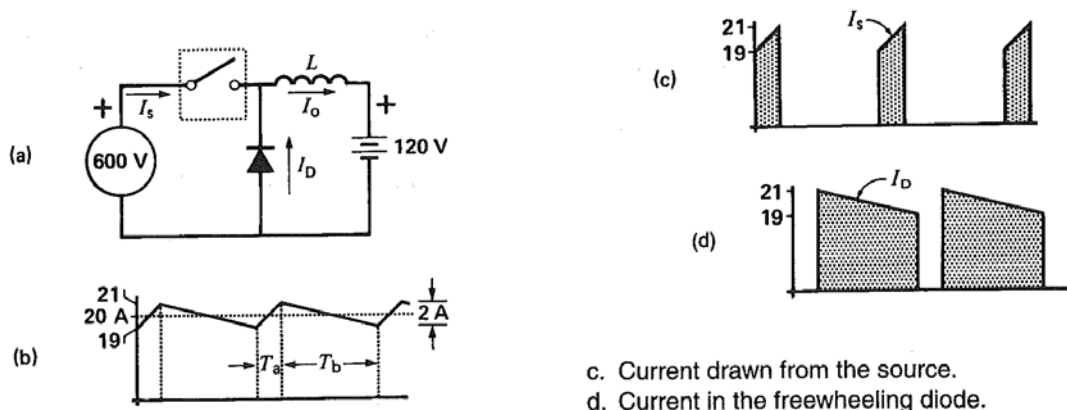


Figure 21.61

- a. Circuit of Example 21-11.
- b. Current in the load.

c) The duty cycle. (3 points)

The duty cycle is: $D = \frac{E_o}{E_s} = \frac{120}{600} = 0,2$

d) The inductance of the inductor. (3 points)

d. During interval T_a the average voltage across the inductor is $(600 - 120) = 480 V$.
 The volt-seconds accumulated by the inductor during this interval is $A_{(+)} = 480 V \times 1 ms = 480 mV \cdot s = 0.48 V \cdot s$. The change in current during the interval is $2 A$; consequently,


$$\Delta I = A_{(+)} / L \quad (2.28)$$

$$2 = 0.48 / L$$


$$L = 0.24 H$$

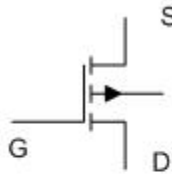1. (1 point)

Draw the symbol and state the typical properties of a thyristor and MOSFET.



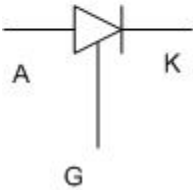
Mosfet: High switching frequency, 200kHz. Max current approx 100A, voltage 1kV.



Thyristor: max switching frequency, 3kHz. Max current 3kA. Max voltage 4kV

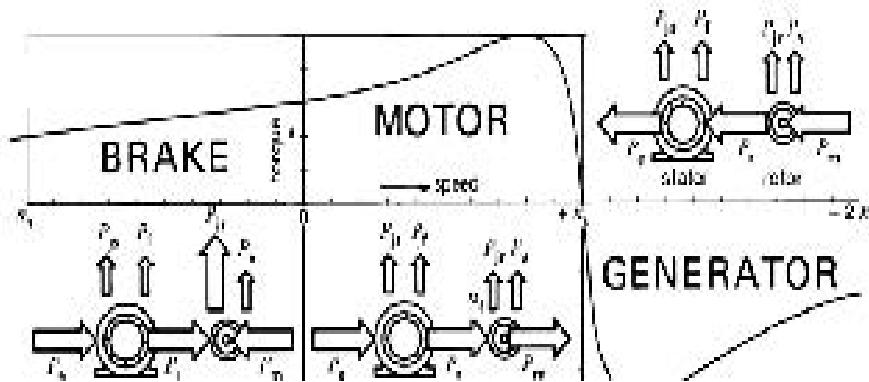
2. (2 point)

Draw the complete torque speed curve of a 3 phase induction machine and mark the brake + motor and generator region.



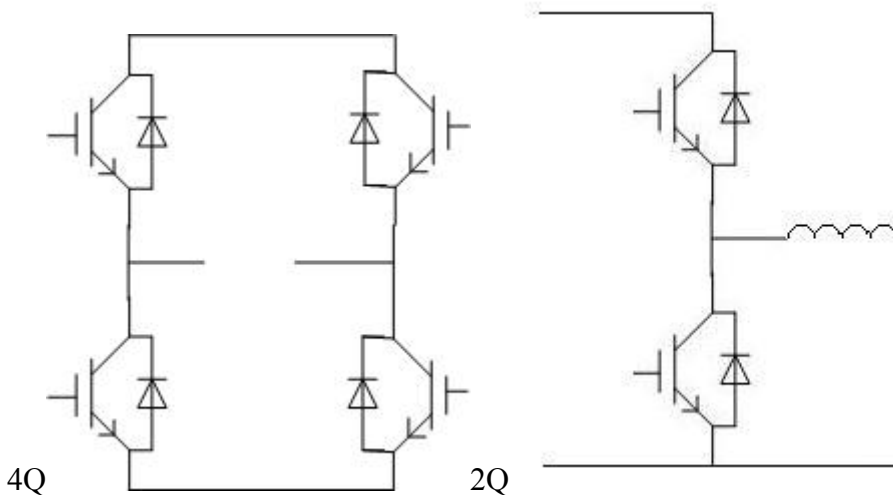3. (2 points)

Draw the schematic of a two quadrant and a four quadrant electronic DC-DC converter with the use of IGBT switches and diodes.



4. (3 points) Simple battery charger.

Draw the voltage between point 2 and 1, 3 and 1 and 4 and 1 and current I of the circuit from fig. 21.11

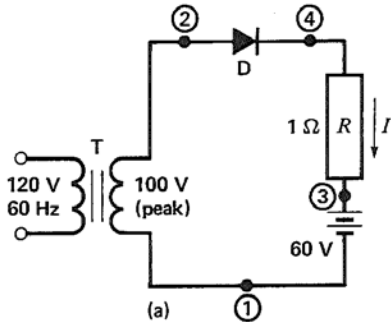


Figure 21.11

a. Simple battery charger circuit.

486 ELECTRICAL AND ELECTRONIC DRIVES

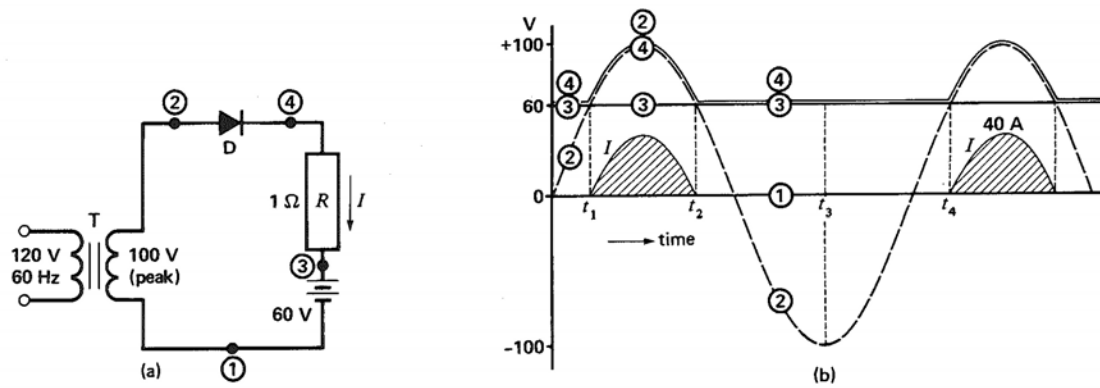


Figure 21.11


a. Simple battery charger circuit.

b. Corresponding voltage and current waveforms.

5. (1 point)

What is the definition of “power factor” PF?

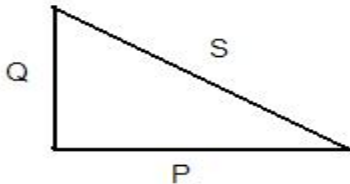5) (1 point) $pf = \frac{P}{S}$, power factor is de cos van de hoek tussen spanning en stroom. En



6. (1 point)

Explain the meaning of the following terms.

1) Anode 2) Cathode 3) Inverter

Anode: positive pole. Cathode: negative pole. Inverter: e.g. Dc to AC