

Uitwerking opgaven 1 t/m 9 tentamen Elektronische Schakelingen II (ET2405-d2):

1. B

2. A

3. $f_0 = \frac{1}{2\pi\sqrt{L_2C_2}}$

4. +/- 5%

5. $H(s) = \frac{Y(s)}{U(s)} = \frac{R(1+s^2L_2C_2)}{s^3R^2L_2(C_2C_3+C_1C_3+C_1C_2)+s^2RL_2(C_1+2C_2+C_3)+s(R^2C_3+L_2+R^2C_1)+2R}$

6. laagdoorlaatfiltercurve met een notch op $f_0 = \frac{1}{2\pi\sqrt{L_2C_2}}$

7. 3

8.

$$\begin{aligned}
H(s) &= \frac{Y(s)}{U(s)} = \frac{R(1+s^2L_2C_2)}{s^3R^2L_2(C_2C_3+C_1C_3+C_1C_2)+s^2RL_2(C_1+2C_2+C_3)+s(R^2C_3+L_2+R^2C_1)+2R} \\
&= \frac{n_2s^2+n_0}{p_3s^3+p_2s^2+p_1s+p_0} = \frac{n_2s^2}{p_3s^3+p_2s^2+p_1s+p_0} + \frac{n_0}{p_3s^3+p_2s^2+p_1s+p_0} \\
&= H_2(s) + H_1(s)
\end{aligned}$$

uitwerken van $H_1(s)$:

$$p_3\ddot{y}_1(t) + p_2\dot{y}_1(t) + p_1y_1(t) + p_0y_1(t) = n_0u(t)$$

$$x_1(t) = y_1(t)$$

$$x_2(t) = \dot{x}_1(t) = \dot{y}_1(t)$$

$$x_3(t) = \dot{x}_2(t) = \ddot{x}_1(t) = \ddot{y}_1(t) = y_2(t)$$

$$\dot{x}_3(t) = \frac{n_0}{p_3}u(t) - \frac{p_2}{p_3}x_3(t) - \frac{p_1}{p_3}x_2(t) - \frac{p_0}{p_3}x_1(t)$$

De totale toestandsbeschrijving wordt:

$$y(t) = y_1(t) + y_2(t) = x_1(t) + \frac{n_2}{n_0}x_3(t)$$

$$A = \begin{pmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -\frac{p_0}{p_3} & -\frac{p_1}{p_3} & -\frac{p_2}{p_3} \end{pmatrix}$$

$$B = \begin{pmatrix} 0 \\ 0 \\ \frac{n_0}{p_3} \end{pmatrix}$$

$$C = \left(1 \quad 0 \quad \frac{n_2}{n_0}\right)$$

$$D = 0$$

9. valt eenvoudig uit bovenstaande SS-beschrijving af te leiden