



EE1320: Measurement Science

Lecture 4: Instrumentation Amplifiers

Dr. ir. Michiel Pertijs, Electronic Instrumentation Laboratory

May 14, 2013


Course program 2013

week	date	topic
4.1	Tu 23/4	#1 intro measurements and meas. systems
	Fr 26/4	#2 sensors
4.3	Tu 7/5	#3 sensor readout and signal conditioning
4.4	Tu 14/5	#4 instrumentation amplifiers
	We 15/5	intermediate test
4.5	Tu 21/5	#5 analog-to-digital converters
4.6	We 29/5	#6 measurement instruments I
4.7	Tu 4/6	#7 measurement instruments II
	We 5/6	intermediate test
4.8	Tu 11/6	tutorial
4.11	We 3/7	final exam


Lecturer: dr. ir. Michiel Pertijs

room HB 15.050, M.A.P.Pertijs@tudelft.nl, 015-2786823

Last time... signal conditioning

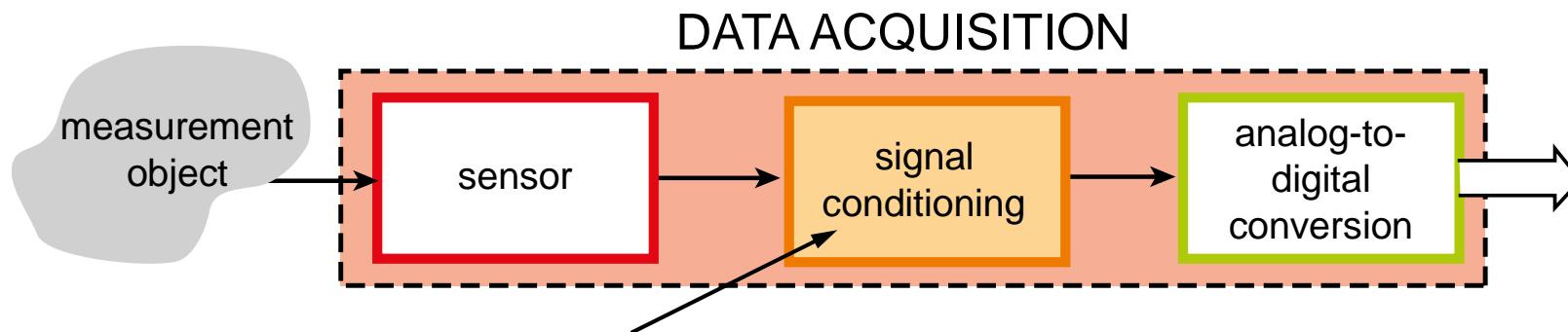

- Signal conditioning needed to adjust output signal of the sensor to the input of the ADC
- Opamps are suitable building blocks for sensor readout
 - non-inverting amplifier, transimpedance amplifier, inverting amplifier, charge amplifier
- Opamp non-ideal properties influence the transfer and sometimes have to be compensated for
 - offset voltage, bias current, offset current



Today: bridge circuits and instrumentation amplifiers


- Bridge circuits with resistors
- Differential and common-mode signals
- Common-mode rejection
- Opamp difference amplifier
- 3-opamp instrumentation amplifier




Overview study material

- Slides: Wheatstone bridge
- Regtien 1.2: common-mode rejection
- Regtien 12.1.4, 12.1.5: difference- en instrumentation amplifiers

Balance measurements

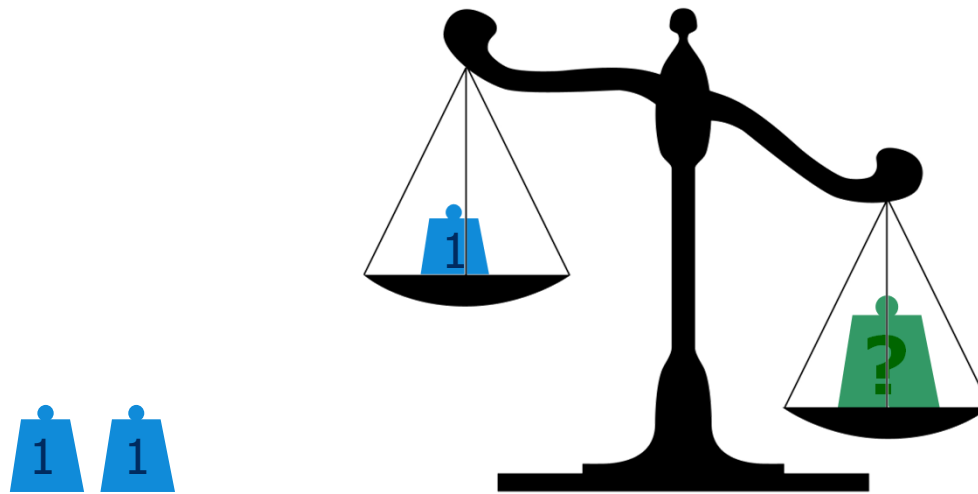

The Wheatstone bridge

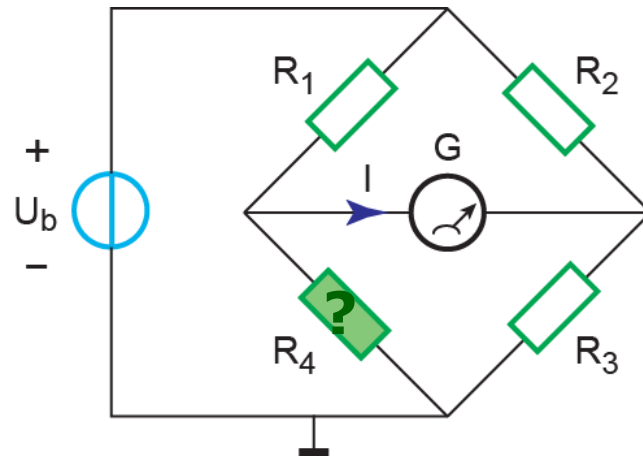


Sir Charles Wheatstone
(1802 – 1875)

- Known resistors R_1, R_2, R_3
Unknown resistor R_4
- Galvanometer G measures current I due to unbalance
- Point of balance ($I = 0$) if $\frac{R_1}{R_4} = \frac{R_2}{R_3} \Rightarrow R_4 = \frac{R_1 R_3}{R_2}$

The Wheatstone bridge


- With voltage readout

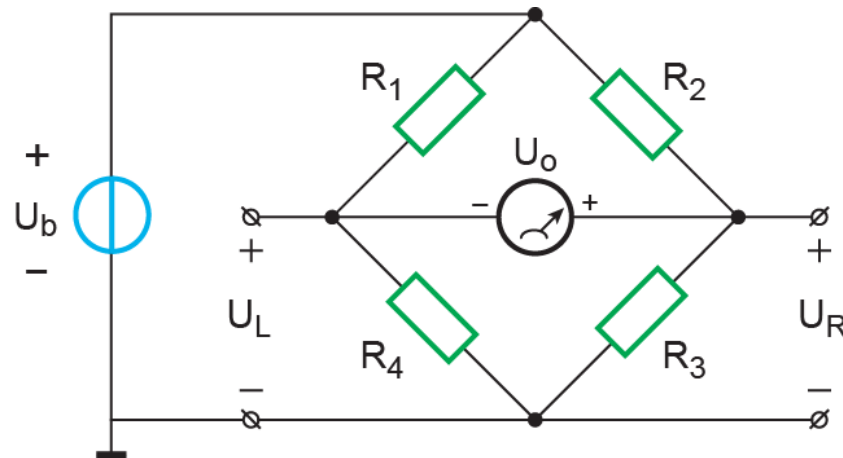

- Left divider: $U_L = \frac{R_4}{R_1 + R_4} U_b$
- Right divider: $U_R = \frac{R_3}{R_2 + R_3} U_b$
- Output voltage:

$$\begin{aligned} U_o &= U_R - U_L \\ &= \frac{R_1 R_3 - R_2 R_4}{(R_2 + R_3)(R_1 + R_4)} \cdot U_b \end{aligned}$$

The Wheatstone bridge

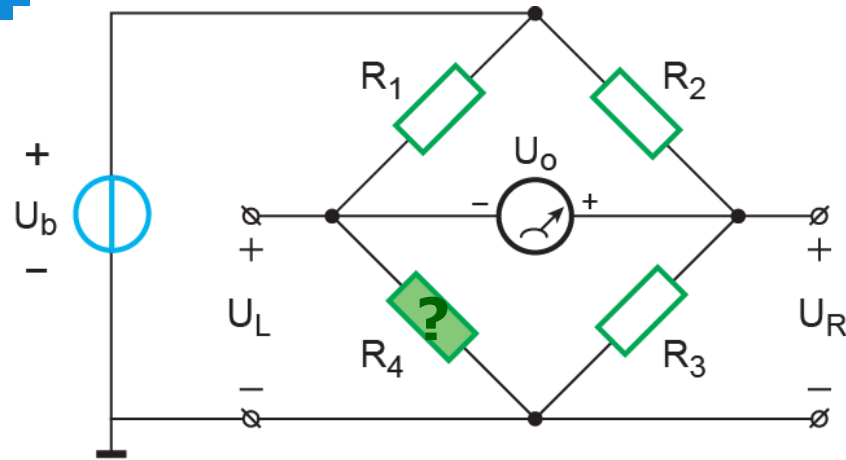


$$U_o = U_R - U_L$$
$$= \frac{R_1 R_3 - R_2 R_4}{(R_2 + R_3)(R_1 + R_4)} \cdot U_b$$

- Balance measurement: let $R_2 = R_3 = R \Rightarrow U_o = \frac{R_1 - R_4}{2(R_1 + R_4)} \cdot U_b$

$$U_o > 0 \Rightarrow R_4 < R_1$$

$$U_o < 0 \Rightarrow R_4 > R_1$$

Resistive sensor in a Wheatstone bridge

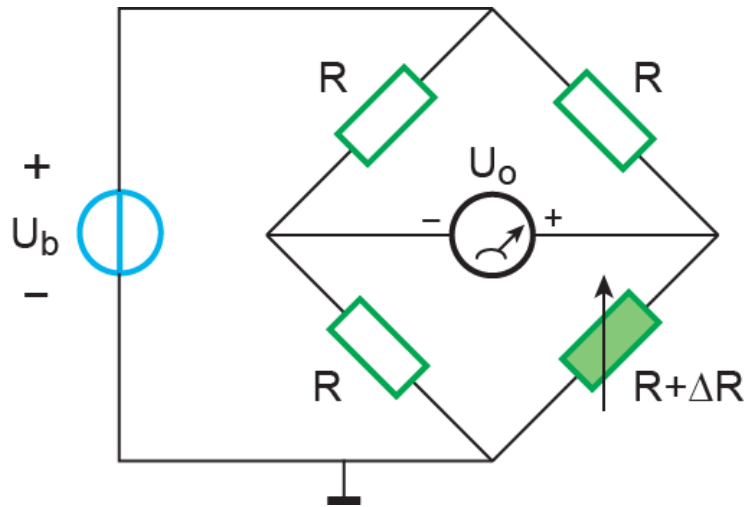

$$U_L = \frac{1}{2} U_b$$

$$U_R = \frac{R + \Delta R}{2R + \Delta R} U_b \cong \frac{1}{2} \left(1 + \frac{\Delta R}{2R} \right) \cdot U_b$$


$$U_o = U_R - U_L \cong \frac{\Delta R}{4R} U_b$$

$$\Rightarrow \frac{U_o}{U_b} \cong \frac{\Delta R}{4R}$$

- **Ratiometric** measurement: U_o measured relative to U_b
(U_o / U_b) is measure for $\Delta R / R$
- Absolute value of U_b is not important!


Bridge configurations

quarter bridge

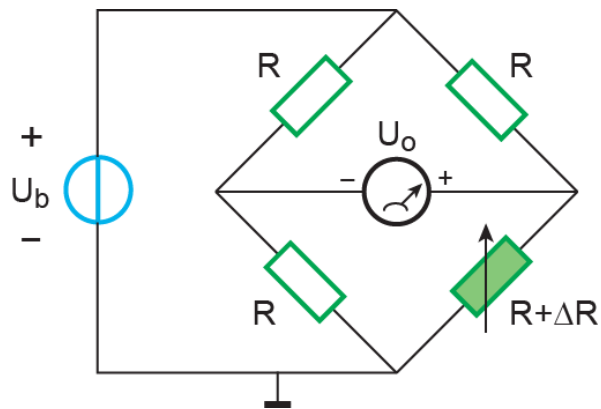


$$\frac{U_o}{U_b} \cong \frac{\Delta R}{4R}$$

half bridge

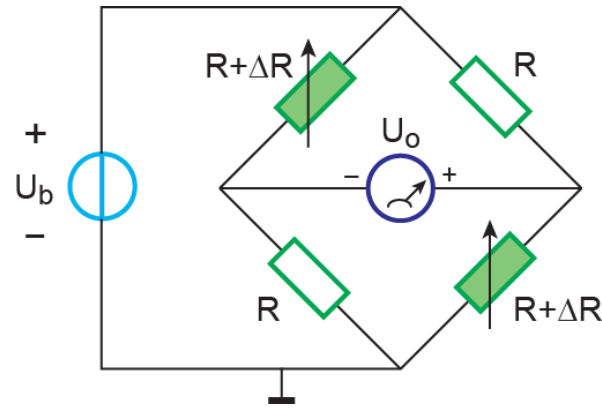



$$\frac{U_o}{U_b} \cong \frac{\Delta R}{2R}$$

full bridge

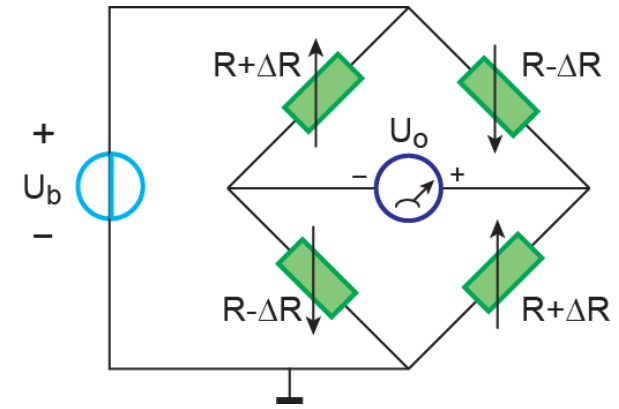


$$\frac{U_o}{U_b} \cong \frac{\Delta R}{R}$$

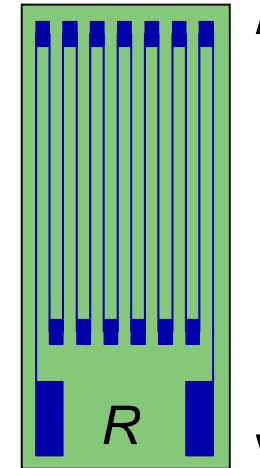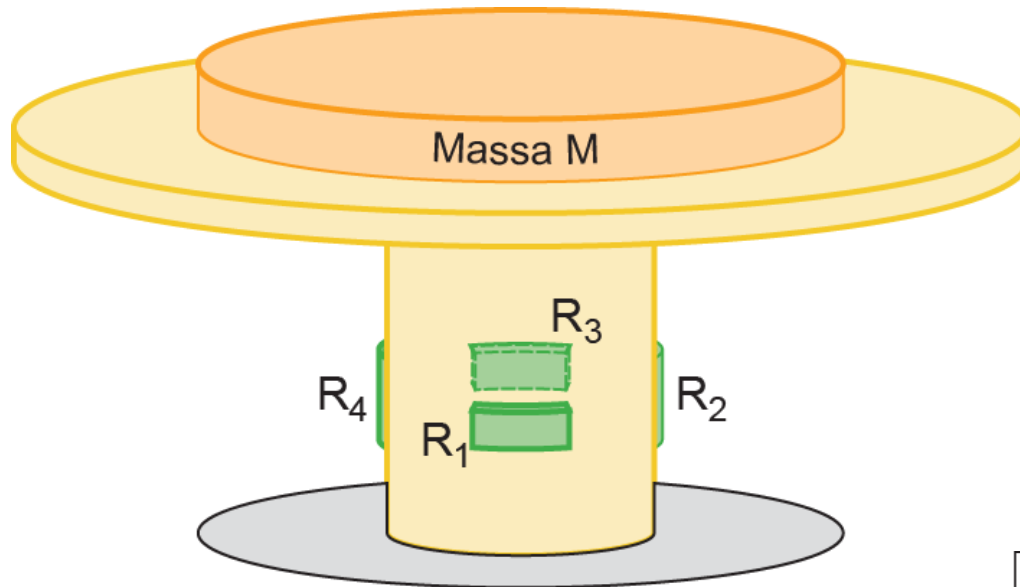Example bridge configurations: weighing scale with strain gauges




$$\frac{\Delta R}{R} = k \cdot \frac{\Delta L}{L}$$

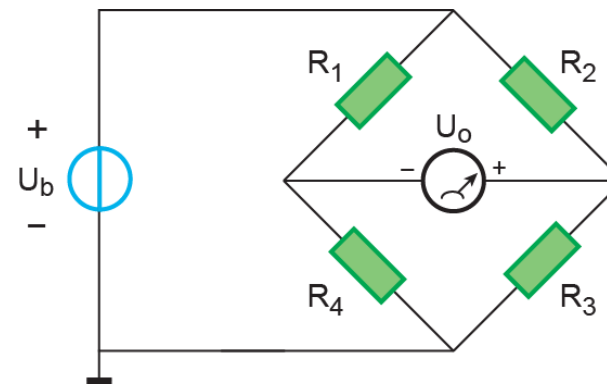- quarter, half, full?
- Temperature effect?




Readout of bridge circuits

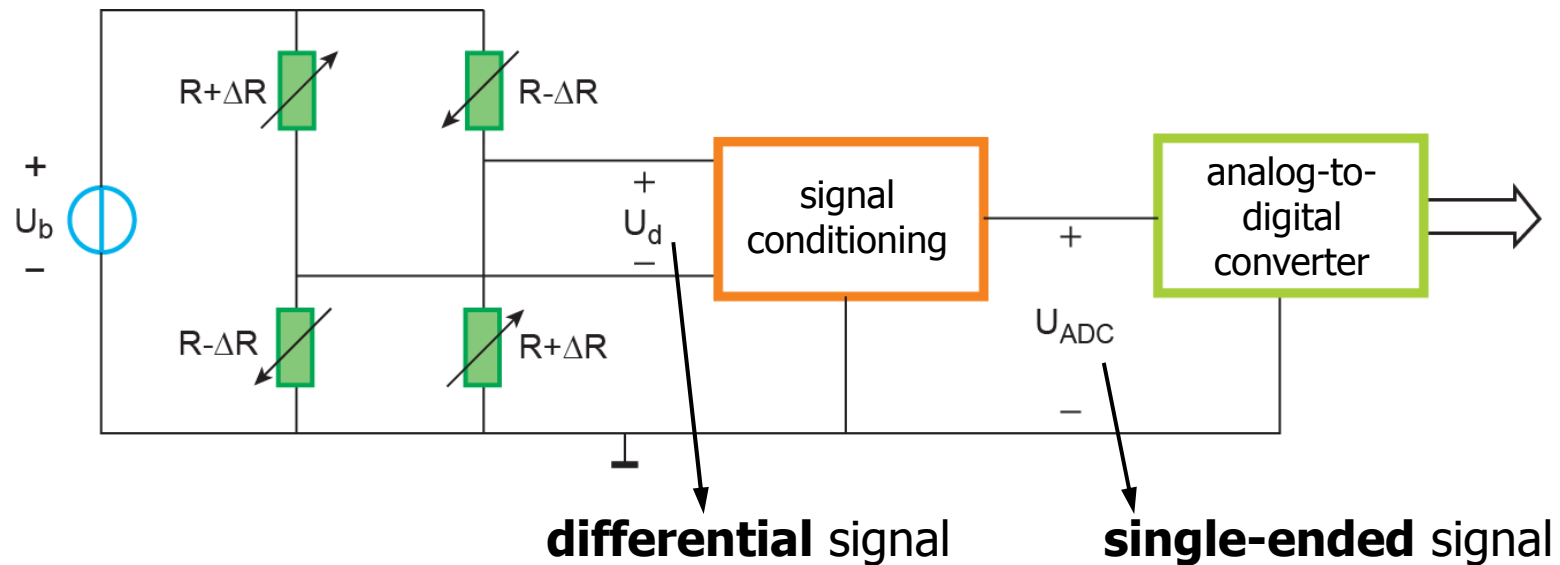

- Here, signal-conditioning takes care of:
 - converting the differential signal to a signal referenced to ground (*single-ended* signal)
 - amplification
 - readout of the bridge without significantly loading it

Differential and common-mode signals

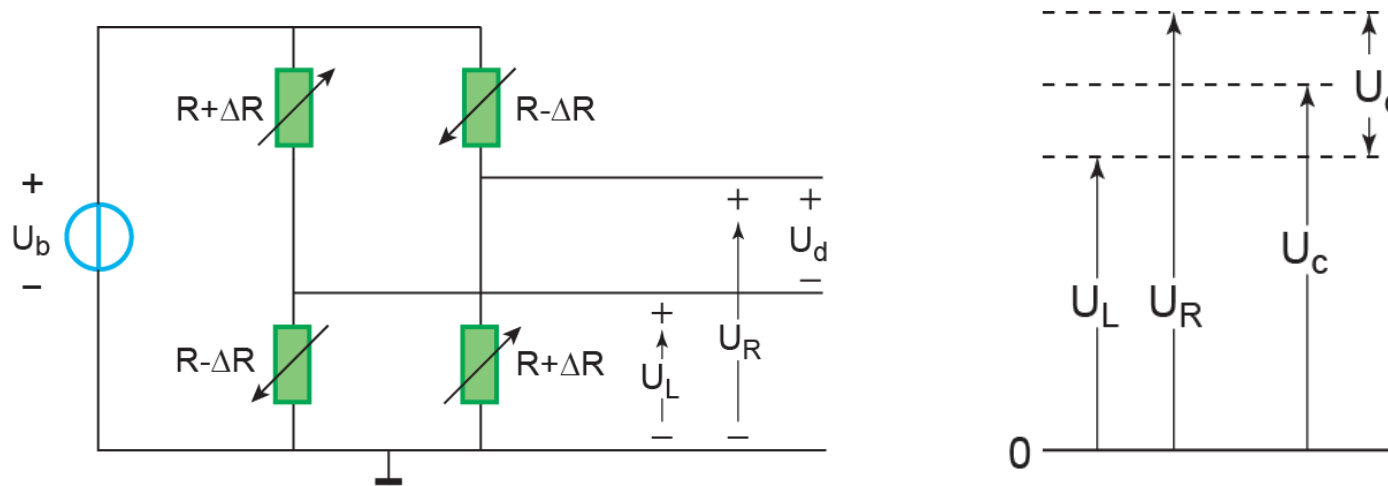


- Differential signal: $U_d = U_R - U_L = \frac{\Delta R}{R} U_b$
- Common-mode signal: $U_c = \frac{U_R + U_L}{2} = \frac{U_b}{2}$
- $U_L = U_c - \frac{U_d}{2}$ $U_R = U_c + \frac{U_d}{2}$

Differential and common-mode signals



- $U_L = 1 \text{ V}$
 $U_R = 4 \text{ V}$
 - $U_L = -4 \text{ V}$
 $U_R = 2 \text{ V}$
 - $U_C = 3 \text{ V}$
 $U_d = 1 \text{ V}$
- $U_d =$
 $U_c =$
- $U_d =$
 $U_c =$
- $U_L =$
 $U_R =$

Differential and common-mode signals

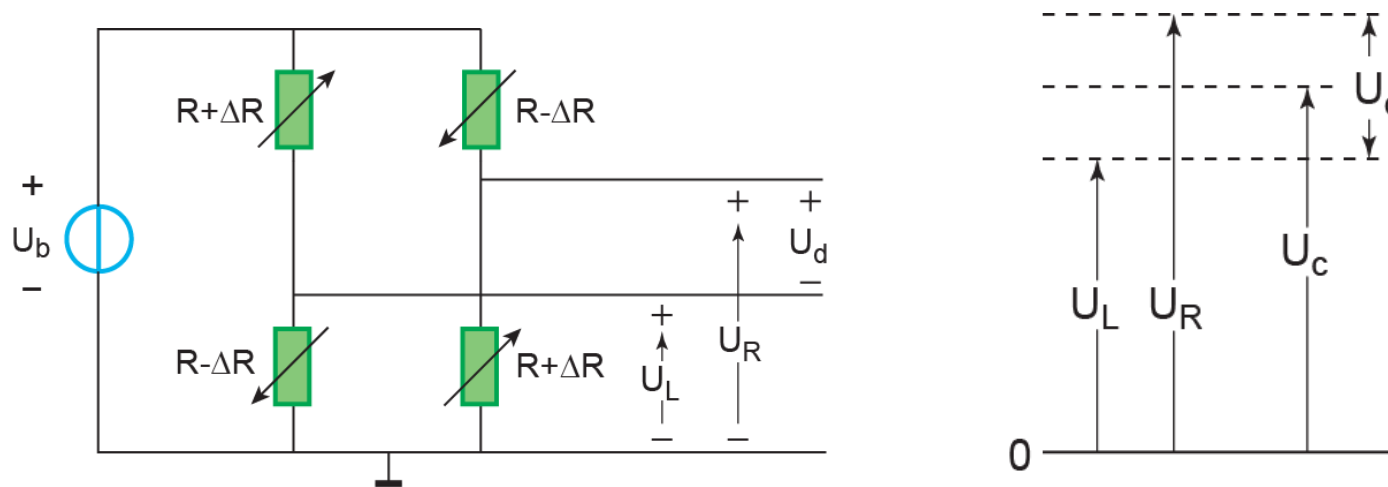

- Differential signal is often **much** smaller than common-mode signal:


For example: $U_b = 1 \text{ V}$, $\Delta R / R = 1\% \Rightarrow$

$$U_d = \frac{\Delta R}{R} U_b = 10 \text{ mV}$$

$$U_c = \frac{U_b}{2} = 0.5 \text{ V}$$

50x

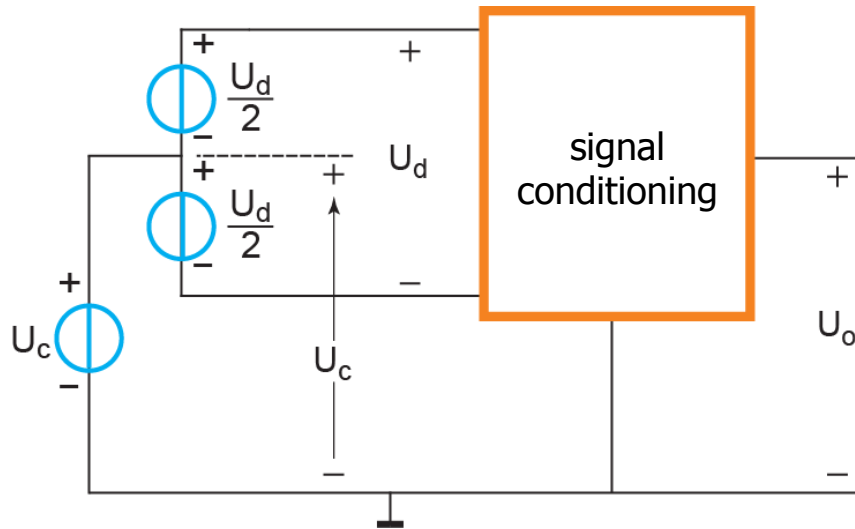Common-mode en differential amplification



- Differential signal U_d is the information-carrying signal of interest and has to be amplified:


$$U_o = G_d \cdot U_d$$

- Common-mode signal U_c should *not* contribute to output signal

- In practice: output *is* dependent on U_c : $U_o = G_d \cdot U_d + G_c \cdot U_c$

⇒ finite **common-mode rejection**

Common-mode rejection ratio (CMRR)

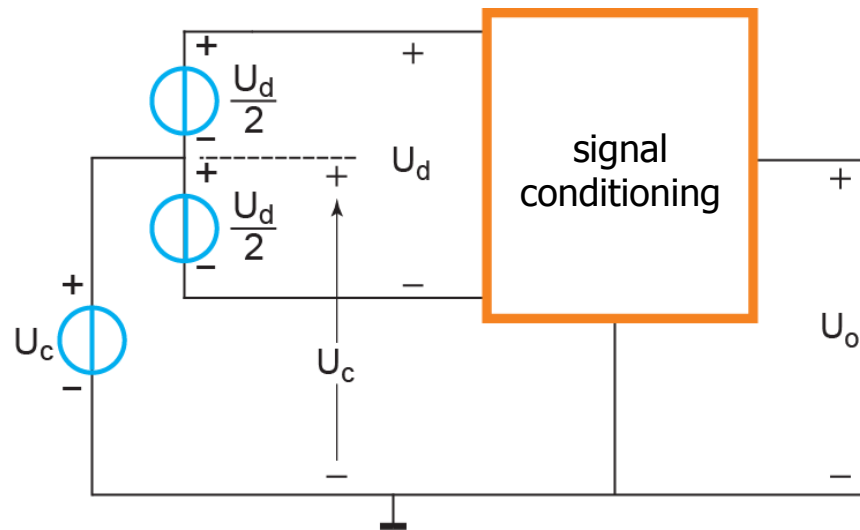


- $U_o = G_d \cdot U_d + G_c \cdot U_c$

- CMRR: $H = \frac{G_d}{G_c} = \frac{dU_o/dU_d}{dU_o/dU_c}$

- Often expressed in dB: $20 \cdot {}^{10}\log(|H|)$ [dB]
- Example: a CMRR of $H = 1000$ (60 dB) means that $\Delta U_d = 1$ mV and $\Delta U_c = 1$ V give an equal contribution ΔU_o to the output

Importance of a high CMRR

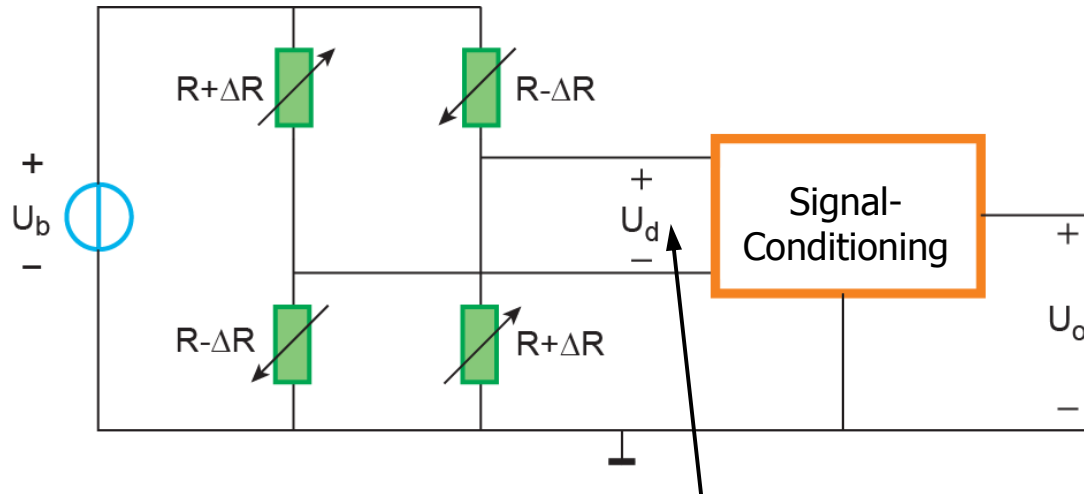

$$H = \frac{G_d}{G_c} = \frac{dU_o / dU_d}{dU_o / dU_c}$$


small differential signal U_d on a **large** common-mode signal U_c

- Determine how high the CMRR must be such that:
 ΔU_o due to U_c is smaller than ΔU_o due to $\Delta R / R = 1\%$



Difference amplifier

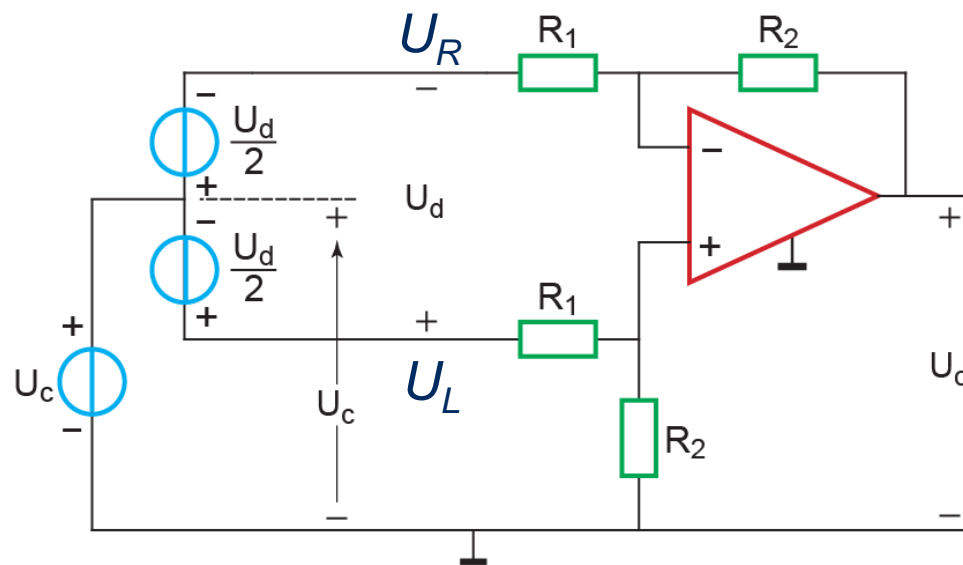
- Can be used to amplify a voltage difference



- Determine the differential gain $G_d = U_o / U_d$




Limitations of difference amplifiers

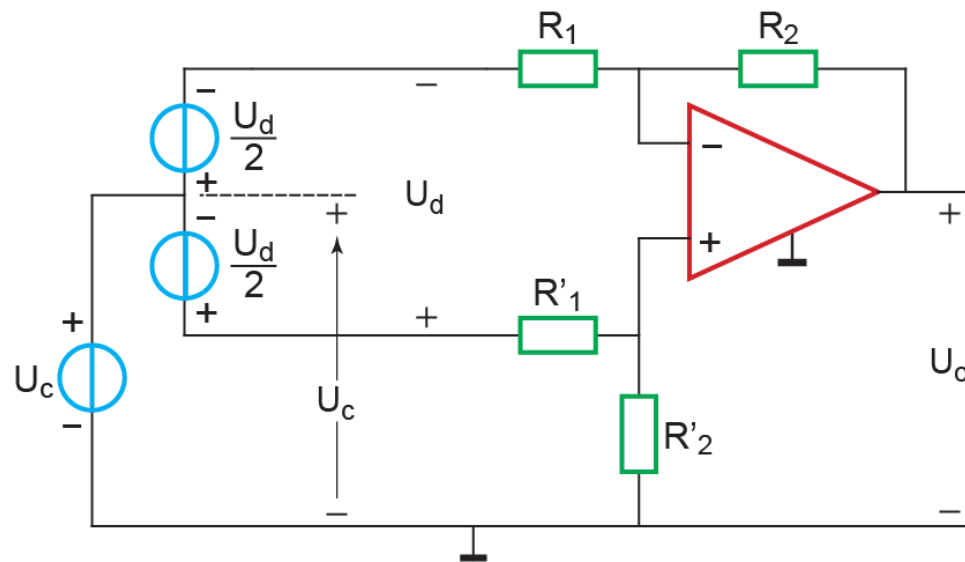


- Resistors impose a load on the source
- Practical resistors have tolerances:
 - $\Rightarrow R'_1 \neq R_1, R'_2 \neq R_2$
 - \Rightarrow inverting and non-inverting transfer is not exactly equal
 - \Rightarrow output is influenced by U_c !!

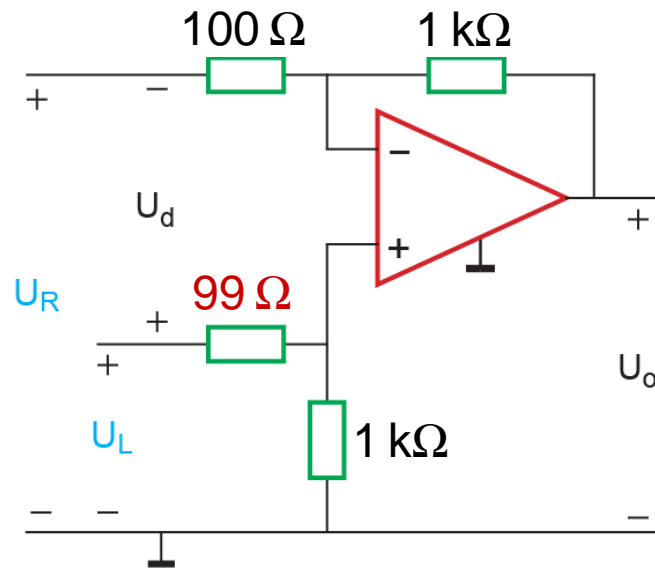Example: determine the common-mode rejection of a difference amplifier




- **Common-mode rejection ratio** $H = \frac{G_d}{G_c} = \frac{dU_o / dU_d}{dU_o / dU_c} = ???$

3-opamp instrumentation amplifier

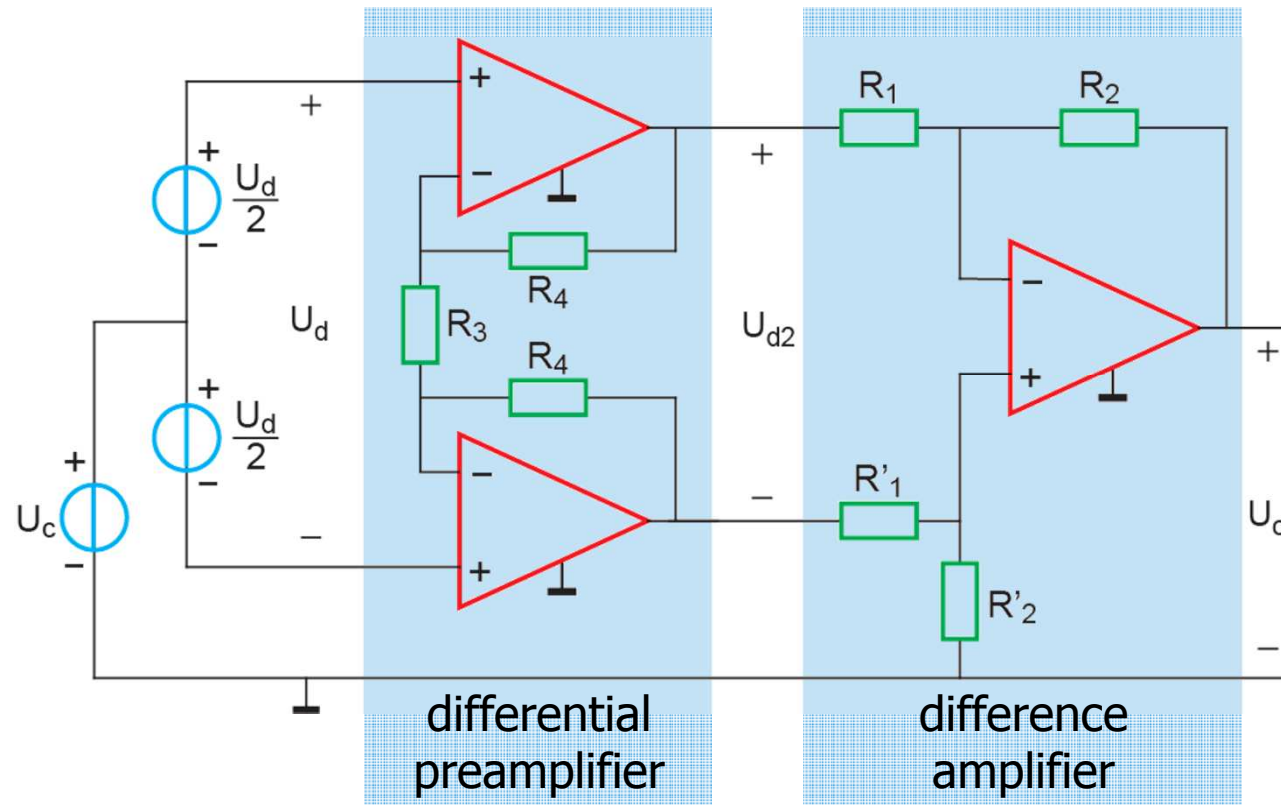

- Advantages:
- higher CMRR than differential amplifier
 - higher input impedance (does not load source)

3-opamp instrumentation amplifier

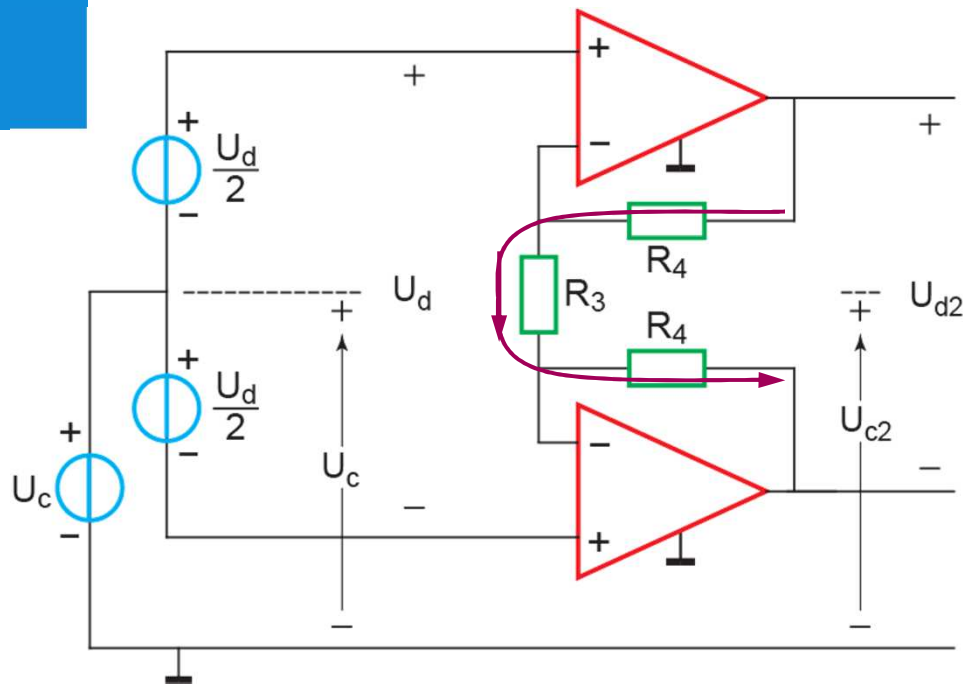

- Virtual grounds opamps \Rightarrow

$$U(R_3) = U_d \Rightarrow I(R_3) = \frac{U_d}{R_3}$$

- This current flows through resistors $R_4 \Rightarrow$


$$U_{d2} = \frac{R_3 + 2R_4}{R_3} U_d = G_{dd} \cdot U_d$$

- So, differential voltage is **amplified** by a factor G_{dd}

- Common-mode voltage at output **equals** that at input:

$$U_{c2} = U_c$$

3-opamp instrumentation amplifier

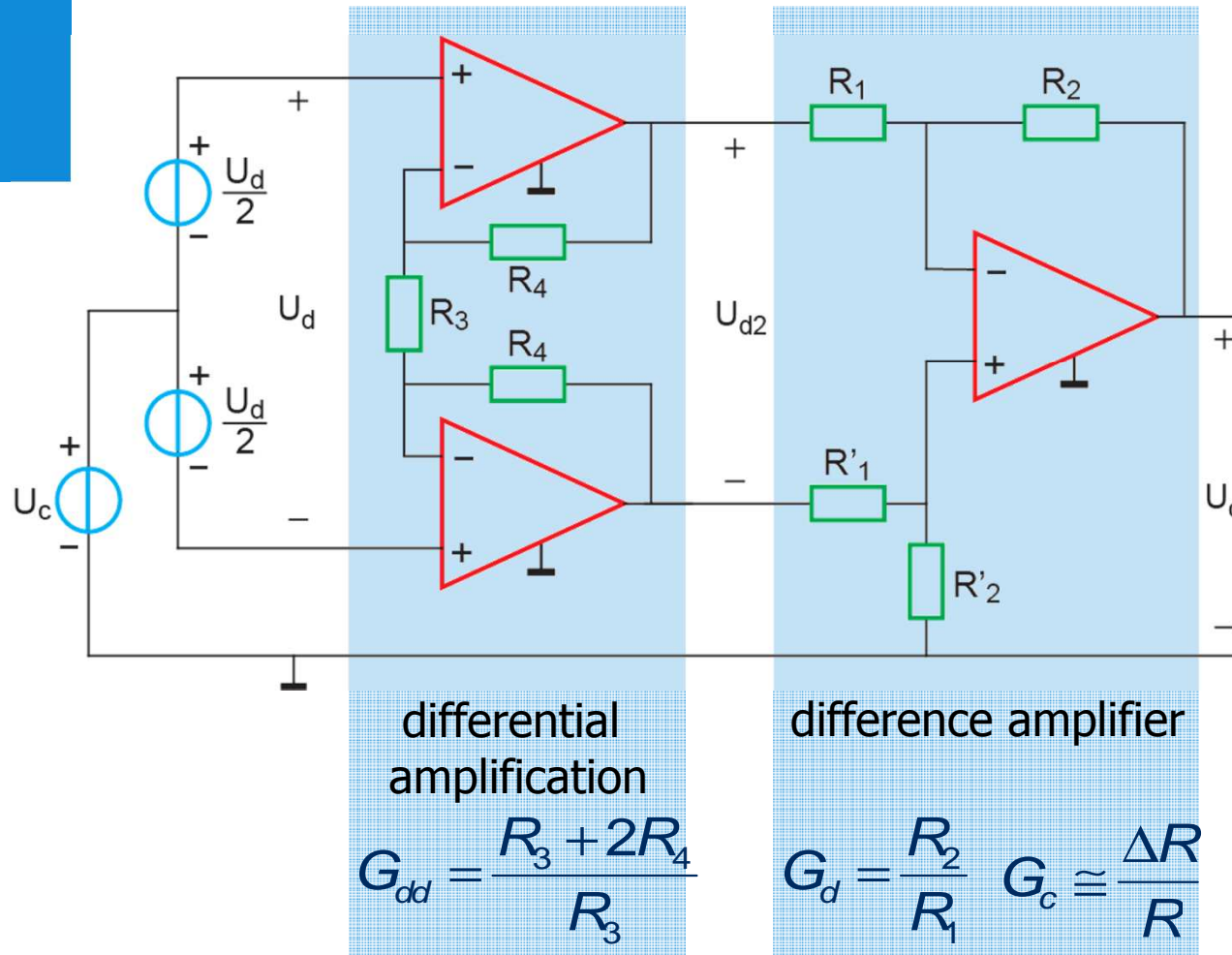

- total gain:


$$G_{d,tot} = \frac{R_3 + 2R_4}{R_3} \cdot \frac{R_2}{R_1}$$

- total CMRR:

$$H_{tot} = G_{dd} \frac{G_d}{G_c}$$

- So, CMRR is G_{dd} times better than that of only a difference amplifier!

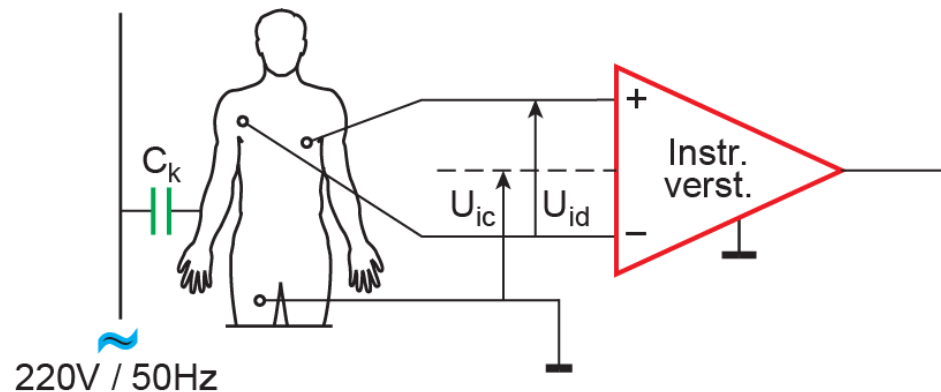Example: bio-potential measurement with an instrumentation amplifier



- ECG signal:
 $U_{id} \sim 10 \mu\text{V}$,
DC – 100 Hz
- Interference: capacitively coupled line voltage:
 $U_{ic} \sim 1 \text{ mV}$,
50 Hz

- Distortion in frequency range ECG signal \Rightarrow filtering is not possible
- But: distortion is mostly common-mode signal \Rightarrow use instrumentation amplifier with sufficiently high CMRR

Summary

- Wheatstone bridge: balance measurement of resistive sensors, mostly suitable for small $\Delta R/R$
- Differential signals of interest (such as output bridge circuit) often superimposed on (unwanted) common-mode signal
- Common-mode rejection ratio (CMRR): measure of the degree to which an amplifier suppresses the common-mode signal
- Opamp differential amplifier: amplifies differential voltage, but
 - input resistors load the source
 - tolerances of components limit the achievable CMRR
- 3-opamp instrumentation amplifier
= differential preamplifier + difference amplifier
 - Less load on the source: high input impedance
 - CMRR increases with gain of the preamplifier

What's next?

- Study:
 - Regtien sections 1.2, 12.1.4, 12.1.5
- Practice:
 - See the exercises on Blackboard!
- Questions, things unclear? Let me know!
M.A.P.Pertijs@tudelft.nl

Next time:
analog-digital convertors