

EE1320: Measurement Science

Lecture 6: Measurement Instruments I

Dr. ir. Michiel Pertijs, Electronic Instrumentation Laboratory

May 29, 2013

Course program 2013


week	date	topic
4.1	Tu 23/4	#1 intro measurements and meas. systems
	Fr 26/4	#2 sensors
4.3	Tu 7/5	#3 sensor readout and signal conditioning
4.4	Tu 14/5	#4 instrumentation amplifiers
	We 15/5	intermediate test
4.5	Tu 21/5	#5 analog-to-digital converters
4.6	We 29/5	#6 measurement instruments I
4.7	Tu 4/6	#7 measurement instruments II
	We 5/6	intermediate test
4.8	Tu 11/6	tutorial
4.11	We 3/7	final exam

Lecturer: dr. ir. Michiel Pertijs

room HB 15.050, M.A.P.Pertijs@tudelft.nl, 015-2786823

Last time...

analog-to-digital converters

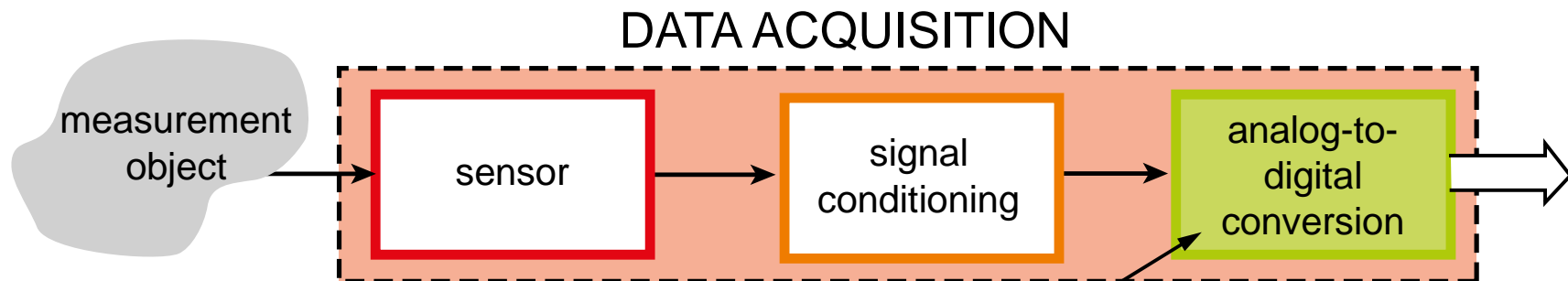

- Basic principles
 - Sampling
 - Quantization
- Three important ADC types:
 - Flash ADCs
 - Dual-slope ADCs
 - Successive-approximation ADCs



Today: measurement instruments

- Measurement instruments
 - voltage measurement
 - current measurement
 - resistance measurement



Overview study material


- Regtien 20.1.1: multimeters
- Regtien 5.1.3: loading errors and impedance matching
- Four-wire resistance measurement (slides)
- Regtien 2.1.2: amplitude measures (peak, rms, etc.)

Multimeters



Voltage measurement

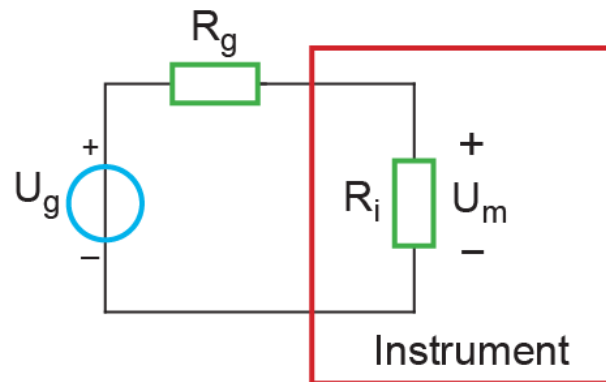- Practical voltage meters impose a load on the source




$$U_m = \frac{R_i}{R_g + R_i} U_g = \underbrace{\left(1 - \frac{R_g}{R_g + R_i}\right)}_{\text{gain error / tracking error}} \cdot U_g$$

- For a small gain error: $R_i \gg R_g$ (*voltage matching*)

Voltage measurement

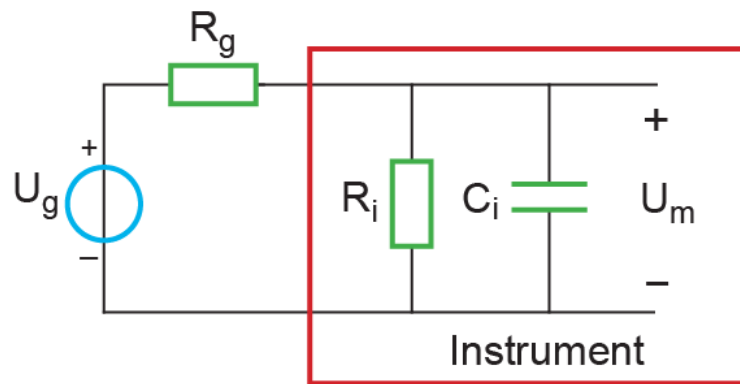- At higher frequencies, the capacitive load also comes into play




$$U_m = \frac{Z_i}{R_g + Z_i} U_g = \underbrace{\left(1 - \frac{R_g}{R_g + Z_i} \right)}_{\text{frequency dependent gain error}} \cdot U_g$$

- Input impedance: $Z_i = R_i \parallel C_i = R_i \frac{1}{1 + j\omega R_i C_i}$

⇒ Larger gain errors at higher frequencies

Current measurement

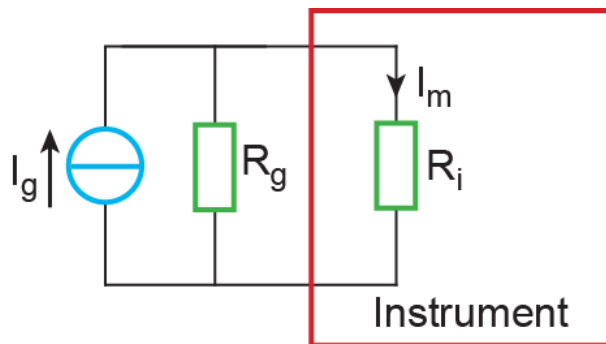- Current meters also impose a load on the source




$$I_m = \frac{R_g}{R_g + R_i} I_g = \underbrace{\left(1 - \frac{R_i}{R_g + R_i} \right)}_{\text{gain error / tracking error}} \cdot I_g$$

- For a small gain error: $R_i \ll R_g$ (*current matching*)
- Inductive load leads to gain errors that increase with frequency

Resistance measurement

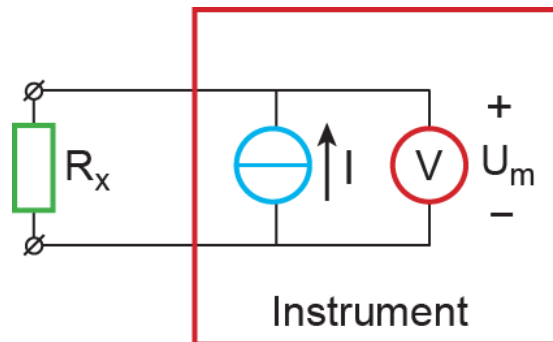
- Basic principle: send a current through the resistor and measure the voltage drop



$$R_m = \frac{U_m}{I} = R_x$$

Resistance measurement

- Wiring induces an offset error

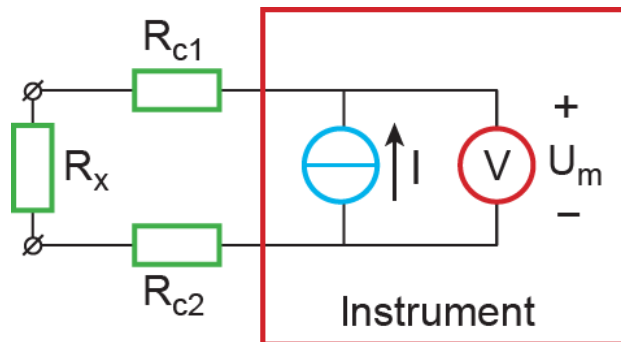

$$R_m = \frac{U_m}{I} = R_x + \underbrace{R_{c1} + R_{c2}}$$


offset error
due to series resistances

How can you solve this???



Four-wire measurement


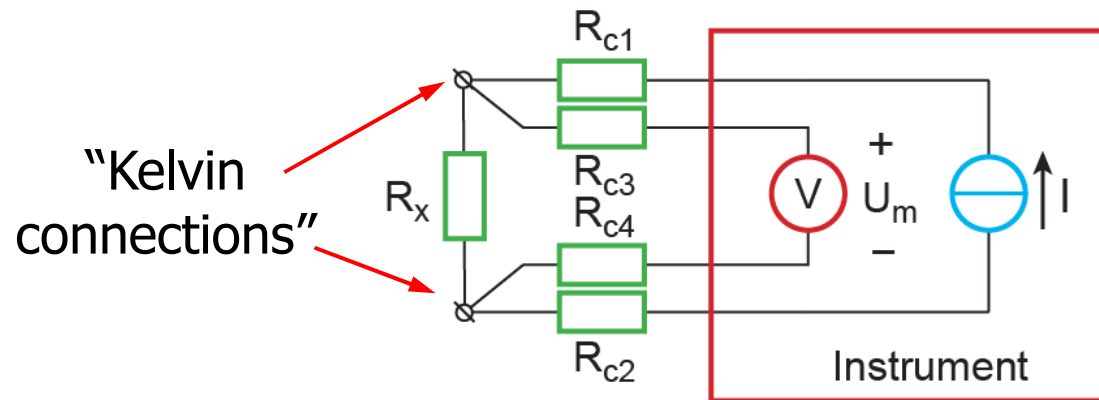
- Four-wire measurement prevents errors due to series resistances:
 - voltage drop across R_{c1} en R_{c2} is not measured
 - voltage drop across R_{c3} en R_{c4} is zero (no current)




$$R_m = \frac{U_m}{I} = R_x$$

Impedance matching

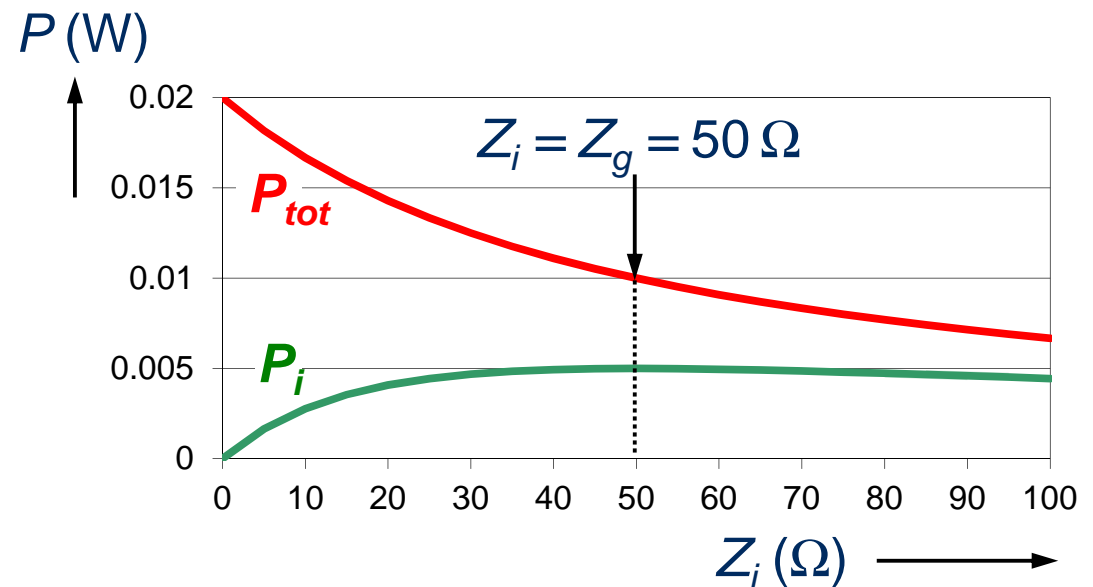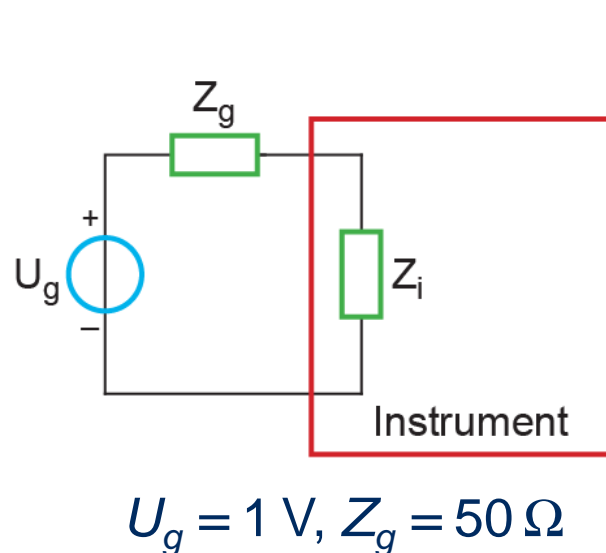- **Non-energetic** matching: no load imposed on source
 - voltage measurement with $Z_i \gg Z_g$
 - current measurement where $Z_i \ll Z_g$
- **Energetic** matching / impedance matching: power transfer is maximized: $Z_i = Z_g$




Impedance matching

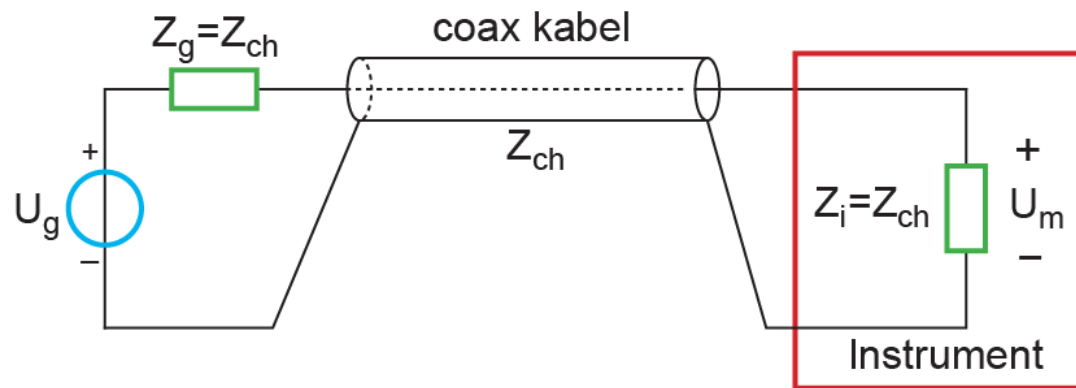

- Especially important at high frequencies, when the wavelength is comparable to the cable length
- Cable acts as a **transmission line**
- Impedance matching is needed to prevent **reflections**


Characteristic impedance

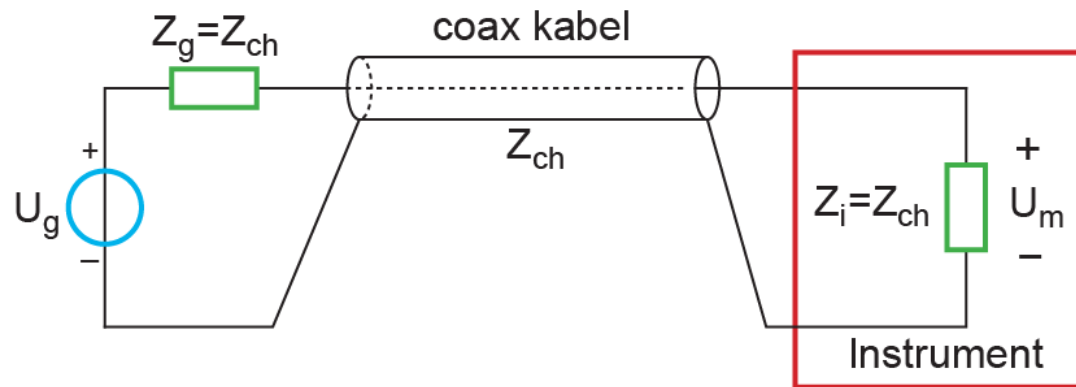

- Impedance matching: source impedance = input impedance = **characteristic impedance** of the cable
- Characteristic impedance is determined by cable geometry: often **50Ω** for coax measuring cables
- Ideal lossless cable $\Rightarrow U_m = U_g / 2$


Amplitude measurement of periodic signals

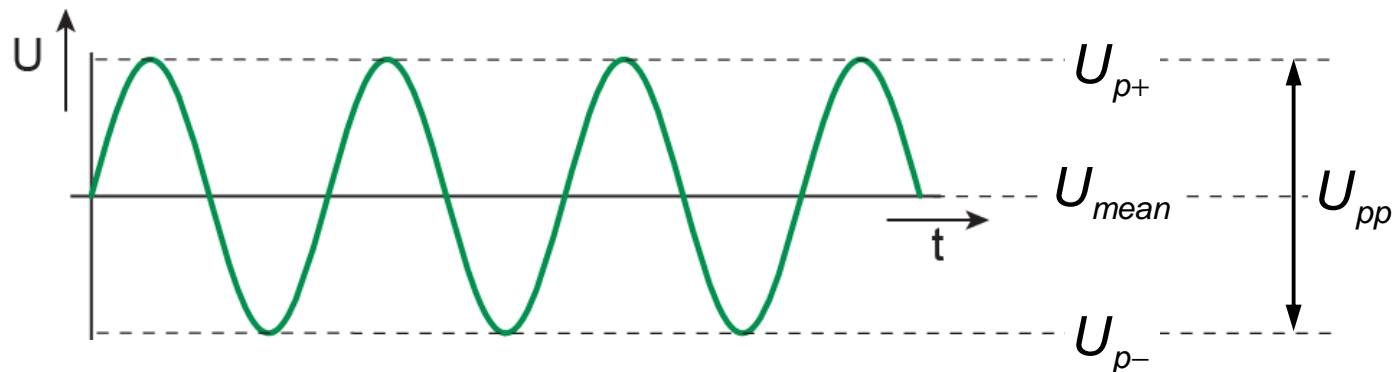- Average value, peak value, peak-to-peak value



Amplitude measurement of periodic signals

- **Root-mean-square (rms) value**


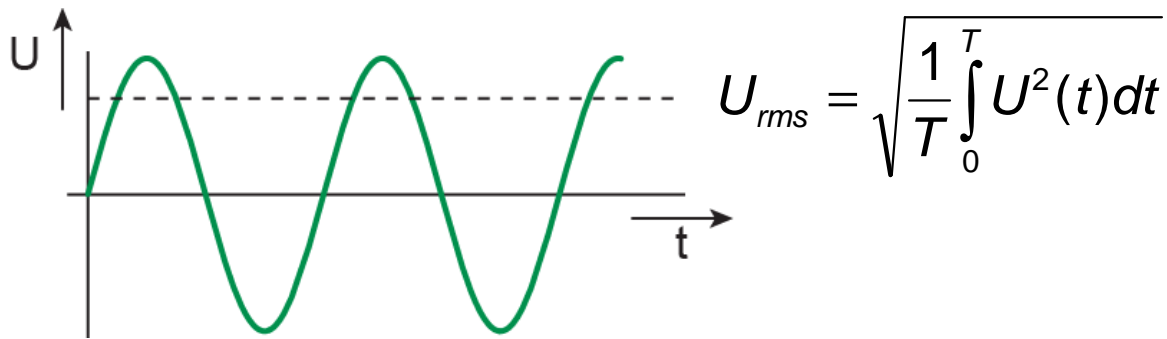


- Measure for the signal power:
 $U(t)$ dissipates the same average power in a resistor as a DC voltage of U_{rms}

- **Crest factor:** $CF = \frac{U_{p+}}{U_{rms}}$ Sine? $CF = \sqrt{2}$


AC measurement with a rectifier

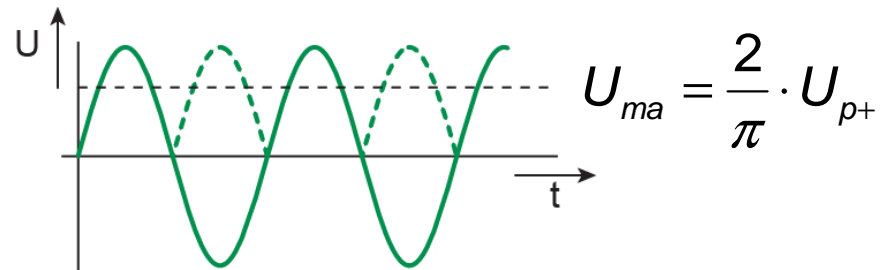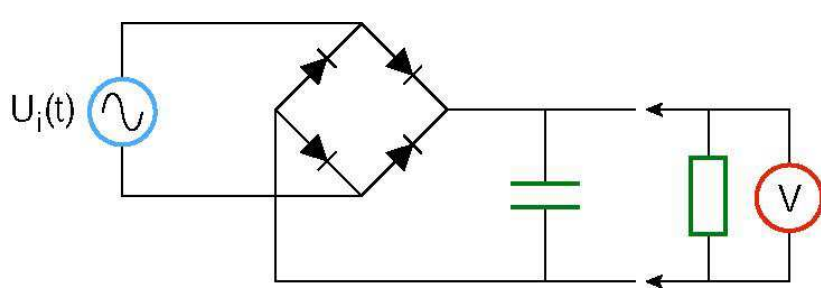- Some instruments estimate the rms value U_{rms} based on the average of the modulus U_{ma} and a correction factor




- correction factor for a sine:
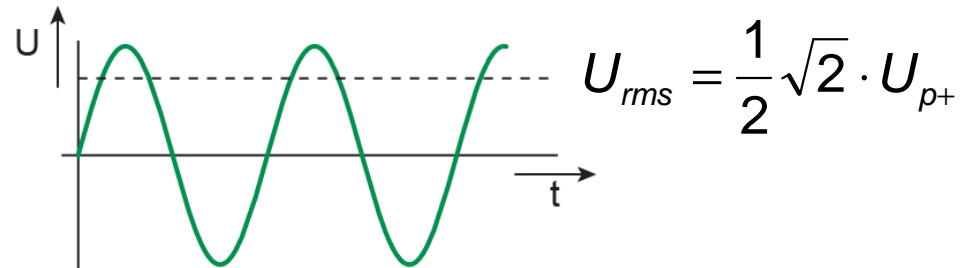
$$U_{rms} = \frac{\pi}{2\sqrt{2}} \cdot U_{ma} \cong 1.11 \cdot U_{ma}$$



- Correction factor is strongly dependent on the waveform!

Exercise: triangular waveform

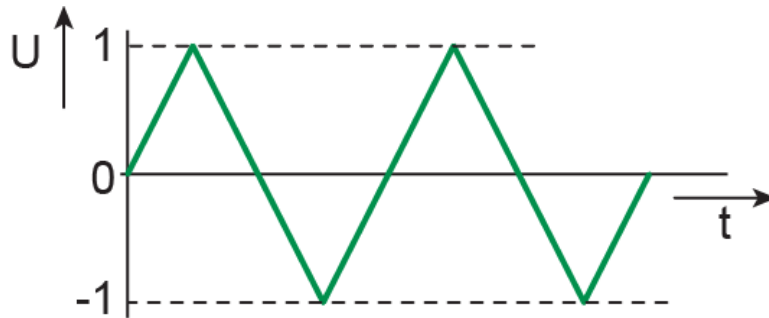


$$U_{p+} = 1$$

$$U_{pp} = 2$$

$$U_{rms} = \frac{1}{3}\sqrt{3}$$

$$U_{ma} = \frac{1}{2}$$

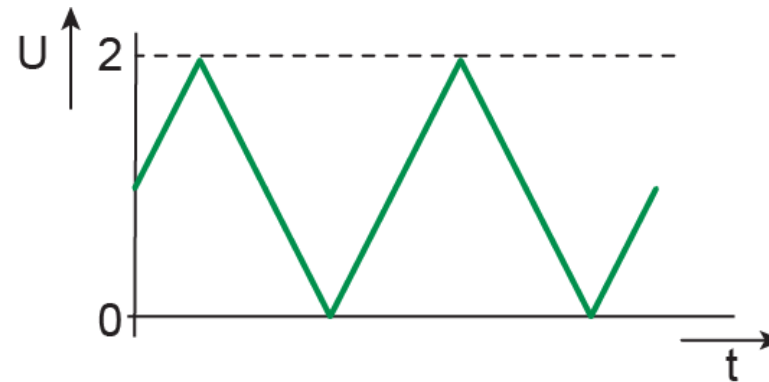


$$U_{p+} =$$

$$U_{pp} =$$

$$U_{rms} =$$

$$U_{ma} =$$

Exercise: triangular waveform

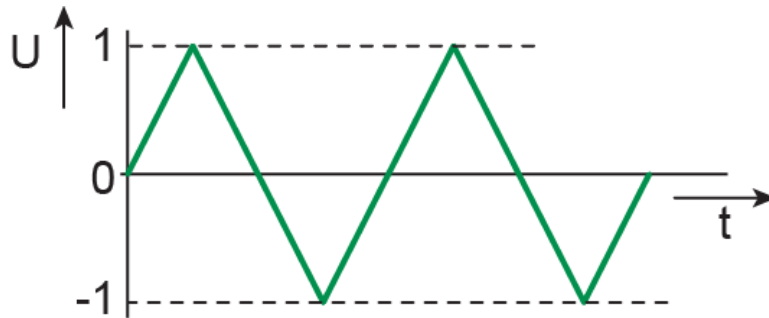


$$U_{p+} = 1$$

$$U_{pp} = 2$$

$$U_{rms} = \frac{1}{3}\sqrt{3}$$

$$U_{ma} = \frac{1}{2}$$

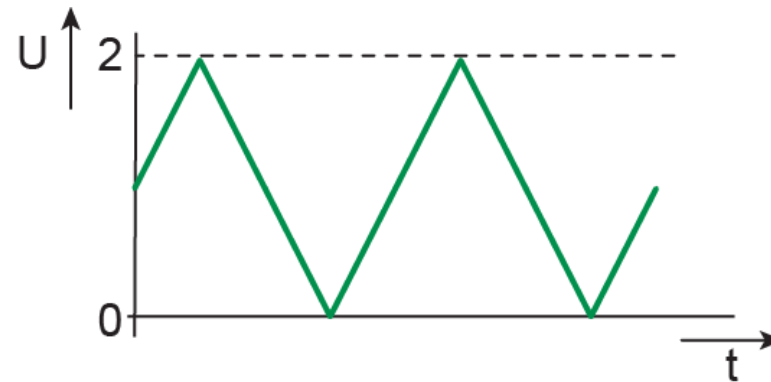

$$U_{p+} = 2$$

$$U_{pp} = 2$$

$$U_{rms} = \sqrt{1^2 + \left(\frac{1}{3}\sqrt{3}\right)^2} = \sqrt{1 + \frac{1}{3}} = \frac{2}{\sqrt{3}}$$

$$U_{ma} = U_{mean} = 1$$



Summary

- Voltage and current measurement
 - input impedance yields gain errors (scale errors)
 - at high frequency, impedance matching is needed for signal transfer without reflections
 - several measures exist for the amplitude of AC signals
- Resistance measurement
 - 2-wire measurement results in errors due to cable resistance
 - solution: 4-wire measurement with Kelvin connections

What's next?

- Study:
 - Regtien sections 2.1.2, 5.1.3, 20.1.1, slides
- Practice:
 - See Blackboard for exercises!
- Questions, things unclear? Let me know!
M.A.P.Pertijs@tudelft.nl

Next time:
Measurement instruments II