

# VLSI Test Technology and Reliability (ET4076)



Lecture 9 (2)

## **Built-In-Self Test**

(Chapter 15)

Said Hamdioui

Computer Engineering Lab  
Delft University of Technology  
2009-2010

# Learning aims

---



- Describe the concept and the architecture of BIST
- Compare BIST different implementations
- List the pros and cons of BIST
- Develop a BIST at higher level

# Contents

---

- Motivation
- General BIST Architecture
- BIST Hierarchy
- BIST Building blocks
- Aliasing
- BIST Cost
- Logic BIST implementation
  - Test-Per-Clock BIST
  - Scan Based Test
- Memory BIST
- Summary

# BIST Motivation.....(1)

  

# BIST Motivation.....(2)

- To solve variety of **test problems**
  - Solve Test-Access problem (Lack of direct pin access)
    - Increasing chip logic-to-pin ratio – harder observability
  - Ability to carry out “At Speed Test”
    - Increasing difficulty in performing at speed test using ATE
  - Useful for field test and diagnosis
    - Less expensive than a local ATE
  - Improve diagnosis (system, board, component)
    - Increasingly dense devices and fast clocks
  - Reduce test cost
    - Increasing test generation and application times
  - Shortage of test/DFT engineers
  - Hard testability insertion
    - Designers unfamiliar with gate-level logic, since they design at behavioral level

# BIST Motivation.....(3)

---

## □ Other advantages

- Reduce chip pin count = reduced # ATE driver/sensor channels
- Reduce program runtime (depends on # of tests and clock frequency)
- Lower system test effort
- Improved system maintenance and repair
- Improved component repair
- Lower test development cost
  - BIST can be automatically added with CAD tools
- Can test many units in parallel

# BIST Motivation.....(4)

---

## □ In the past

- BIST was seen as **“one off”** investment
- Once it has been used and device passed the tests, there was no further use of BIST

=> **Hard to economically justify BIST**

## □ Today

- Boundary scan changed the view
- Access of BIST through boundary scan
- BIST can be re-run at all stages of the product cycle


- Especially system level for diagnostic purposes

=> **Various form of BIST are being requested**

- By designers in system companies
- By EDA companies to respond with appropriate test-synthesis tools
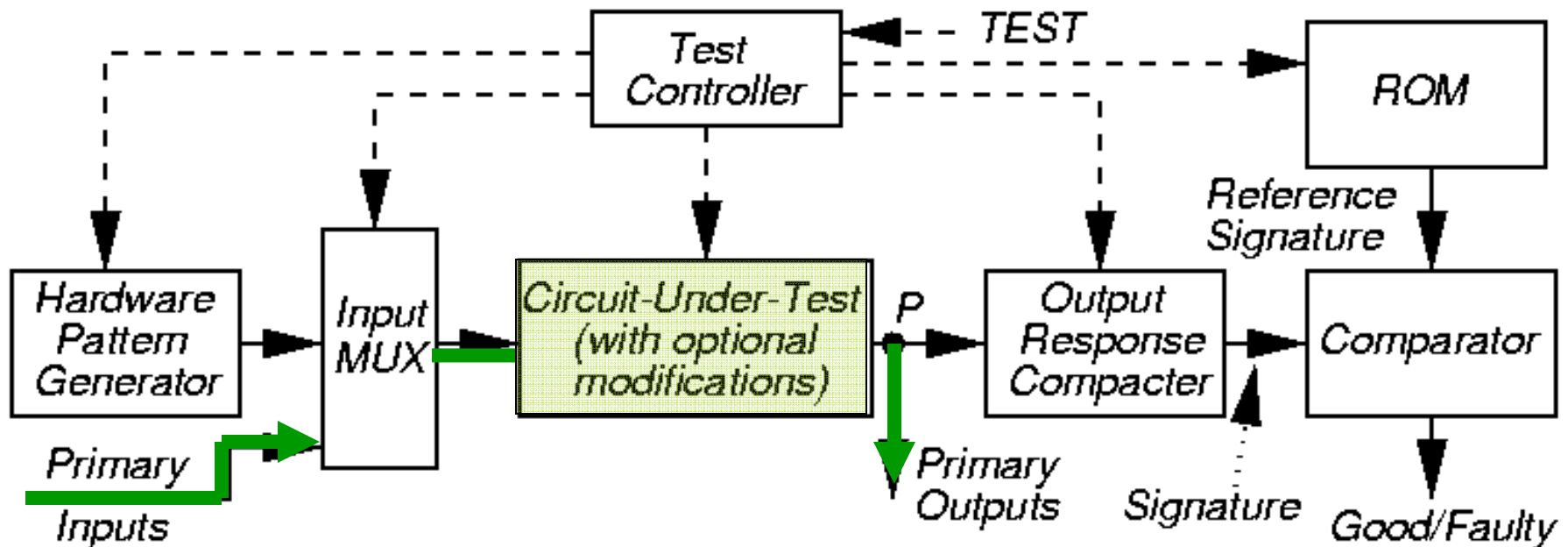
# General BIST Architecture


- BIST cannot test wires (and transistors):
  - From PI pins to Input MUX
  - From POs to output pins
  - Can be tested using ATE or JTAG
- In normal mode: PIs → input MUX → Circuit → POs




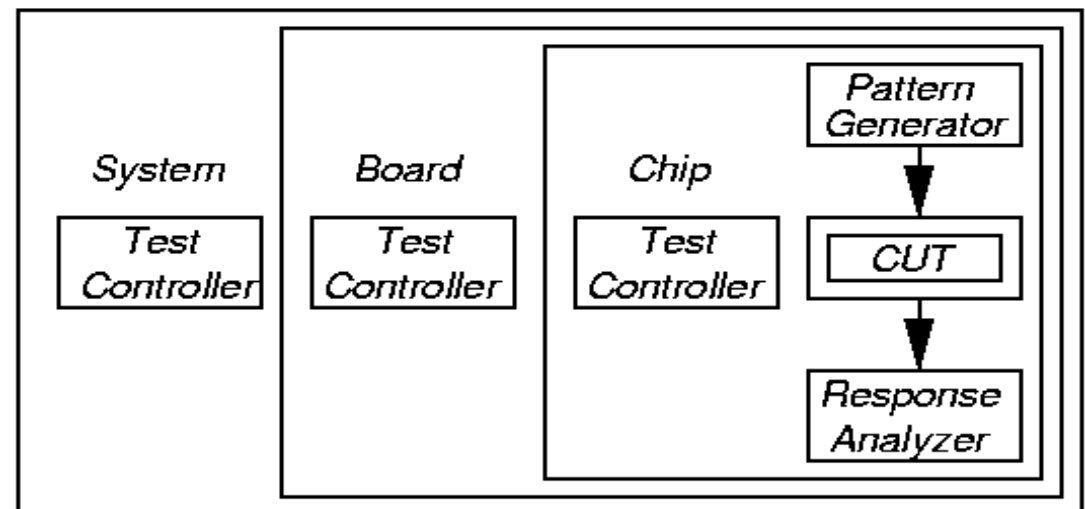
# BIST Hierarchy

- BIST Hierarchy at all three levels of packaging
  - System has multiple PCBs, each with multiple chips
- System Test controller can activate self-test simultaneously on all boards
- Board Test Controller can activate self-test on all chips
  - Chip Test Controller executes self-test and transmits results to Board Test Controller
  - Board Test Controller accumulates results from all chips and transmits them to System Test Controller
  - System Test Controller use the results to e.g., isolate the faulty chips and boards
  
- BIST Diagnosis effective only if very high fault coverage considered



# BIST Building blocks....Pattern generator

## □ Many approaches


- ROM
  - Very expensive in chip area
- LFSR: Linear Feedback Shift Register
  - Generate Pseudo-random tests (1M or more)
  - Use very little hardware
  - Currently the preferred BIST pattern generation method
- Binary counters
  - Generate exhaustive test sequence
  - Too much test time if # of PIs is huge
  - Use more hardware than LFSR
- LFRS combined with few patterns in ROM
  - To augment the fault coverage
- Modified counters
- ...

# BIST Building blocks....Pattern generator

- LFSR: Linear Feedback Shift Register
  - A shift register with feedback from the last stage and others
  - It has no other input beside the clock
  - Outputs of FFs form the test pattern
  - Number of unique test patterns is equal to the # of the states of the circuit
    - Determined by the # and locations of feedbacks
  - Two types:
    - **Standard LFSR** (External XOR LFSR)
    - **Modular LFSR** (Internal XOR LFSR)
  - Example: Standard LFSR
  - Characteristic polynomial
 
$$f(x) = 1 + x + x^3$$

Initialized to 001 (7 patterns)


X0	1	0	0	1	0	1	1	1	0	..
X1	0	0	1	0	1	1	1	0	0	..
X2	0	1	0	1	1	1	0	0	1	..

 

# BIST Building blocks....Pattern generator
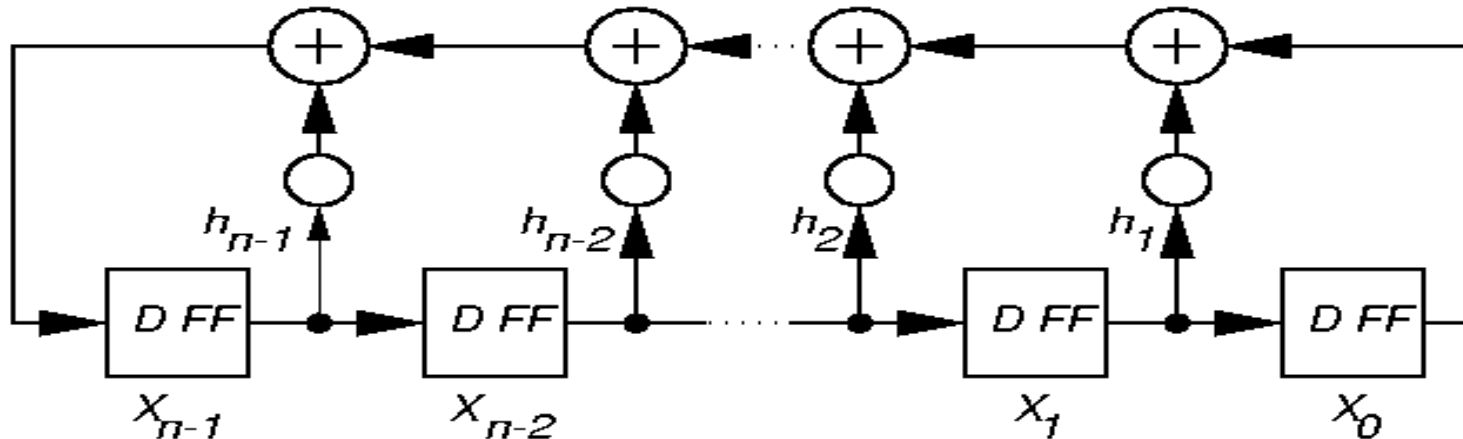
## □ Generic Standard LFSR:

- Produces patterns algorithmically – repeatable
- Has most of desirable random # properties
- Need not cover all  $2^n$  input combinations
- Long sequences needed for good fault coverage




$$\begin{bmatrix} X_0(t+1) \\ X_1(t+1) \\ \vdots \\ X_{n-3}(t+1) \\ X_{n-2}(t+1) \\ X_{n-1}(t+1) \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 & \dots & 0 & 0 \\ 0 & 0 & 1 & \dots & 0 & 0 \\ \vdots & \vdots & \vdots & \ddots & \vdots & \vdots \\ 0 & 0 & 0 & \dots & 1 & 0 \\ 0 & 0 & 0 & \dots & 0 & 1 \\ 1 & h_1 & h_2 & \dots & h_{n-2} & h_{n-1} \end{bmatrix} \begin{bmatrix} X_0(t) \\ X_1(t) \\ \vdots \\ X_{n-3}(t) \\ X_{n-2}(t) \\ X_{n-1}(t) \end{bmatrix}$$

$$X(t+1) = T_s X(t) \quad (T_s \text{ is } \textit{companion matrix})$$

# BIST Building blocks....Pattern generator
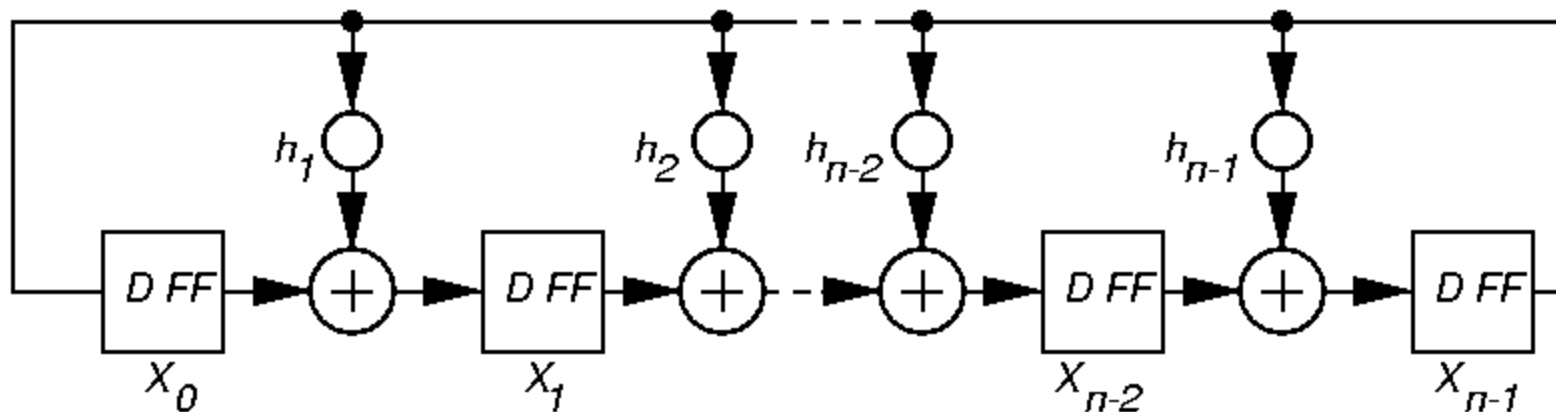
## Generic Modular LFSR

- Described by *companion matrix*  $T_m = T_s^T$  ;  $X(t + 1) = T_m \times X(t)$
- Equivalent to standard External XOR LFSR
  - With a different state assignment; Faster – usually does not matter
  - Same amount of hardware



$$\begin{bmatrix} X_0(t+1) \\ X_1(t+1) \\ X_2(t+1) \\ \vdots \\ X_{n-3}(t+1) \\ X_{n-2}(t+1) \\ X_{n-1}(t+1) \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & \dots & 0 & 0 & 1 \\ 1 & 0 & 0 & \dots & 0 & 0 & h_1 \\ 0 & 1 & 0 & \dots & 0 & 0 & h_2 \\ \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots \\ 0 & 0 & 0 & \dots & 0 & 0 & h_{n-3} \\ 0 & 0 & 0 & \dots & 1 & 0 & h_{n-2} \\ 0 & 0 & 0 & \dots & 0 & 1 & h_{n-1} \end{bmatrix} \begin{bmatrix} X_0(t) \\ X_1(t) \\ X_2(t) \\ \vdots \\ X_{n-3}(t) \\ X_{n-2}(t) \\ X_{n-1}(t) \end{bmatrix}$$


# BIST Building blocks....Pattern generator

## LFSR Theory (see book)

- Cannot initialize to all 0's (it hangs)
- If  $X$  is initial state, progresses through states  $X, T_S X, T_S^2 X, T_S^3 X, \dots$
- *Matrix period:*
  - Smallest  $k$  such that  $T_S^k = I$
  - $k$  is LFSR cycle length
- Described by **characteristic polynomial:**
$$f(x) = |T_S - I X| \quad (= |T_m - I X| \text{ if modular LFSR})$$
$$= 1 + h_1 x + h_2 x^2 + \dots + h_{n-1} x^{n-1} + x^n$$
- Maximal-length LFSR if period  $K=2^n-1$

# BIST Building blocks....Pattern generator

FC versus pattern count

 


(a) Top curve -- random pattern testing with acceptable fault coverage.  
(b) Bottom curve -- unacceptable random pattern testing.

- Bottom: Random-Pattern Resistant circuit (like PLAs)
  - Requires **weighted pseudo-random pattern generation**
  - Or insertion of testability hardware

# BIST Building blocks....Pattern generator
 
## □ Weighted Pseudo-Random Pattern Generation



- If  $p(1)$  at all PIs is 0.5,  $p_F(1) = 0.5^8 = 1/256$

$$p_F(0) = 1 - (1/256) = 255/256$$

- Will need enormous # of random patterns to test a stuck-at 0 fault on  $F$  -- LFSR  $p(1) = 0.5$ 
  - We must not use an **ordinary** LFSR to test this
- IBM – holds patents on weighted pseudo-random pattern generator in ATE



# BIST Building blocks....Response Compaction

---


- Severe amounts of data in CUT response to LFSR patterns
  - Example:
    - Generate 5 million random patterns
    - CUT has 200 outputs
    - Leads to: 5 million x 200 = **1 billion** bits response
  
- Uneconomical to store and check all of these responses on chip
  
- Responses must be compacted

# BIST Building blocks....Response Compaction

## Different approaches

 
### Parity Testing

- Parity bit calculated using modulo 2 summation
- i.e.,  $(\sum r_i) \text{ modulo } 2$



 
### One Counting

- Number of 1s in the response stream is counted


 
### Transition Counting

- Number of transitions  $0 \rightarrow 1$  and  $1 \rightarrow 0$  in the response counted
- i.e.,  $\sum (r_i \text{ XOR } r_{i+1})$



# BIST Building blocks....Response Compaction

## Signature analysis using LFSR


- Single-Input Signature Register/ Analyzer (SISR)
- Also known as **Cyclic Redundant Check Code CRCC**
  - Treat data bits from circuit POs to be compacted as a decreasing order coefficient polynomial
  - SISR divides the **PO polynomial** by its **characteristic polynomial**
    - Leaves remainder of division in LFSR
    - Must initialize LFSR to *seed value* (usually 0) before testing
  - After testing
    - compare signature in LFSR to known good machine signature
- Critical: Must compute good machine signature

# BIST Building blocks....Response Compaction

## Single-Input Signature Register (SISR)

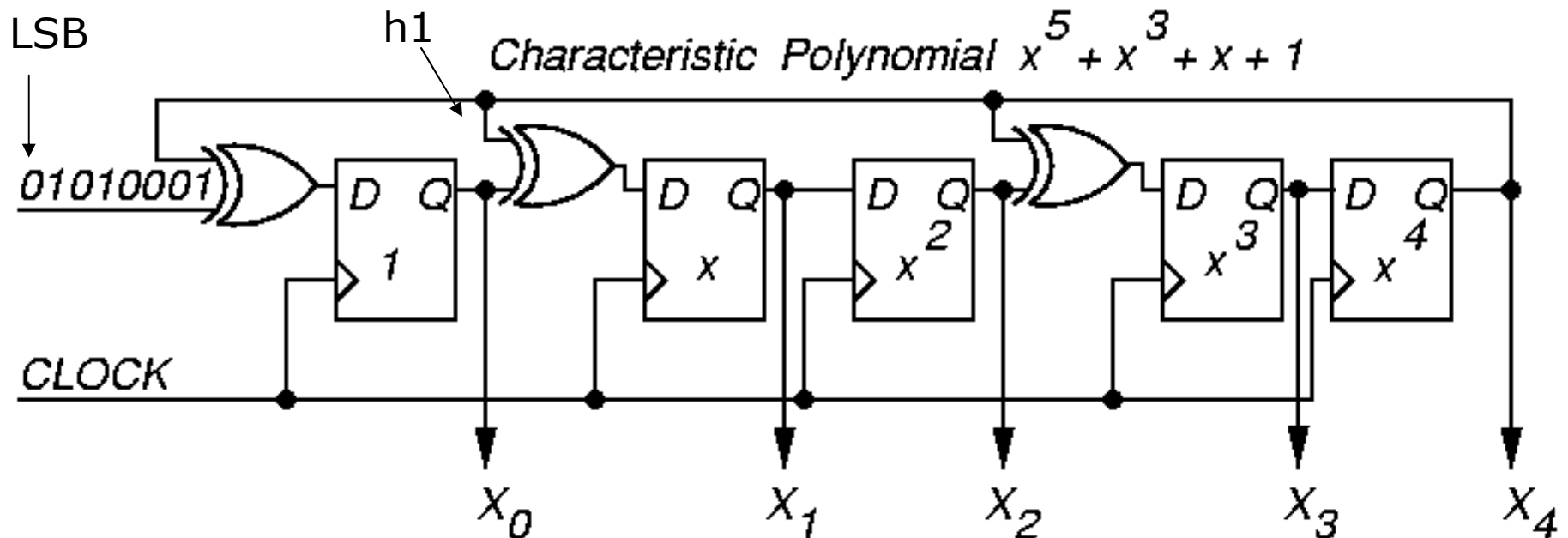Example:

- LFSR seed value is **0000**
- PO polynomial: 10001010  $\rightarrow x^7 + x^3 + x$
- Characteristic polynomial:  $x^5 + x^3 + x + 1$
- Remainder of division:  $x^3 + x^2 + 1$  (= **01101**)



# BIST Building blocks....Response Compaction


- **Problem Single-Input Signature Register (SISR)**
  - Too much hardware if one of these is put on each *primary output* (PO)
  - E.g., if 200 outputs,  $200 \times 5$  FFs, and  $3 \times 200$  XOR gates will be required for the previous example
  
- **Solution:**
  - **MISR: Multiple-Input Signature Register**
  - compacts all outputs into one LFSR
    - Works because LFSR is linear – obeys superposition principle
    - Superimpose all responses in one LFSR
    - Final remainder is XOR sum of remainders of polynomial divisions of each PO by the characteristic polynomial

# BIST Building blocks....Response Compaction

## Multiple-Input Signature Register

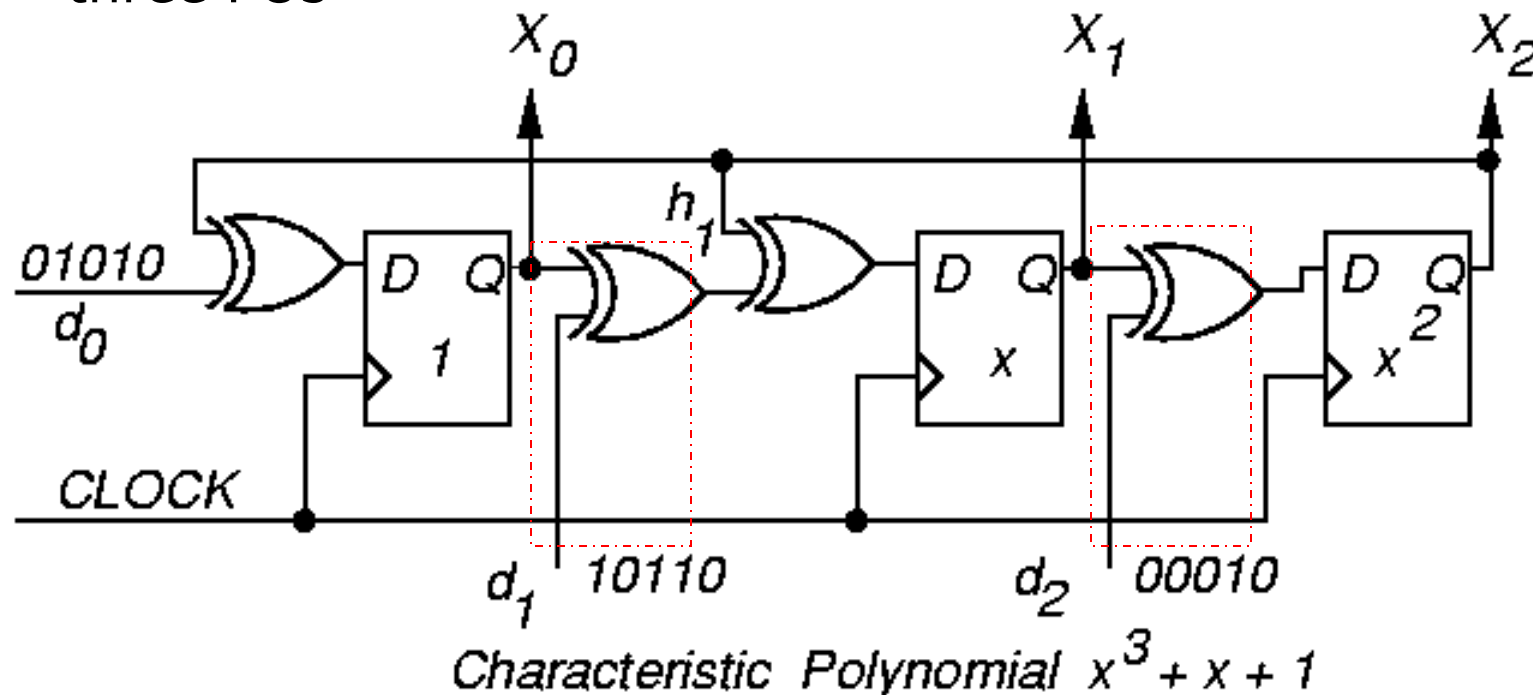
Example:

- PO polynomials:
  - PO1=d0=01010  $\rightarrow x^3+x$
  - PO2=d1=01101  $\rightarrow x^3+x^2+1$
  - PO3=d2=01000  $\rightarrow x^3$
- Characteristic polynomial:  $x^3+x+1$
- Resulting signature is the XOR of the three different signatures due to the polynomial division of each of the three POs


 
# Aliasing

- When using compaction, the resulted compacted signature may be identical to the fault-free signature => **aliasing**
  - **It lowers the fault coverage**
- Example
  - Transition count (TC)




Fault will be **not detected** as TC=2 in both cases

# Aliasing

- Parity checking
  - Aliasing frequently occurs
- One counting
  - Permutes placement of 0's and 1's
- Count transition
  - Alias less than one counting
  - It checks for correct number of 0's and 1's AND also *partially* the **correct ordering** of 0's and 1's
- MISR
  - Aliasing depends on k: polynomial degree (e.g., k=3 for  $x^3+x+1$  )
  - The larger k, the smaller the aliasing
  - Aliasing probability is about  **$1/2^k$**
  - MISR has more aliasing than LFSR on single PO



# Aliasing .....Experiment Hardware

 

- 3 bit exhaustive binary counter for pattern generator

Pattern <i>abc</i>	Responses			
	Fault-free	a sa1	f sa1	b sa1
000	0	0	1	0
001	1	1	1	0
010	0	1	1	0
011	0	1	1	0
100	0	0	1	1
101	1	1	1	1
110	1	1	1	1
111	1	1	1	1
Signatures				
Transition count	3	3	0	1
LFRS	001	101	001	010

# BIST Costs


---

- Chip area overhead and pin overhead:
  - Test controller
  - Hardware pattern generator
  - Hardware response compacter
  - Testing of BIST hardware
  - At least 1 pin needed to activate BIST operation
- Performance overhead
  - Extra path delays due to BIST
- *Yield loss*
  - Due to increased chip area or more chips in system because of BIST
- Reliability reduction
  - Due to increased area
- Increased BIST hardware complexity
  - happens when BIST hardware is made testable


# Logic BIST implementation.....Classification
 
## □ Test-Per-Clock BIST

- Also called Concurrent Built-In Logic Block Observer **CBILBO**
- FFs at the inputs of the kernel/circuit are configured as parallel pattern generation (e.g., LFSR)
- FFs at the output of the kernel/circuit are configured as signature analyzer (e.g. SISR, MISR)
- (Faults are tested every clock period)



(a) Test-per-clock system.

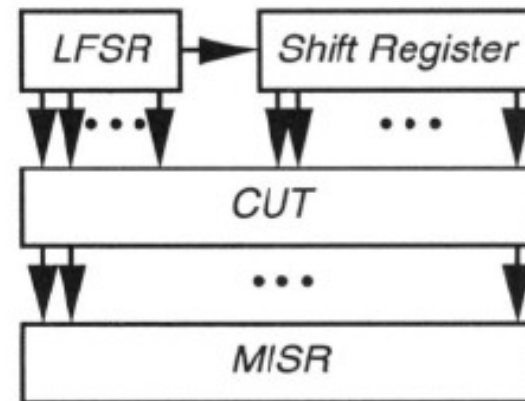


(b) Large input count test-per-clock system.

## ■ Test-Per-Scan BIST

# Logic BIST implementation.....Classification
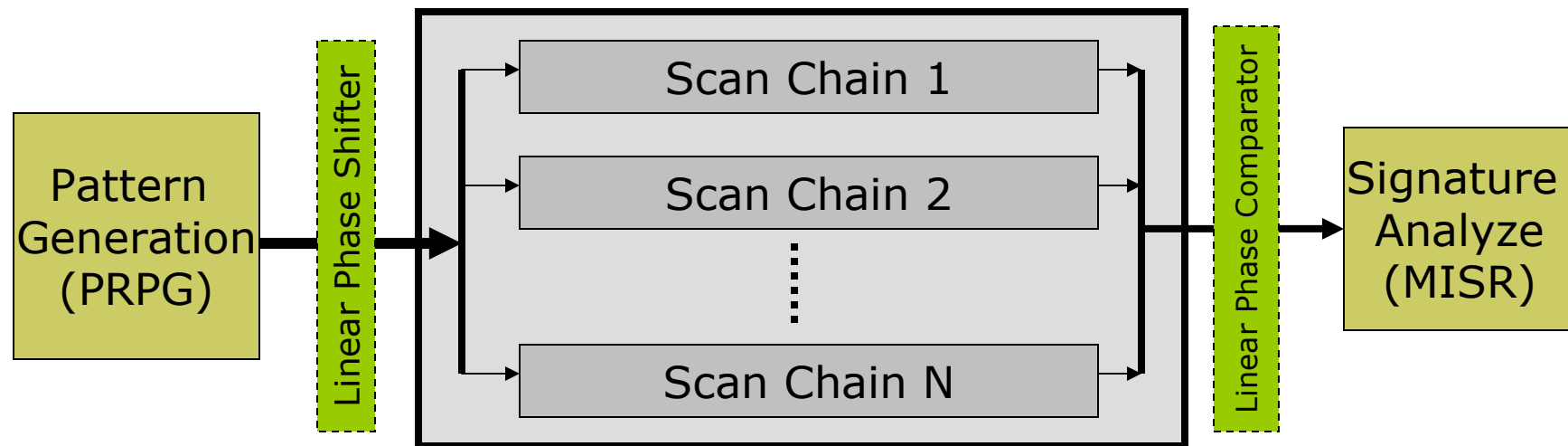
## Test-Per-Scan BIST

- ❑ Also called **STUMPS** (**S**elf-**T**est **U**sing **M**ISR and **P**arallel **S**RSG)
- ❑ The FFs of the circuit are configured as one or more scan chains
- ❑ Pattern generator and Signature analyzer are added to the circuit
- ❑ Testing of a faults is done in many clock cycles (scan-in test vector, conduct the test, scan-out the response)
- ❑ Take significantly more time than Test-Per-Clock BIST
- ❑ To reduce the length of PRPG and MISR and improve the randomness of PRPG, optional Linear Phase Shifter and Comparator are used



# Logic BIST implementation.....Comparison

## □ Hardware overhead

- Test-Per-Clock BIST requires the replacement of the circuit FFs with special configurable registers (normal, scan, pattern generator, signature analyzer)
- Scan based BIST requires the replacement of circuit FFs with scan FFs; it also requires additional registers for pattern generation and signature analyzer.
- Area overhead for Scan Based BIST is lower only if the circuit is large.

## □ Test application

- Test-Per-Clock BIST supports at speed-testing
  - Covers faults due transients in power/ground lines due to switching
- Scan based BIST requires SCL+1 for a single test
  - SCL: length of the longest scan path
- Scan based BIST can be implemented at the chip level
  - Even if the modules do not have BIST circuitry (but include scan design)
- Scan based BIST most used in industry

# Memory BIST

## General architecture


- Input Test generator
  - Address & Data
- Output analyzer
  - Compare & pass/fail
  - Response Data Evaluation
- Overall controller
  - Communication

## Cost

- Some design effort
- Learning curve
- Chip area
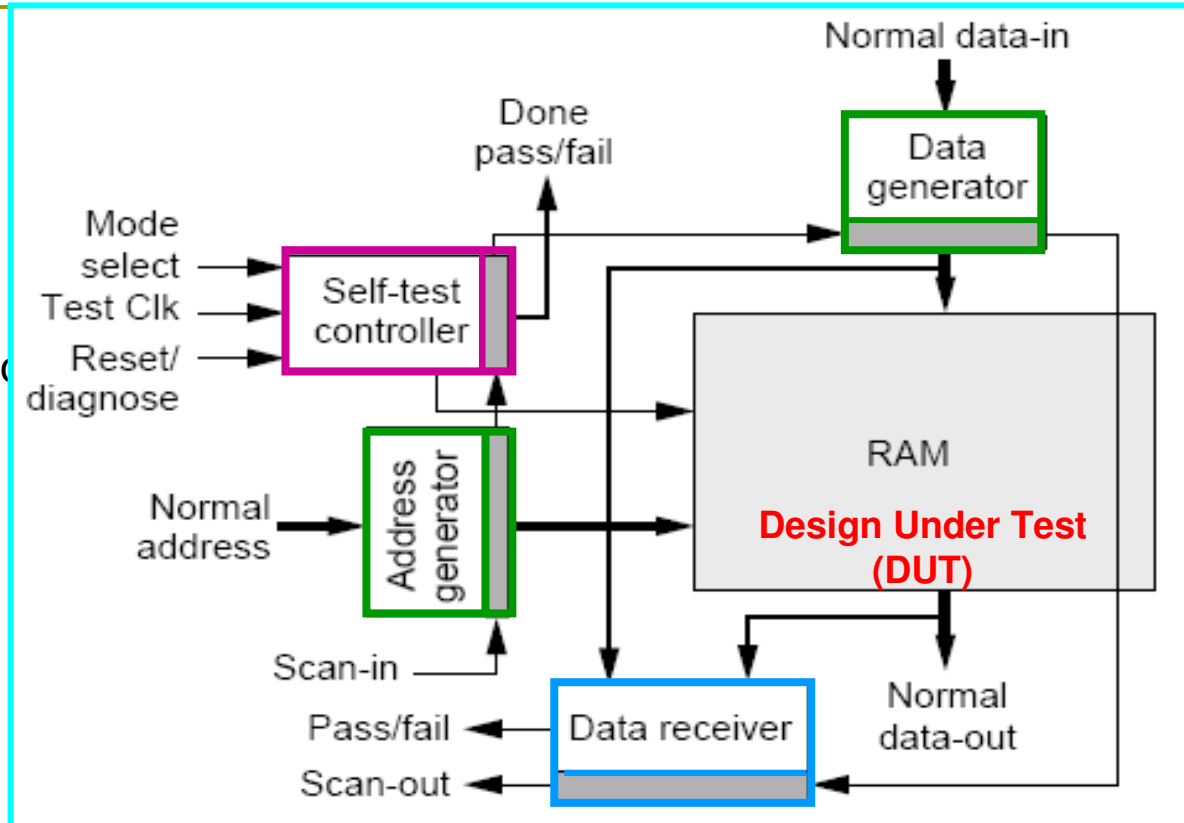
## Advantages

- + Short test time as compared with scan
- + The only practical & cost-effective solution for large embedded memories (>16KB?)
- + At speed testing
- + Diagnosis capabilities
- + No expensive ATE required



# Summary (1)

---

- BIST architecture
  - Pattern generator
  - Response compaction
  - Comparator
  - Test controller
  
- Preferred BIST methods
  - LFSR pattern generator
  - MISR response compacter
  
- Two ways to implement BIST
  - Test-per-clock (CBILBO)
  - Test-per-scan (STUMPS)

# Summary(2)

---

## □ BIST benefits:

- At-speed testing for delay & stuck-at faults
- Drastic ATE cost reduction
- Field test capability
- Faster diagnosis during system test
- Less effort to design testing process
- Shorter test application times

## □ BIST cost

- Overhead
  - Test controller, extra circuit delay, Input MUX, pattern generator, response compacter, DFT to initialize circuit & test the test hardware, at least one additional pin
- Performance overhead and yield loss