

VLSI Test Technology and Reliability (ET4076)



Lecture 2 (p2)

Fault Modeling
(Chapter 4)

Said Hamdioui

Computer Engineering Lab
Delft University of Technology
2009-2010

Previous lecture

- What are the different test stages?
- What is the difference between parametric and functional/structural testing? Give examples.
- What does DUT, ATE, and multi-site testing mean?
- How can be ATE cost reduced?
- ..

Learning aims of today

- Describe the difference between a defect and a fault model
- Describe some common defects
- Describe common used fault models
- Define the fault set of a combinational circuits
- Use the concept of fault equivalence and fault dominance to reduce the fault set

Contents

- ❑ Functional versus structuring testing
- ❑ Level of abstraction
- ❑ Why model faults?
- ❑ Failure mechanisms
- ❑ Defect classification
- ❑ Common fault models
- ❑ Stuck-at faults
 - ❑ Single stuck-at faults
 - ❑ Fault equivalence
 - ❑ Fault dominance and checkpoint theorem
 - ❑ Classes of stuck-at faults and multiple faults
- ❑ Transistor faults

Some definitions

□ Defect

- An **unintended** difference between the implemented hardware and its intended design
- E.g., process defects, age defects, ...

□ Error of faulty behavior

- A **wrong** output signal produced by a defective system.
- An “effect” whose cause is some “defect”

□ Fault model


- A representation of a “defect” at an “abstract function level”

Functional versus structural testing

- Assume 10 input AND function
 - To guarantee that the circuit function correctly, $2^{10} = 1024$ input patterns needs to be evaluated
 - Too long test time
 - Not realistic for real circuits (with several hundred of inputs)
 - **This is Functional Test**
 - Useful for verification of design (before manufacturing)

- **Structural test**
 - Use fault models
 - Allow the development of test algorithms
 - Reduces the test complexity
 - (Technology independent fault models and tests)


Model and level of abstraction

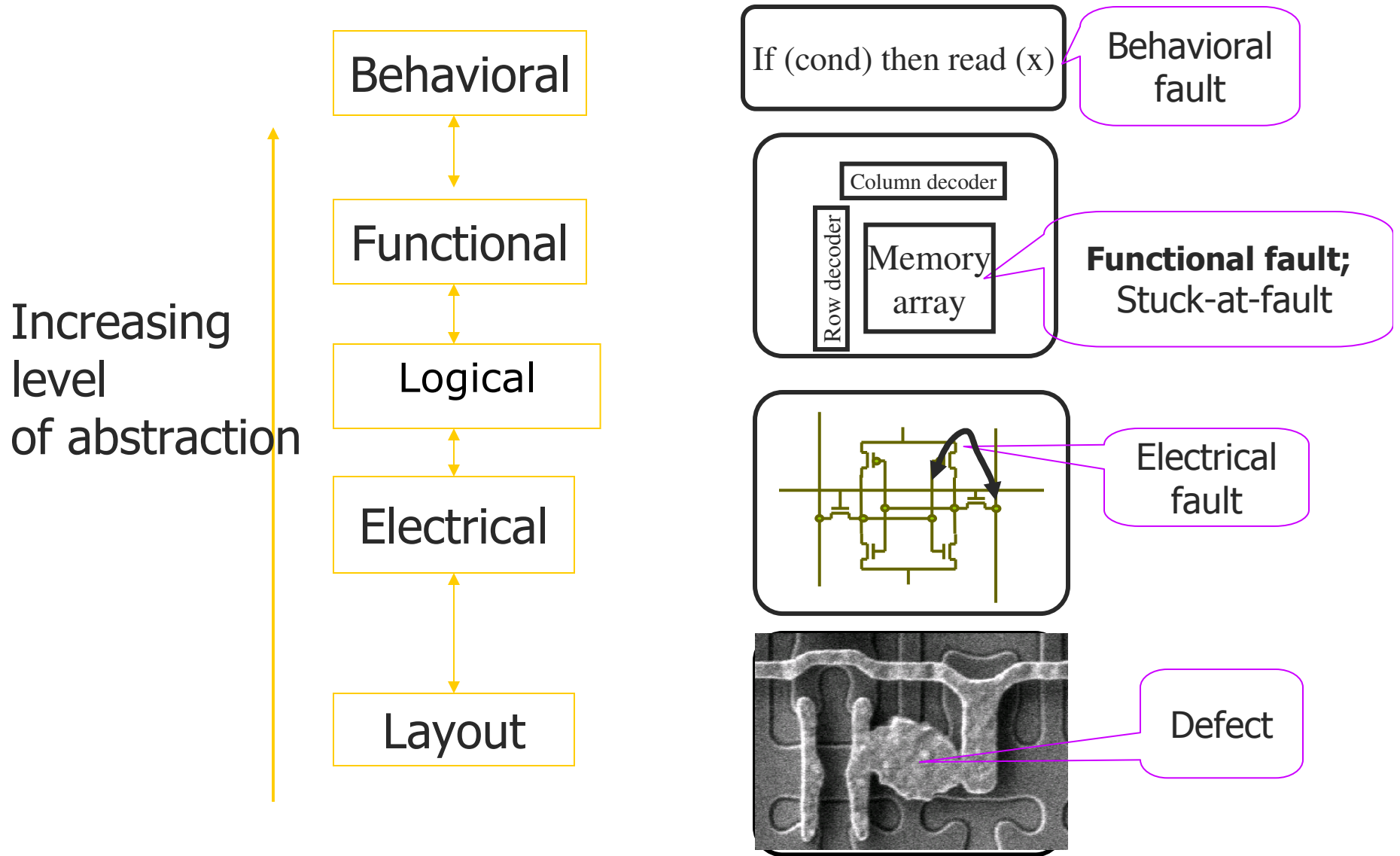

Why Model Faults?

- ❑ I/O function tests inadequate for manufacturing (functionality versus component and interconnect testing)
- ❑ Real defects (often mechanical) too numerous and often not analyzable
- ❑ A fault model identifies targets for testing
- ❑ A fault model makes analysis possible
- ❑ Effectiveness measurable by experiments

Failure mechanisms.....*Classification*

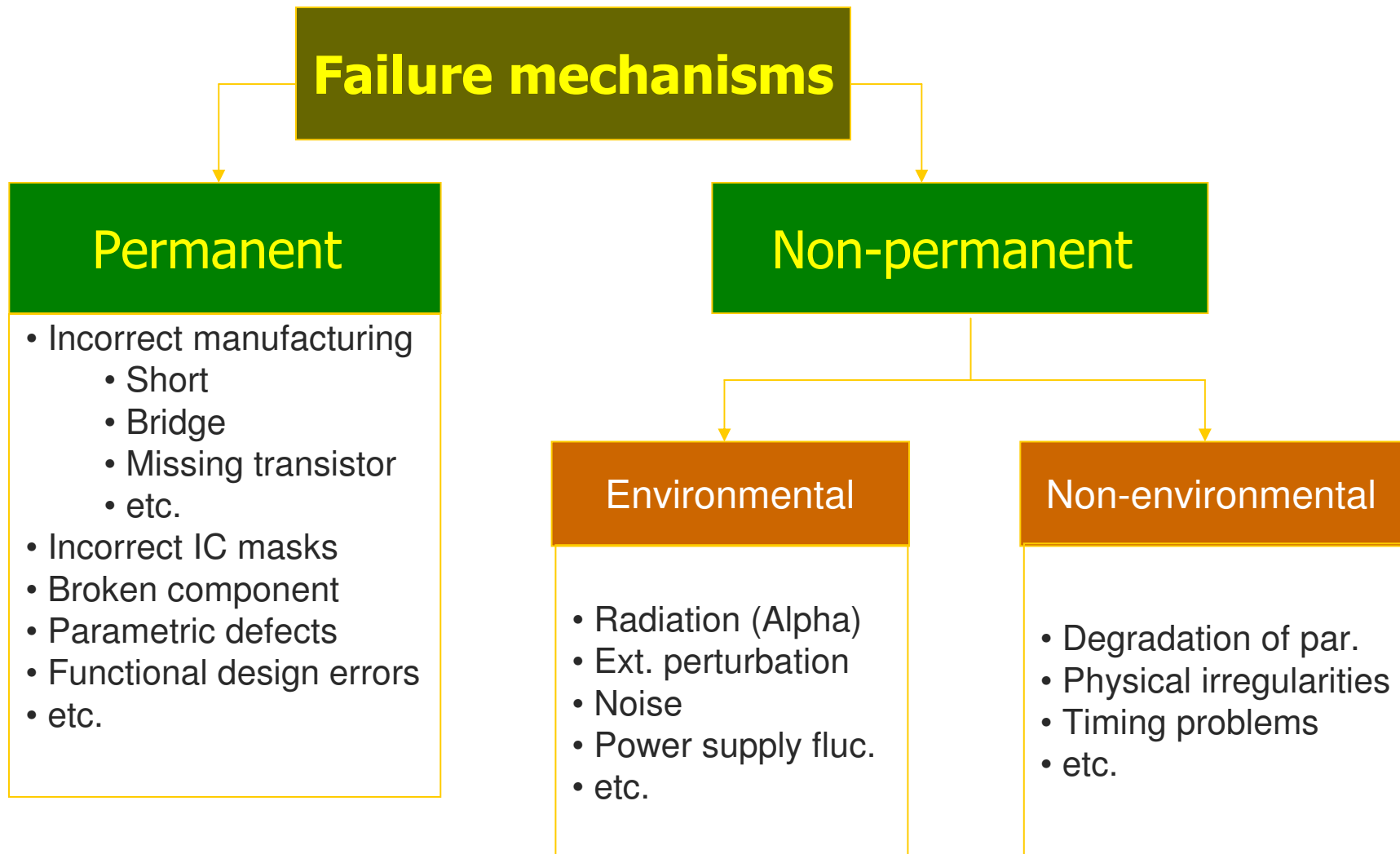


Failure mechanisms

Real Defects in Chips

- Processing defects
 - Missing contact windows
 - Parasitic transistors
 - Oxide breakdown
 - . . .
- Material defects
 - Bulk defects (cracks, crystal imperfections)
 - Surface impurities (ion migration)
 - . . .
- Time-dependent failures
 - Dielectric breakdown
 - Electromigration
 - . . .
- Packaging failures
 - Contact degradation
 - Seal leaks
 - . . .

Failure mechanisms.... *Use of copper*

 - ❑ Example of open defects on the data lines of memory, found by failure analysis using scanning electron microscopy (SEM)
- ❑ Cause permanent and delay faults
- ❑ Copper wiring is difficult to deposit on silicon which causes opens




Ref. Infineon, DE

**Manufacturing shift toward copper wiring
Increases susceptibility to opens**

Failure mechanisms..... *Crosstalk*

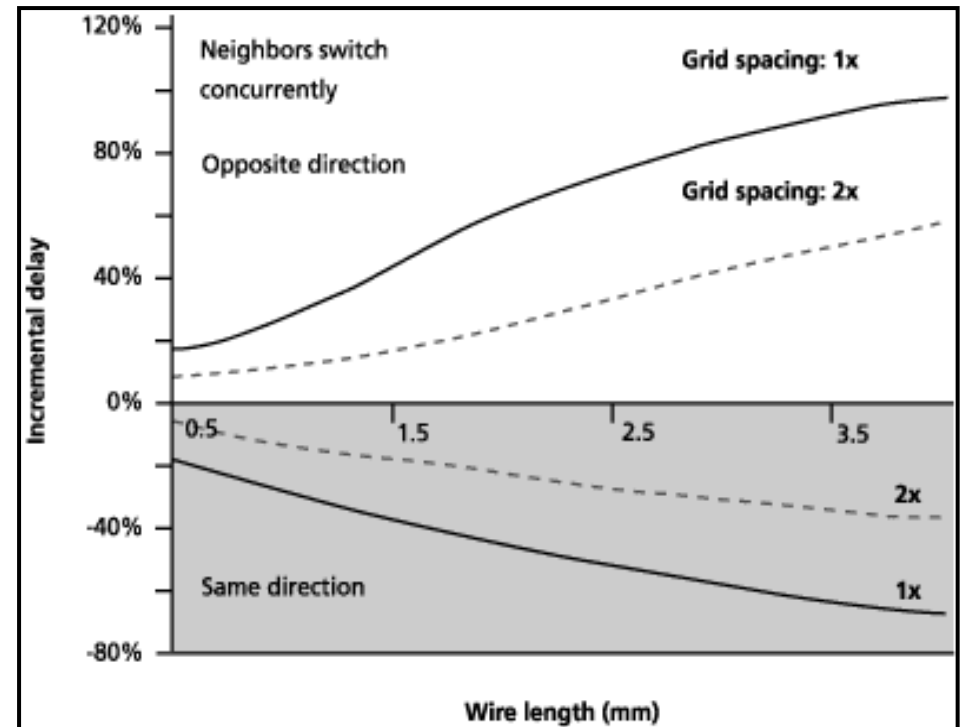
- ❑ Crosstalk and delay increase with:
 - increasing wire length
 - shrinking dimensions
- ❑ Delay causes non-permanent faults
- ❑ These faults are difficult to detect
- ❑ Becomes a hot topic with scaling technology



Continued increase in integration density increases susceptibility to crosstalk

Failure mechanisms .. *Proximity effects*

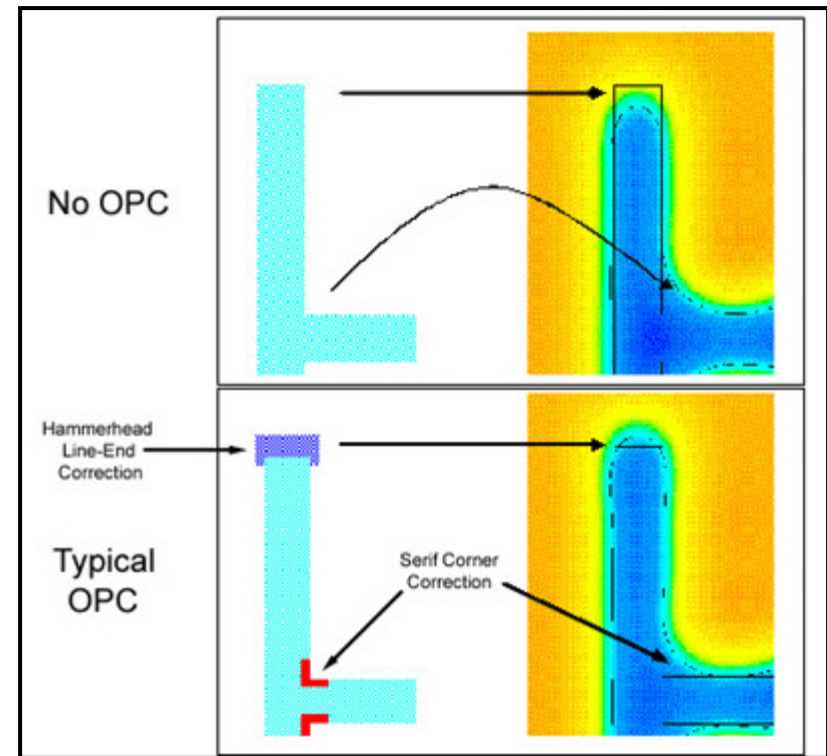- ❑ Small feature sizes are difficult to manufacture due to proximity effects
- ❑ Optical proximity correction (OPC) improves the quality of shapes on silicon
- ❑ Correction algorithms are becoming too complex



Ref: Synopsys website

**Continued decrease in feature sizes
increases on-chip variations in behavior**

Observed *PCB* Defects

Defects on Printed Circuit Board (PCB) are different from that of VLSI chips

Defect classes	Occurrence frequency (%)
Shorts	51
Opens	1
Missing components	6
Wrong components	13
Reversed components	6
Bent leads	8
Analog specifications	5
Digital logic	5
Performance (timing)	5


Ref.: J. Bateson, *In-Circuit Testing*, Van Nostrand Reinhold, 1985.

Common Fault Models

- ❑ **Single stuck-at faults**
- ❑ **Bridging faults**
- ❑ PLA faults (missing cross-point, extra cross-point, ...)
- ❑ **Delay faults** (transition, path, ...)
- ❑ **Intermittent faults** (appears and disappear within ΔT)
- ❑ **Memory faults**
- ❑ **Multiple faults**
- ❑ **Transistor faults** (stuck-open and stuck-short faults)
- ❑ Behavior faults (processors: instruction fault, branch fault,)
- ❑ Analog faults
- ❑ ...
- ❑ For more examples, see the book (p. 60-70)

Single stuck at fault!!!


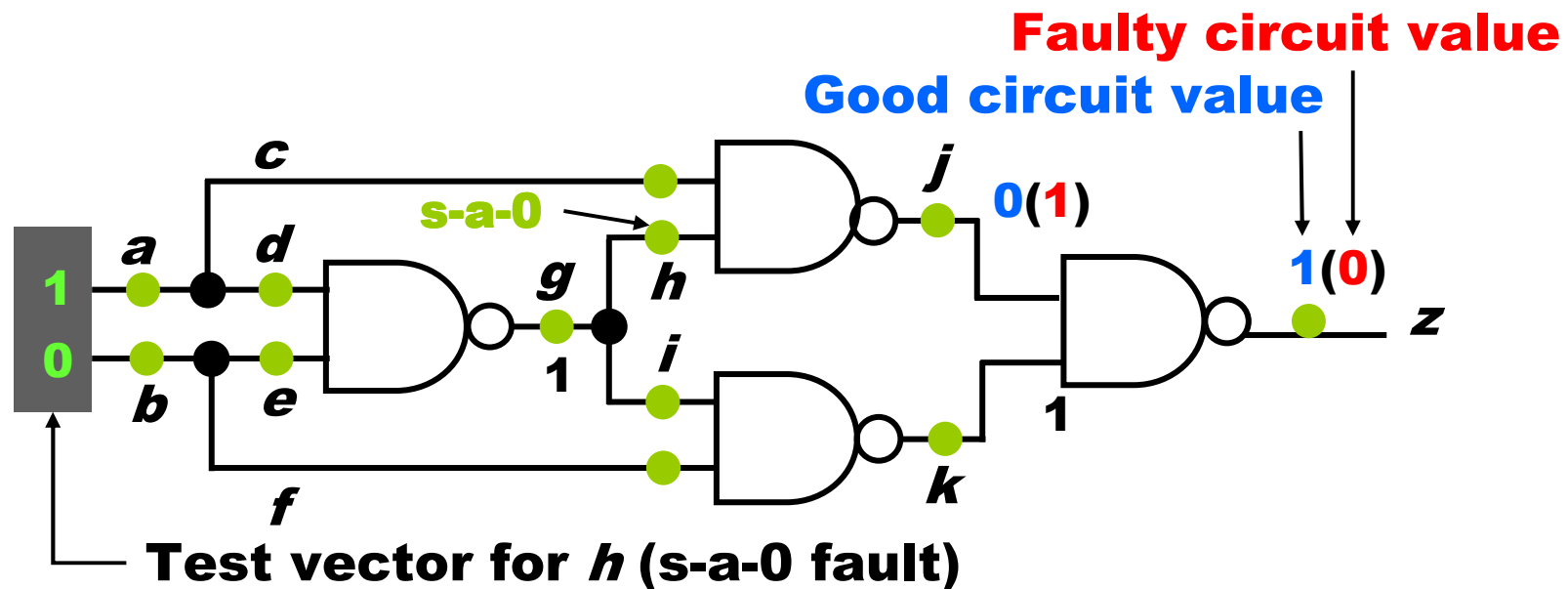
- Three properties define a single stuck-at fault
 - Only one line is faulty
 - The faulty line is permanently set to 0 or 1
 - The fault can be at an input or output of a gate
- Example: XOR circuit has 12 fault sites (●) and 24 single stuck-at faults
 - Fault sensitization, Fault propagation, Line justification







Fault equivalence

- Number of fault sites in a Boolean gate circuit:
 $= \#PI + \#gates + \#(fanout\ branches)$.
- **Fault equivalence:**
Two faults f_1 and f_2 are equivalent if all tests that detect f_1 (f_2) also detect f_2 (f_1).
- If faults f_1 and f_2 are equivalent then the corresponding faulty functions are identical (*indistinguishable*).
- **Fault collapsing:**
All single faults of a logic circuit can be divided into disjoint equivalence subsets, where all faults in a subset are mutually equivalent. A collapsed fault set contains one fault from each equivalence subset.

Fault equivalence.... Equivalence rules

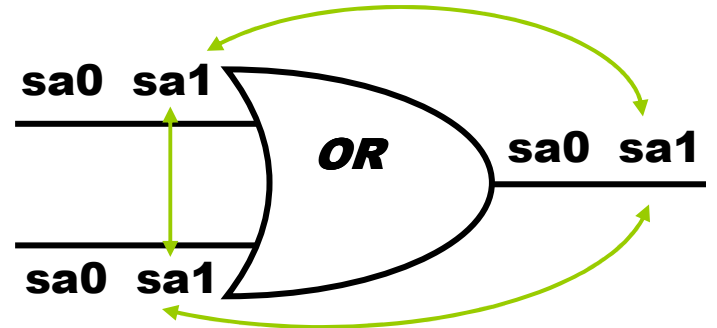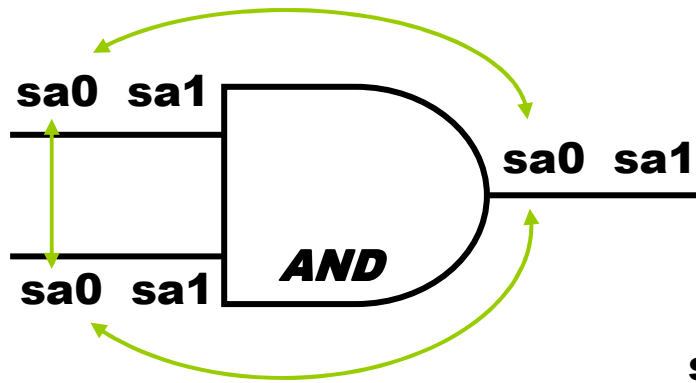


WIRE

 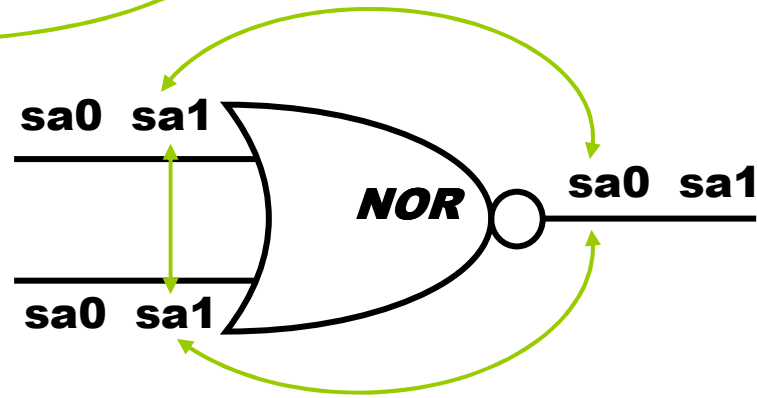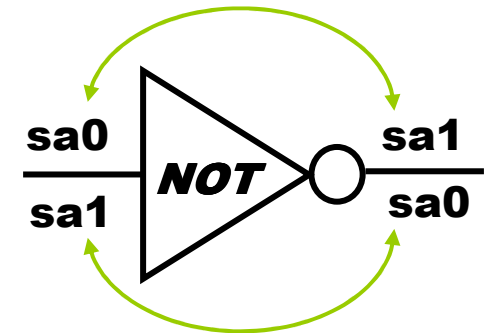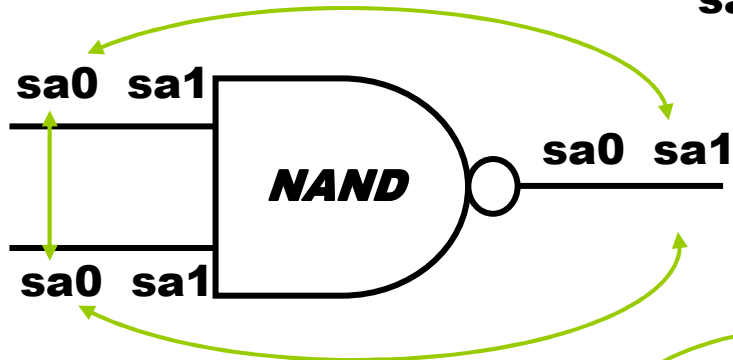

Fault equivalence..... Example

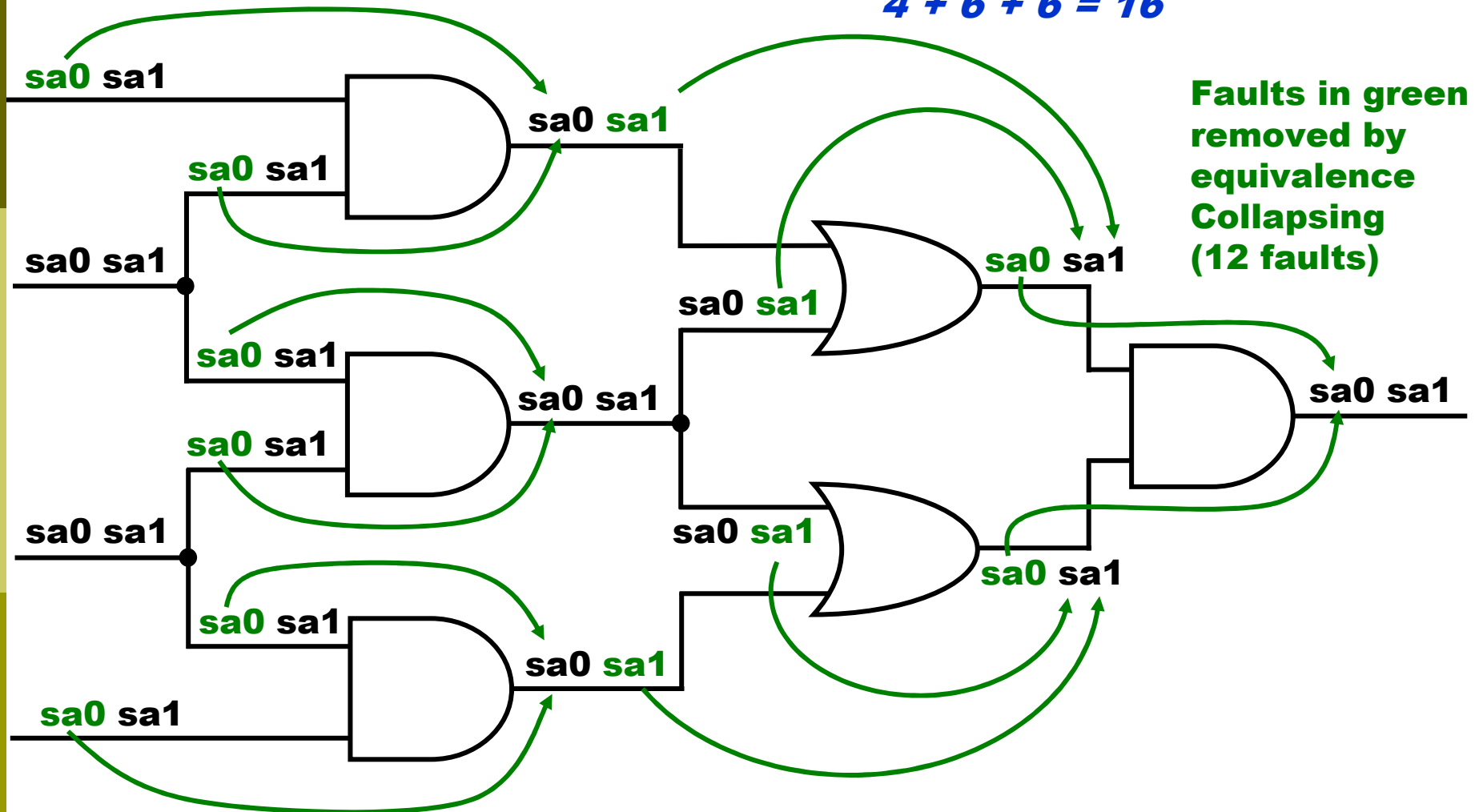**Number of fault sites:
4 + 6 + 6 = 16**





Collapse ratio = $\frac{20}{32} = 0.625$

Fault dominance

- If **all** tests of some fault F1 detect another fault F2, then F2 is said to **dominate** F1.
- Dominance fault collapsing: If fault F2 dominates F1, then F2 is removed from the fault list.
- When dominance fault collapsing is used, it is sufficient to consider only the input faults of Boolean gates. See the next example.
- In a tree circuit (without fanouts) PI faults form a dominance collapsed fault set.
- If two faults dominate each other then they are equivalent.


Fault dominance..... Example

 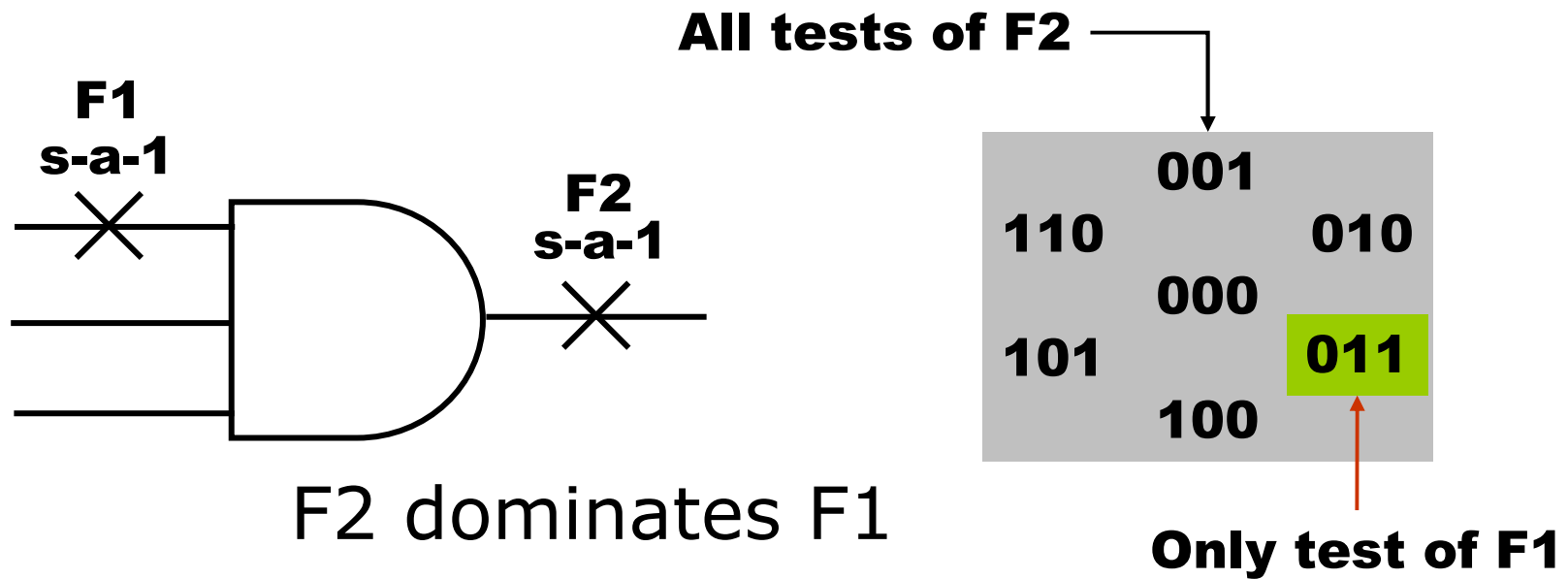

A dominance collapsed fault set

Checkpoints

 - Primary inputs and fanout branches of a combinational circuit are called **checkpoints**.
- **Checkpoint theorem:** A test set that detects all single (multiple) stuck-at faults on all checkpoints of a combinational circuit, also detects all single (multiple) stuck-at faults in that circuit.



Classes of stuck-at faults

- Following classes of single stuck-at faults are identified by fault simulators:
 - **Potentially-detectable fault** -- Test produces an unknown (X) state at *primary output* (PO); detection is probabilistic, usually with 50% probability.
 - **Redundant fault** -- No test exists for the fault.
 - **Untestable fault** -- Test generator is unable to find a test.
 - *Initialization fault* -- Fault prevents initialization of the faulty circuit; can be detected as a potentially-detectable fault.
 - *Hyperactive fault* -- Fault induces much internal signal activity without reaching PO.

Multiple Stuck-at Faults


- ❑ A multiple stuck-at fault means that any set of lines is stuck-at some combination of (0,1) values.
- ❑ Not consider in practice
- ❑ The total number of single and multiple stuck-at faults in a circuit with k single fault sites is $3^k - 1$.
- ❑ A single fault test can fail to detect the target fault if another fault is also present, however, such **masking** of one fault by another is rare.
- ❑ Statistically, single fault tests cover a very large number of multiple faults (**~99.6%**).

Transistor (Switch) Faults

- MOS transistor is considered an ideal switch and two types of faults are modeled:
 - **Stuck-open** -- a single transistor is permanently stuck in the open state.
 - **Stuck-short** -- a single transistor is permanently shorted irrespective of its gate voltage.
- Detection of a stuck-open fault requires **two vectors**.
- Detection of a stuck-short fault requires the measurement of **quiescent current** (I_{DDQ}).


Transistor FaultsStuck-Open

□ Example (NOR gate)

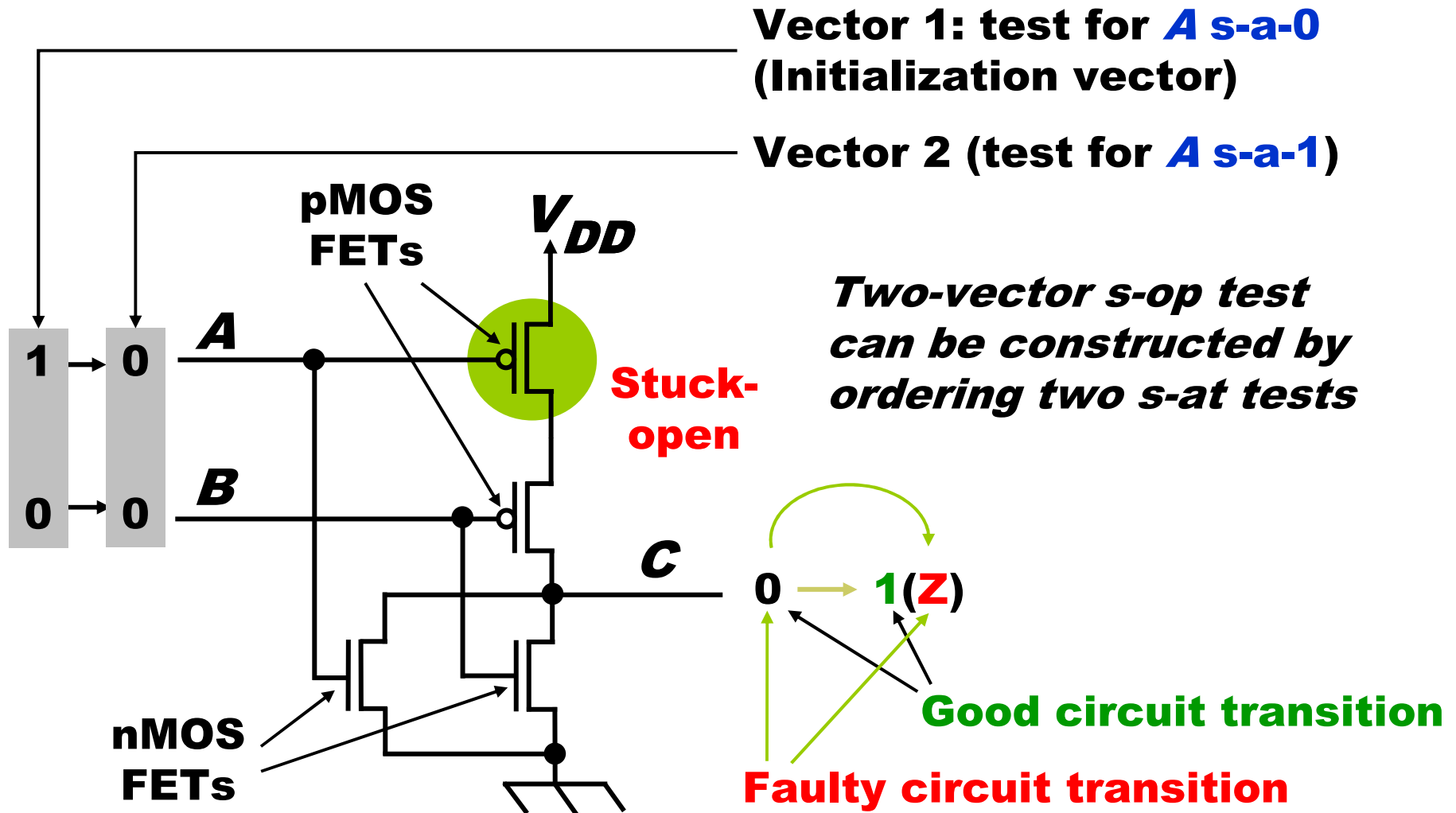

Transistor FaultsStuck-Short

□ Example (NOR gate)

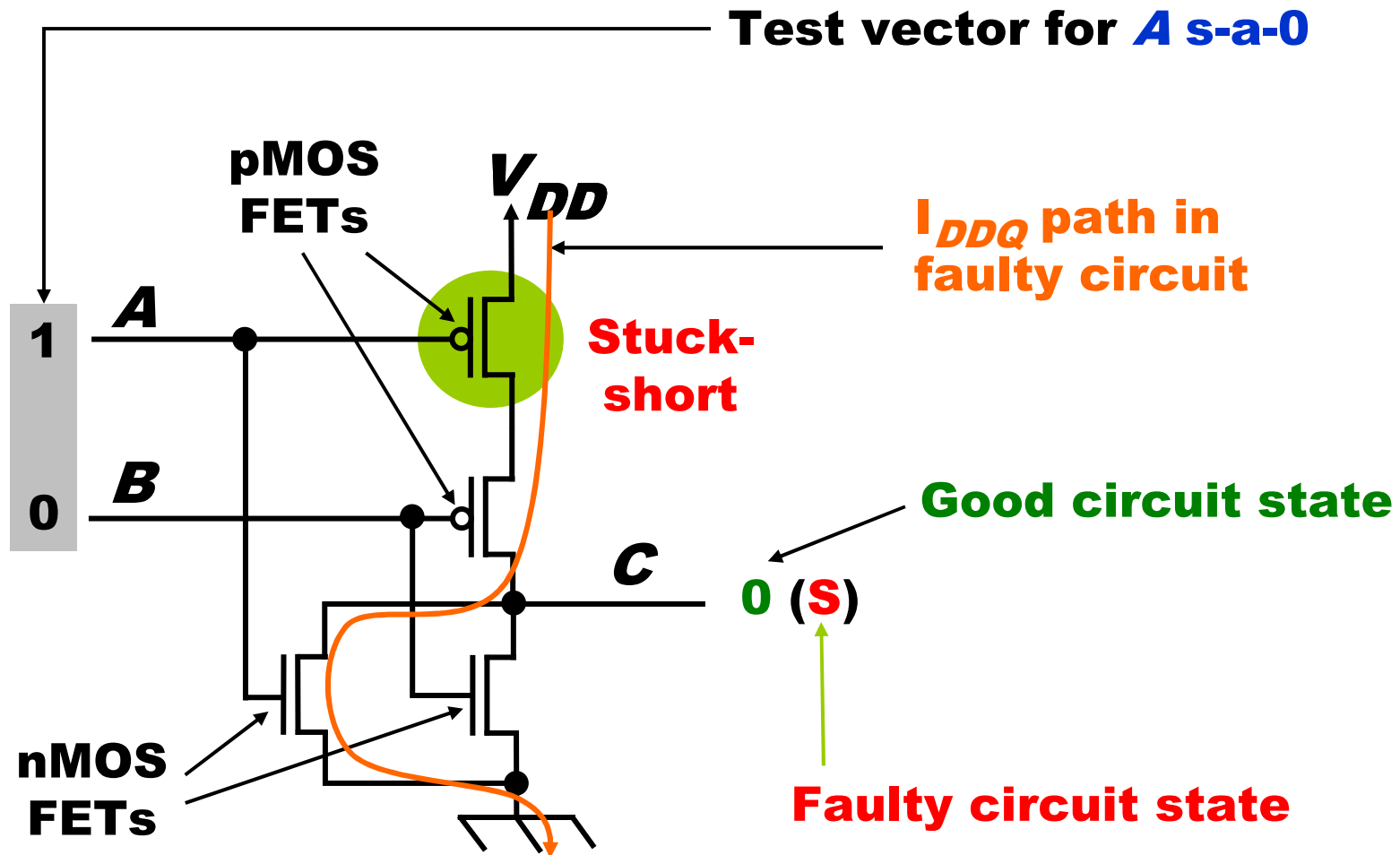

Summary

- ❑ Fault models are analyzable approximations of defects and are essential for a test methodology.
- ❑ For digital logic single stuck-at fault model offers best advantage of tools and experience.
- ❑ Many other faults (bridging, stuck-open and multiple stuck-at) are largely covered by stuck-at fault tests.
- ❑ Stuck-short and delay faults and technology-dependent faults require special tests.
- ❑ Memory and analog circuits need other specialized fault models and tests.

- 
- Next lecture –
we will talk about ...

Fault Simulation