

Oscillators

Aleksandar Tasic
Electronics Research Laboratory

Job Advertisement

- RF/analog circuits design experience
 - LNA, mixer, VCO, PLL, filter, A/D, PA
- CAD proficiency
 - Cadence, ADS, Spice
- Packaging, measurement, and PCB design skills are strongly encouraged
- Programming in C is an asset
- Salary experience based, 80.000 – 120.000

UMTS VCO Requirements

<i>VCO design parameters</i>	<i>Design requirement</i>
Oscillating frequency	2.1GHz
Tuning range	400MHz
Voltage swing	0.7V
Phase noise	-110dBc@1MHz
Supply voltage	3V
Power consumption	10mW

Technology parameters	Values
Technology	BiCMOS
Number of metals	4
Transit frequency	50GHz
MIM capacitors	available
Varactors	available

Outline

- Oscillator Classification, Oscillation Condition and Frequency
- LC Oscillators
- Oscillation Signal Steady-State Amplitude
- Interpretation of Noise in Oscillators
- Linear Phase-Noise Model
- Spectral Analysis of Phase Noise
- Design Procedure for LC-Oscillator
- Simulations/Layout/Measurements

Oscillator Definition

- An oscillator is a tunable circuit that generates a stable periodical signal, which is in the limit independent of the initial conditions.

$$\frac{d^2}{dt^2} x(t) + f(x(t)) \frac{d}{dt} x(t) + \omega^2 x(t) = 0$$

oscillation signal non-linear function angular frequency

- A non-linear system that should be of a second order (with two time constants).


Oscillator Classification – Time Constants Based

frequency dominated by	oscillator order
1 time constant	1st-order oscillator
2 time constants	2nd-order oscillator
...	...

Oscillator Classification – Resonator Based

- Resonator oscillators
 - LC oscillators, negative resistance oscillators
 - good phase noise properties
 - poor quadrature accuracy
- Resonatorless oscillators
 - Ring oscillators
 - poor phase noise properties
 - good quadrature accuracy
 - Relaxation oscillators
 - poor phase noise properties
 - good quadrature accuracy

Oscillator Positive Feedback Model

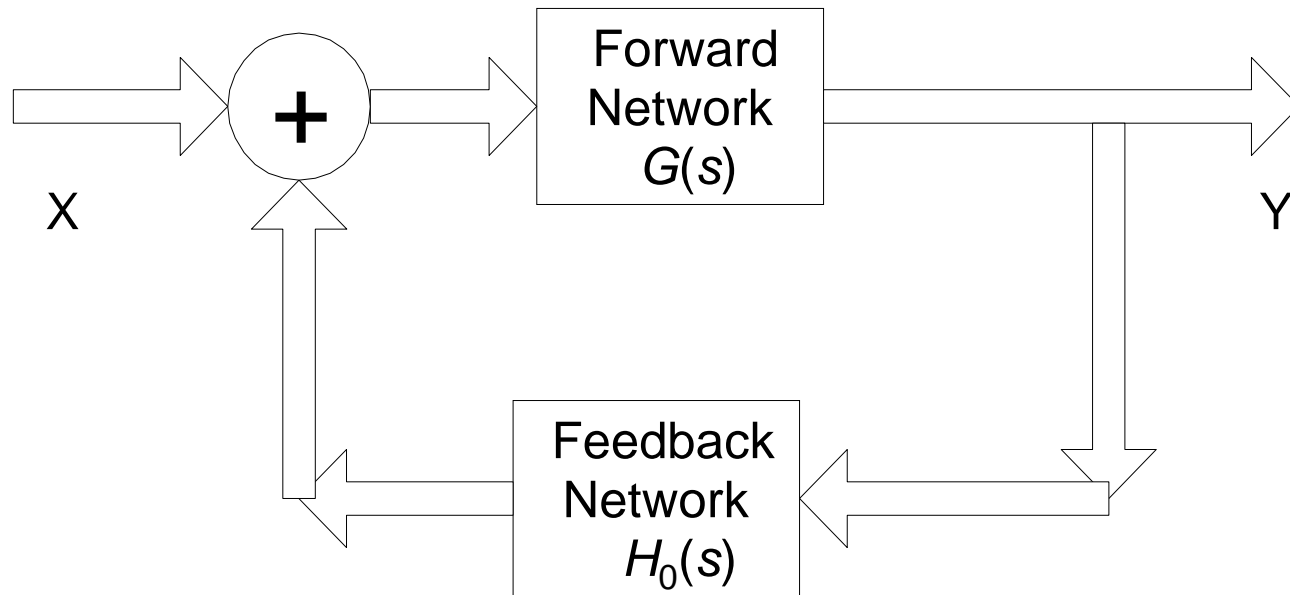


$$H(s) = \frac{Y(s)}{X(s)} = \frac{G(s)}{1 - G(s)H_0(s)}$$

Oscillation Condition


- Barkhausen's criteria
 - Loop-gain module > 1 (start up)
$$|T(j\omega)| = |G(j\omega) \cdot H_0(j\omega)| > 1$$
 - Loop-gain module equals 1 (steady state)
$$|T(j\omega)| = |G(j\omega) \cdot H_0(j\omega)| = 1$$
 - Phase shift around the loop equals 360°
$$\angle(T(j\omega)) = 2\pi$$

Oscillator Models

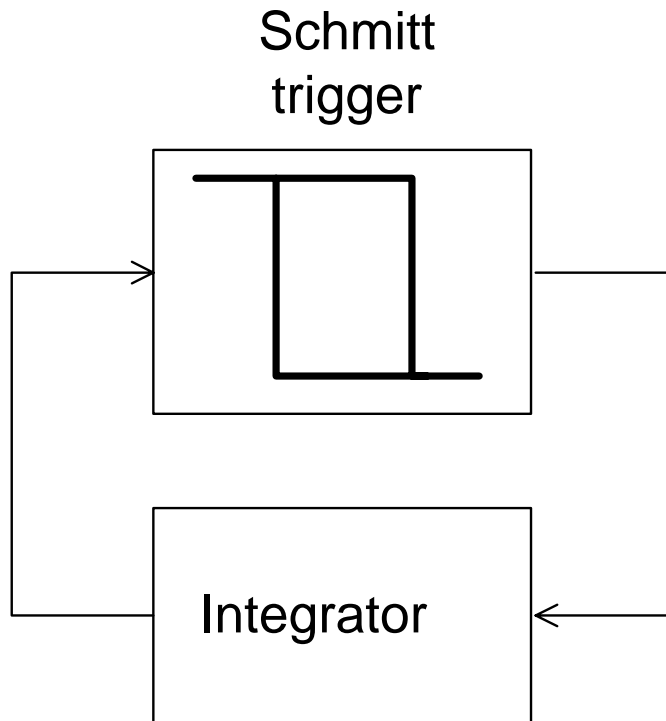
- 1st-order oscillator
 - 1st-order timing constant
 - Schmitt trigger



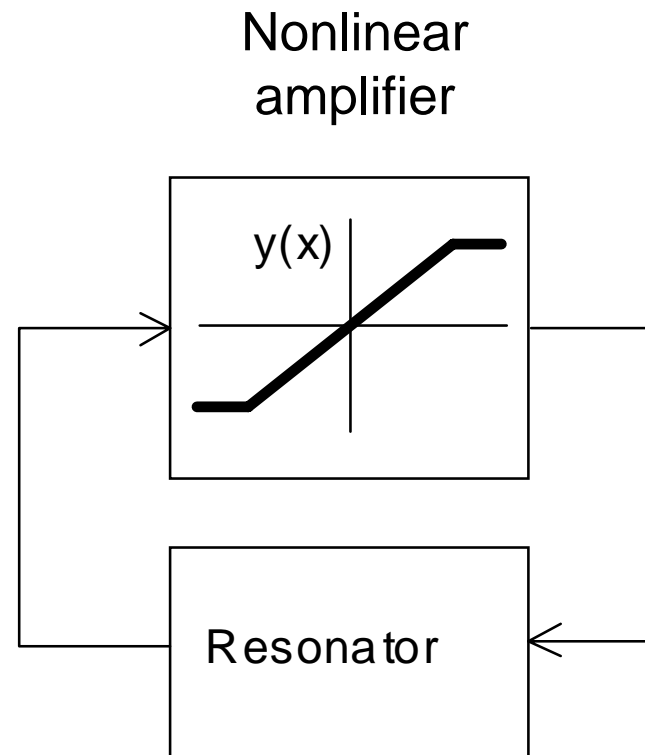
- 2nd-order oscillator
 - 2nd-order timing constant
 - amplitude limiter




LC oscillator

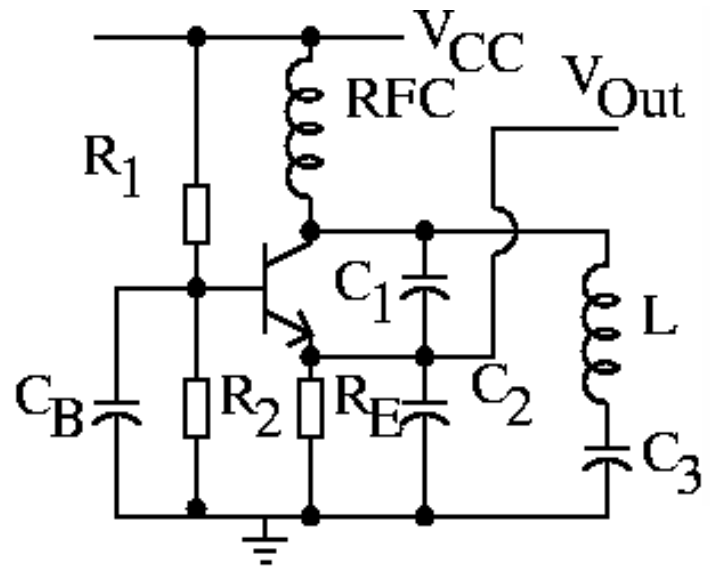


RC ring oscillator

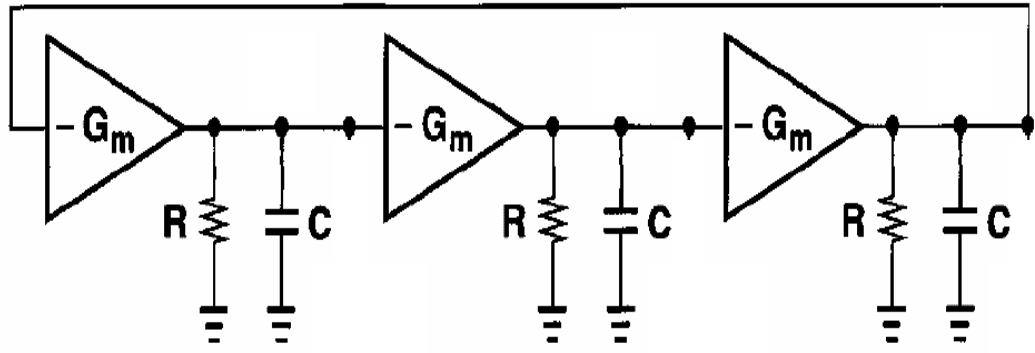

1st-order oscillator

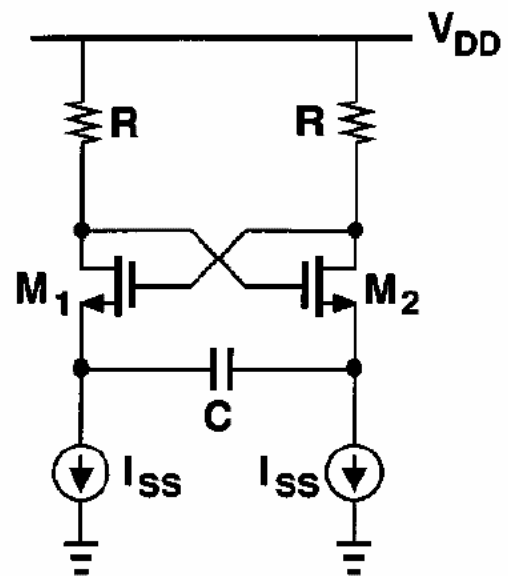

injection-lock ring oscillator

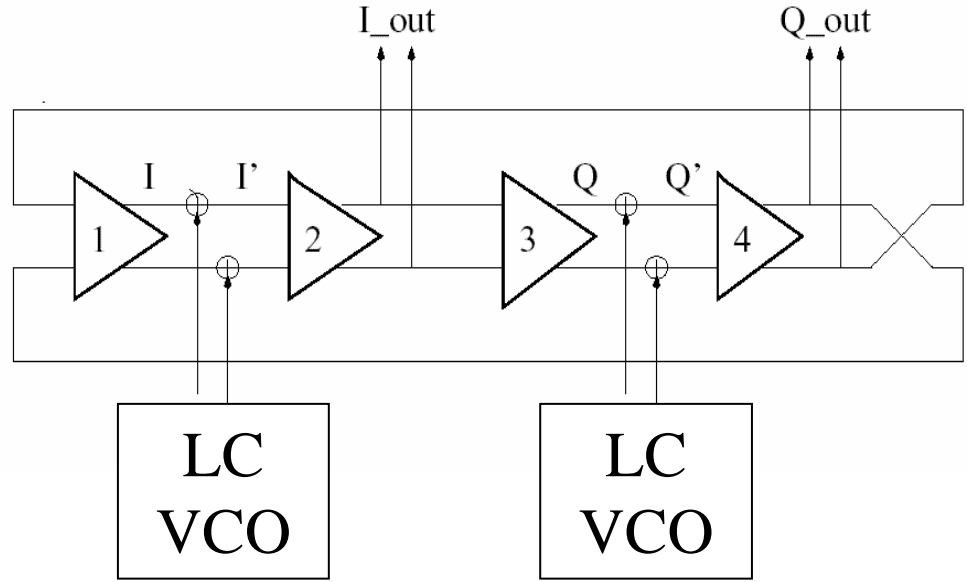


Oscillator Application

- Frequency conversion
 - Downconversion in receivers
 - Upconversion in transmitters
- Clock generation
- Channel selection
- Modulation/demodulation

LC Oscillators

Generalized LC Oscillator Circuit


- Single transistor model

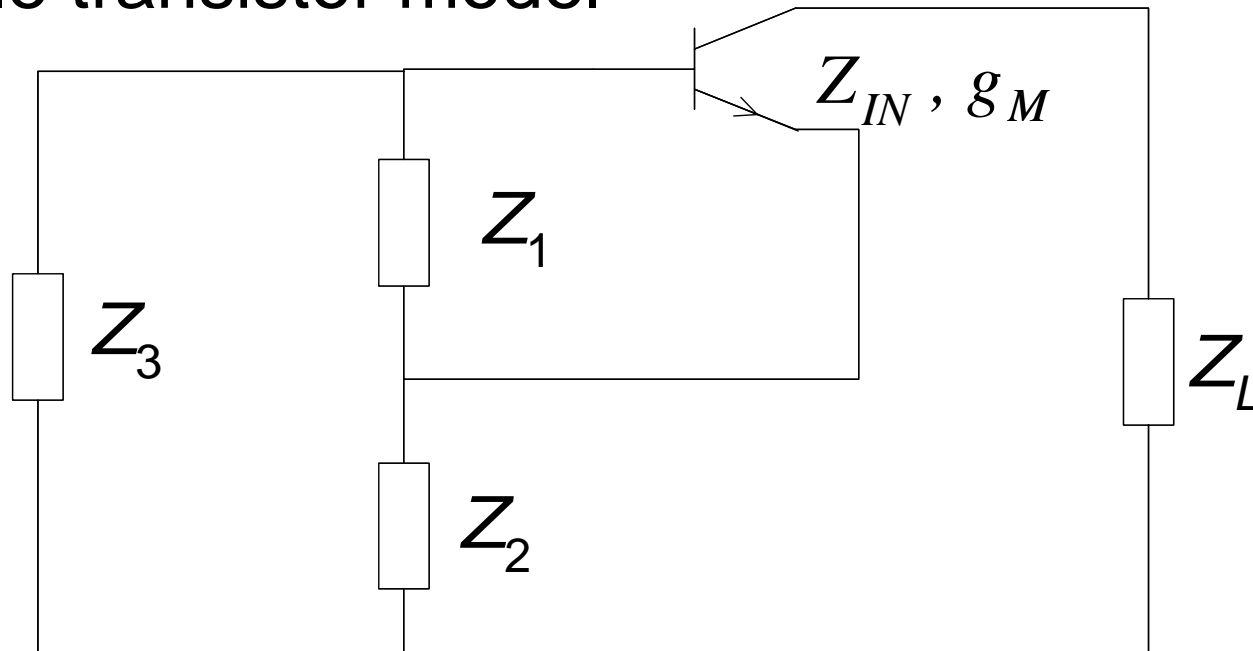

- Loop-gain approach: $T(j\omega)=1$
- Impedance matrix approach: $\det(\mathbf{Z})=0$ (or $\det(\mathbf{Y})=0$)

$$(Z_1 + Z_3)(Z_{IN} + Z_1) + Z_1 Z_{IN} (1 + g_M Z_2) = 0$$


Examples of LC Oscillator

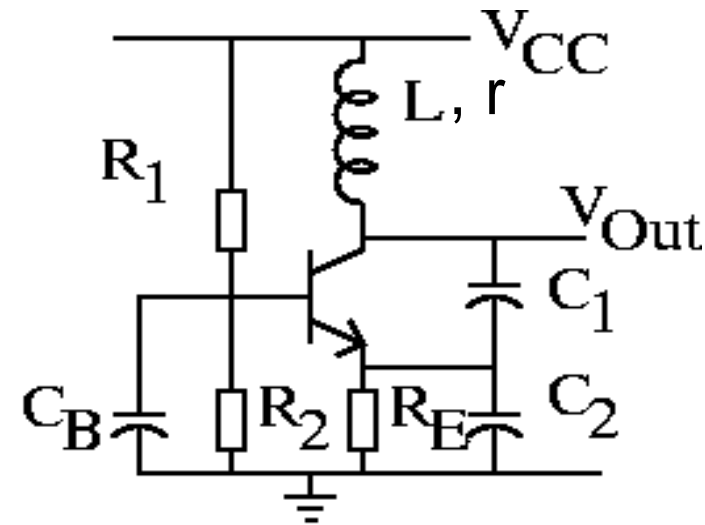


Colpitts

$$\omega_0 = \frac{1}{\sqrt{LC_1 C_2 / (C_1 + C_2)}}$$

$$(1-n)\omega_0^2 C_1 C_2 r < g_m$$

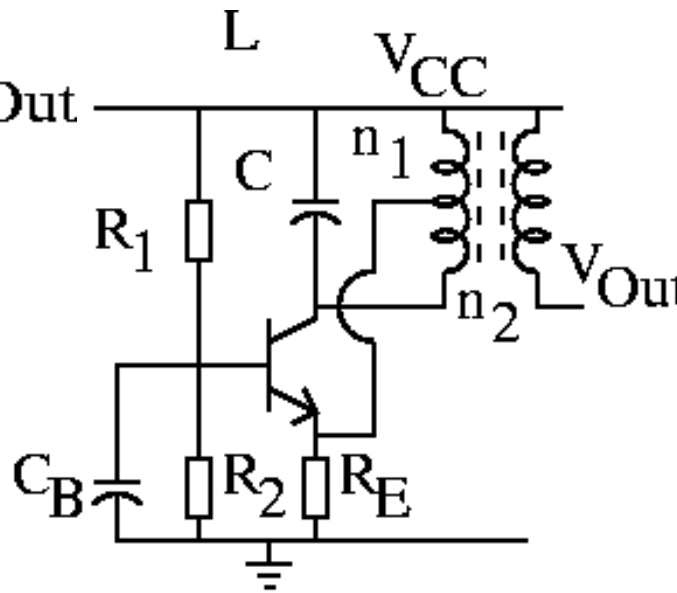


Hartley

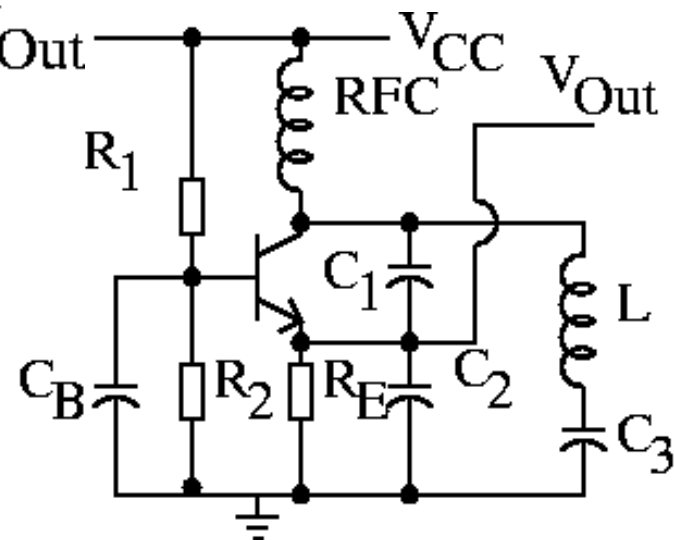


Clapp

Negative Resistance Oscillator

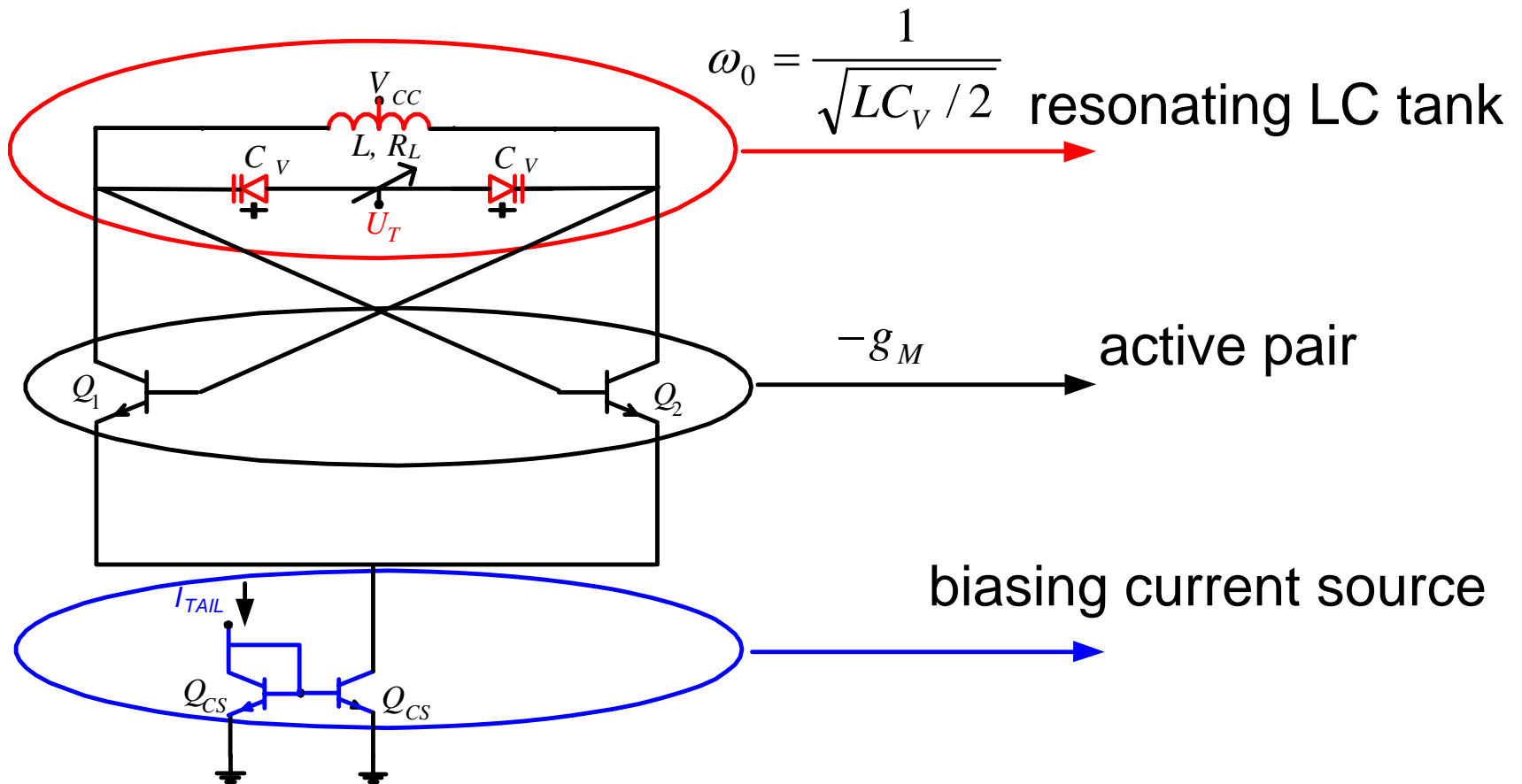

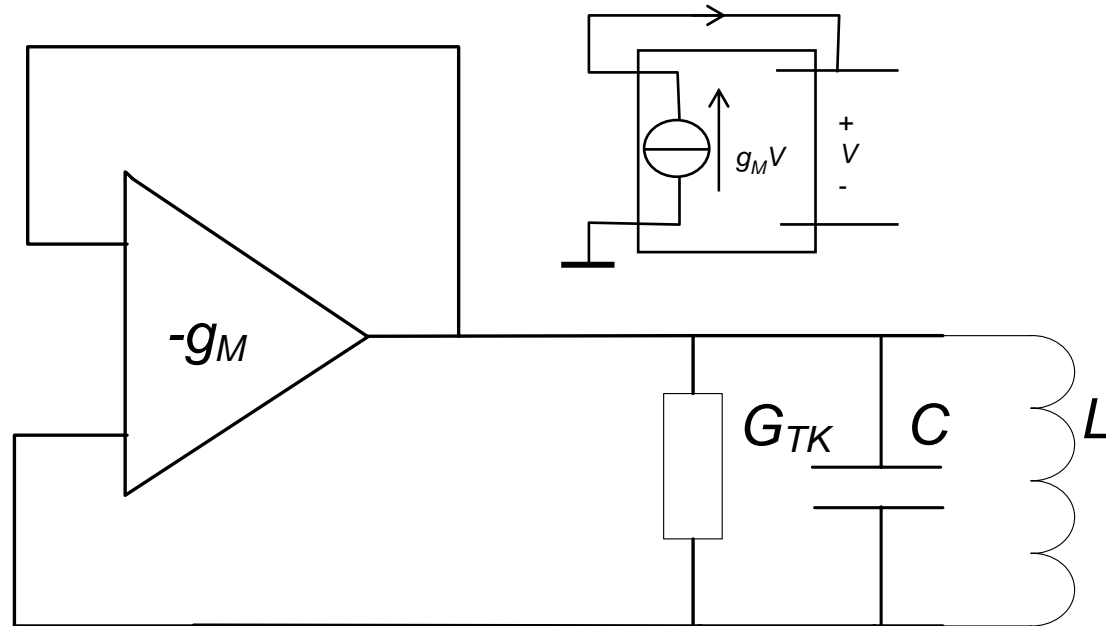Negative Resistance Oscillator - Simplified Model





- oscillation condition

$$g_M > G_{TK} \quad g_M = g_m / 2$$

- oscillation frequency

$$\omega = \omega_0 = 1 / \sqrt{LC} \quad C = C_V / 2$$

LC Tank

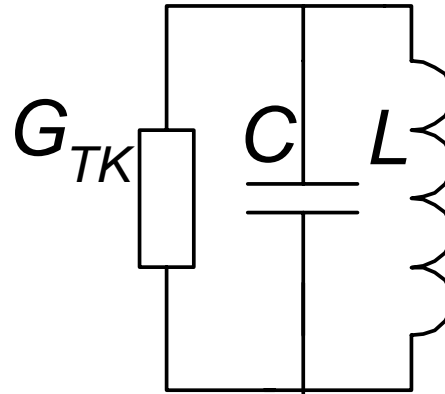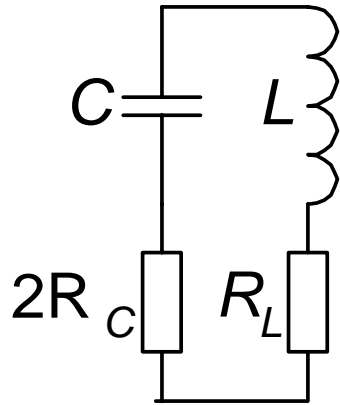

- tank conductance



$$G_{TK} = \frac{R_L}{(\omega_0 L)^2} + 2R_C (\omega_0 C)^2$$

$$G_{TK} = \frac{1}{\omega_0 L} \left(\frac{1}{Q_L} + \frac{1}{Q_C} \right)$$

- quality factors

$$Q_L = \frac{\omega_0 L}{R_L} \quad Q_C = \frac{1}{\omega_0 C_V R_C}$$

Resonator Impulse Response

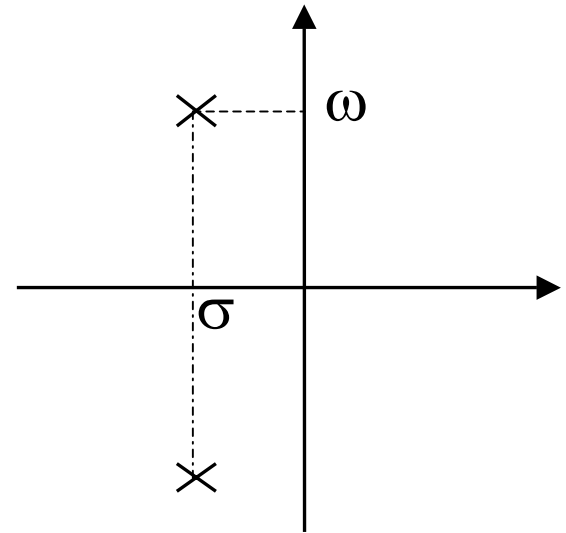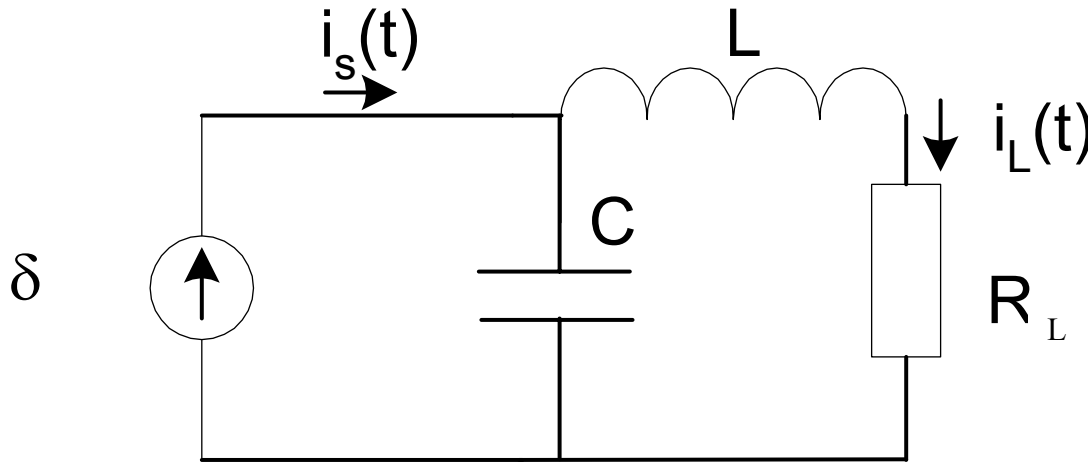

$$s_i = \sigma \pm j\omega$$

resonator pole pattern


$$H(s) = \frac{I_L(s)}{I_S(s)} = \frac{1}{LC} \frac{1}{s^2 + sR_L/L + 1/LC}$$

$$i_L(t) = \left(\frac{I_L(s)}{I_S(s)} \right)^{-1} = \sum_{i=0}^n \frac{P(s_i)}{Q(s_i)'} e^{s_i t}$$

$$i_L(t) = \frac{\omega_0 e^{\sigma t}}{\sqrt{1 - (\sigma / \omega_0)^2}} \sin \omega t \quad \omega = \omega_0 \sqrt{1 - (\sigma / \omega_0)^2} \quad \omega_0 = 1 / \sqrt{LC}$$

$$\sigma = -R_L / 2L$$

Oscillator System Transfer Function

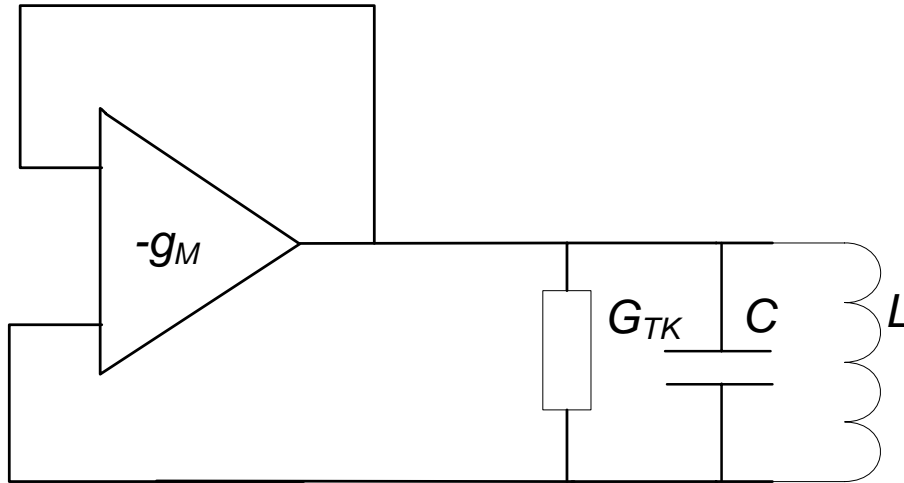


$$H(s) = \frac{Z(s)}{1 - g_M Z(s)}$$

$$H(s) = \frac{1}{C} \frac{s}{s^2 + s(G_{TK}/C - g_M/C) + 1/LC}$$

- oscillation condition and frequency

$$g_M > G_{TK}$$

$$\omega = \omega_0 = 1/\sqrt{LC}$$

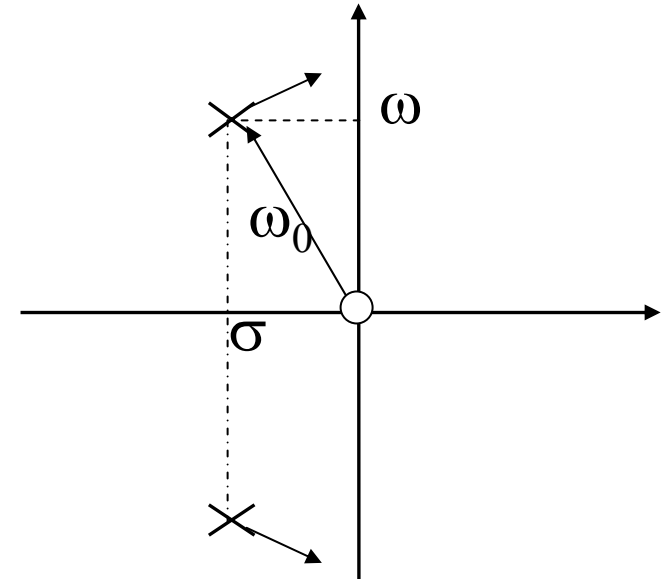

system pole pattern


Steady-State Oscillation Signal Amplitude

Sub-Outline


- Differential Pair Characteristic
- Large-Signal Conductance
- Steady-State Oscillation Signal Amplitude

Amplitude Stabilization


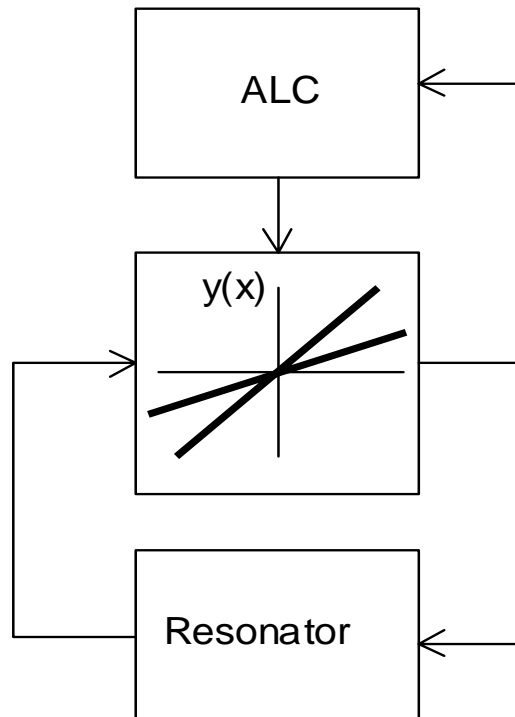
- Amplitude regulator
 - amplitude control mechanism



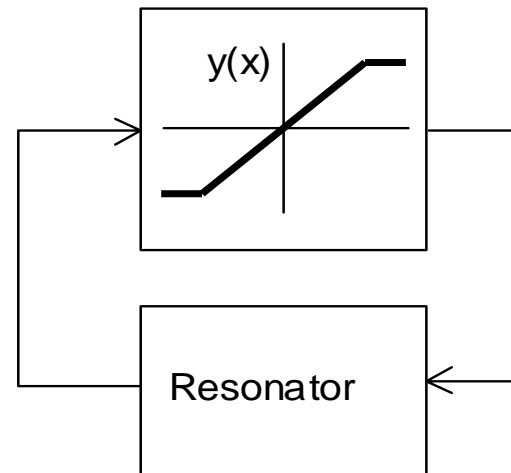- Nonlinear amplifier
 - well defined nonlinearity
 - timing reference loss compensation
 - loop-gain control



Differential Characteristic

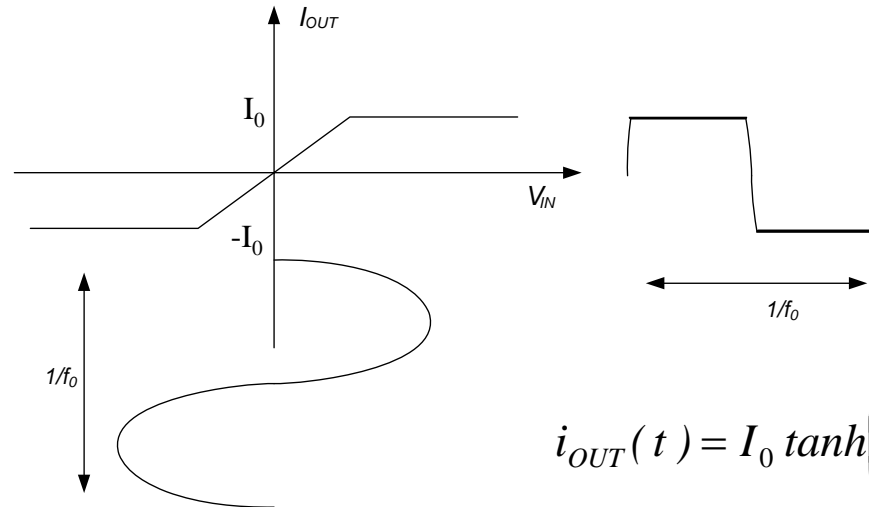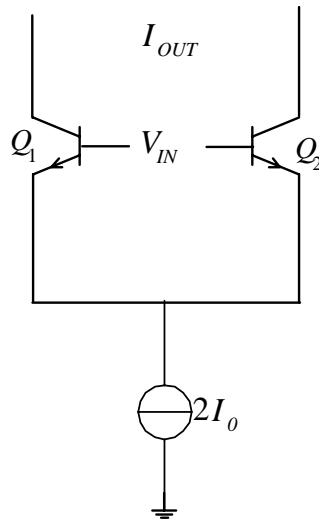

$$i_{OUT}(t) = I_0 \tanh\left(\frac{x}{2} \cos \omega t\right)$$

$$v_{IN}(t) = V_1 \cos \omega t$$

$$x = V_1 / V_T \quad V_1 \gg V_T$$

- current harmonic content

$$i_{OUT}(t) = I_1 \cos \omega t + I_3 \cos 3\omega t + I_5 \cos 5\omega t + \dots = I_0 \sum_n a_{2n-1} \cos(2n-1)\omega t$$


$$I_n(x) = I_0 a_n(x) \quad a_n(x) = \frac{1}{\pi} \int_{-\pi}^{\pi} \tanh\left(\frac{x}{2} \cos \theta\right) \cos(n\theta) d\theta$$

Large Signal (Trans)Conductance

$$G_{M1}(x) = \frac{I_1}{V_1} = \frac{I_0}{V_T} \frac{V_T}{V_1} \frac{I_1}{I_0}$$

$$G_{M1}(x) = g_m \frac{1}{x} \frac{I_1}{I_0} = 2g_M \frac{a_1(x)}{x}$$

$$G_{M1}(x) / g_M = 2 \frac{a_1(x)}{x}$$

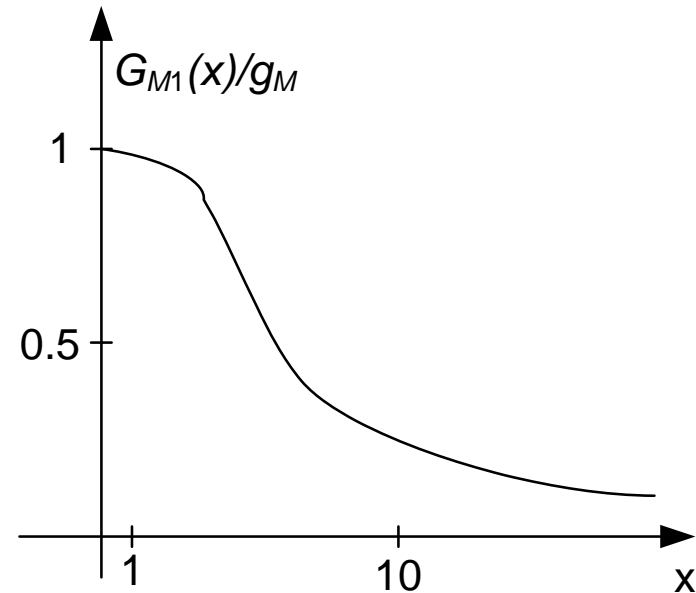

- steady state oscillation condition

$$|G_{M1}(V_1) \cdot H_0(j\omega)| = 1$$

$$\left| \frac{G_{M1}(V_1)}{g_M} \cdot g_M H_0(j\omega) \right| = 1$$

$\frac{\text{large signal fundamental (trans)conductance}}{\text{small signal trans(conductance)}} = \frac{1}{\text{small signal loop gain}}$

Large Signal Components

- output current

$$i_{OUT}(t) = I_1 \cos \omega t + I_3 \cos 3\omega t + I_5 \cos 5\omega t + \dots = I_0 \sum_{n=0}^{\infty} a_{2n-1} \cos(2n-1)\omega t$$

- close to square wave if $V_1 \gg V_T$
- harmonics of the square-wave signal current

$$I_n = \frac{4I_0}{n\pi} = \frac{2I_{TAIL}}{n\pi}$$

Steady State Signal Amplitude

- large signal conductance and steady state oscillation condition

$$G_{M1}(V_1) = \frac{I_1}{V_1} = \frac{I_1}{I_{TAIL}} \frac{I_{TAIL}}{V_1} = \frac{2}{\pi} \frac{I_{TAIL}}{V_1} \quad \frac{G_{M1}(V_1)}{g_M} = \frac{1}{k}$$

- small signal loop gain (k)

$$k = R_{TK} g_M$$

- steady state fundamental amplitude

$$V_1 = \frac{2}{\pi} I_{TAIL} R_{TK}$$

voltage fundamental = tank resistance \times current fundamental

So Far

VCO design parameters	<i>Design requirement</i>
Oscillating frequency	2.1GHz
Tuning range	400MHz
Voltage swing	0.7V
Phase noise	-110dBc@1MHz
Supply voltage	3V
Power consumption	10mW

Technology parameters	<i>Values</i>
Technology	BiCMOS
Number of metals	4
Transit frequency	50GHz
MIM capacitors	available
Varactors	available

Interpretation of Noise in Oscillators

Sub-Outline

- Signal Phasor Description
- Signal Spectral Description
- Phase-Noise Definition
- Phase-Noise Specification

Bennett Noise Interpretation

- White noise spectrum (power spectral density)

$$N(f) = A$$

- One noise component (time domain)

$$n(t) = a_k \cos(\omega_k t + \theta_k)$$


- a_k – known amplitude ($= \sqrt{2A}$)
- ω_k – known angular frequency
- θ_k – random phase (constant and uniform)

Oscillation Signal Description

- Ideal vs. actual oscillation signal


$$V_0 \cos \omega_0 t \text{ vs. } V_0 [1 + a(t)] \cos[\omega_0 t + \theta(t)]$$

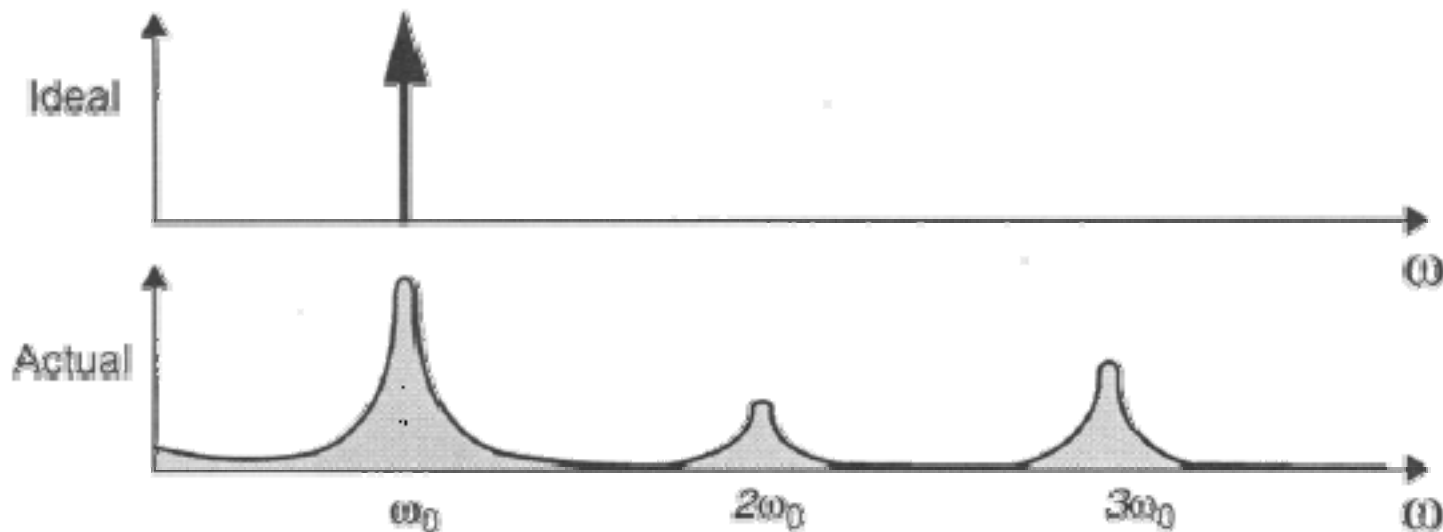- $a(t)$ amplitude modulated component
- $\theta(t)$ phase modulated component



Oscillation Signal Phasor Description


$$v(t)|_{+n(t)} = [1 + a(t)] \cos(\omega_0 t + \theta(t)) \approx \cos(\omega_0 t) + a(t) \cos(\omega_0 t) - \theta(t) \sin(\omega_0 t)$$

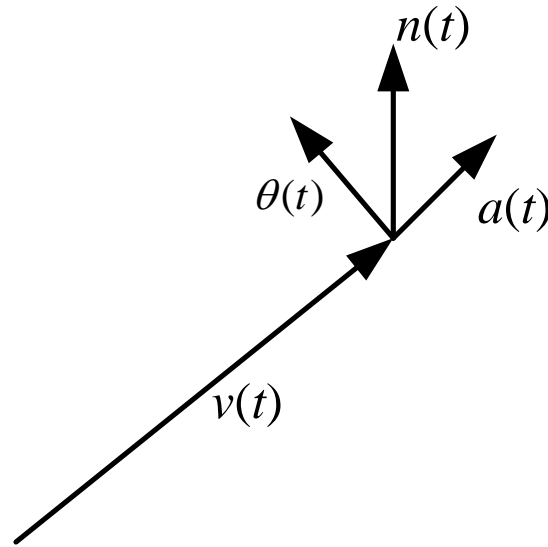

- $a(t)$ in-phase component (AM) can be removed
- $\theta(t)$ quadrature-phase component (PM) is unavoidable


Oscillation Signal Phasor Description

$$v(t)|_{+n(t)} = [1 + a(t)] \cos(\omega_0 t + \theta(t)) \approx \cos(\omega_0 t) + a(t) \cos(\omega_0 t) - \theta(t) \sin(\omega_0 t)$$

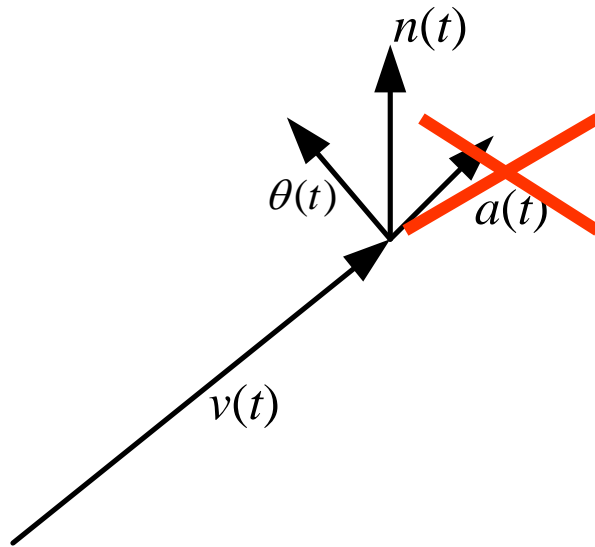

- amplitude control mechanism

Oscillation Signal Spectral Description

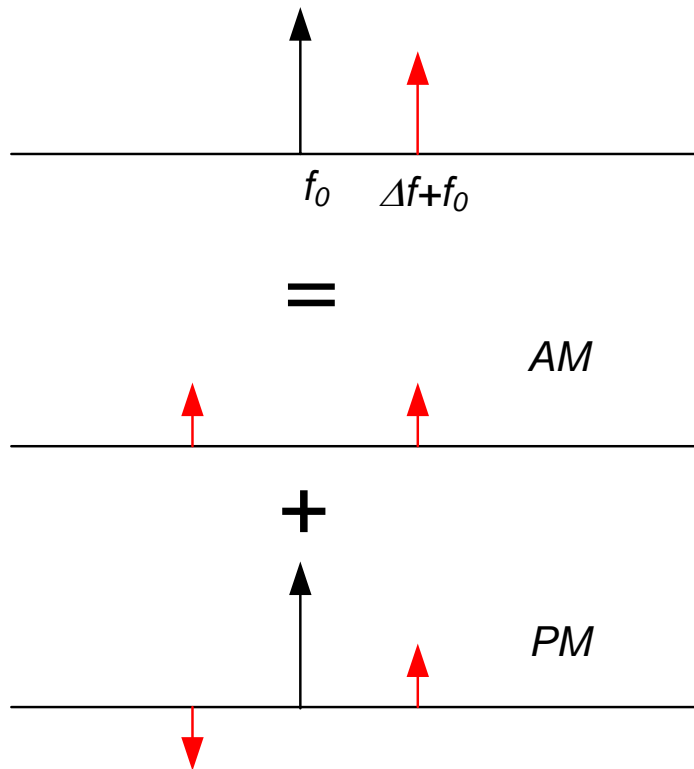


- oscillating signal and noise component

- amplitude modulated component

- phase modulated component

Oscillation Signal Spectral Description

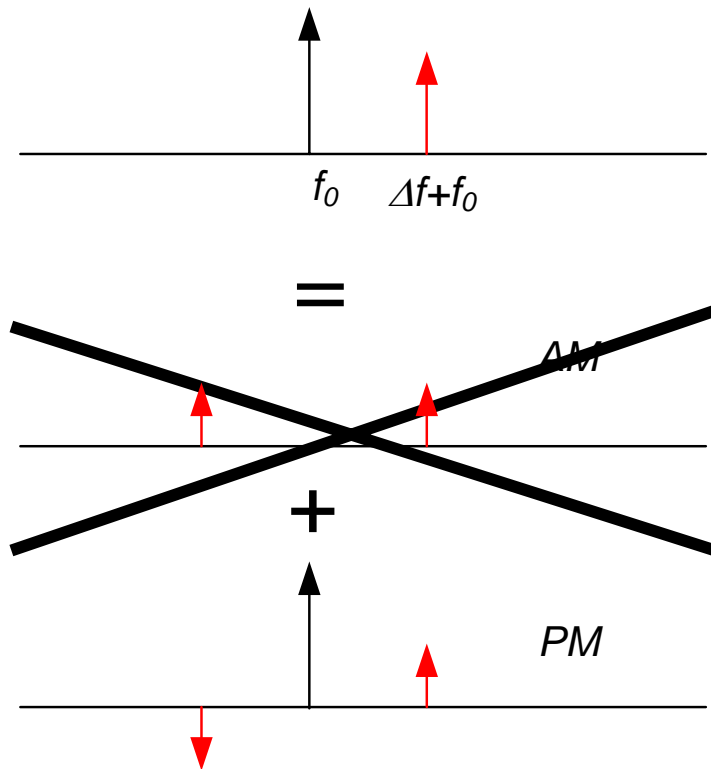


- oscillating signal and noise component
- amplitude control mechanism
- phase modulated component


Phase Spectrum vs. Oscillation Signal Spectrum

$$v(t) = A \cos(\omega_0 t + \theta(t)) = A \cos(\omega_0 t + \theta_k \sin(\omega_k t + \phi_k)) \approx \\ \approx A \cos(\omega_0 t) - A \theta_k \sin(\omega_k t + \phi_k) \sin(\omega_0 t)$$

- phase spectrum

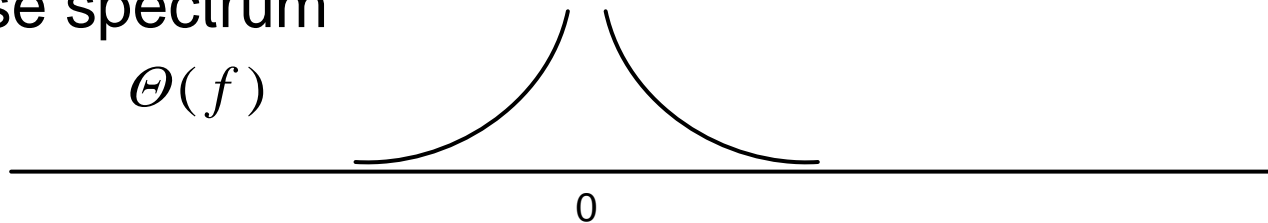


- oscillation signal spectrum

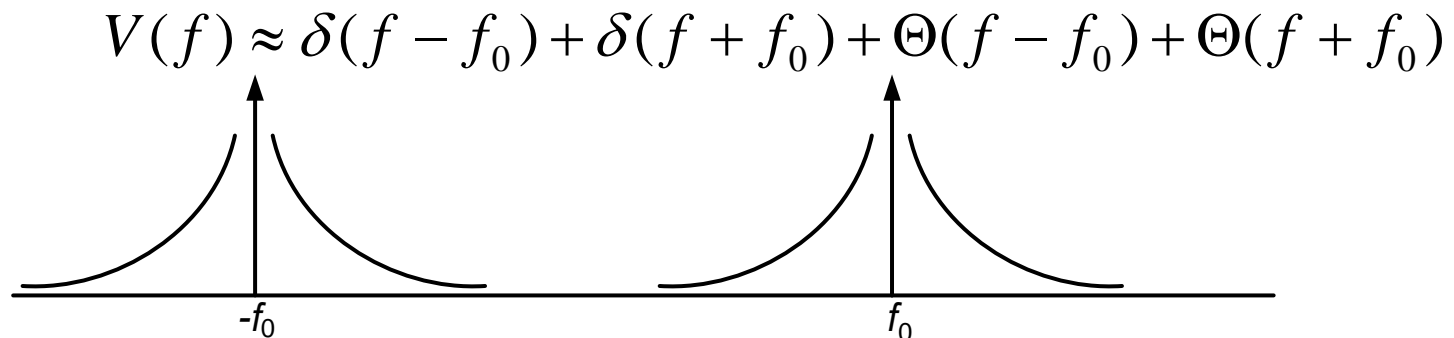

Phase Noise Definition

- ratio of the noise power in a 1Hz bandwidth at frequency $f_0 + \Delta f$ and the carrier power


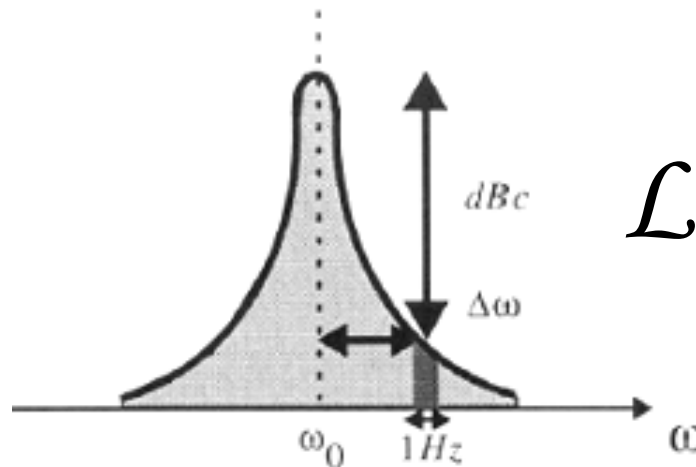
$$\mathcal{L}(\Delta\omega) = 10 \log [P_{side-band}(\omega_0 + \Delta\omega) / P_{carrier}(\omega_0)] \quad [dBc/Hz]$$



Why is Phase Noise Important?


- *Reciprocal mixing*

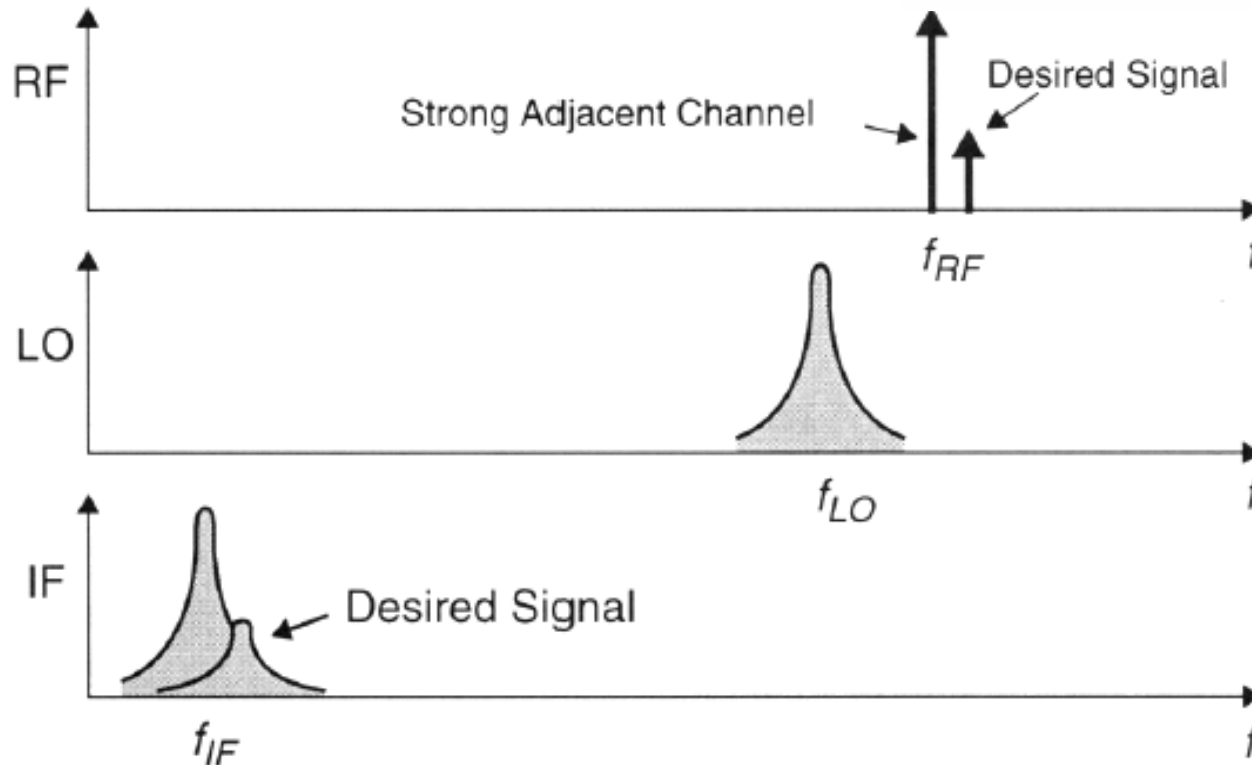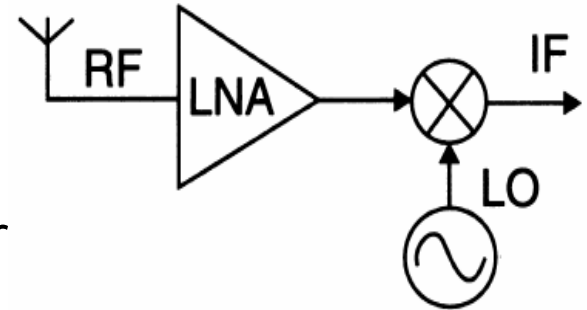- desired signal covered by the phase-noise skirt of the interferer




Phase Noise Specification

- Typical blocking profile

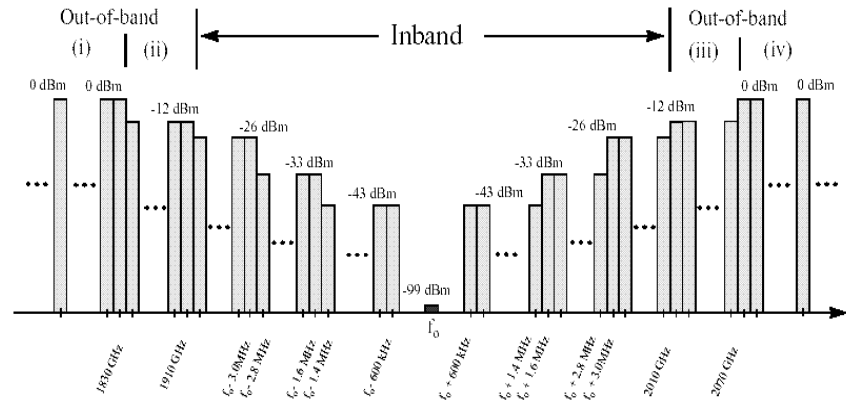

- Spectra of downconverted signals

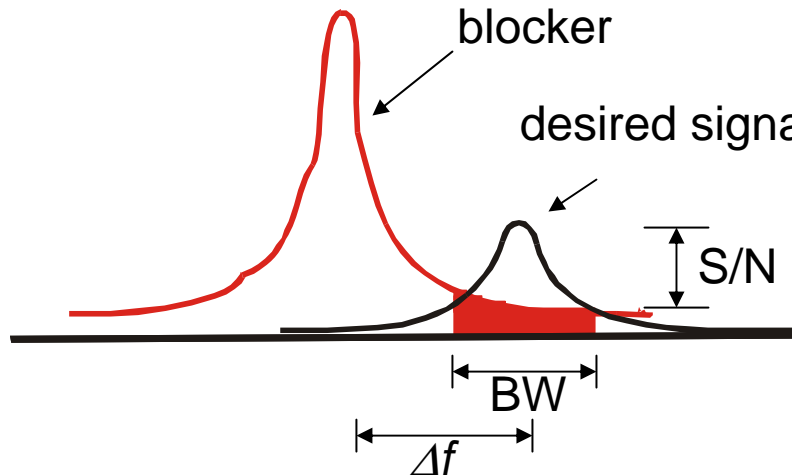

$$S/N = S_{MDS} - N \times BW$$

$$\mathcal{L} = N / S_{BLOCK}$$

$$\mathcal{L}(\Delta f) = S_{MDS} - S_{BLOCK} - 10 \log BW - S/N \text{ [dBc/Hz]}$$