

Structured Electronic Design

Accurate amplification



Right choice

Orthogonalization


Optimization

The criteria

- Clear definition of the function
- *The criteria*

$$C = B \log_2 \frac{S + N}{N}$$

Design procedure?

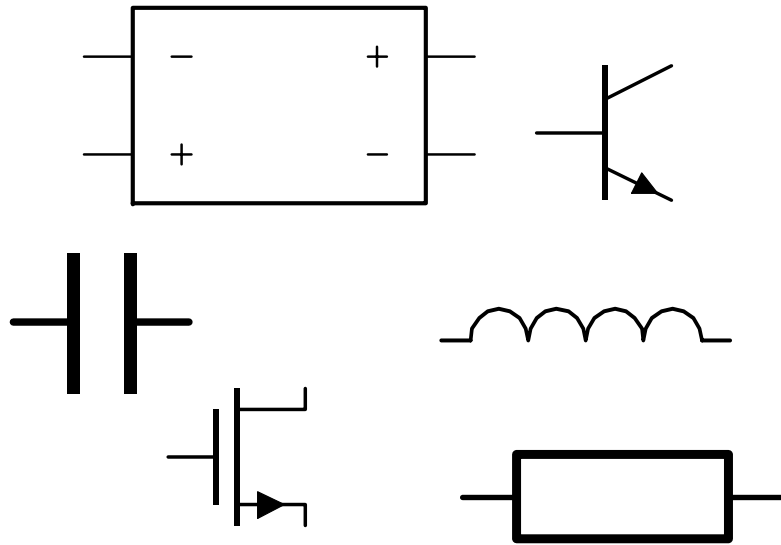

bandwidth – noise – distortion
bandwidth – distortion - noise
noise - bandwidth – distortion
noise – distortion - bandwidth
distortion - noise – bandwidth
distortion – bandwidth - noise





Orthogonality



Hierarchy

Hierarchy

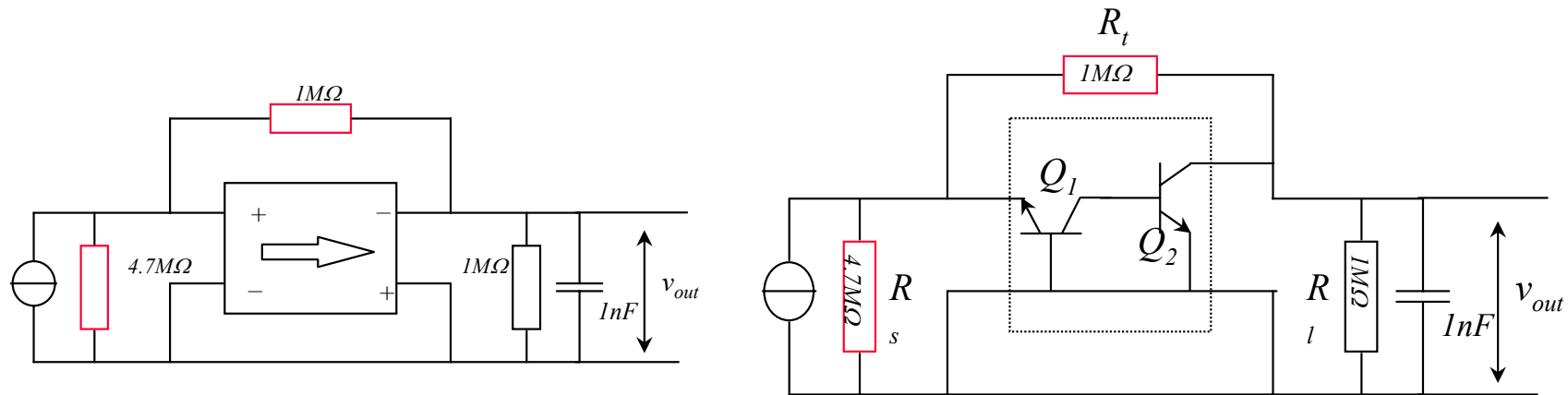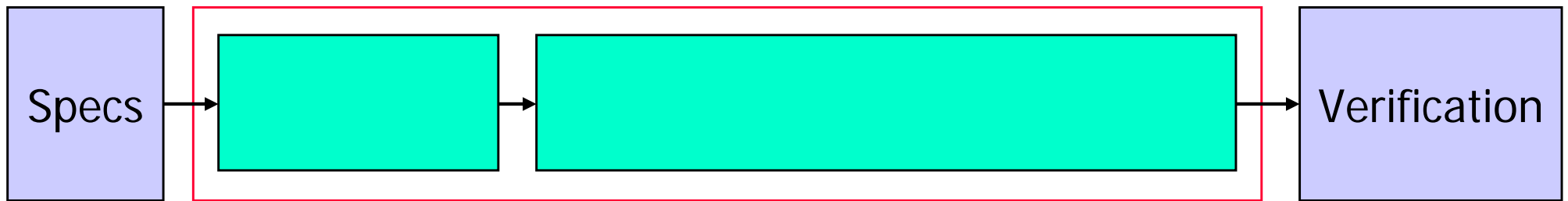


What is an amplifier?



Accurate amplification

Information from source to load

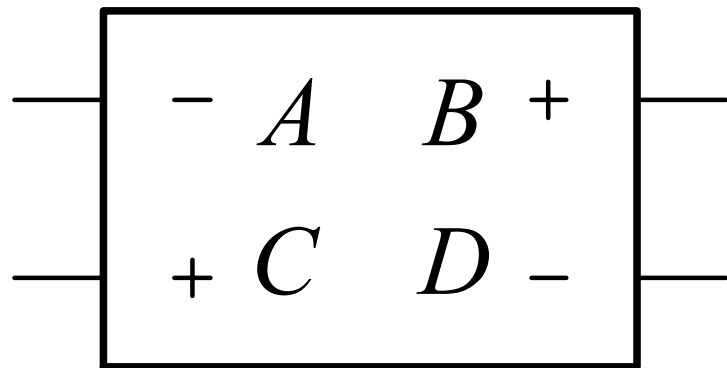- Signal power is enlarged
- Information stays unaltered













A, B, C, D indicate gain
 A, B, C, D constant
 A, B, C, D accurately known

$$\begin{pmatrix} v_{in} \\ i_{in} \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} v_{out} \\ i_{out} \end{pmatrix}$$




Classification

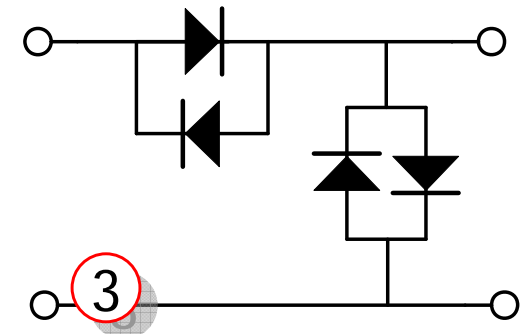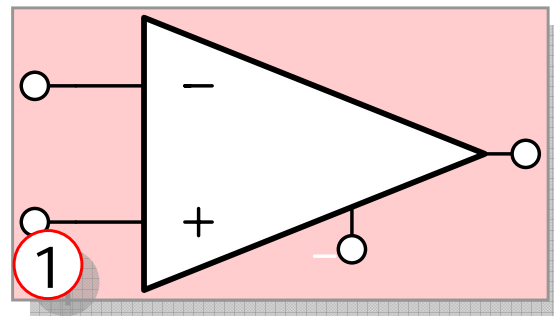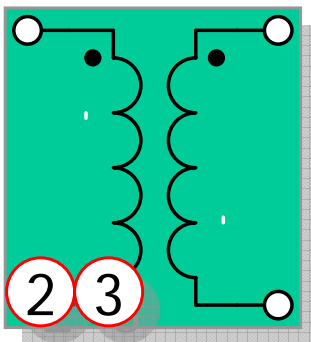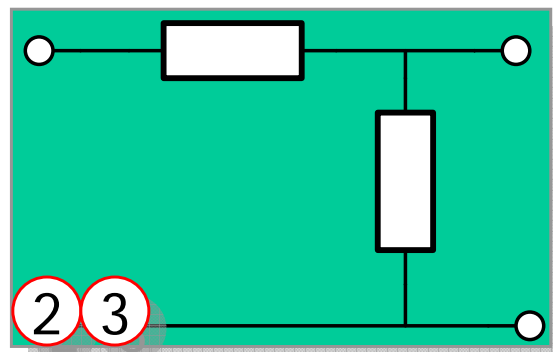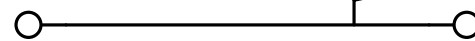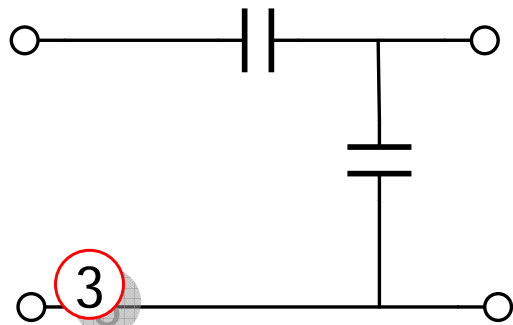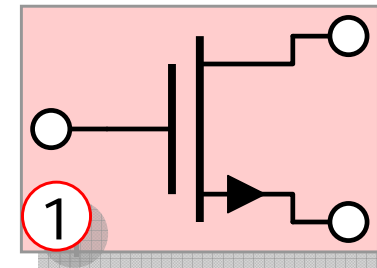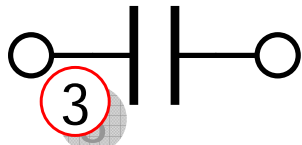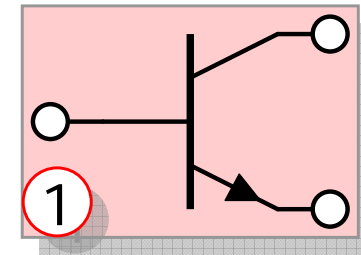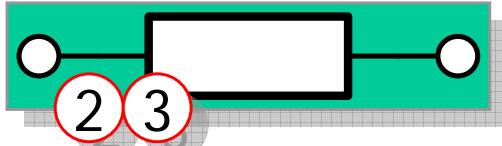1. *A,B,C,D* indicate gain
2. *A,B,C,D* constant
3. *A,B,C,D* accurately known



Classification of available components

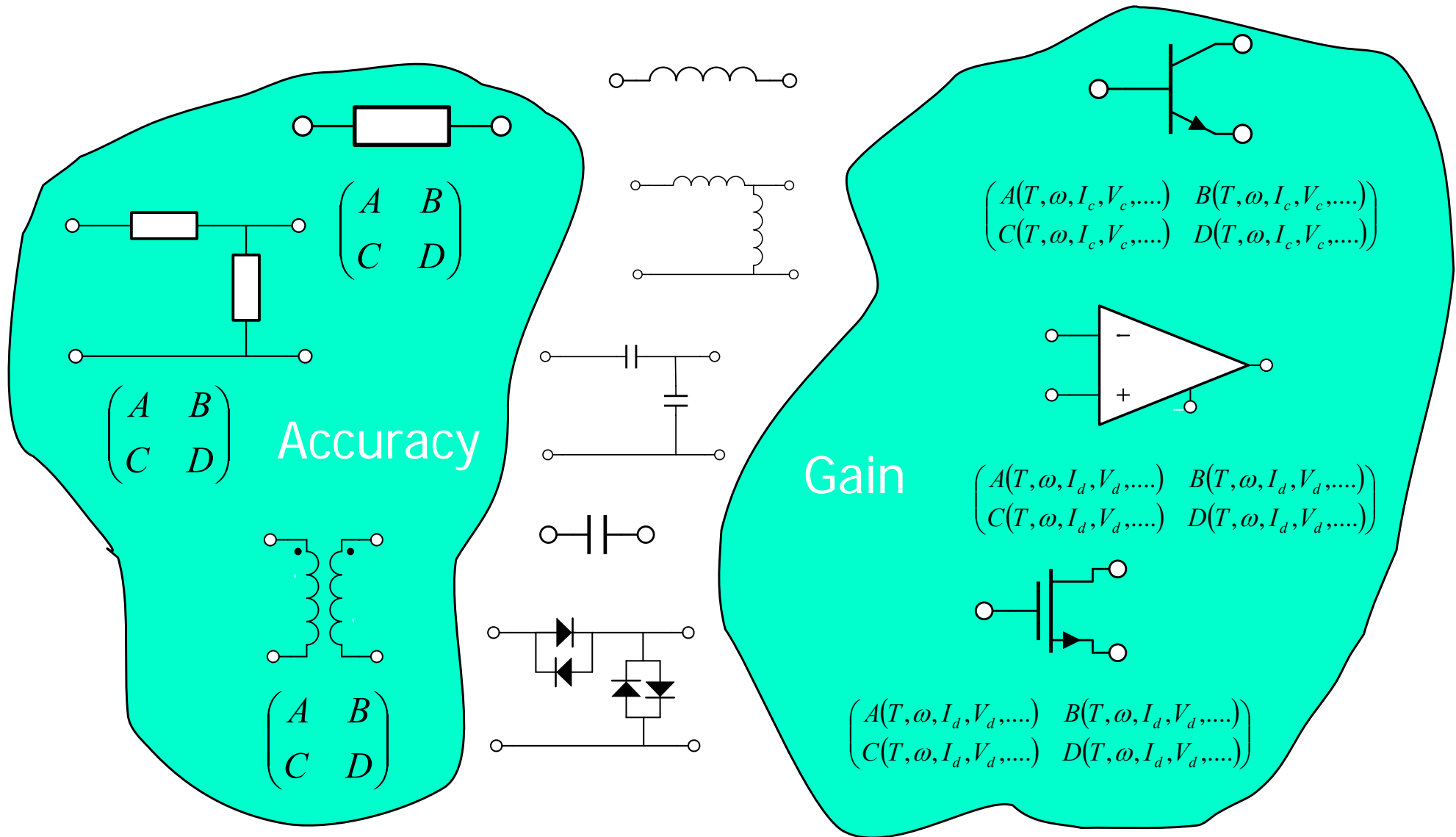

Accurate elements

Elements with gain

The big question.

A, B, C, D indicate gain
 A, B, C, D constant
 A, B, C, D accurately known

Classification of available components


How can we combine the properties of the two orthogonal sets in one system in a perfect way?

Accurate elements


Elements with gain

ET8016-2008


11

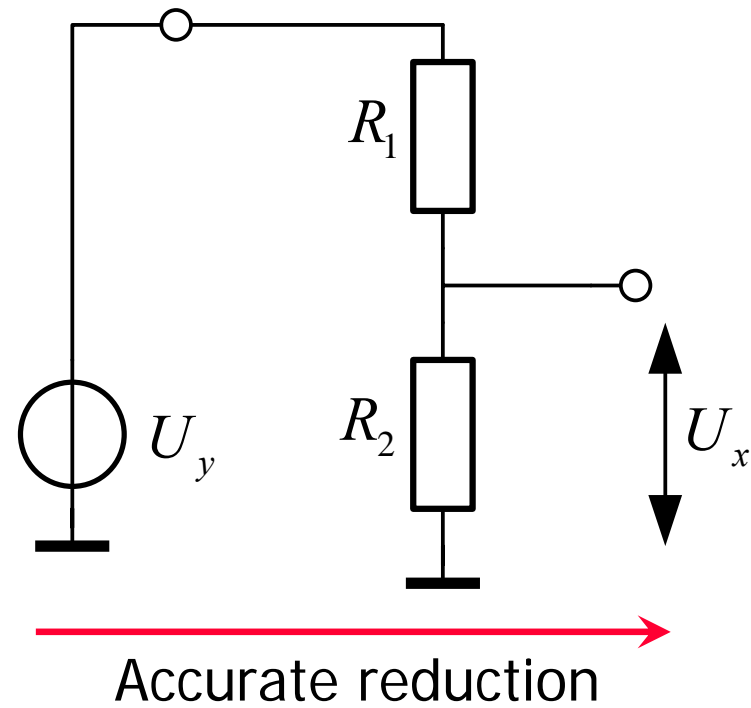

$$U_x = \frac{R_2}{R_1 + R_2} U_y$$

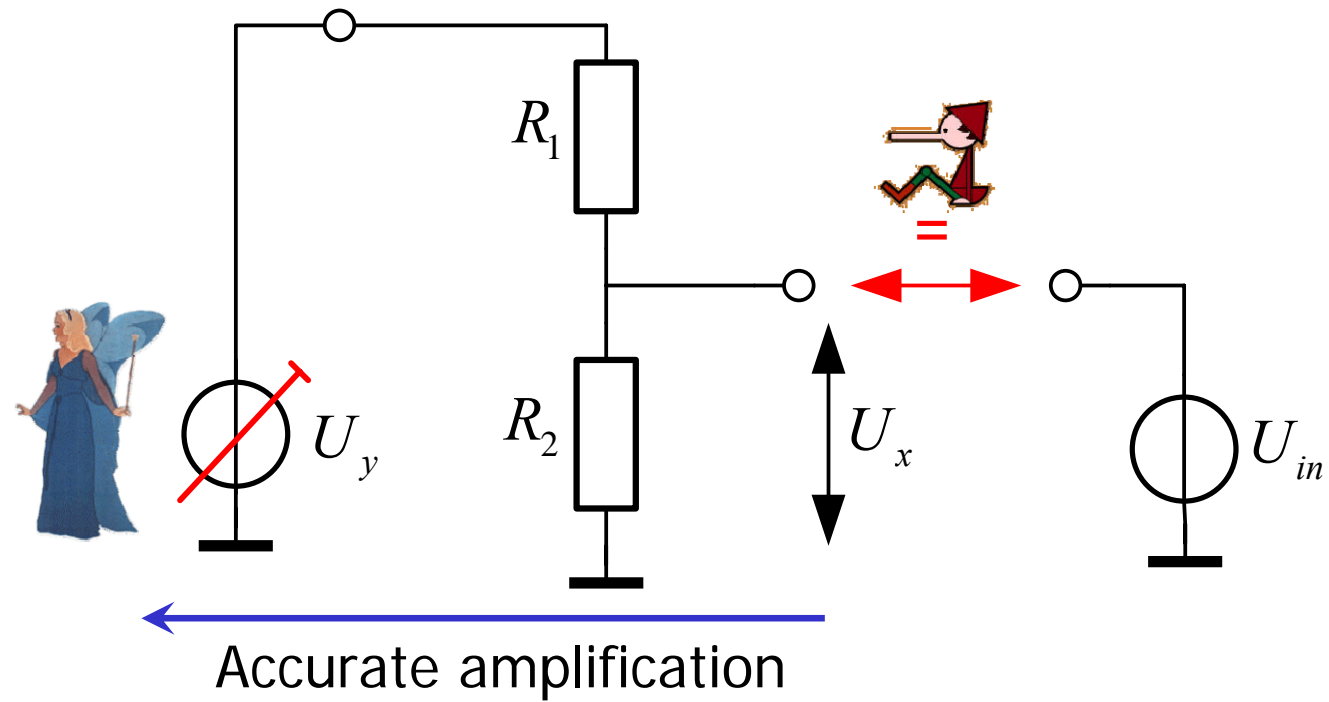


$$U_x = \frac{R_2}{R_1 + R_2} U_y$$

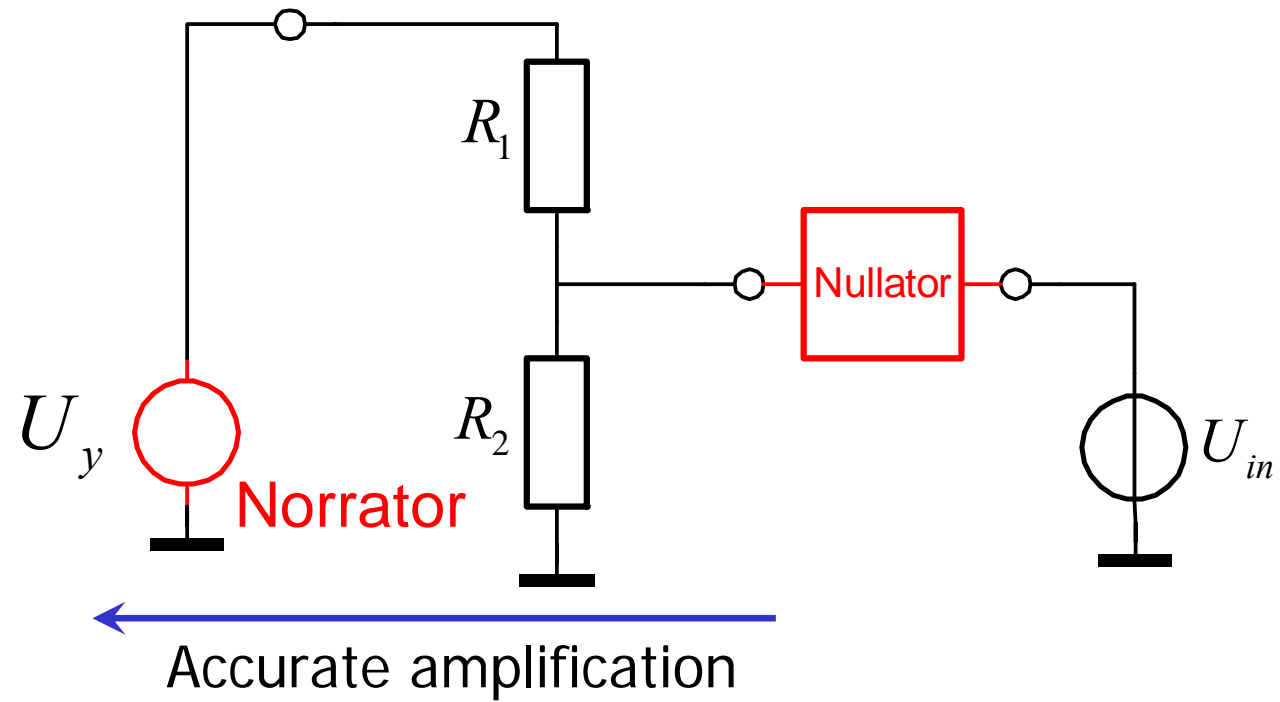


$$U_y = \frac{R_1 + R_2}{R_2} U_{in}$$

Negative feedback

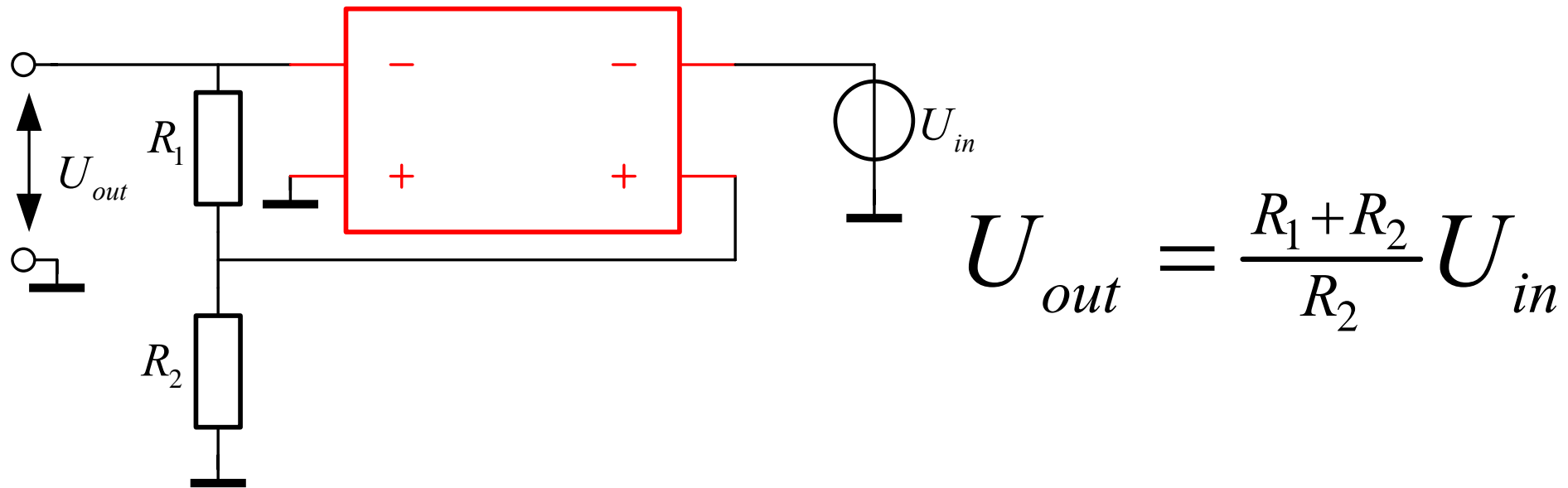

- Nullor + *passive* components \Rightarrow accurate amplifier
- The ***perfect*** method
- Nullor = simplest model for active circuit

Hierarchy

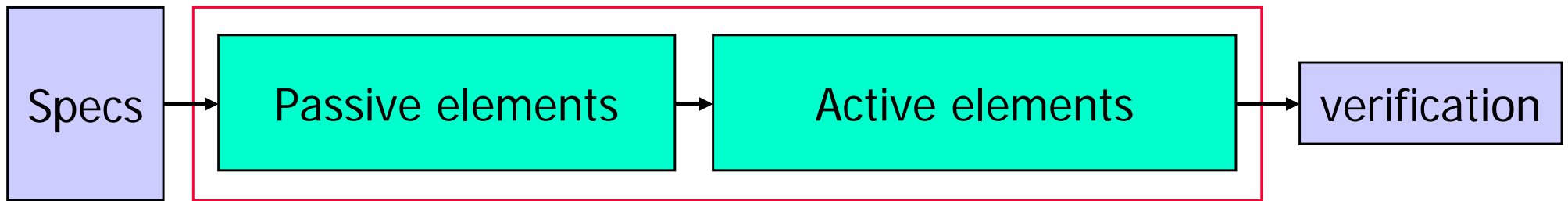

- Accurate reduction
- ONLY passive elements
- Gain
- ONLY active elements

Only!!



Amplifier design in **two orthogonal steps**


1) design of feedback network with nullor in the loop

Nullor: absolute design freedom

- No noise
- No distortion
- No bandwidth limitations

2) design of the active circuit

The general negative feedback system

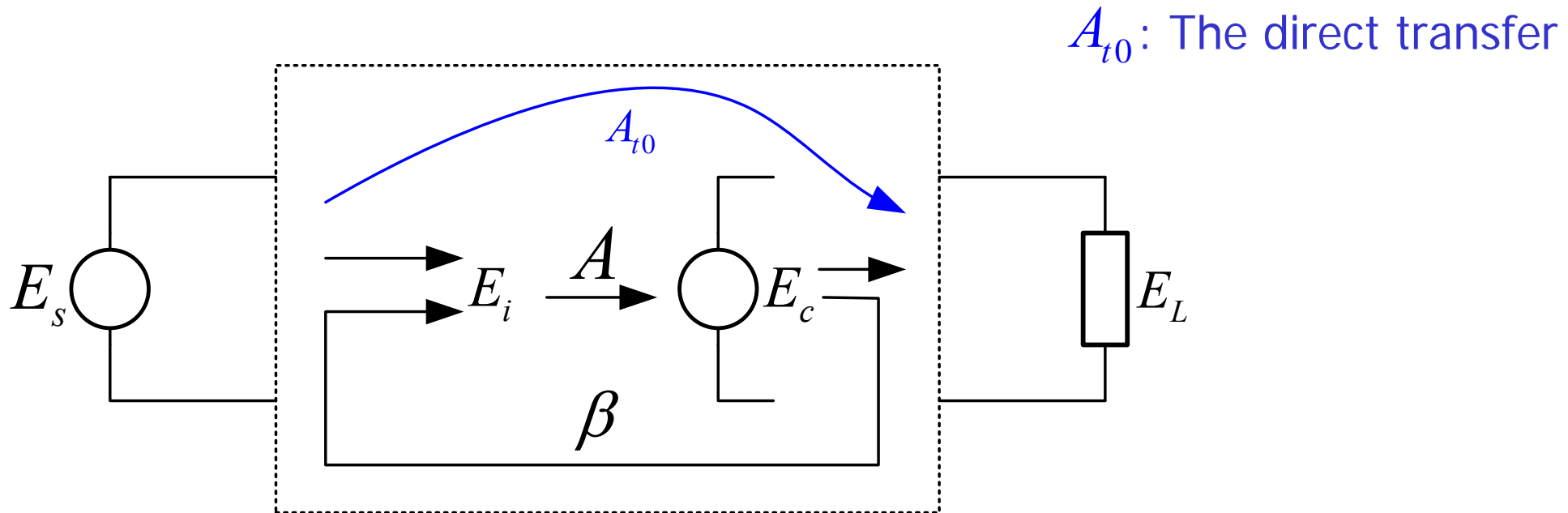


$$E_L = A_{t0} E_s + E_c$$

$$E_i = E_s + \beta E_c$$

$$E_c = A E_i$$


$$A_{t0} = \left. \frac{E_L}{E_s} \right|_{E_c=0}$$
$$\beta = \left. \frac{E_i}{E_c} \right|_{E_s=0}$$

The overall gain A_t

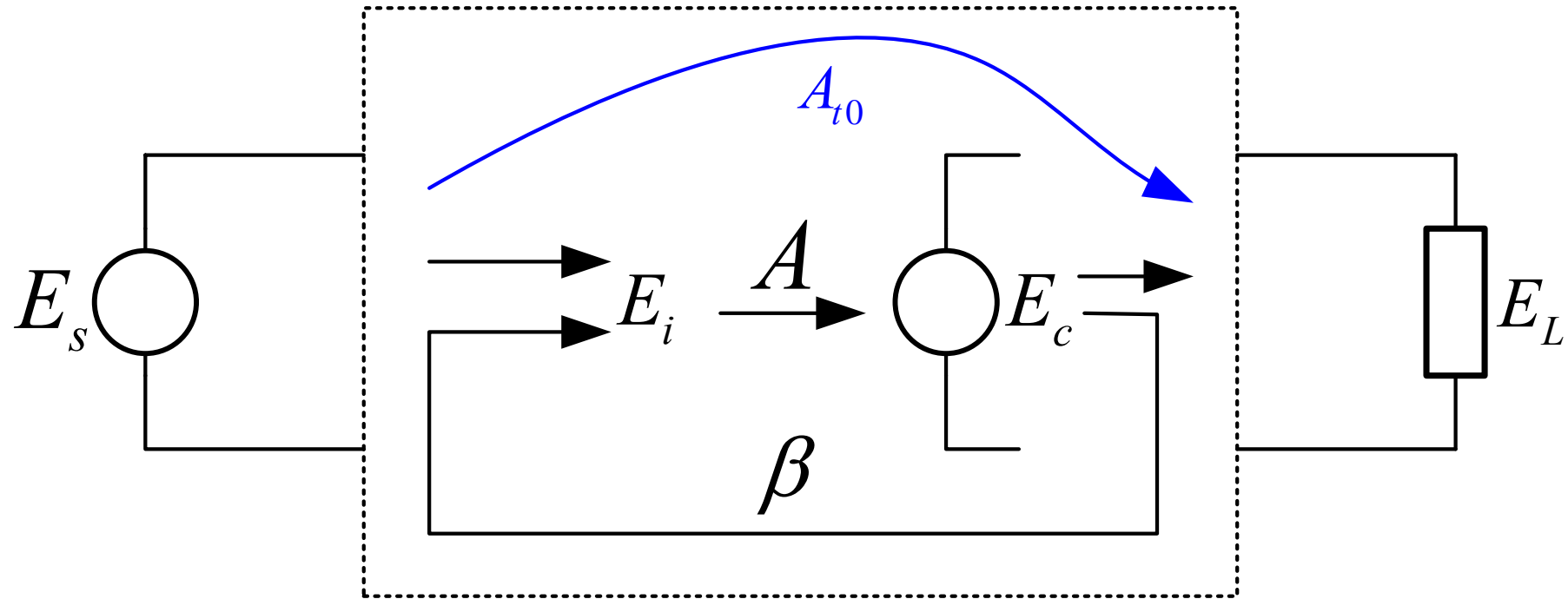


$$A_t = \frac{E_L}{E_s} = A_{t0} + \frac{1}{\beta} \left(\frac{A\beta}{1 - A\beta} \right)$$

The loopgain L

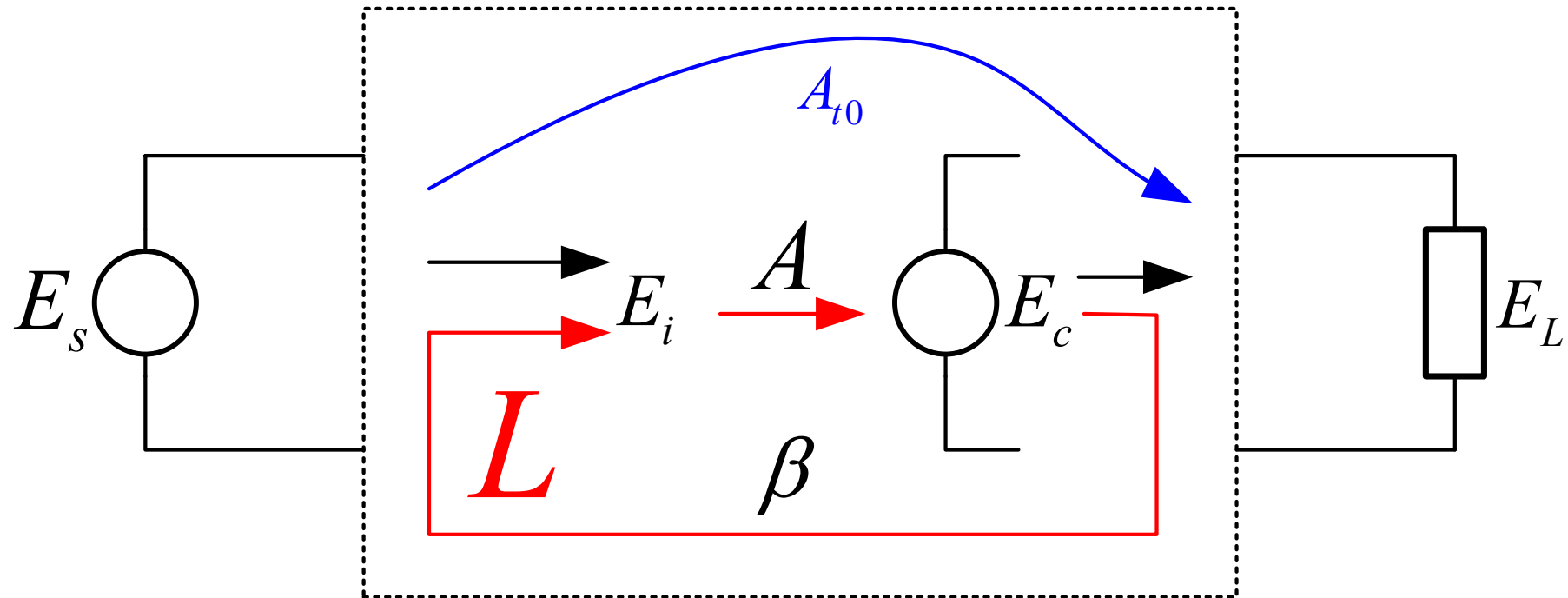

$$A_t = \frac{E_L}{E_s} = A_{t0} + \frac{1}{\beta} \left(\frac{L}{1-L} \right)$$

The asymptotic gain $A_{t\infty}$

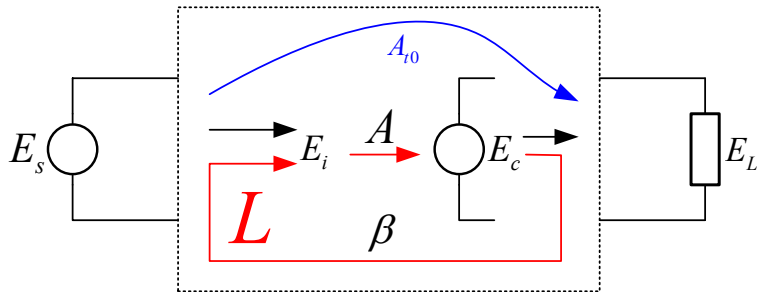


$$A_t = \frac{E_L}{E_s} = A_{t0} + \frac{1}{\beta} \left(\frac{L}{1-L} \right)$$

$$\lim_{L \rightarrow \infty} A_t = A_{t0} - \frac{1}{\beta} = A_{t\infty}$$

The asymptotic gain model
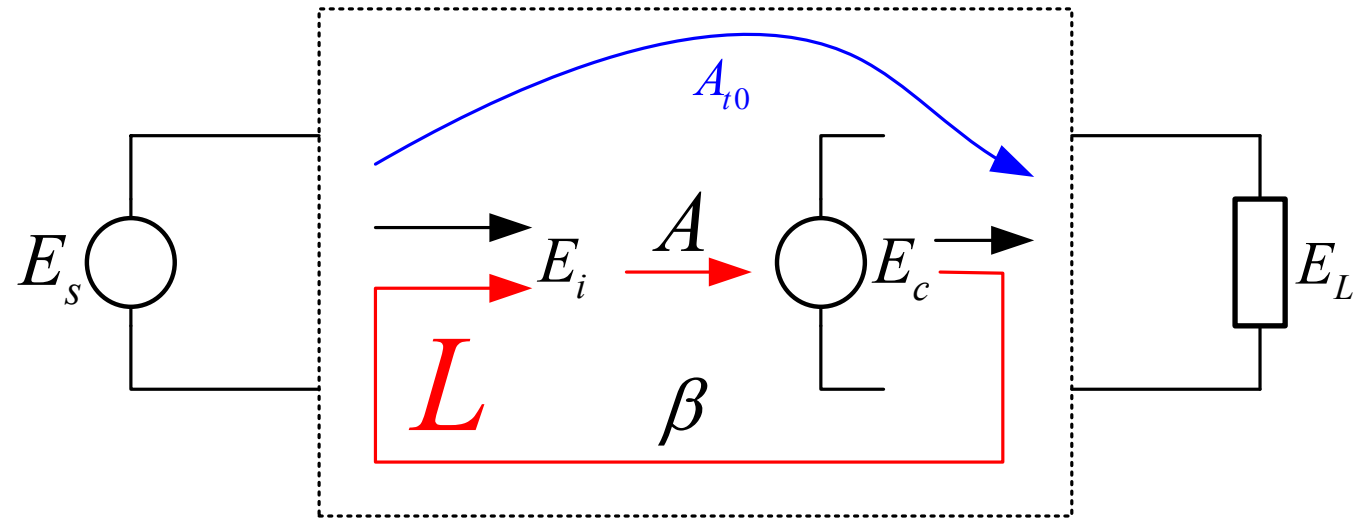
$$A_{t\infty} = A_{t0} - \frac{1}{\beta}$$




$$A_t = \frac{\cancel{A_{t0}}}{1 - L} + A_{t\infty} \frac{-L}{1 - L}$$

$$A_{t0} - \frac{1}{\beta} (!)$$


Hierarchy, Orthogonality

$$A_t = A_{t\infty}$$

Passive elements

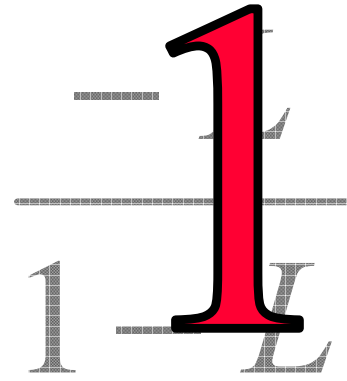

Active Nullor elements

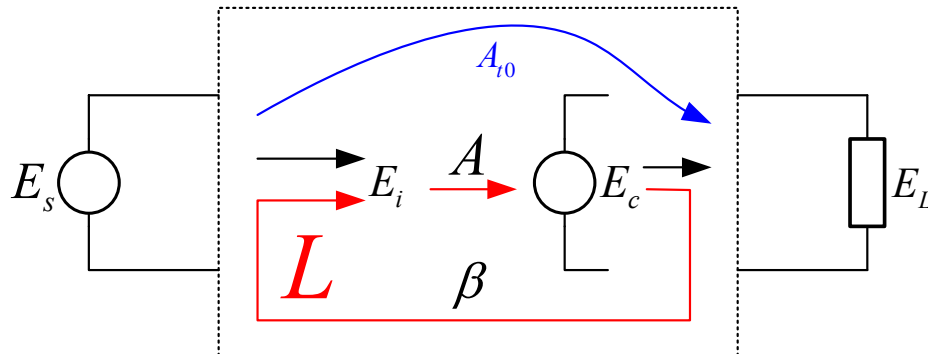

$$A_{t\infty} = A_{t0} - \frac{1}{\beta}$$

$$A_t = A_{t\infty} \frac{-L}{1-L}$$

Amplifier design in two steps


1) design of $A_{t\infty}$ with nullor in the loop

Nullor: absolute design freedom

- No noise
- No distortion
- No bandwidth limitations



2) design of the nullor *approximation*

Hierarchical design

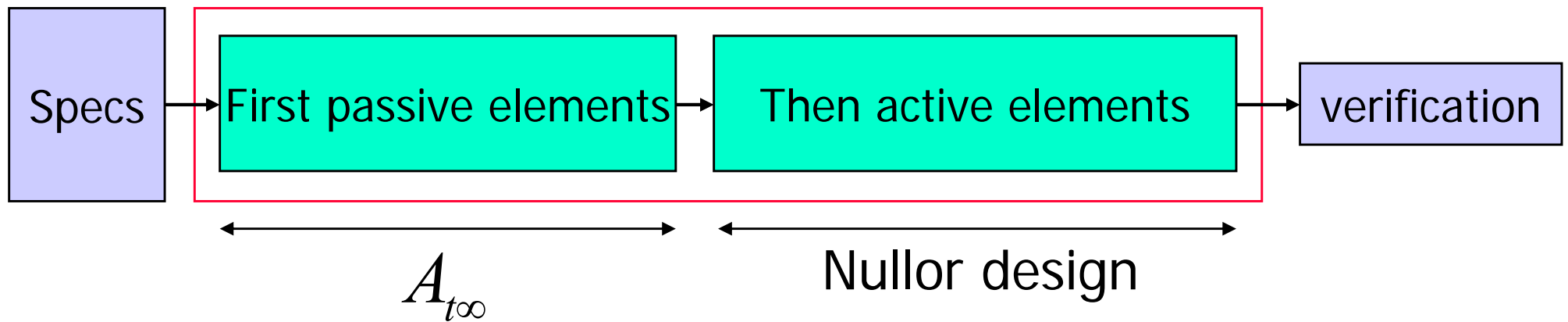

$$A_t = A_{t\infty} \frac{-L}{1-L}$$

More detailed hierarchy..

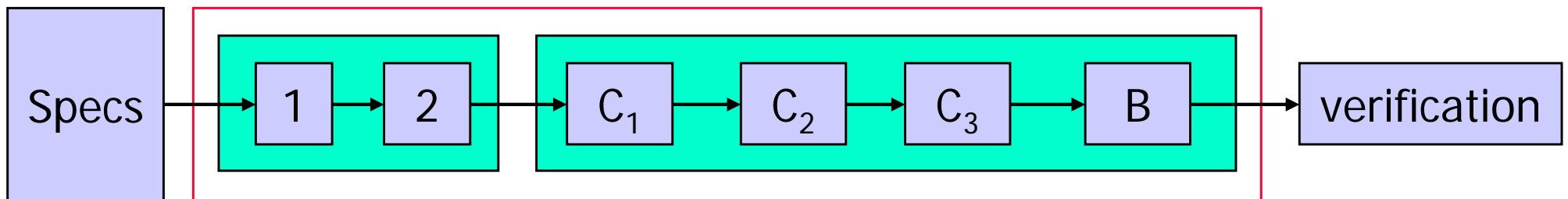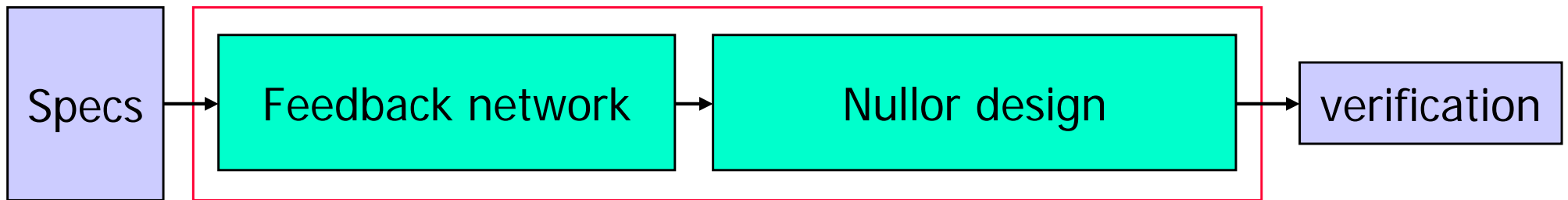

$$C = B^2 \log \frac{S + N}{N}$$


bandwidth - noise - distortion
bandwidth - distortion - noise
noise - bandwidth - distortion
noise - distortion - bandwidth
distortion - noise - bandwidth
distortion - bandwidth - noise

Step 1






Determination amplifier type:

- Specification input and output quantities
- Specification of the transfer






What may have influence and what not?

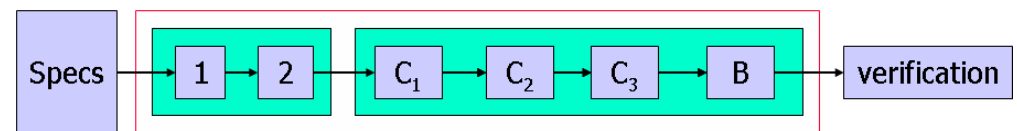

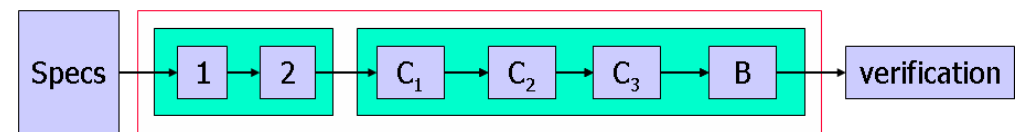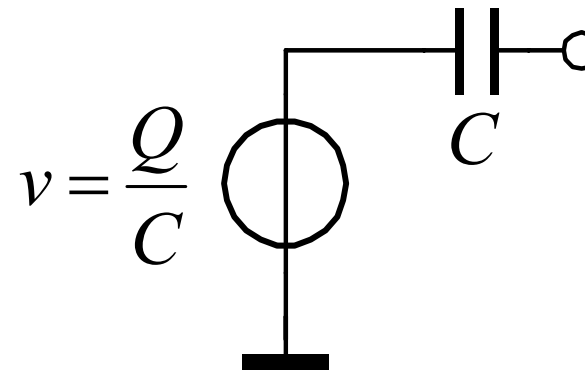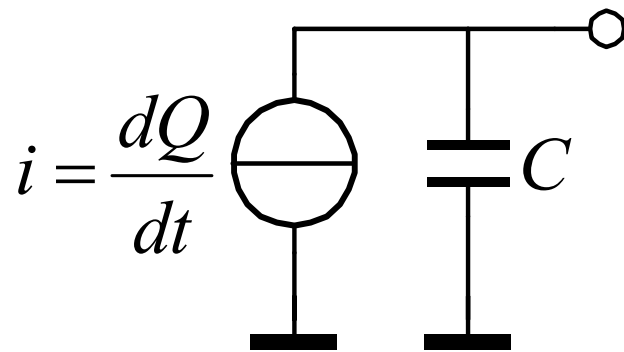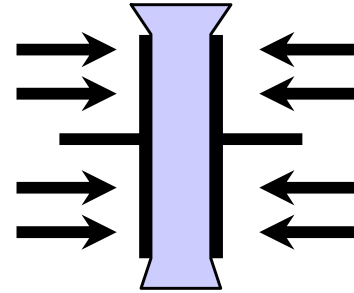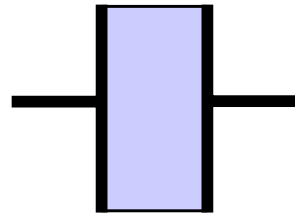Specification input and output quantities




Specification of the transfer

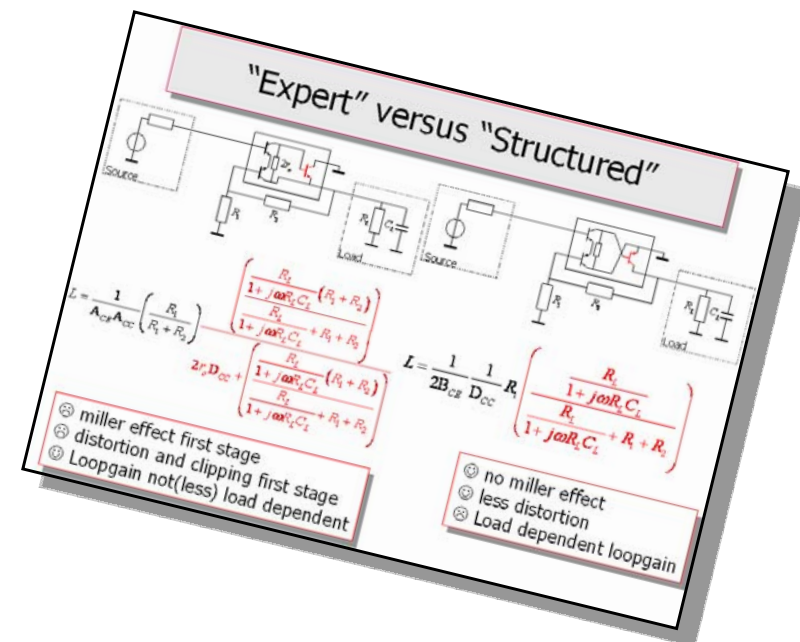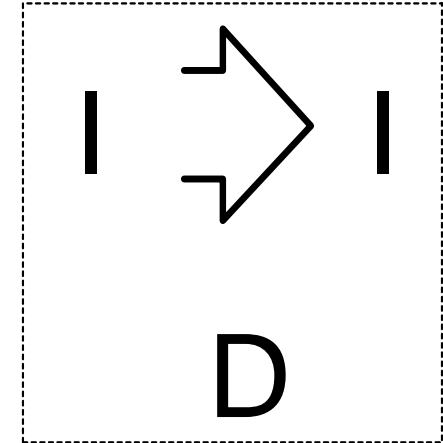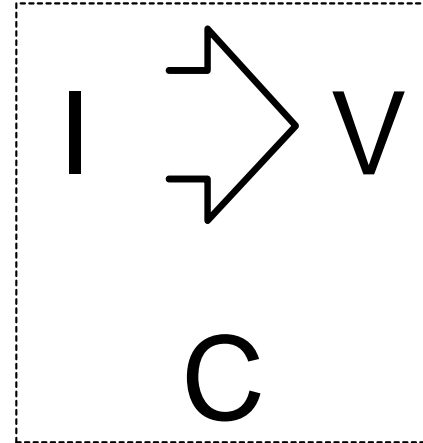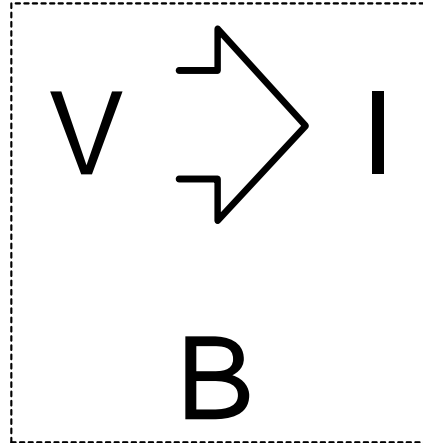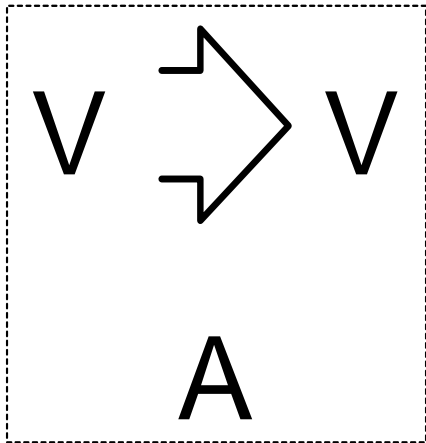


Step 1: the right choice

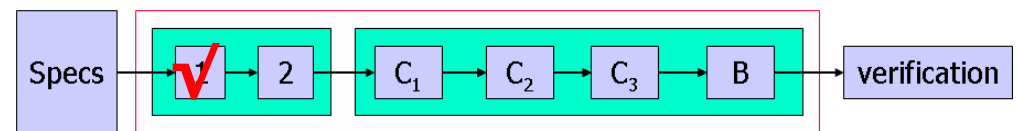- Feed back network determines transfer
- Source impedance *no influence*
- Load impedance *no influence*
- Best nullor implementation
 - No A_{t0} and no influence on L by source and load impedance




Best nullor implementation

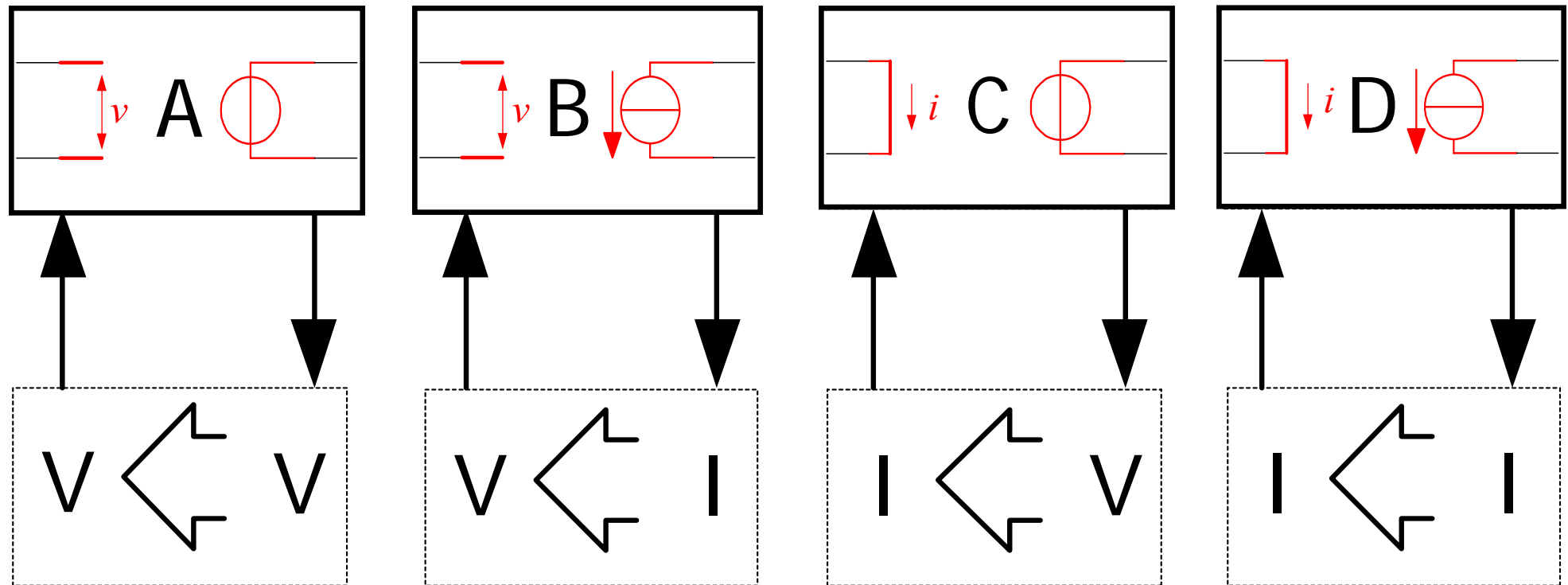

Technological limits

Exercise 1

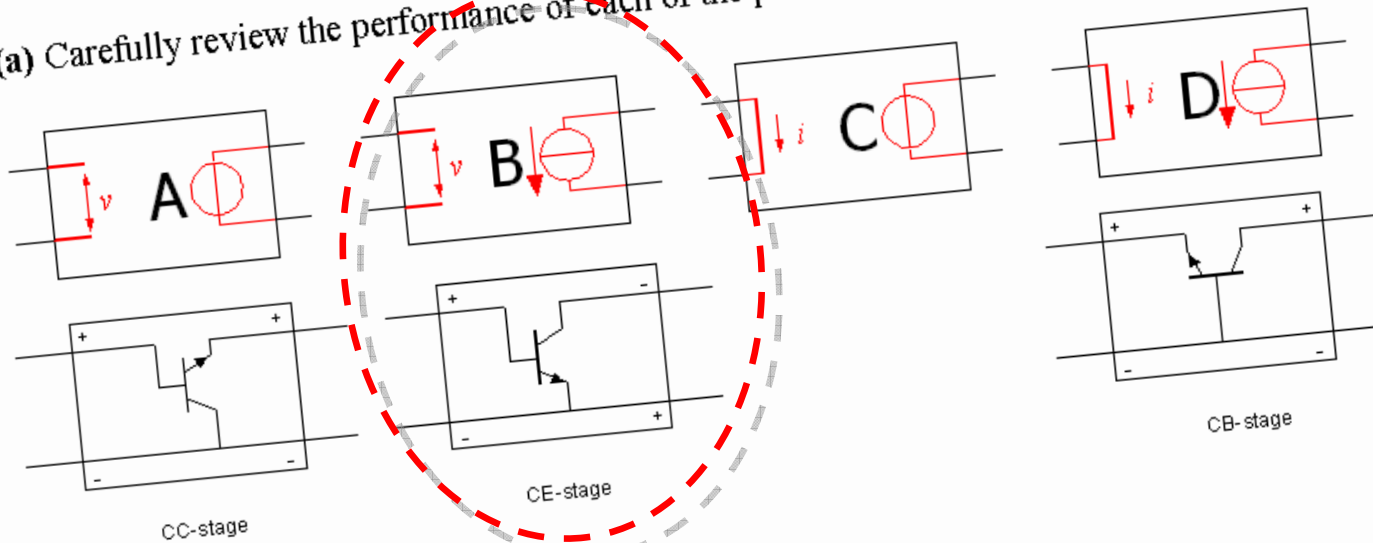
(a) Carefully review the performance of each of the practical implementations below.



Answer questions like:

- What is the (detailed) expected behavior of the ideal blocks?
- How well does the behavior of the practical implementations agree with this?
- What is the gain?
- How well defined are the input and output impedance?
- How reliable are the input and output impedance?
- What is the sensitivity to the source impedance and the load impedance?




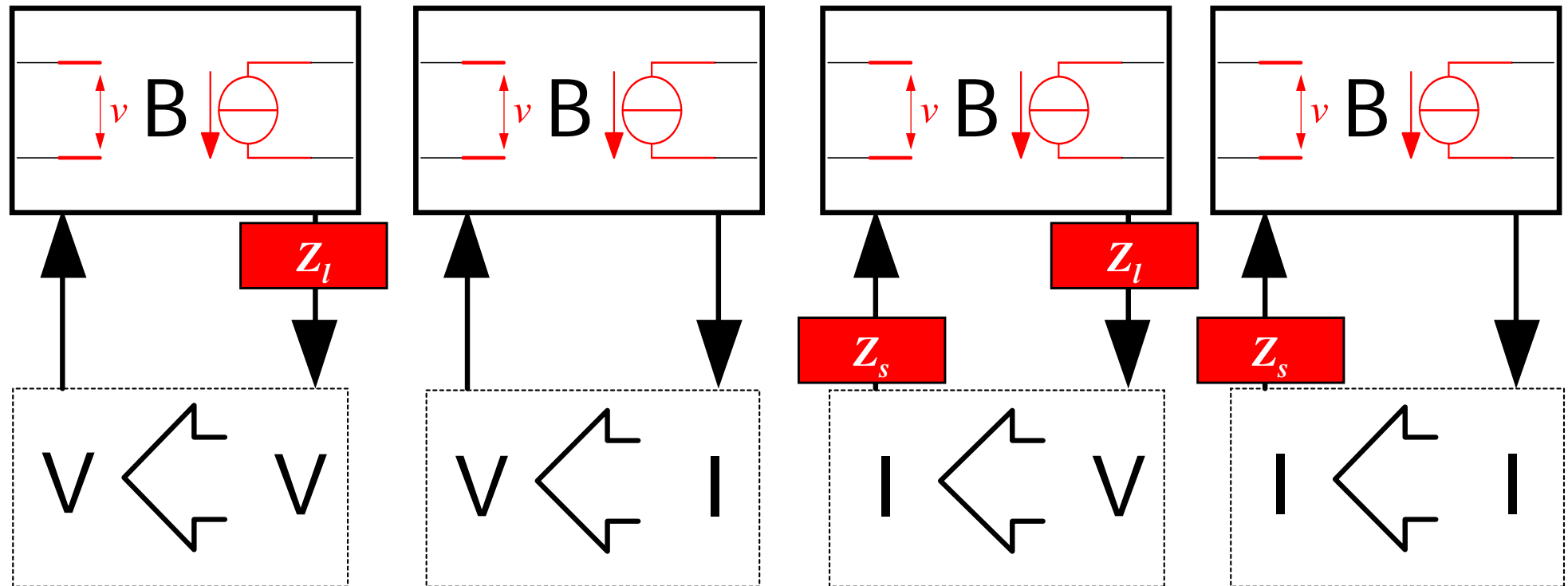
Nullor implementation close to technology



- Remember the best choice
- Know the penalty for the others!


Step 2, the feed back network

The active part *is* a nullor

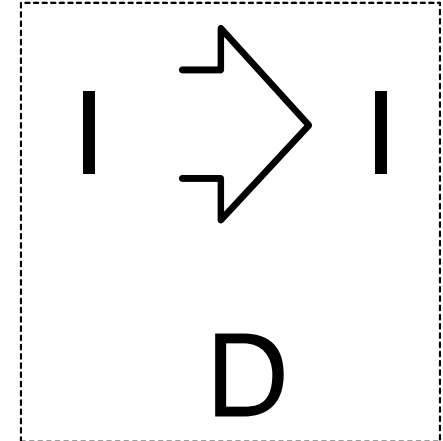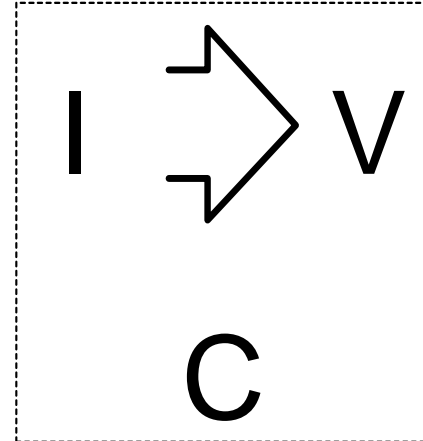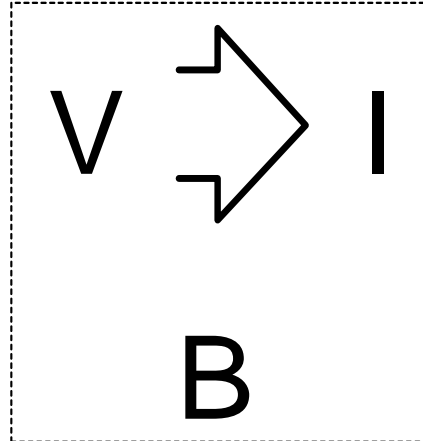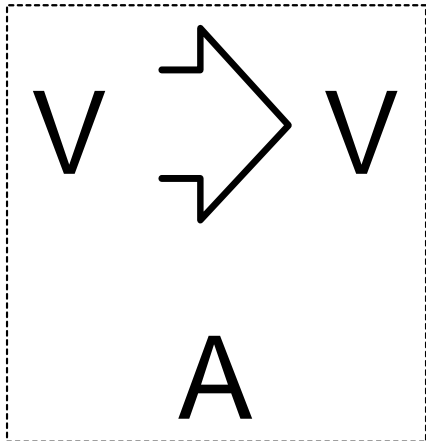


Ideal feedback components
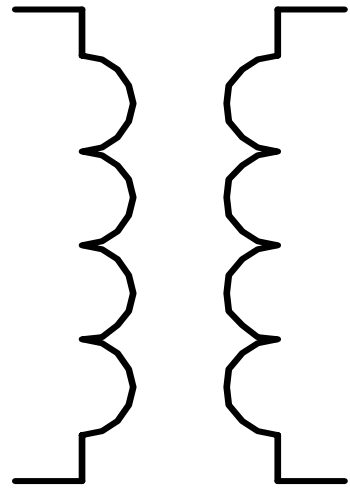
$$\begin{pmatrix} n & 0 \\ 0 & \frac{1}{n} \end{pmatrix}$$



Transformer

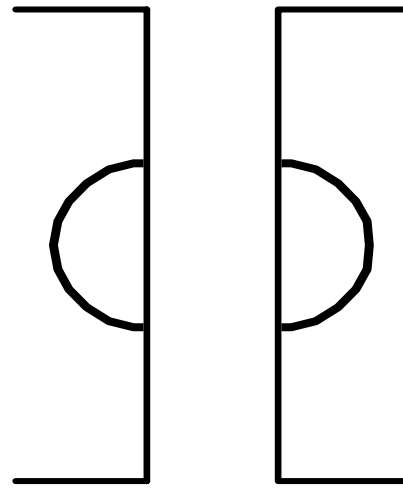


Gyrator

$$\begin{pmatrix} 0 & R \\ \frac{1}{R} & 0 \end{pmatrix}$$

- No power dissipation
- No noise production
- No noise enlargement
- No excess voltages or currents
- Galvanic separation


Voltage amplifier

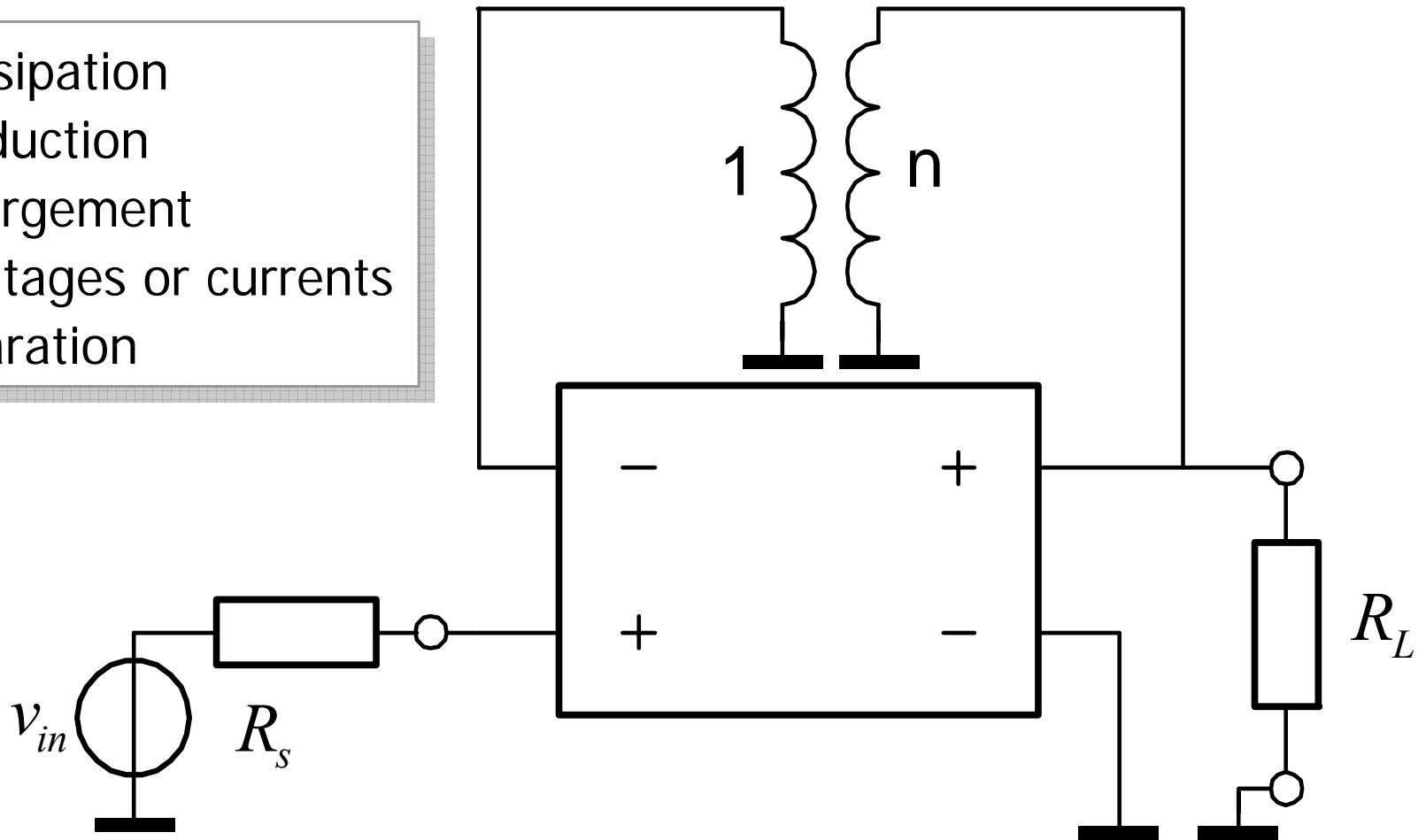- No power dissipation
- No noise production
- No noise enlargement
- No excess voltages or currents
- Galvanic separation




Noise influence

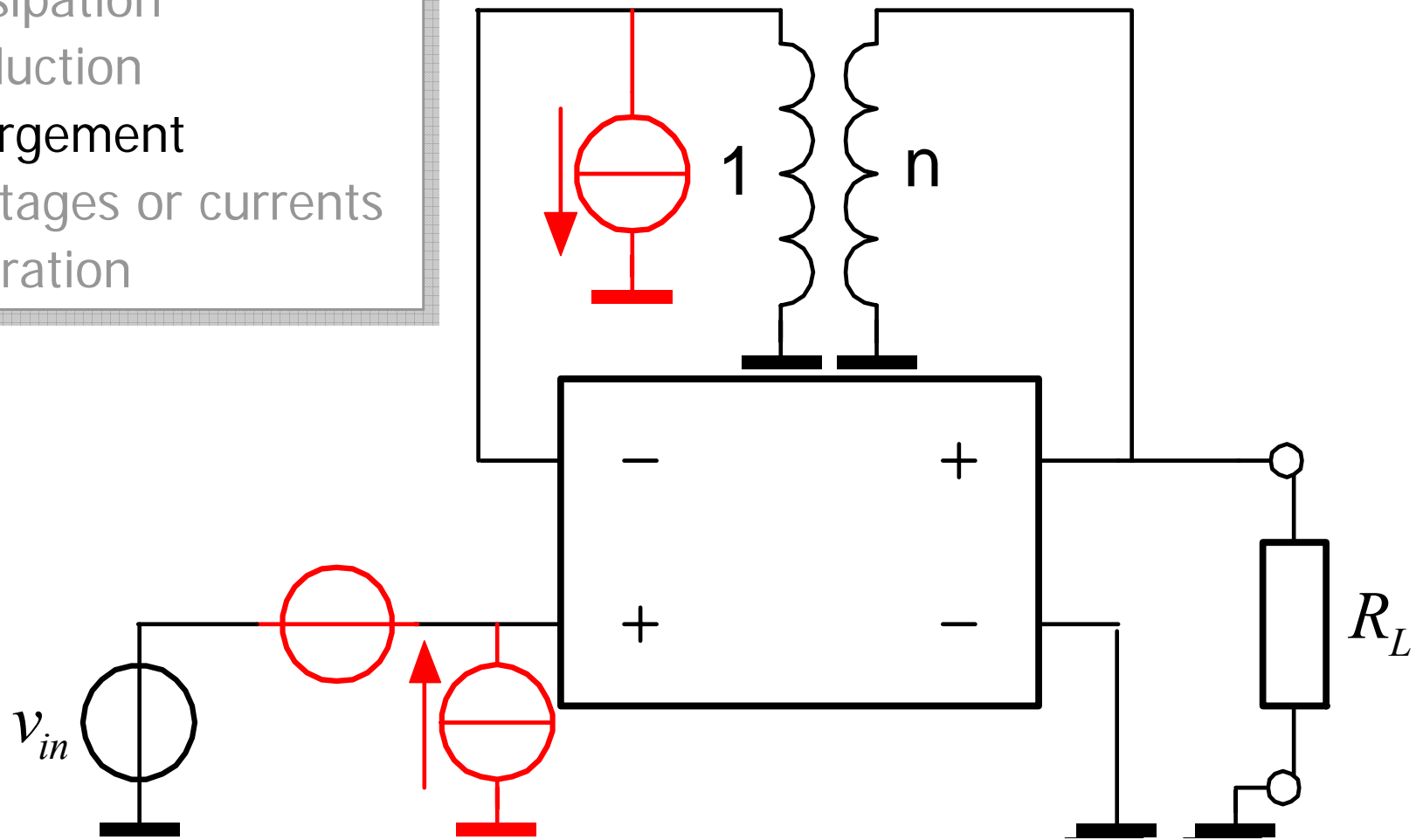- No power dissipation
- No noise production
- **No noise enlargement**
- No excess voltages or currents
- Galvanic separation




Noise influence

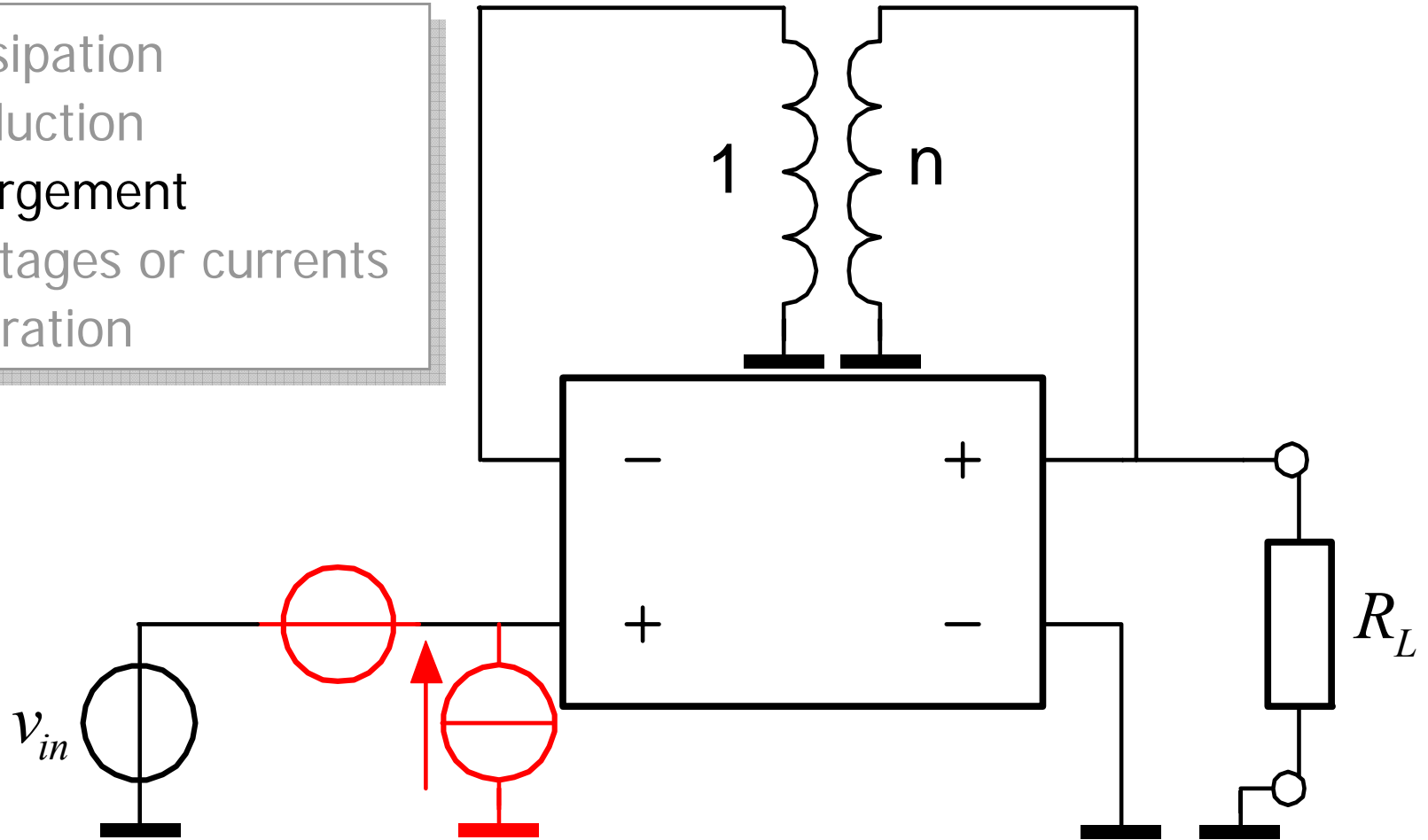- No power dissipation
- No noise production
- **No noise enlargement**
- No excess voltages or currents
- Galvanic separation




Noise influence impedance network


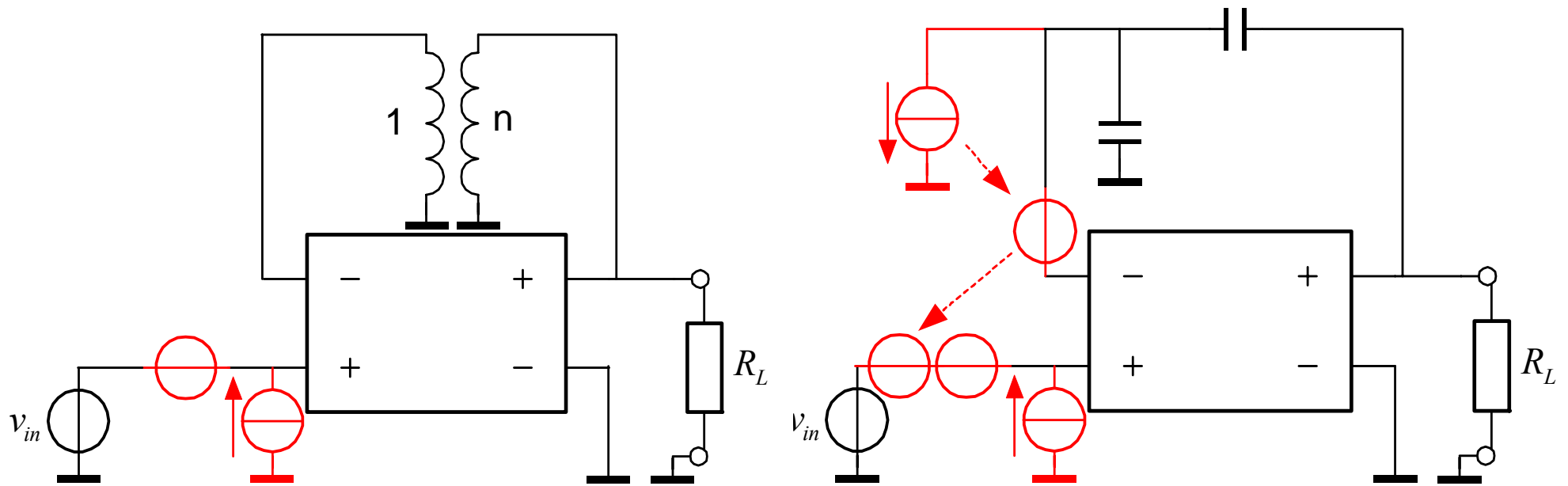


Trans-impedance amplifier

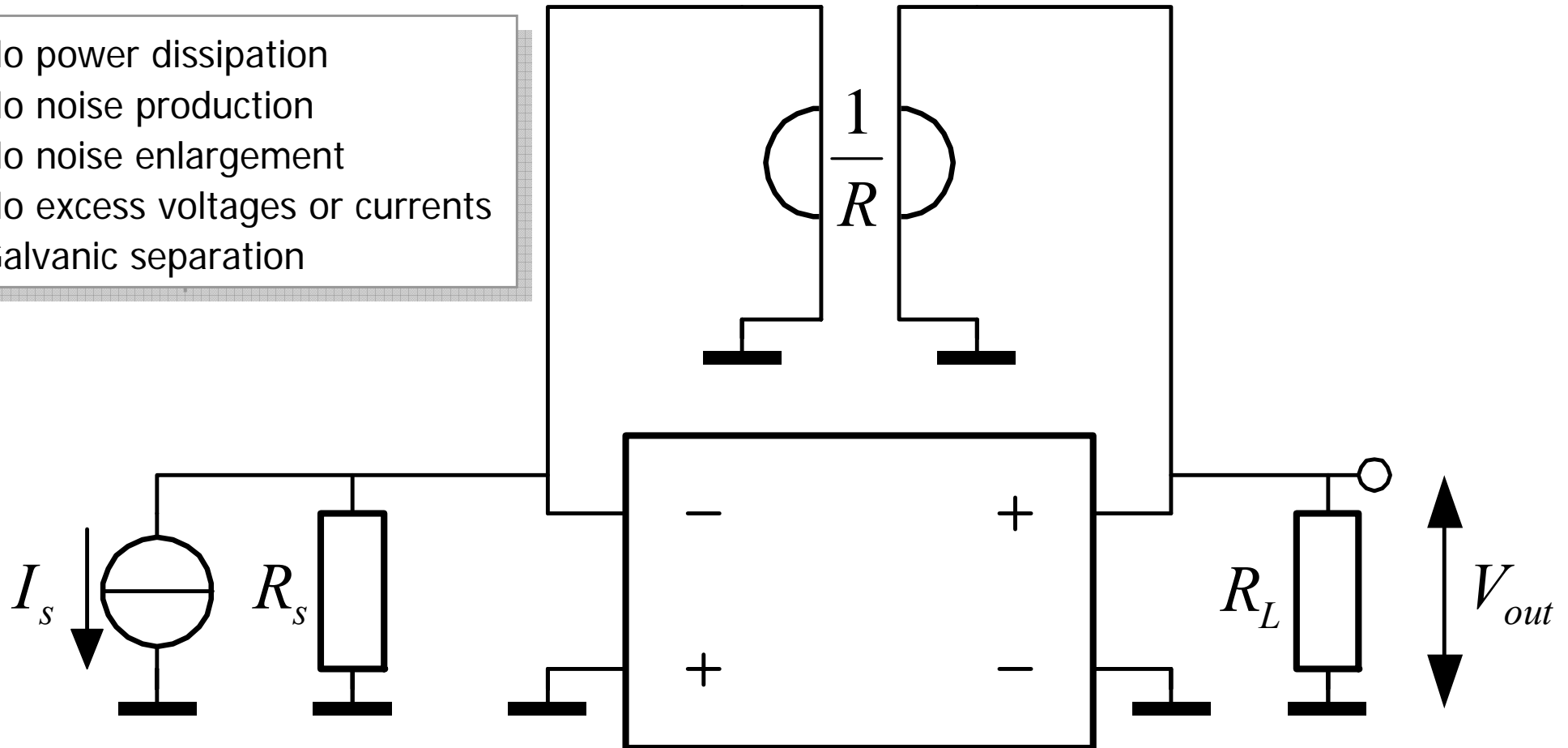- No power dissipation
- No noise production
- No noise enlargement
- No excess voltages or currents
- Galvanic separation




Ideal versus reality: transformer

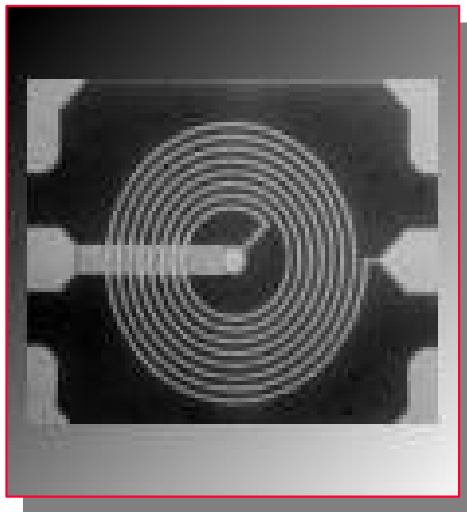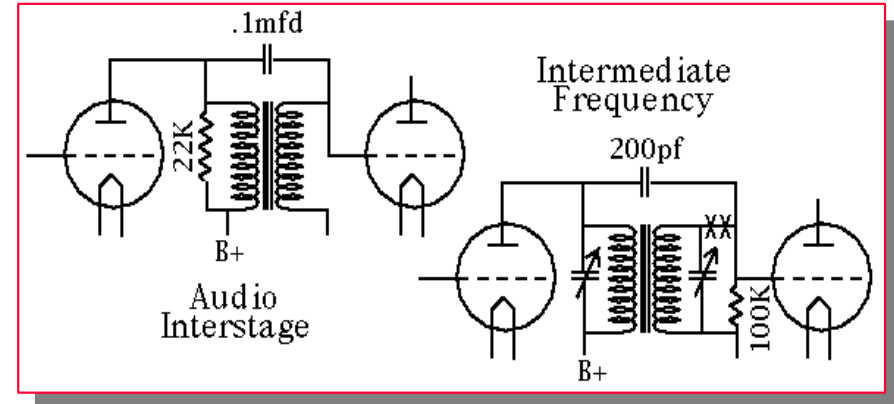

Not always feasible


- Parasitic impedances
- Limited frequency range
- Non-linearity (saturation)
- Technological problems

Ideal versus reality: gyrator

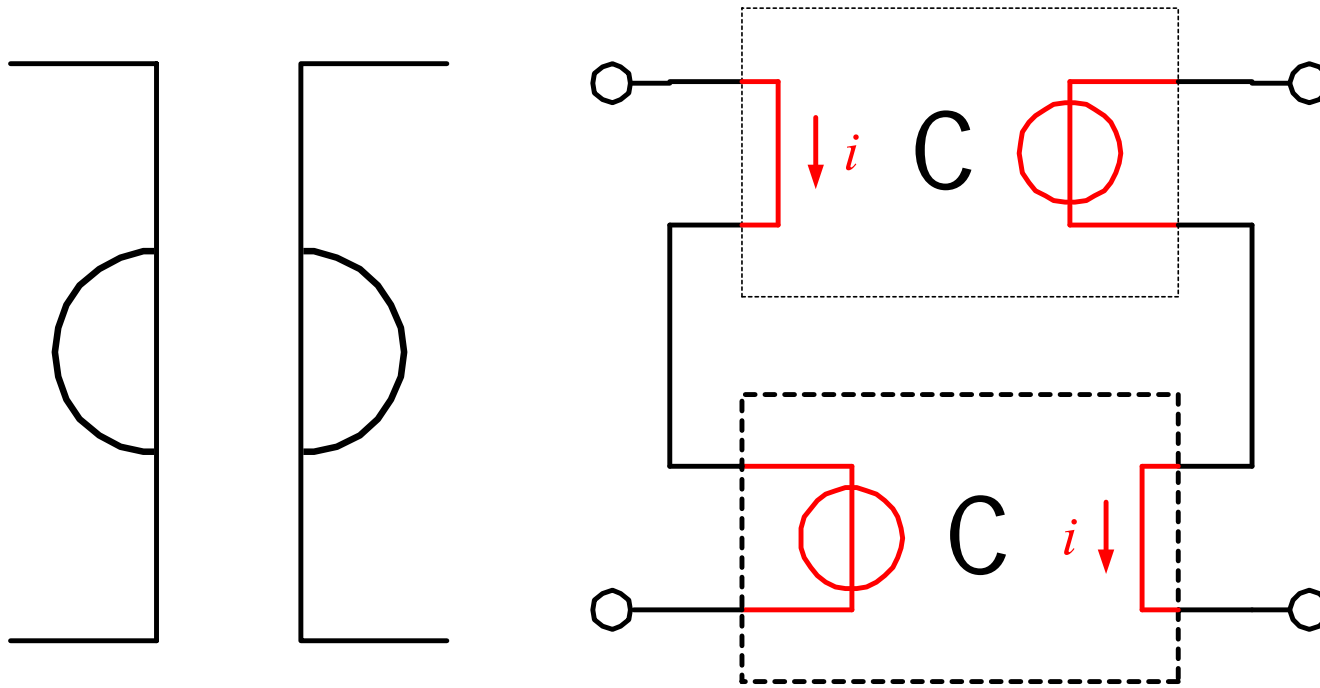


- Needs controlled sources (active elements)
- Practical implementation produces noise
- Non-linearity
- Bandwidth restrictions

"Poor mans" gyrator

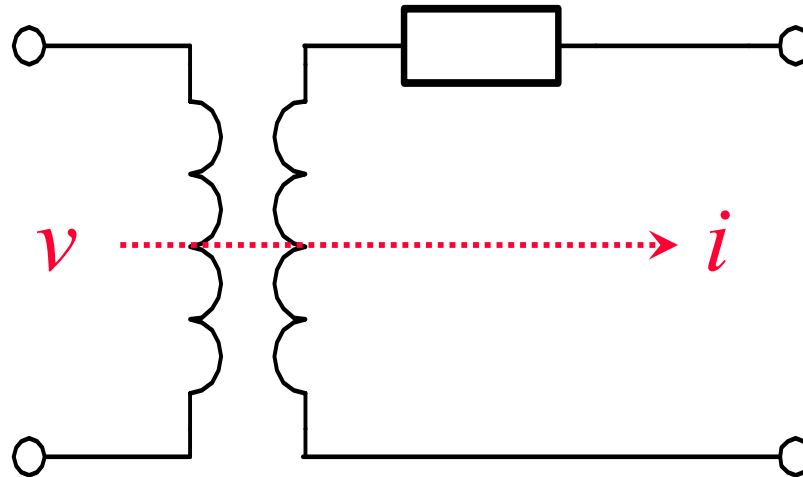

- ☹ Feature lost : No power dissipation
- ☹ Feature lost : No noise production
- ☹ Feature lost : No noise enlargement
- ☹ Feature lost : No excess voltages or currents
- ☺ Galvanic separation

"Very poor mans" gyrator

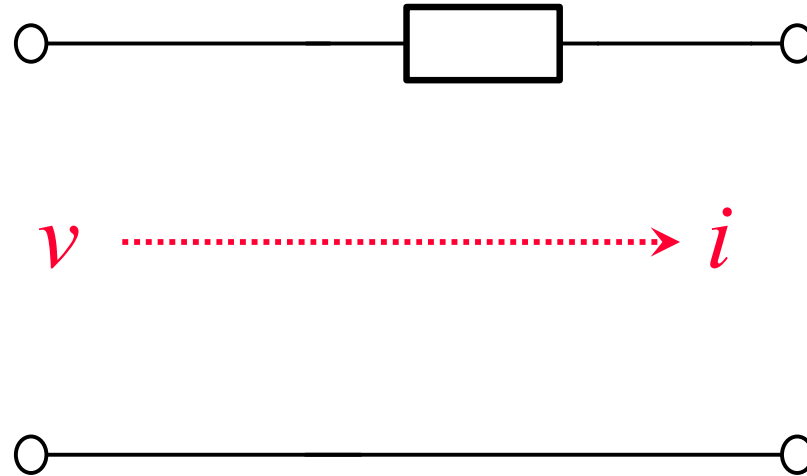

- ☹ Feature lost: No power dissipation
- ☹ Feature lost : No noise production
- ☹ Feature lost : No noise enlargement
- ☹ Feature lost : No excess voltages or currents
- ☹ Feature lost : Galvanic separation
- ☹ Direct connection between input and output node


Why use the ideal transformers and gyrator?

Absolute minimum of:





- Power consumption
- Current swing
- Voltage swing
- Noise





(The specifications)

If already this it not enough.....

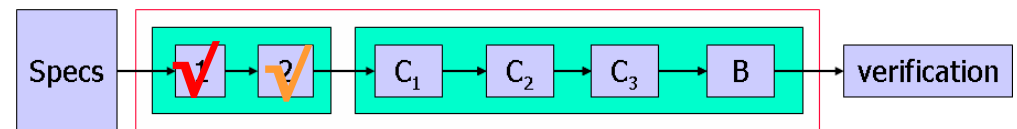


Common feed back networks

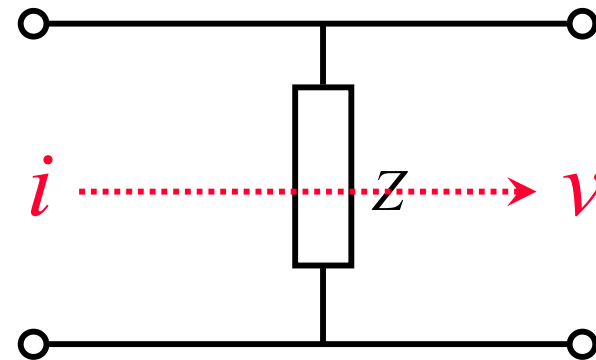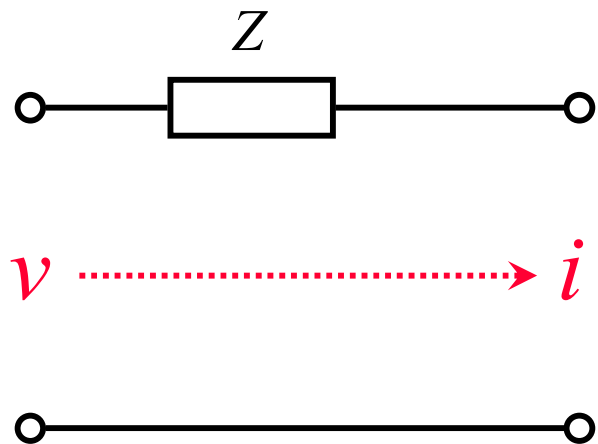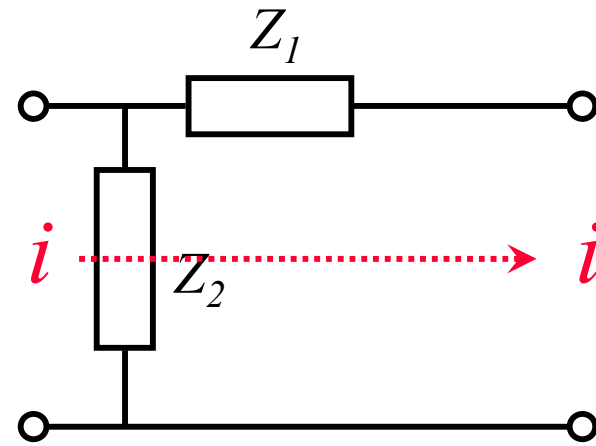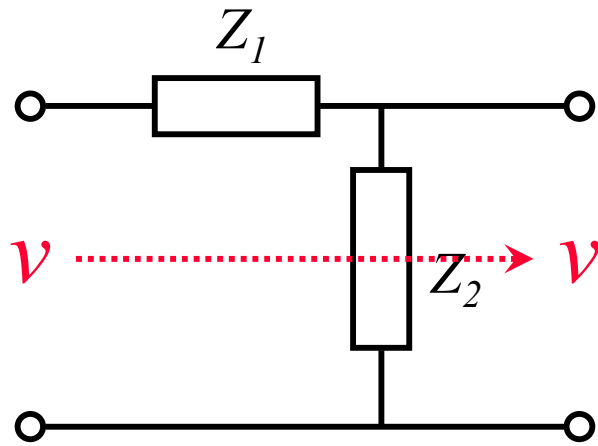

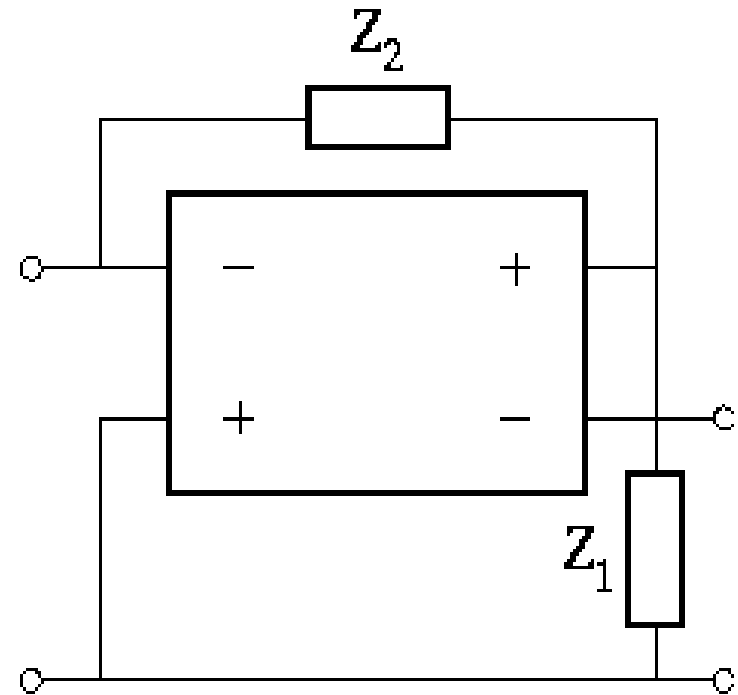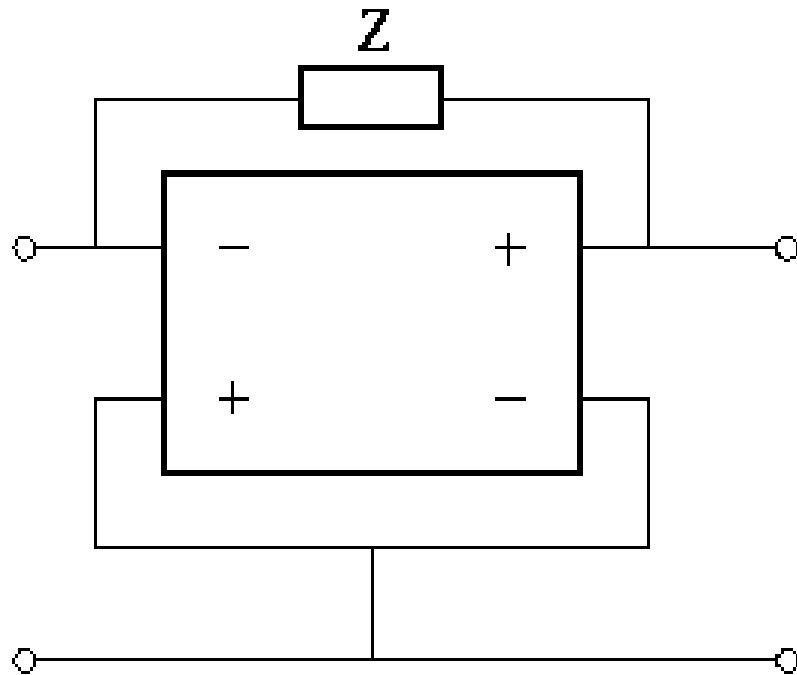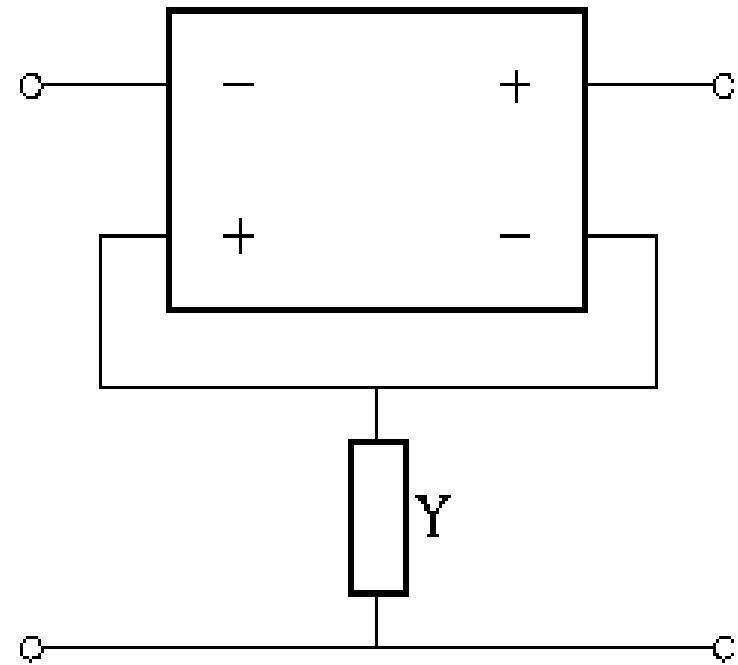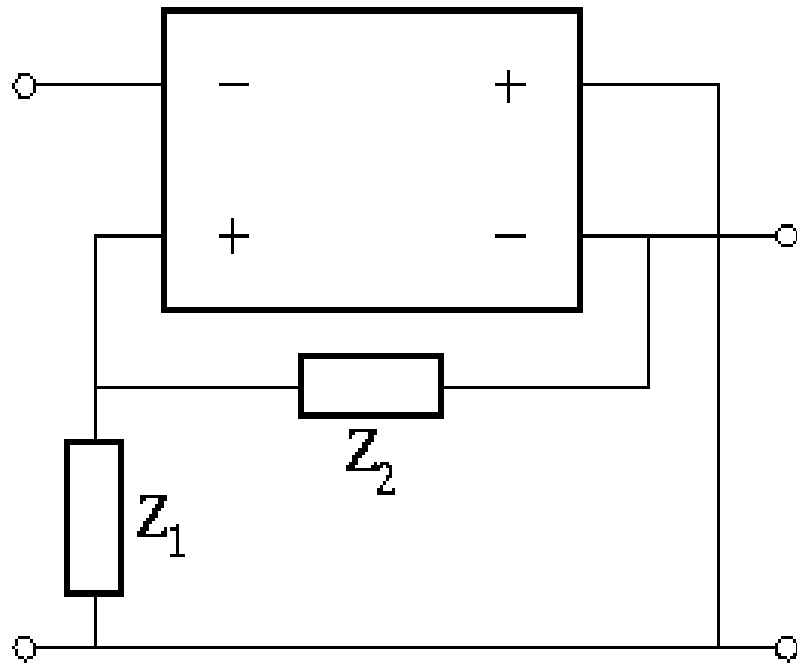


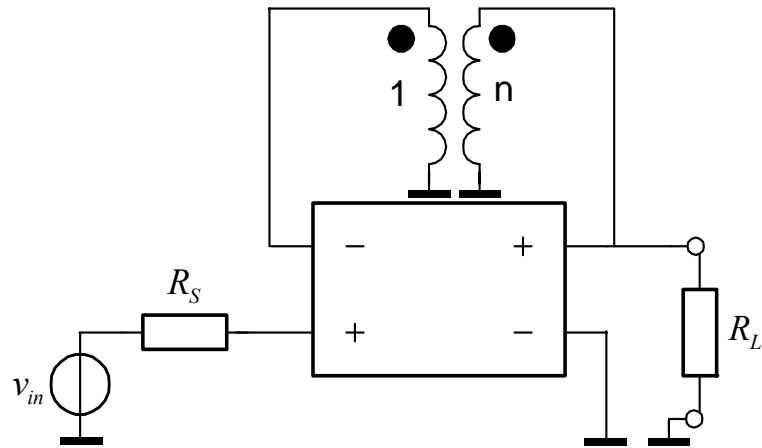Common feed back networks : Reduced flexibility




Non-inverting voltage amplifier

$$C = B^2 \log \frac{S + N}{N}$$
















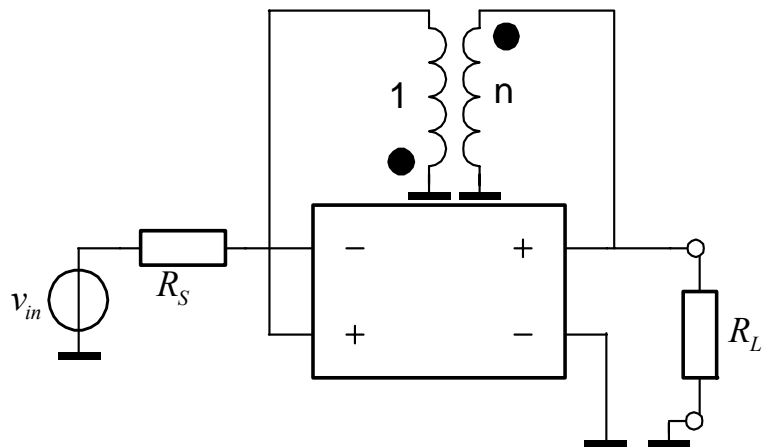


Inverting voltage amplifier

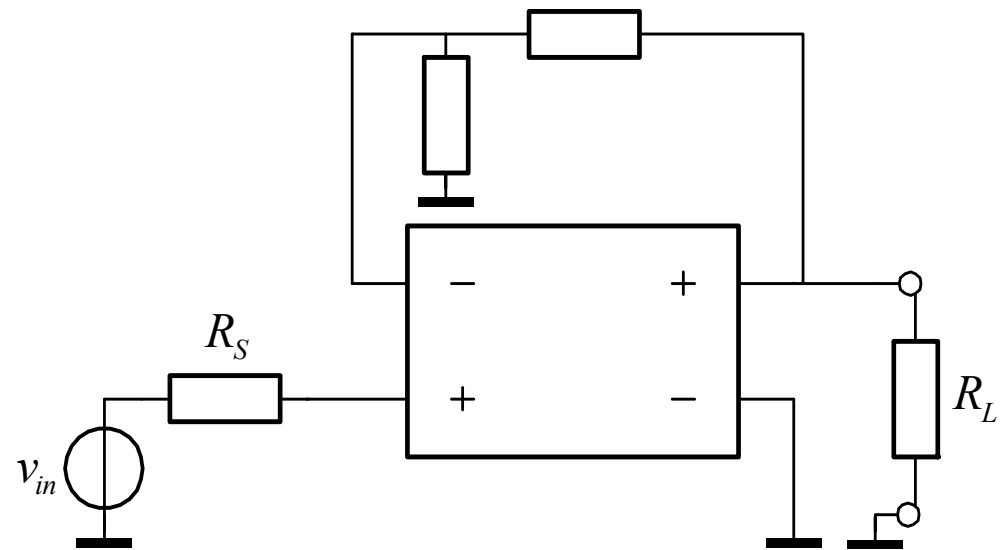

Non-inverting voltage amplifier

Negative feedback networks

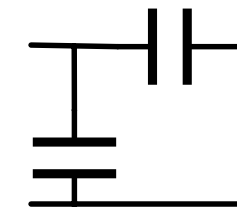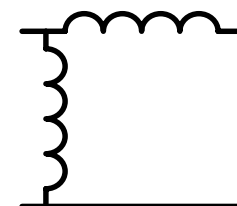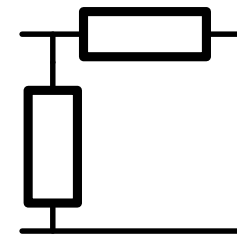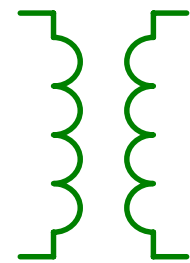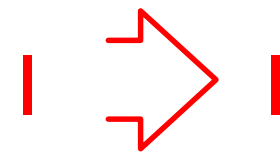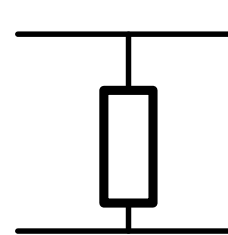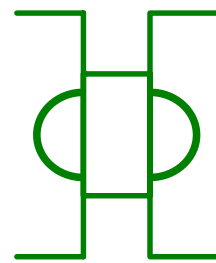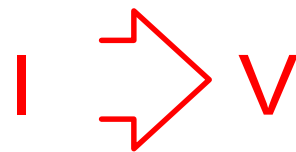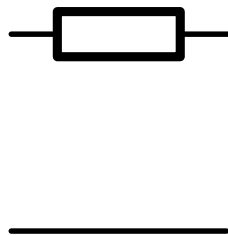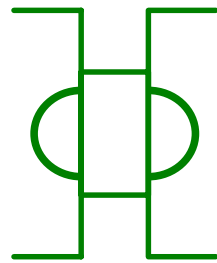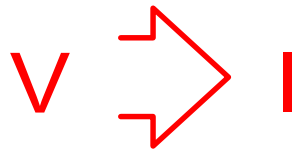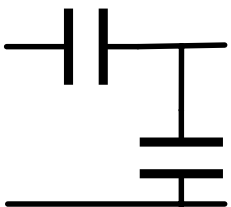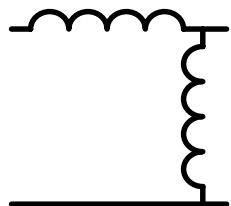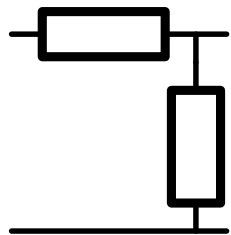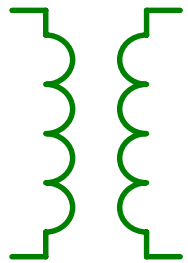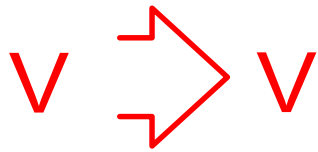


Impedance networks:

- Produce noise (R)
- Enlarge contribution existing noise sources
- Dissipate power (R)
- Create excess voltage or current
- Galvanic coupling


Accurate Amplification

Information from source to load

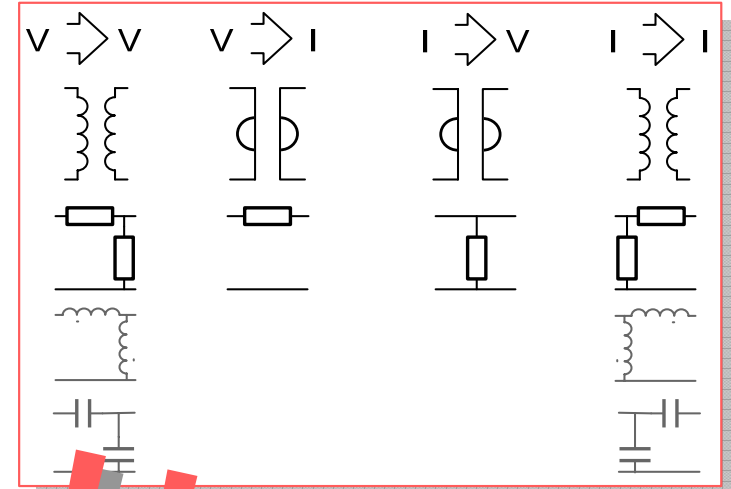- Signal power is enlarged
- Information stays unaltered




Definition

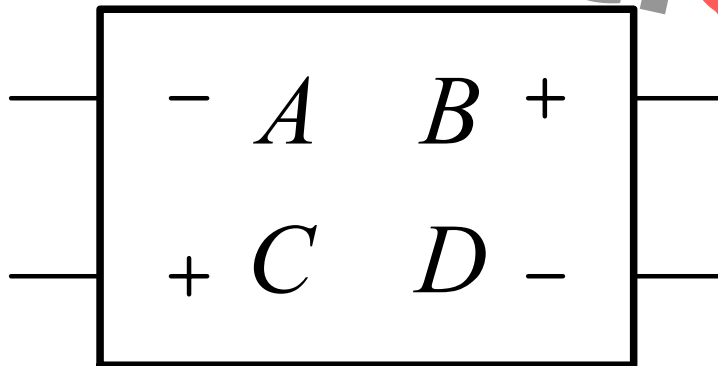

$A, B, C, D < 1$!!!!!!
 A, B, C, D constant
 A, B, C, D accurately known

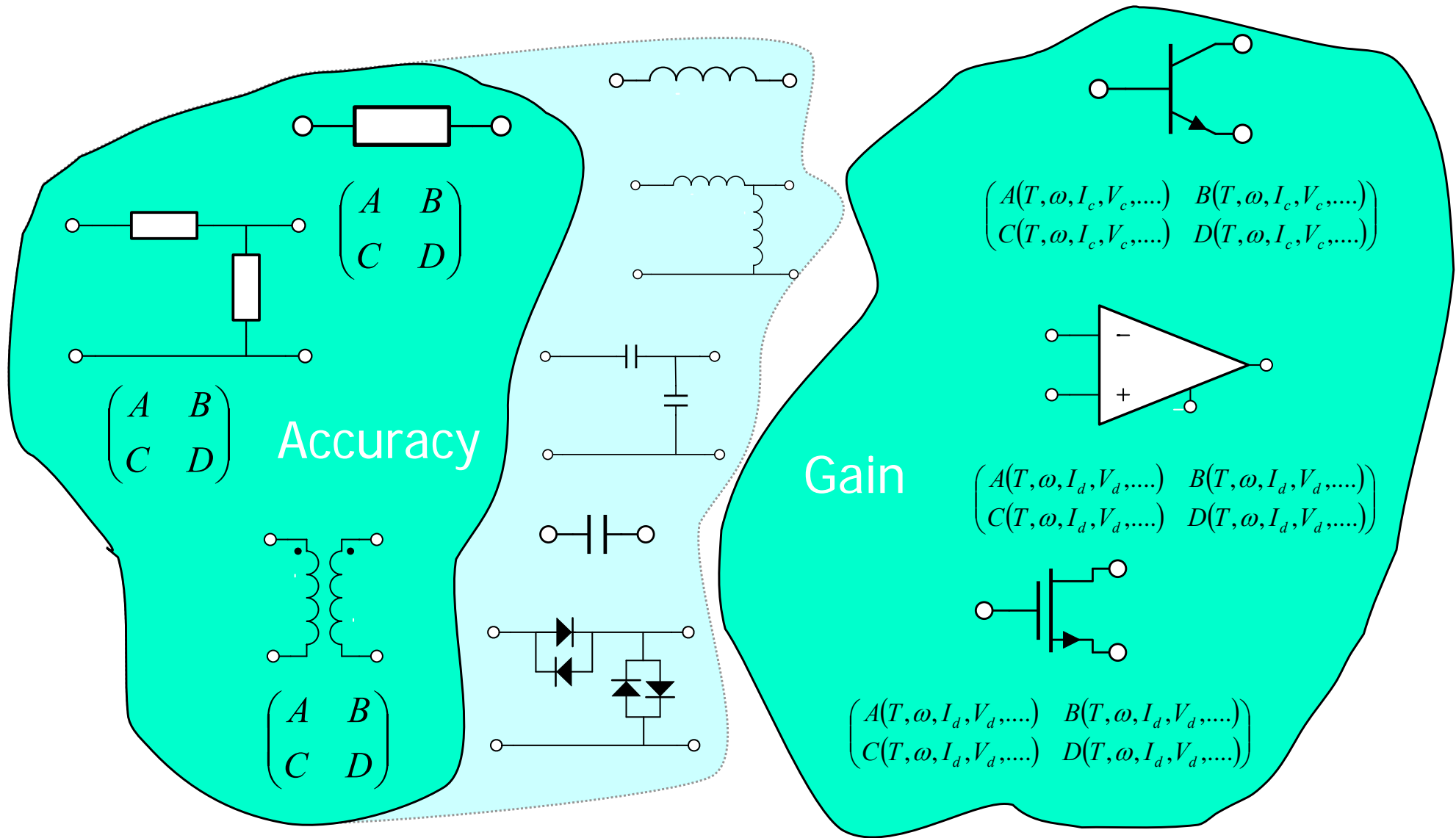
Common classification of available components




Accurate elements

Elements with gain

Exactly according to the definition

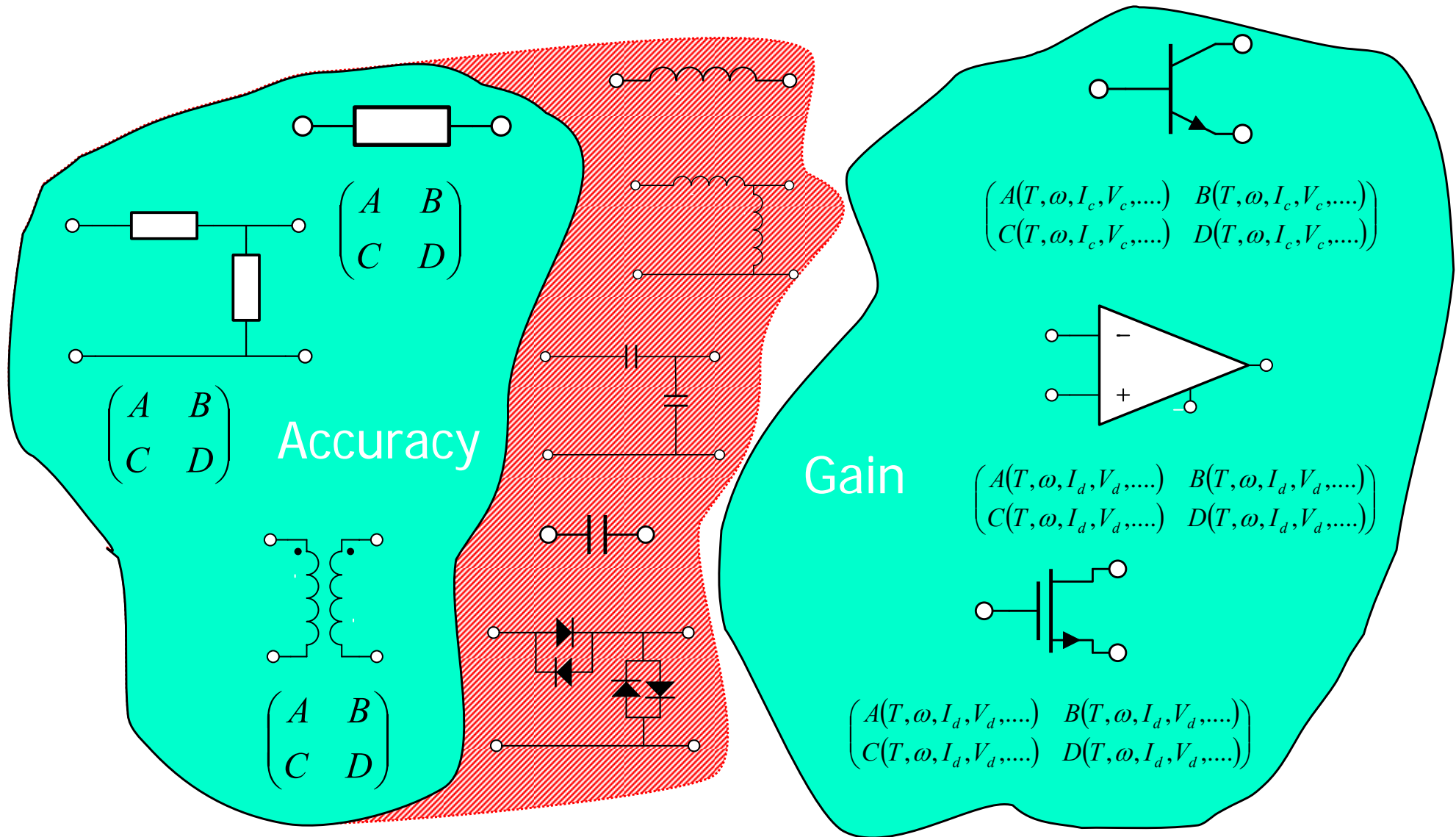

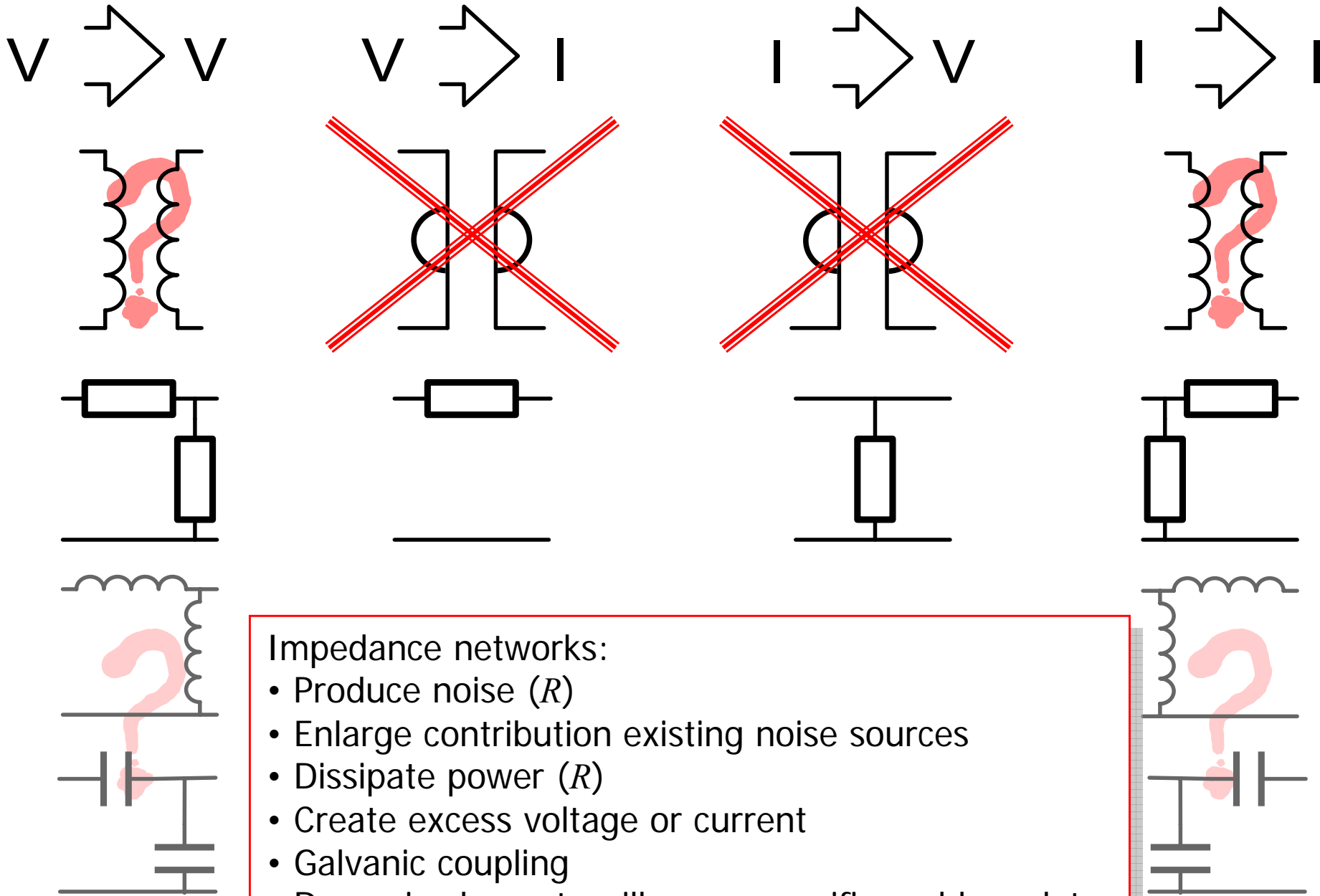
**An amplifier is a non-dynamic circuit.
Why would there be dynamic elements in the feedback network?**



Impedance networks:

- Produce noise (R)
- Enlarge contribution existing noise sources
- Dissipate power (R)
- Create excess voltage or current
- Galvanic coupling
- Dynamic elements will cause specific problems later

Conclusion

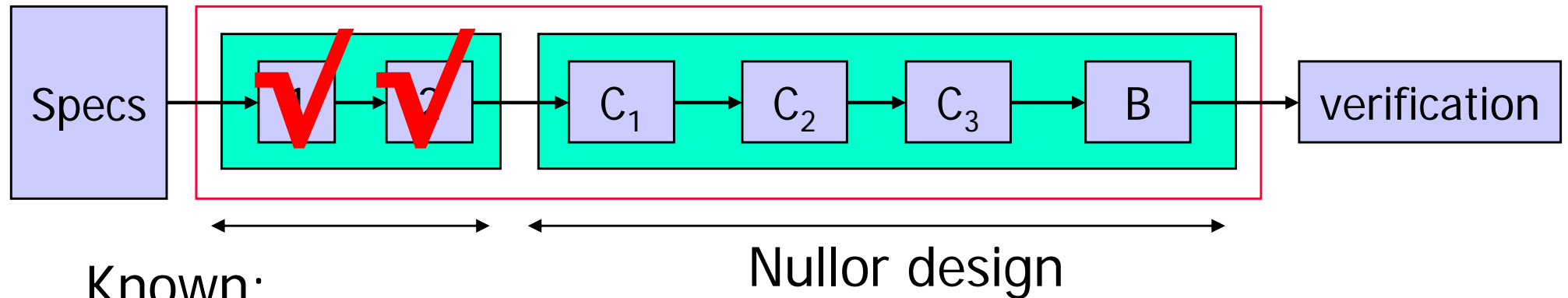

- Topology
- Best nullor implementation
- Voltage and current swing
- Power consumption
- Minimal noise level
- Penalties for “second-best” choices

