 


# Structured Electronic Design

Building the nullor: Frequency behavior





Topology

Best nullor implementation

Voltage and current swing

Power consumption

Noise level : First stage (type, bias parameters)

Clipping level : Last stage (type, bias parameters)

Minimal loopgain necessary to suppress weak distortion


# Bandwidth

All nullor stages large gain

First stage  $\Rightarrow$  noise

Last stage  $\Rightarrow$  clipping

Loopgain reduces weak distortion

 


# What do we want?

An amplifier with the desired bandwidth


An amplifier with a “nice” frequency behavior

A simple bandwidth estimation method

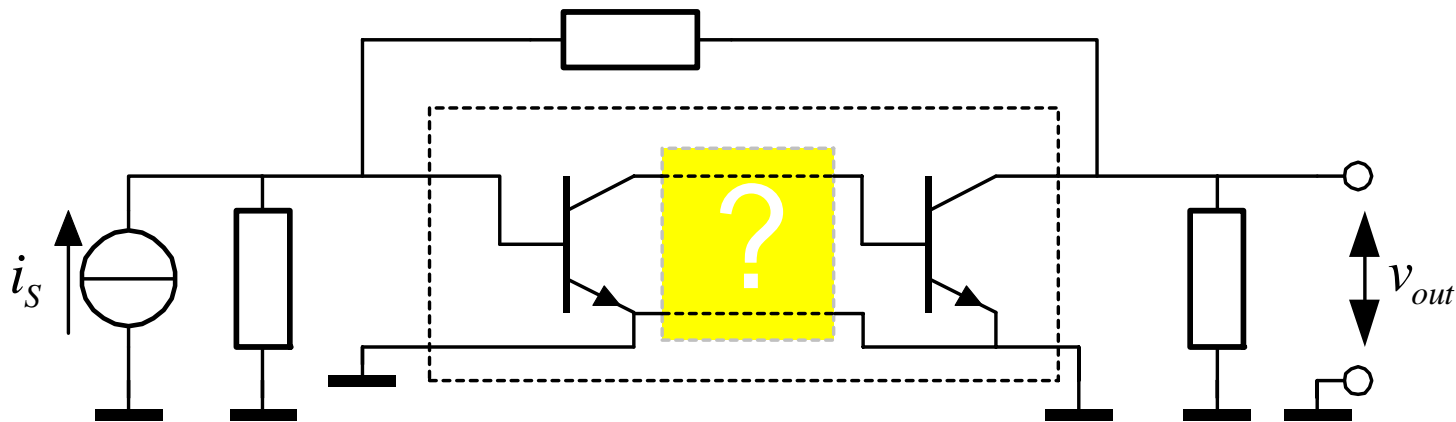


# An amplifier with the desired bandwidth

$$C = B_{inf}^2 \log \frac{S + N}{N}$$

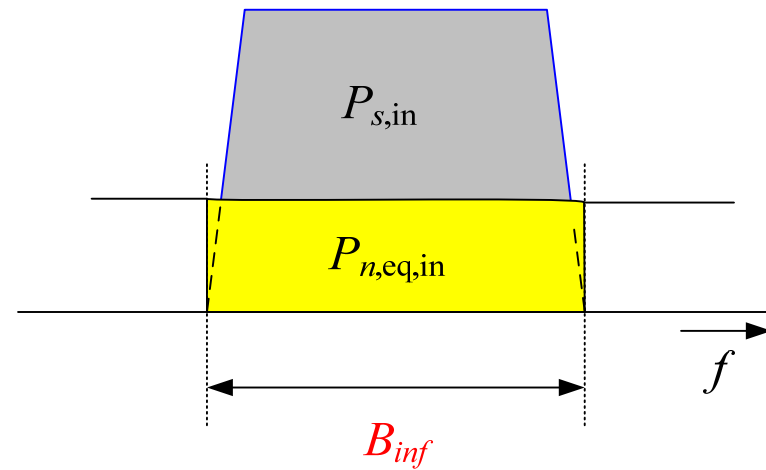


Usually a  
biasing problem

Bandwidth  
optimization

 


# "Nice" frequency behavior

**All-pole** Butterworth characteristic

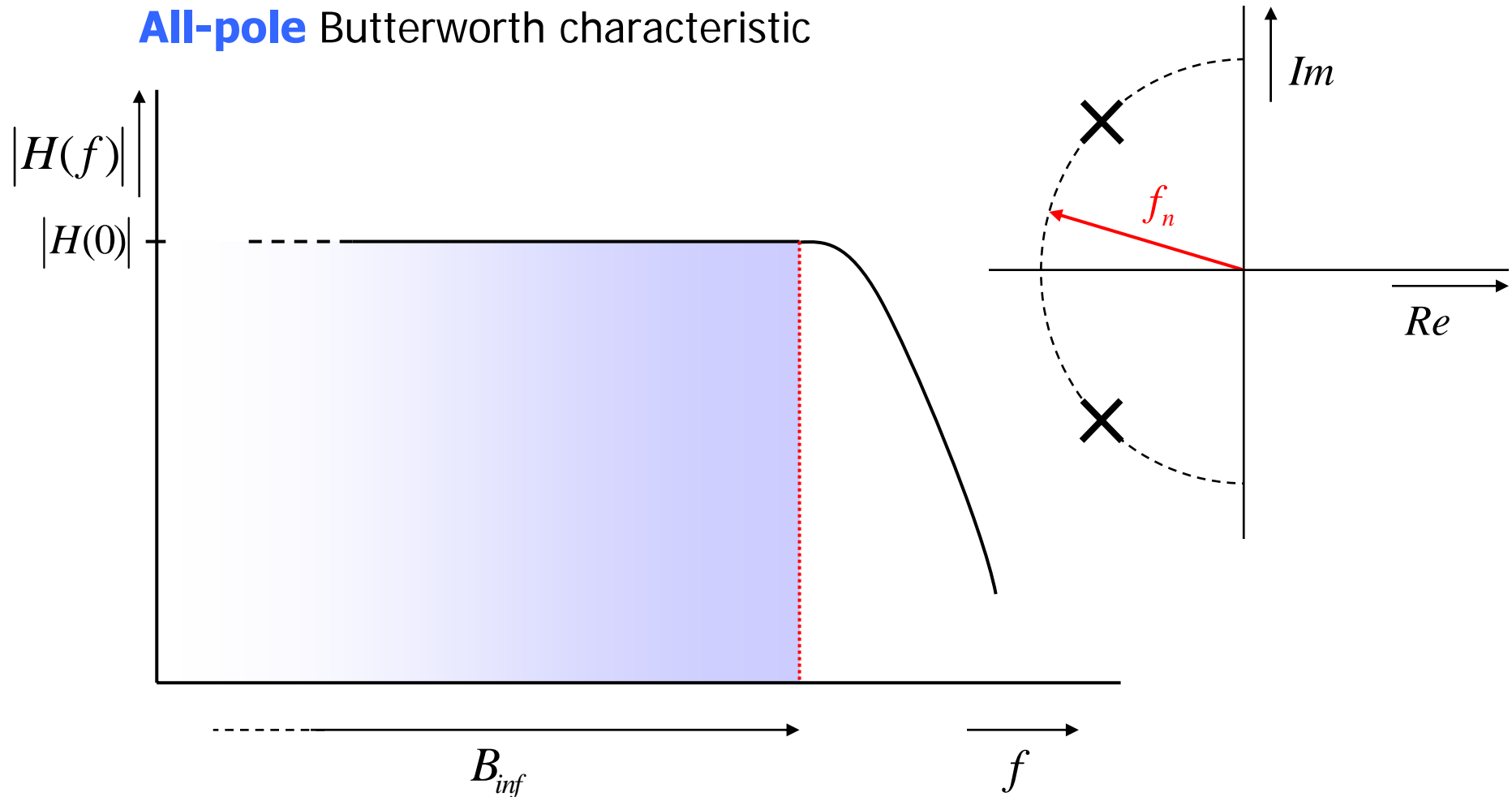

# Butterworth poles

 

$$H(s) = \frac{H(0)}{s^2 - s(p_a + p_b) + p_a p_b}$$


$$CP = s^2 - s(p_a + p_b) + f_n^2$$

Characteristic Polynomial

$$f_n^2 = p_a p_b$$



# Bandwidth estimation

 

What will be the bandwidth in this case?

How many stages are needed?

Can the poles be in Butterworth position?


Which poles?

# Frequency dependent loop gain

$$A_t = A_{t\infty} \frac{-L(s)}{1-L(s)}$$

$$CP = 1 - L(s)$$
 
# Amplifier with a “nice” frequency behavior



$$A_t(s) = A_{t\infty} \frac{-L(s)}{1-L(s)}$$

$$A_t(s) = A_{t\infty} \frac{-L(s)}{1-L(s)}$$

$$L(s) = \frac{L(0)}{\left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right)}$$

$$A_t(s) = A_{t\infty} \frac{-L(0)}{\left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right) - L(0)}$$

$$A_t(s) = A_{t\infty} \frac{-L(0)}{\frac{s^2}{p_1 p_2} - s\left(\frac{1}{p_1} + \frac{1}{p_2}\right) + 1 - L(0)}$$

$$CP(s) = s^2 - s(p_1 + p_2) + [1 - L(0)] p_1 p_2$$

$$CP(s) = s^2 - s(p_a + p_b) + f_n^2$$

# *LP* -product: Bandwidth prediction

$$CP(s) = s^2 - s(p_a + p_b) + f_n^2$$

$$CP(s) = s^2 - s(p_1 + p_2) + [1 - L(0)] p_1 p_2$$

- **If** Butterworth position
- **Then**  $[1 - L(0)] p_1 p_2$  predicts the bandwidth

$$f_n = \sqrt[n]{|[1 - L(0)] \prod_{1}^n p_n|} = \sqrt[n]{LP}$$

# Synthesis rule

Maximum attainable bandwidth :  $B_{\max} = \sqrt[n]{LP}$

- $B_{\max} < B_{spec}$  : Specification **never** reached
- $B_{\max} > B_{spec}$  : **Chance** on success,

**if** the poles can be brought into Butterworth position

Enough  $LP$ -product is **necessary** but **not sufficient**


# Determining the $LP$ -product

$$\left[1 - L(0)\right] p_1 p_2$$

Influence of feed back network?

Influence of source impedance?

Influence of load impedance?

 

Influence of the active part?



# Modeling


A correct model gives a correct prediction




Never confuse models with "the truth"




# A frequency dependent transistor model

 



# Good enough?

 



# The influence of the load impedance

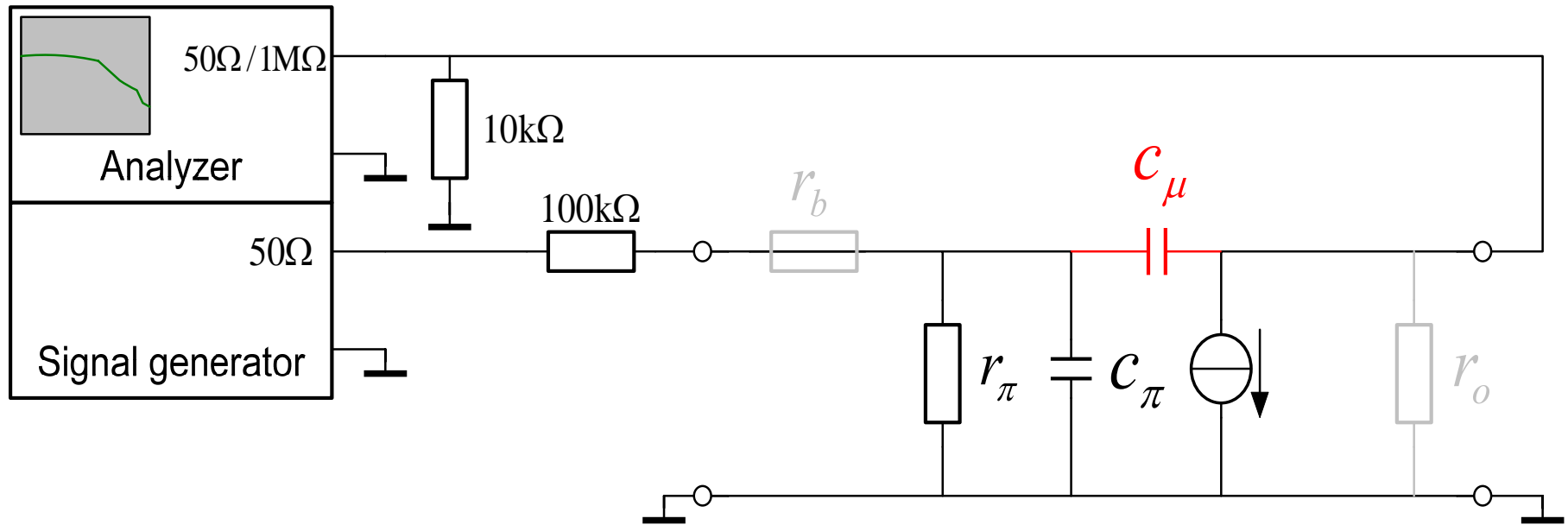



# Looks good...

  


# The difference is in the zero

  

# What if short circuit not good enough?

  


# “Miller effect”

 


$$C_{\mu,eff} = C_\mu (1 + g_m R_{next})$$

$$v_{out} = -v_{be} g_m R_{next}$$

# Check with an ideal short circuit

 

 If an ideal current follower solves the problem,





Insert a CB-stage (cascode).





# Ideal current follower does not help

  

The zero is the cause

- Increase  $V_{bc}$
- Replace transistor
- Elaborate compensation



# Conclusions

- Use simple model, with assumption
  1. Current driven
  2. Output short circuited

Make this true (later) !


- 2 potential problems
  1. RHP zero
  2. Influence of  $C_{\mu}$  and  $r_o$  on the pole positions

Distinguish via ideal current follower

# Contribution to the $LP$ -product

$$CP(s) = s^2 - s(p_1 + p_2) + [1 - L(0)] p_1 p_2$$


$$CP(s) = s^2 - s(p_a + p_b) + f_n^2$$

 

$$L: g_m r_\pi = \beta_F = \frac{1}{D}$$

$$P: \frac{1}{2\pi r_\pi C_\pi}$$
 
$$LP \approx \frac{g_m}{2\pi C_\pi} = f_T$$




Contribution to  $LP$  -product:  $f_{T1}f_{T2}$



$$f_n = \sqrt{|[1 - L(0)] p_1 p_2|}$$
 
$$LP = \frac{C_{\pi 1}}{C_s + C_{\pi 1}} f_{T1} f_{T2} \frac{R_L}{R_s + R_L}$$




# First step: Realize sufficient *LP*-product

Realize :  $B_{\max} = \sqrt[n]{LP} > B_{\text{specified}}$


1. By adding stages
2. By changing the bias of an existing stage

# Additional stages

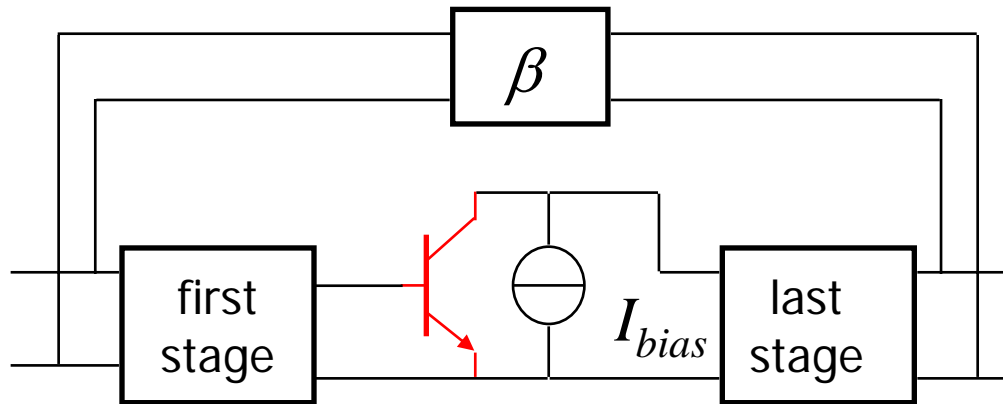


$$I_{bias} = I_{opt, fT}$$

 - A CE/CS stage contributes  $f_T$  to the  $LP$  product
- Maximum  $f_T$  for minimum current



$$LP \approx \frac{g_m}{2\pi C_\pi} = f_T$$
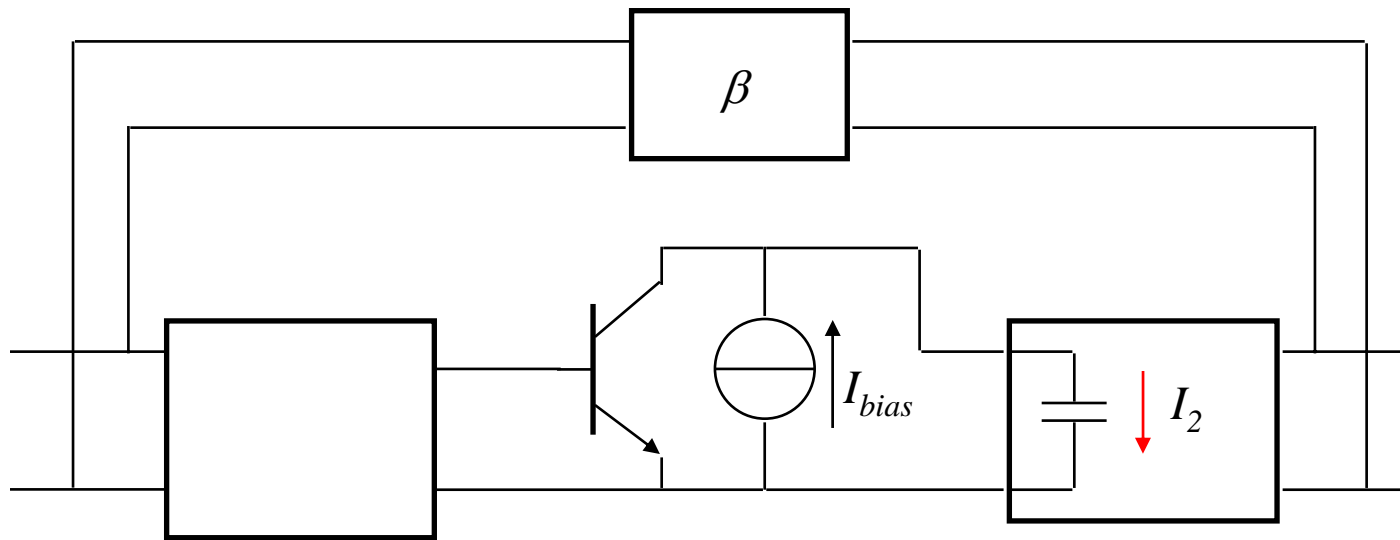
# Maximum $f_T$ for minimum current, AND....




$$I_{bias} = I_{opt, fT}$$

$$I_{bias} > I_2(f_{max})$$



# Changing the bias of an existing stage

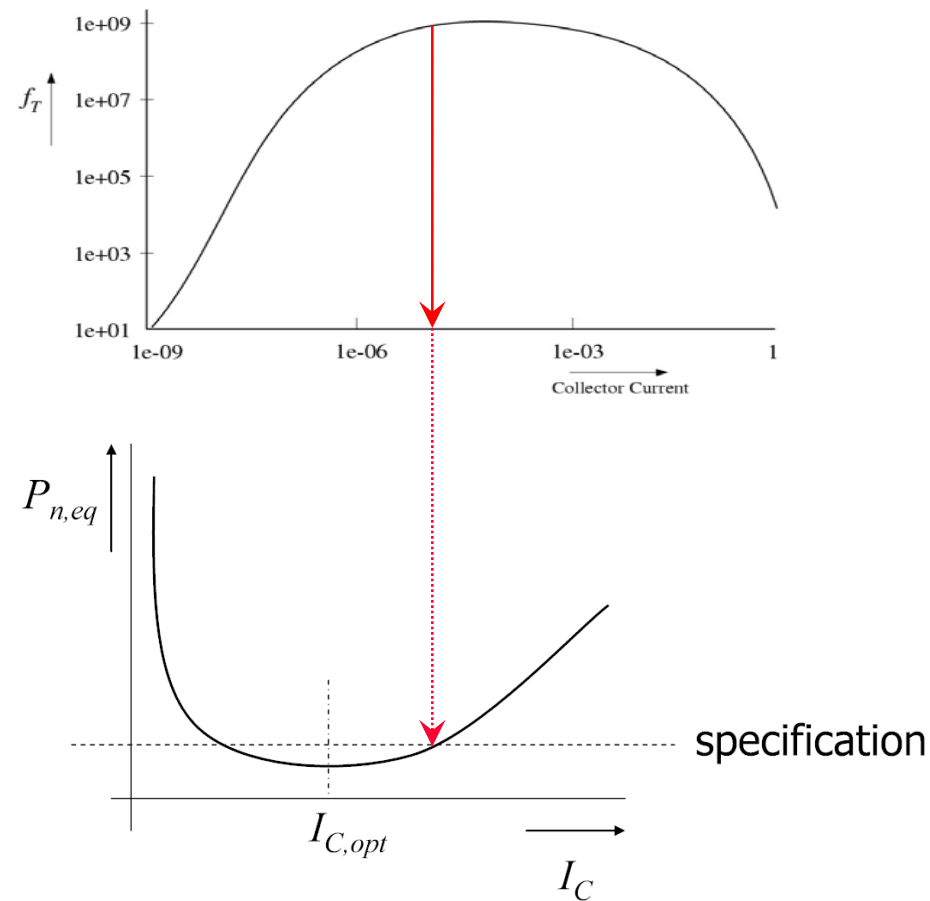

$$B_{inf} \left( 4kTR_s + 4kTr_b + \frac{2qV_T^2}{I_c} + |R_s + r_b|^2 D2qI_c \right)$$

# Making a good prediction


- Must every pole be taken into account?
  - Dominant poles
- What is  $L(0)$  exactly?
  - “DC” loop gain

Our definition:

A dominant pole is a pole that can be brought into Butterworth position.
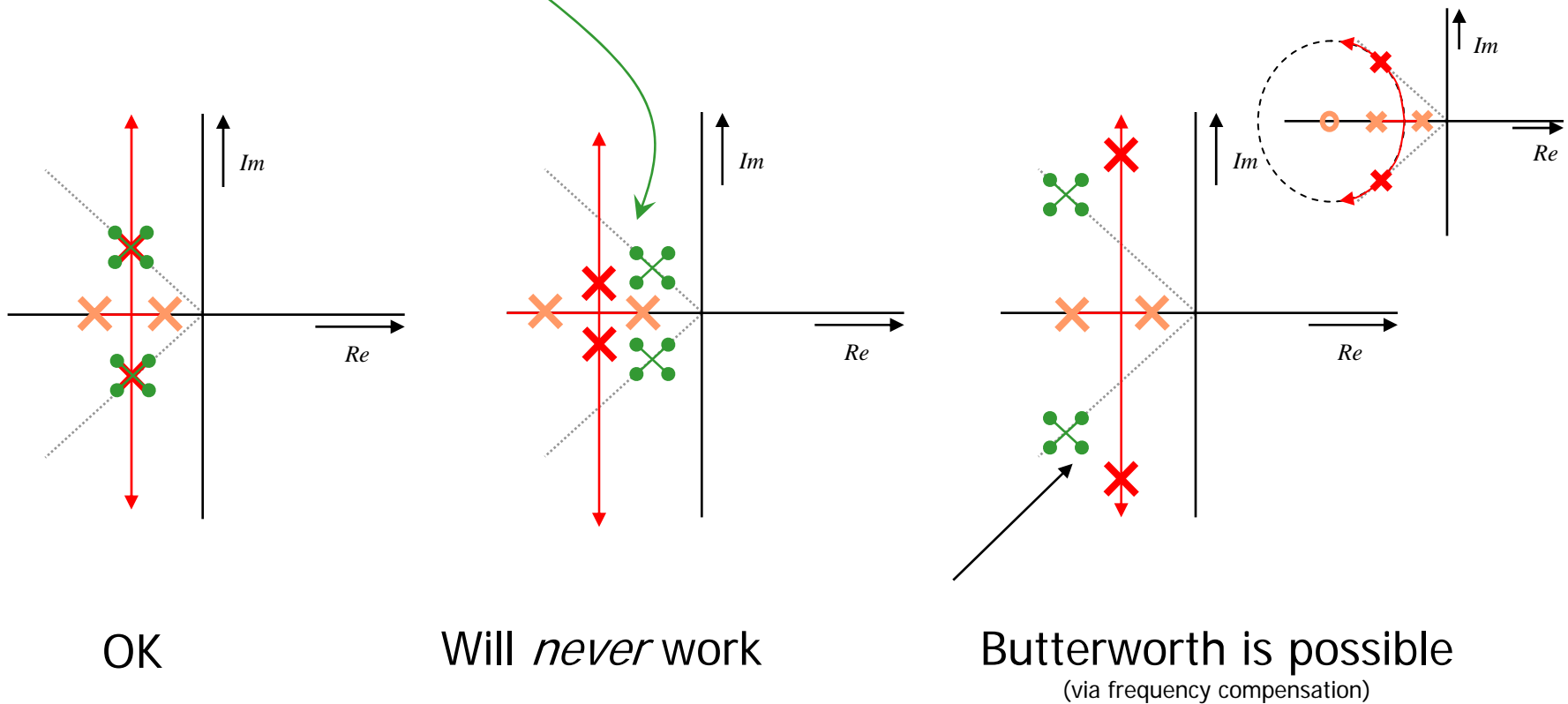
# Dominant poles

- If Butterworth position
- Then  $[1-L(0)] p_1 p_2$  predicts the bandwidth  $CP(s) = s^2 - s(p_a + p_b) + f_n^2$




# Dominant poles

$$\sum_{i=1}^n p_{i,loop} \geq \sum_{i=1}^n p_{i,system}$$


 
## Procedure:

- Determine LP-product
- Sum of loop poles
- Sum of system poles
- Compare
- Reduce order?




# "DC" loop gain

$$L(0) = 0$$

 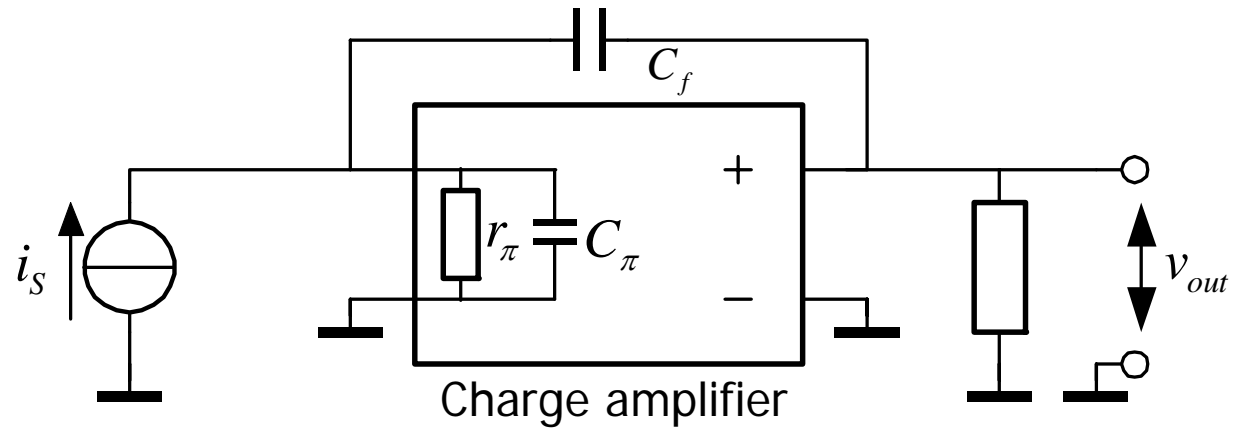


# "DC" loop gain

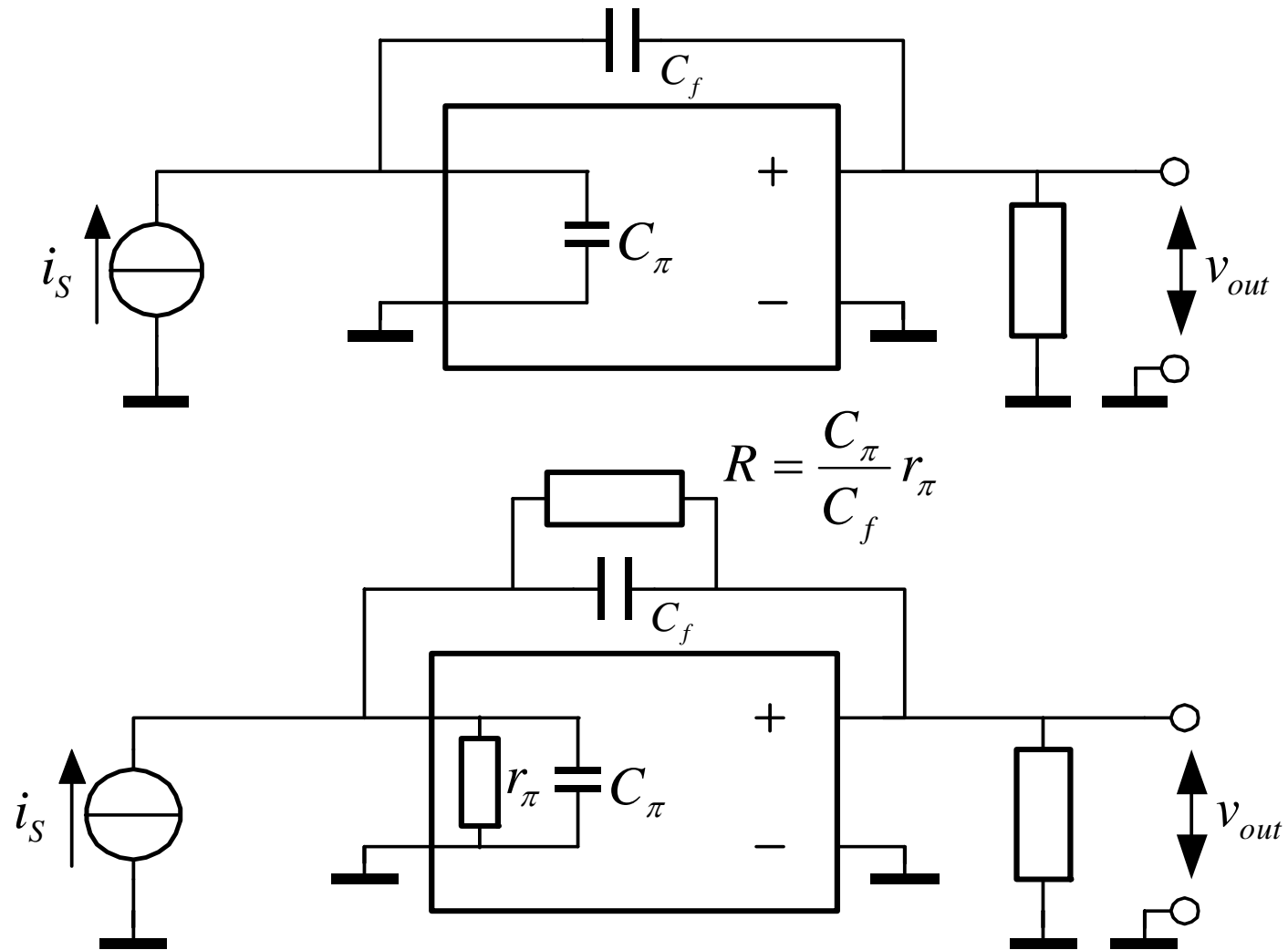

# Conclusions

- $LP$  product **predicts** maximum attainable bandwidth
- Use **dominant** poles (and simple models)
- Pole and zero **positions** are still undefined
  
- When the  $LP$  product is **too low**, the design will **never** reach the required bandwidth
  
- A transistor contributes  $f_T$  to the  $LP$  product
- General  $LP$  product:  $LP = \beta_i \beta_o \beta_T f_{T1} f_{T2} f_{T3}$

# Frequency compensation

 


- First use the **simple** model
  - No  $r_o$ ,  $C_\mu$  and  $r_o$
- Refine models after successful compensation
- *LP* product gives maximum bandwidth


$$CP = s^n + a_{n-1}s^{n-1} + a_{n-2}s^{n-2} + \dots + LP$$




# Frequency compensation methods

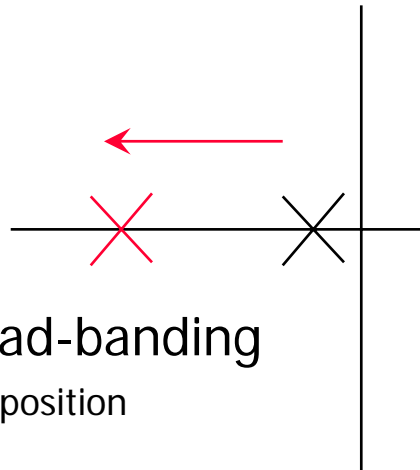

 
Resistive broad-banding  
Change loop pole position



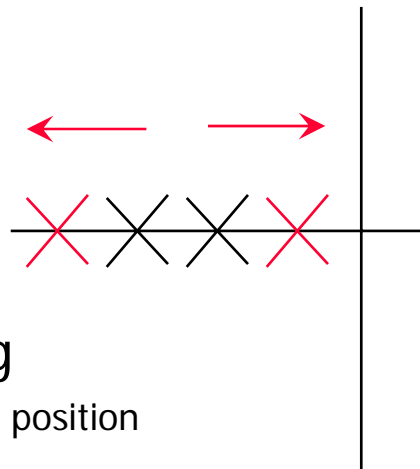Pole-zero cancellation  
Change loop pole position



 Pole splitting  
Change loop pole position



Phantom zero  
Change root locus



# Phantom zero

$$A_t = A_{t\infty} \frac{-L(s)}{1-L(s)} \quad A_{t\infty}(s) = \frac{1}{\beta \left( \frac{s}{n_{ph}} + 1 \right)}$$


Make a zero  $n_{ph}$  in the feedback network  $L(s)_{new} = L(s)_{old} \left( \frac{s}{n_{ph}} + 1 \right)$

$$A_t = A_{t\infty} \frac{-L(s)_{old}}{1-L(s)_{old} \left( \frac{s}{n_{ph}} + 1 \right)}$$


Zero appears in the loop  
 Zero does not appear in the transfer  
 Pole not dominant (should not be)
 
# Phantom zero

- In feedback network
- *Increases* the loop gain for high frequencies
- Extra pole not dominant


 
# Increase loop gain for high frequencies




Extra's:

- Reduces distortion at high frequencies
- Sometimes possible at input or output  
(when source or load impedance have influence ☹)



# Demonstration

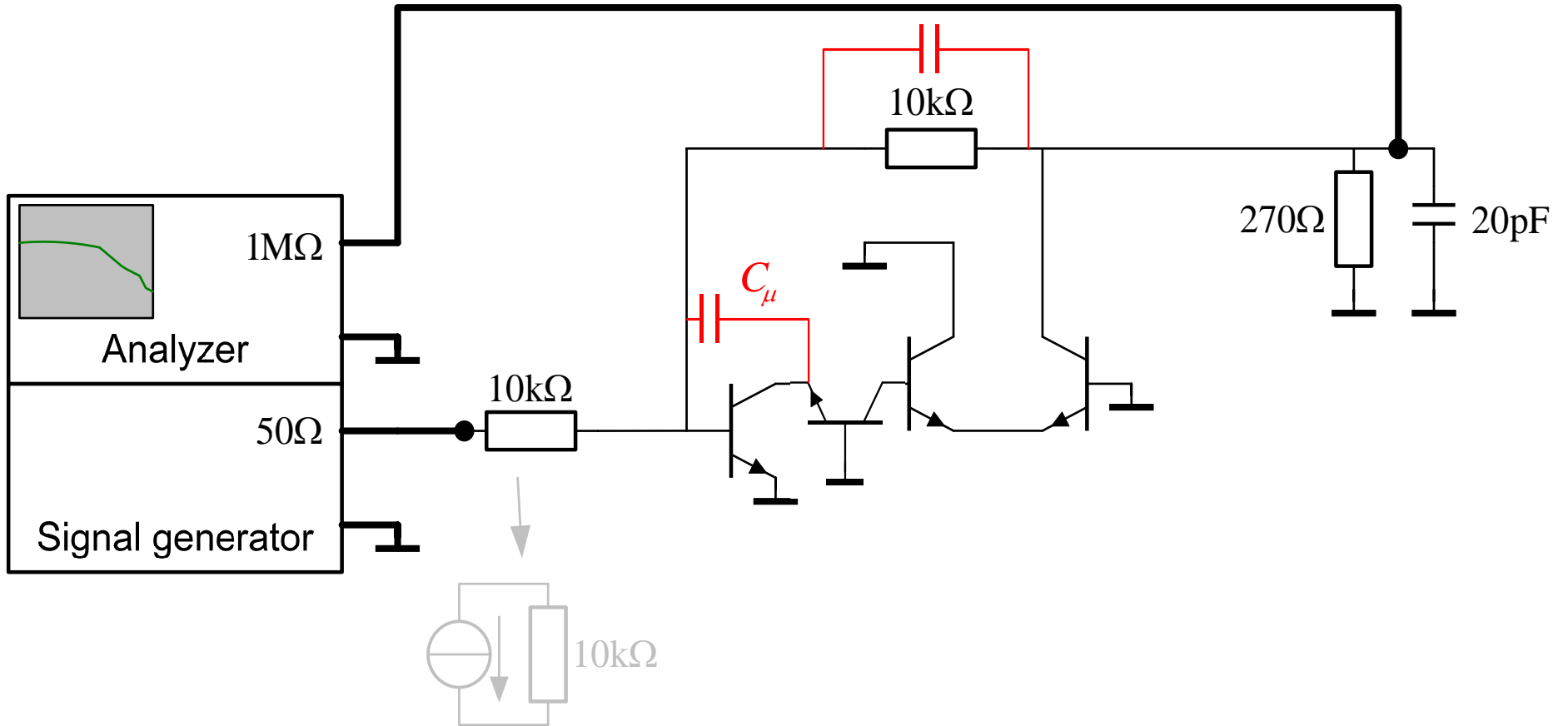

## The other methods

$$A_t = A_{t\infty} \frac{-L(s)}{1 - L(s)}$$

$$A_{t\infty} = \frac{1}{\beta}$$



$$L(s) = A(s)\beta$$

- Pole splitting
- Pole zero cancellation
- Resistive broad-banding

Change frequency behavior of active circuit  
(with a passive component)






# Pole splitting

 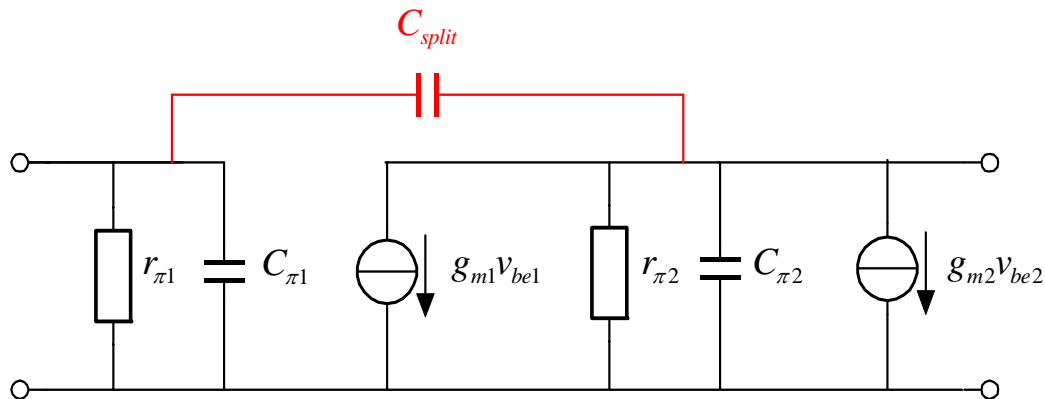

More *local* loopgain for high frequencies

- Input impedance goes down
  - higher input capacitance (miller)
  - input pole goes down
- Output impedance goes down
  - output pole goes up

# Pole splitting

  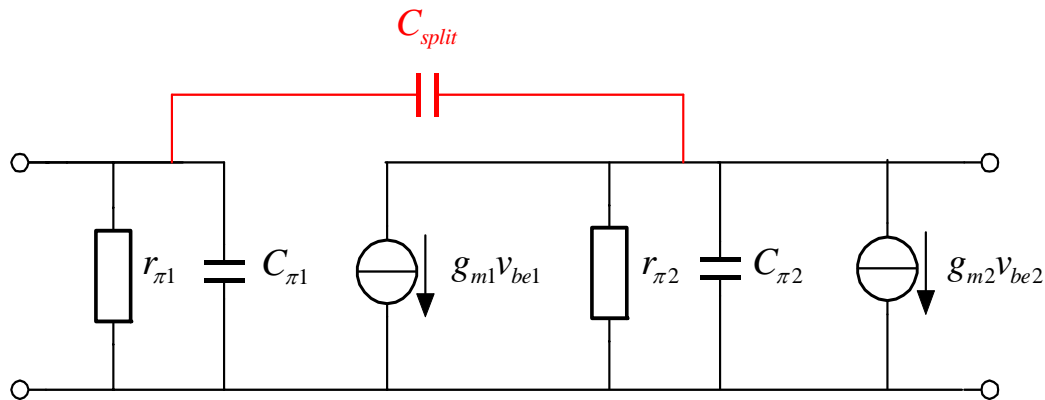


Less overall loopgain:

- Lower  $LP$  -product
- More distortion
- Introduces a zero
- Reduced accuracy



# Pole-zero cancellation

 


Loopgain is reduced for high frequencies

- More distortion, etc.

Does not introduce a zero

# Resistive broad-banding

 



Overall loopgain is reduced even at low frequencies

- Much more distortion

Does not introduce a zero

# After successful frequency compensation

Add  $c_\mu$  and  $r_o$  one by one

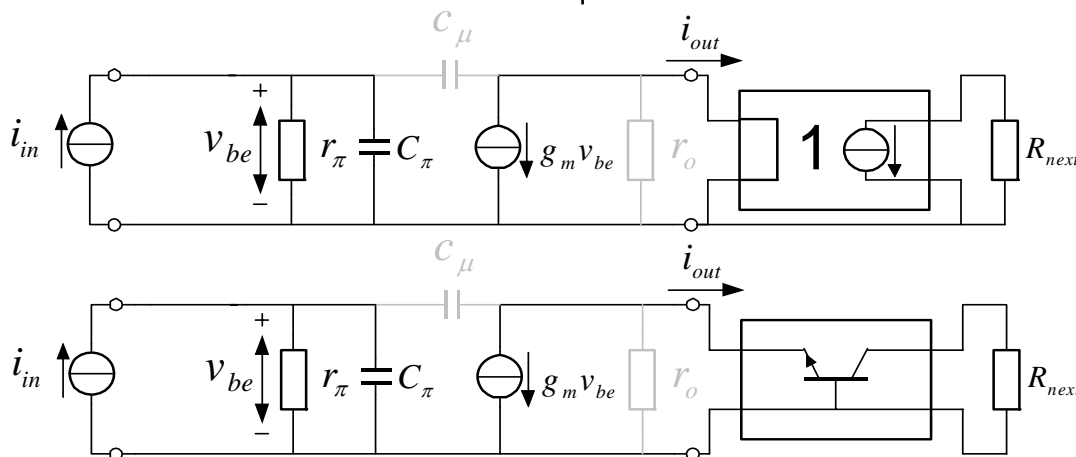 

- Insert CB-stage (cascode)
- Increase  $V_{bc}$
- Replace transistor
- Elaborate compensation


# Conclusions

- Start with **simple** model
- Create sufficient  $LP$ -product with dominant poles
- Do a frequency compensation  
Preferably with a phantom zero
- Insert  $r_o$  and  $C_\mu$  one by one
- Insert ideal current follower if necessary
- Reduce  $C_\mu$  if necessary (deal with zero)
- Replace ideal current followers by CB-stages

Compensation results remains valid


 
# Next time: batteries and real transistors



Biassing