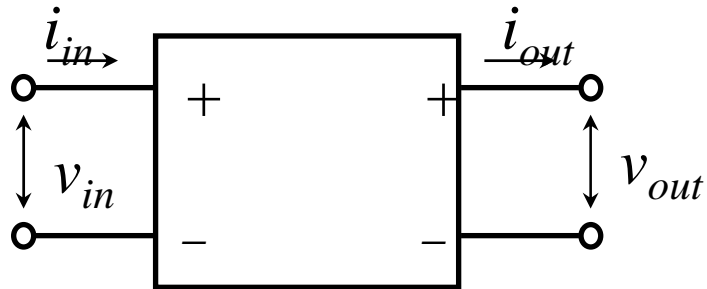


Structured Electronic Design




The two-port and its chain matrix



$$\begin{pmatrix} v_{in} \\ i_{in} \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} v_{out} \\ i_{out} \end{pmatrix}$$

$$A = \left. \frac{v_{in}}{v_{out}} \right|_{i_{out}=0} \quad B = \left. \frac{v_{in}}{i_{out}} \right|_{v_{out}=0} \quad C = \left. \frac{i_{in}}{v_{out}} \right|_{i_{out}=0} \quad D = \left. \frac{i_{in}}{i_{out}} \right|_{v_{out}=0}$$


Nullor

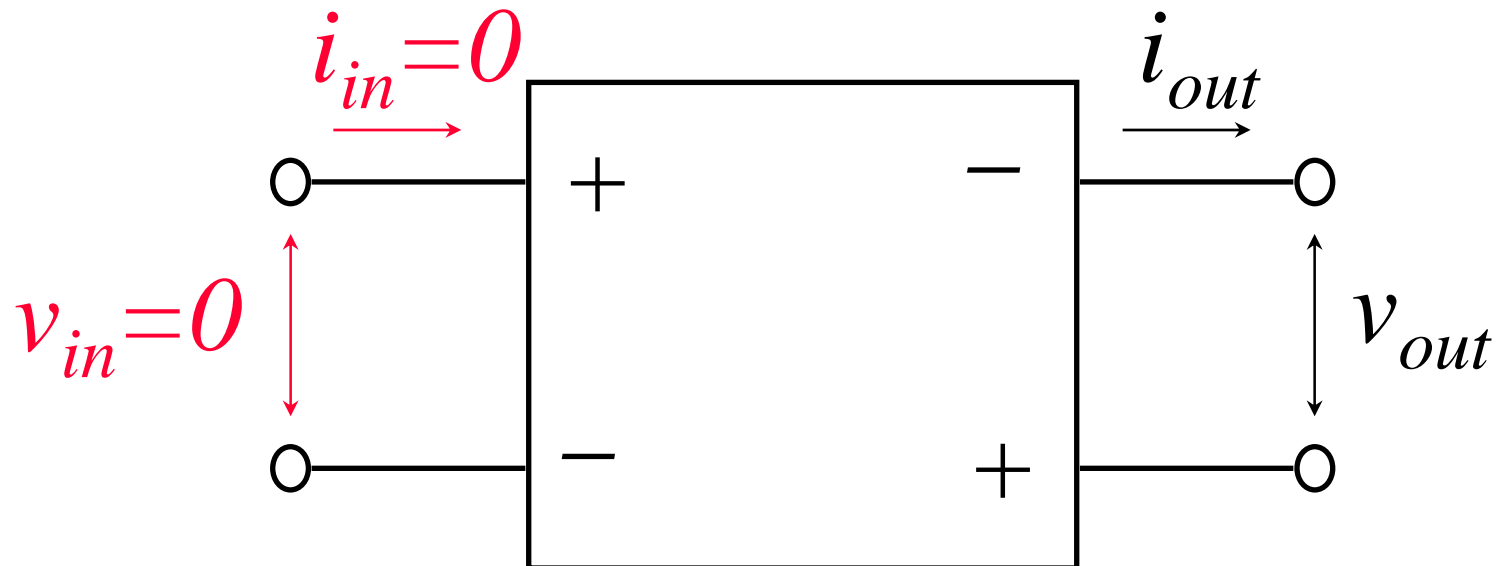


Input current and input voltage of the nullor are made zero via the output signals of the nullor

$$\begin{pmatrix} v_{in} \\ i_{in} \end{pmatrix} = \begin{pmatrix} 0 & 0 \\ 0 & 0 \end{pmatrix} \begin{pmatrix} v_{out} \\ i_{out} \end{pmatrix}$$





Inside the Nullor

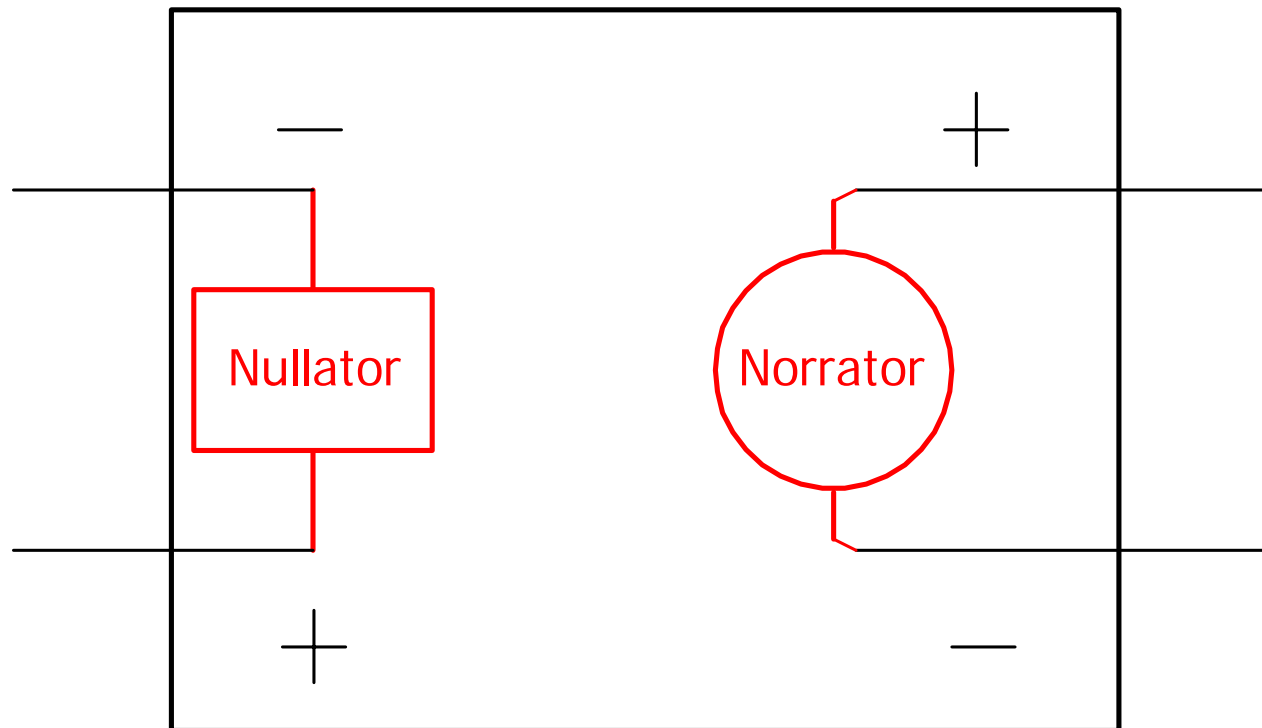


Nullator? Norrator?

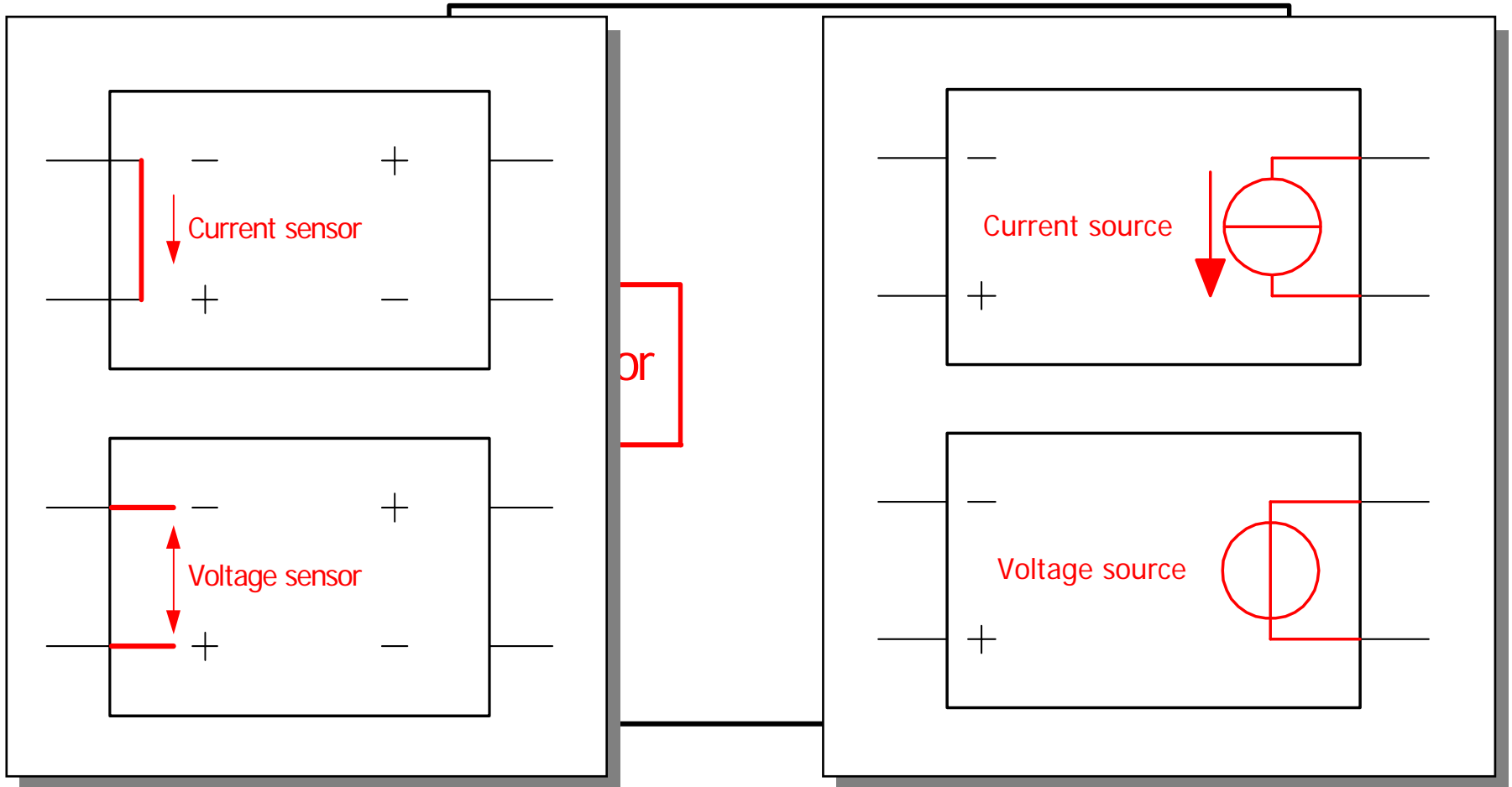


practical nullor implementations

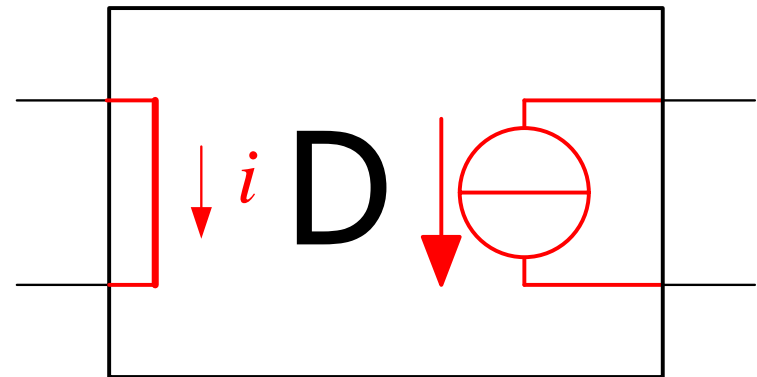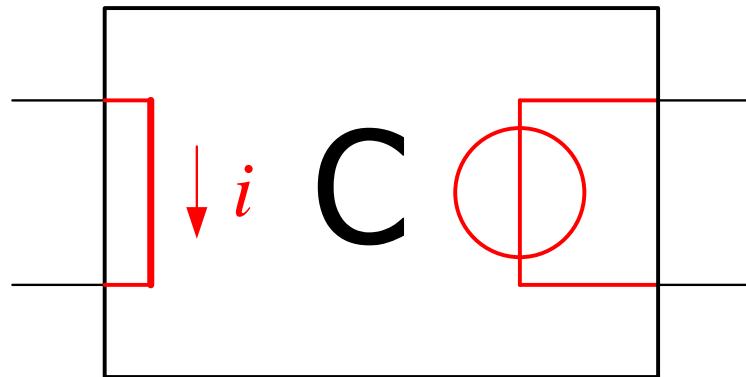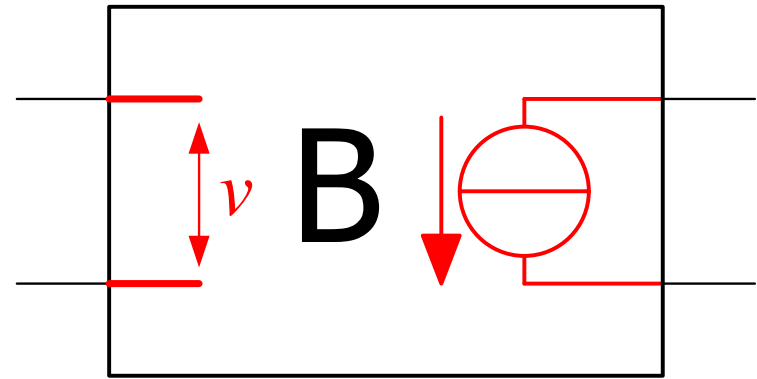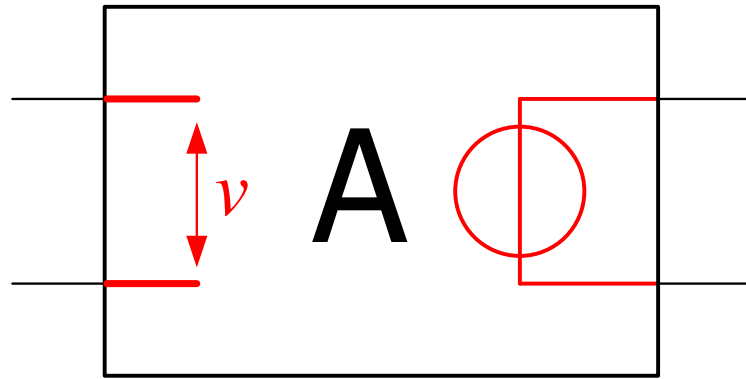


Transistor implementations ?

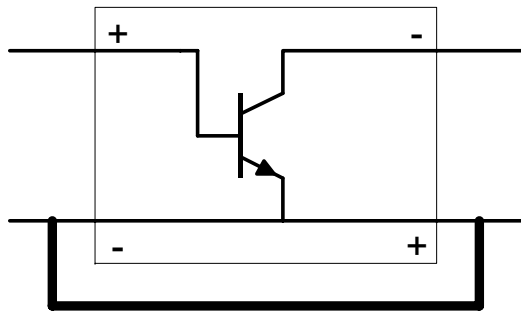


CE-stage

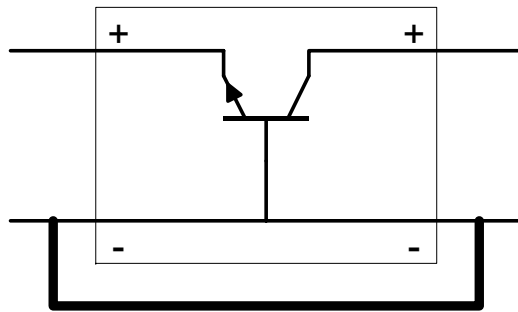


CB-stage

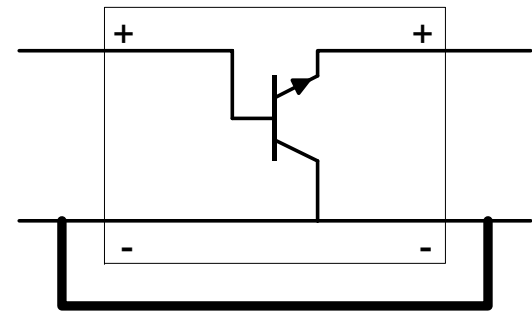


CC-stage

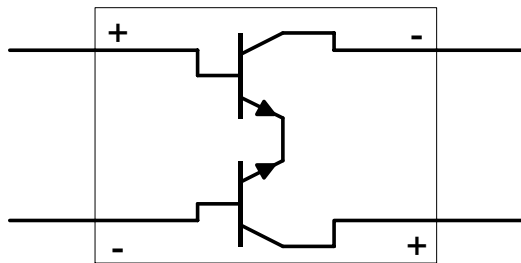

Differential CE-stage





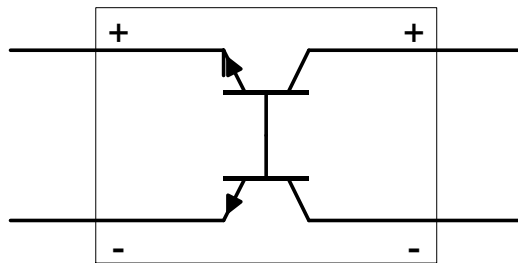


Differential CB-stage

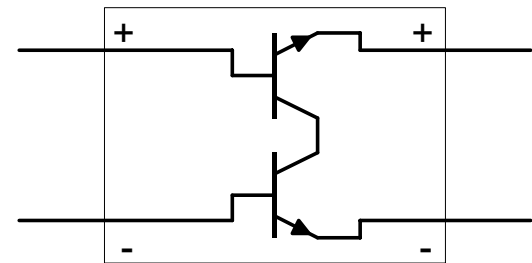


Differential CC-stage

Choose

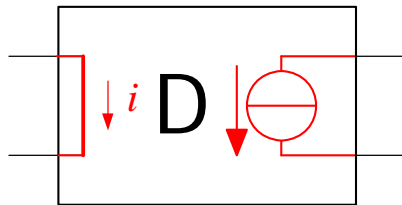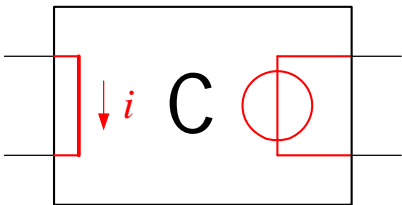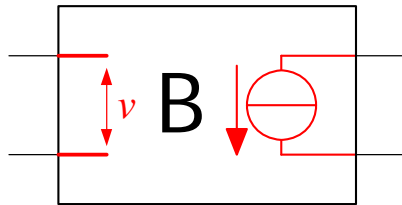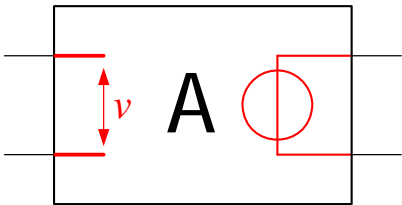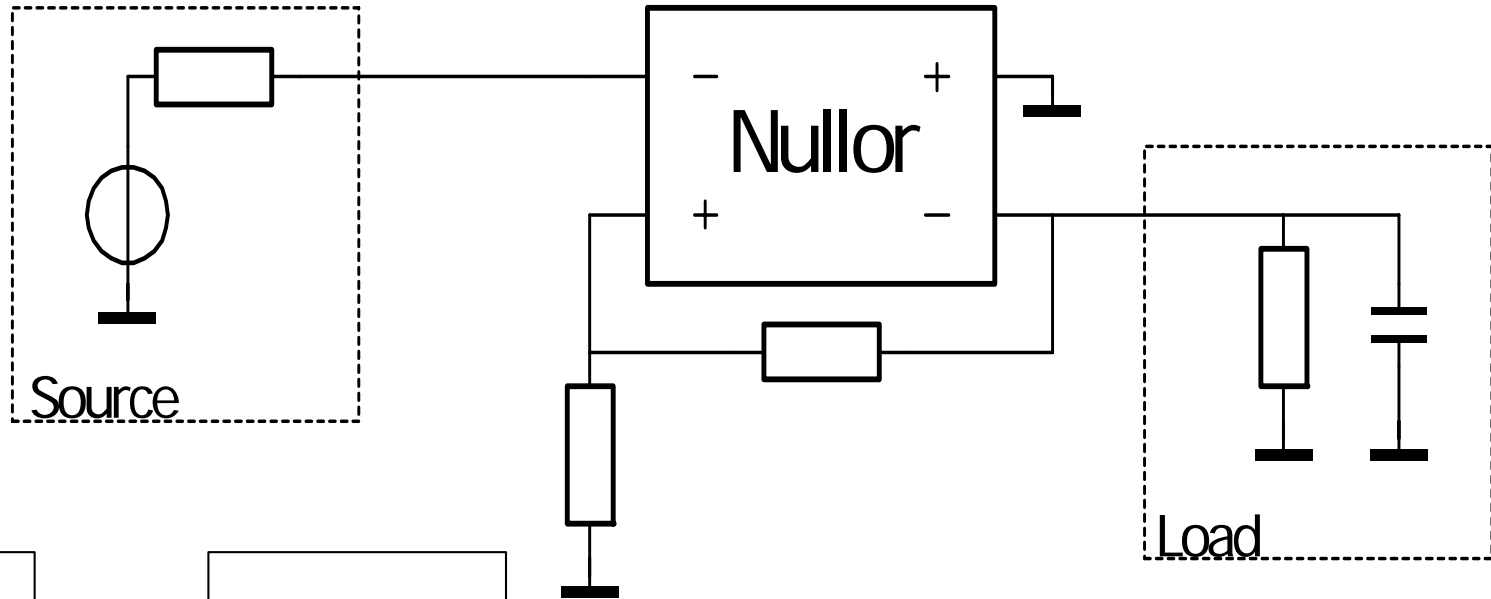

"Expert" versus "logic"

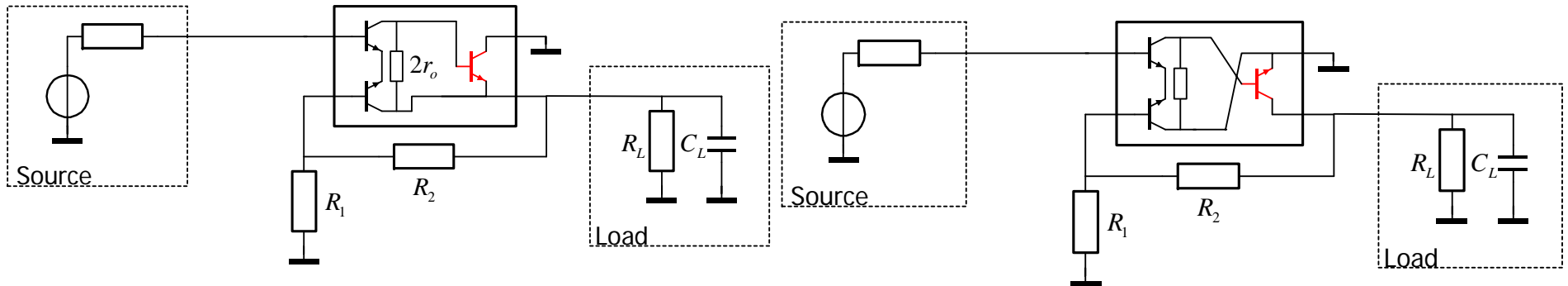

$$L = \frac{1}{A_{CE}A_{CC}} \left(\frac{R_1}{R_1 + R_2} \right) \frac{\left(\frac{R_L}{1 + j\omega R_L C_L} (R_1 + R_2) \right)}{\left(\frac{R_L}{1 + j\omega R_L C_L} + R_1 + R_2 \right)}$$


$$2r_o D_{CC} + \left(\frac{R_L}{1 + j\omega R_L C_L} (R_1 + R_2) \right)$$

$$L = \frac{1}{2B_{CE}} \frac{1}{D_{CC}} R_1 \left(\frac{\frac{R_L}{1 + j\omega R_L C_L}}{\frac{R_L}{1 + j\omega R_L C_L} + R_1 + R_2} \right)$$


- ☹ miller effect first stage
- ☹ distortion and clipping first stage
- ☺ Loopgain not(less) load dependent

- ☺ no miller effect
- ☺ less distortion
- ☹ Load dependent loopgain

Direct transfer A_{t0}

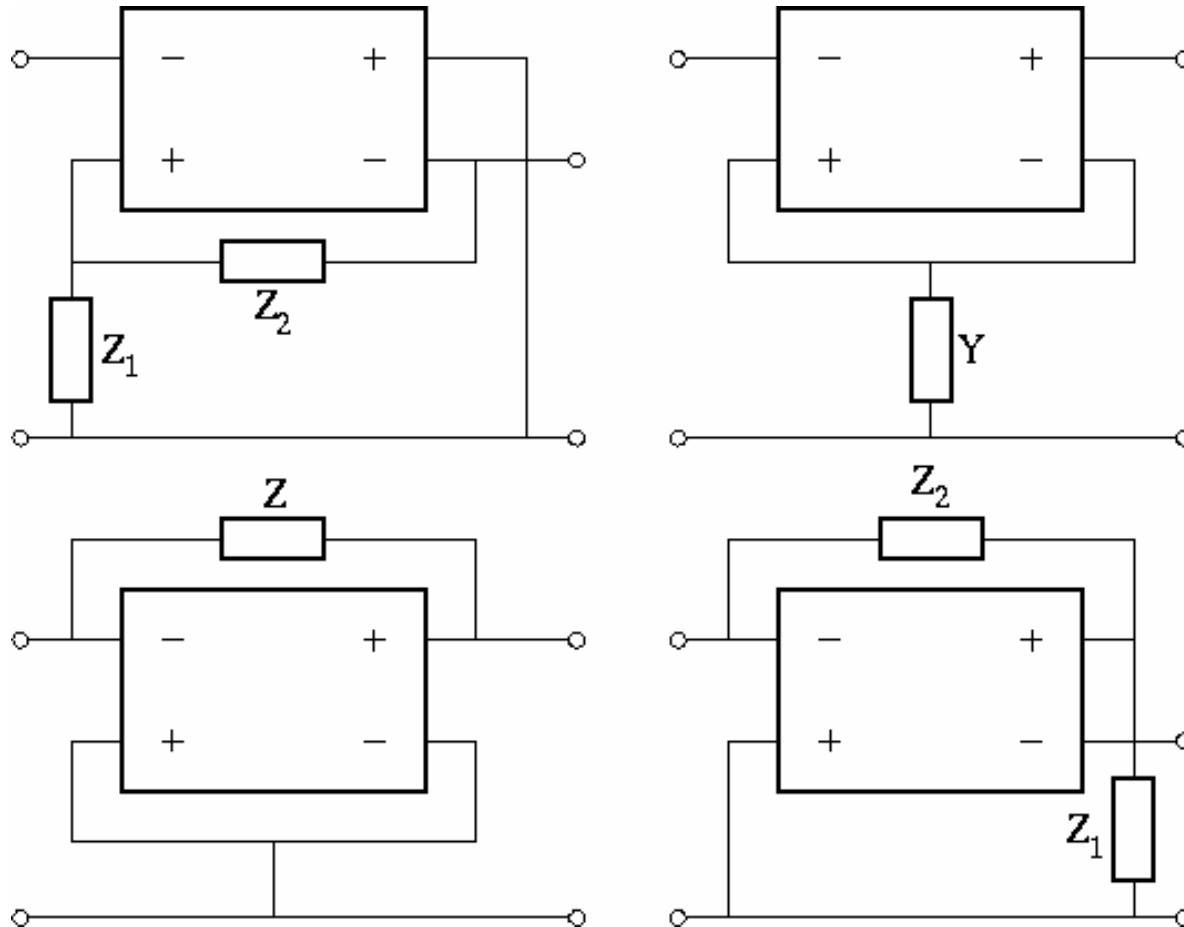

Direct transfer A_{t0}

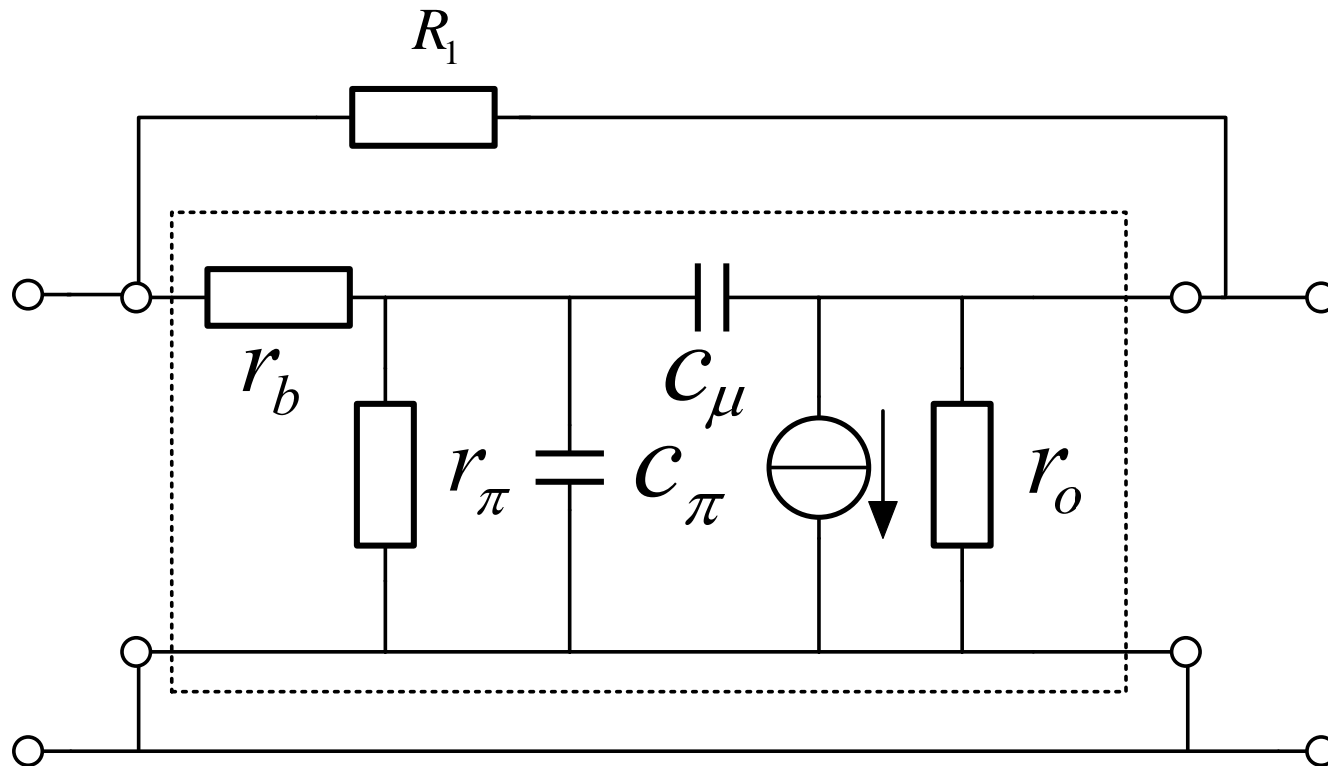

Exercises

Today:

- **You work**
- We walk around and help you when you are desperate
- Work on the exercises in the book, chapter 1
- Handouts exercises 1
- Take your time, there are still more exercise sessions to come
- When you have a result, **check/discuss it with others**, then you will find out if your answer is correct.
- The discussion will help the to understand the “**WHY**” part of the design.
- There will some solutions available at the end of this course
(but probably you do not need them anymore at that time ☺)