

# *Electronic Instrumentation*

Lecturer: Kofi Makinwa

K.A.A.Makinwa@TUDelft.NL

015-27 86466  
Room. HB13.270 EWI building

Also involved:  
Saleh Heidary  
(S.H.Shalmany@TUDelft.NL)

- Synonyms: coherent detection, synchronous demodulation, lock-in amplification, chopping??
- These are all modulation techniques that are used to improve the low frequency performance of measurement systems
- When square-wave modulation is employed, the technique is referred to as chopping

## Theory

Why and when to use?  
Basic principle (time domain)  
Amplitude and phase measurement  
Signal-to-Noise Ratio (frequency domain)  
Switching detector (choppers)

## Summary

### Application example (DEMO 1)

Strain gauges  
Wheatstone bridge  
Coherent detector: design considerations


## When to use it?

- When measuring low-bandwidth or quasi-static signals in the presence of high noise or disturbance levels.
- If a high dynamic range is required

Therefore it is often used to readout sensors e.g.

- (MEMS) Accelerometers (fF capacitance changes)
- Optical (infrared) detectors (fA's of current)
- Magnetic sensors ( mV's )
- Strain gauges ( mV's )

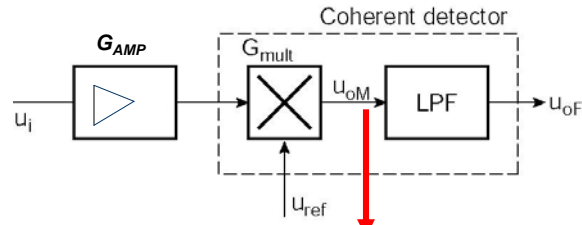**A coherent detector behaves like a bandpass filter**




$$u_{oM} = G_{Amp} G_{mult} [\hat{u}_i \sin(\omega_i t) \hat{u}_r \sin(\omega_r t)]$$

$$u_{oM} = G_{Amp} G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} [\cos((\omega_r - \omega_i)t) - \cos((\omega_r + \omega_i)t)]$$

Now if:  $\omega_r = \omega_i$  (Coherent signals !) then:

$$u_{oM} = G_{Amp} G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} [1 - \cos(2\omega_i t)]$$

DC

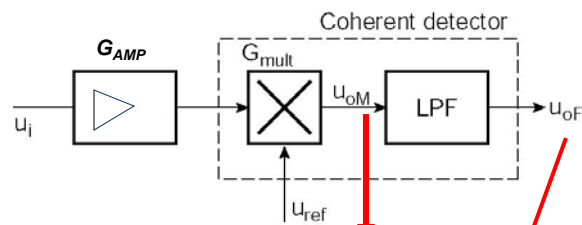

$$u_{oM} = G_{Amp} G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} [1 - \cos(2\omega_i t)]$$

$\omega_r = \omega_i$

The low-pass filter removes the second harmonic:

$$u_{oF} = G_{LPF} G_{Amp} G_{mult} \frac{\hat{u}_r \hat{u}_i}{2}$$


This coherent detector detects the **amplitude** of the input signal.

Note that in this case  $U_i$  and  $U_{ref}$  are in-phase (Synchronous detection).

What if they are not in-phase ????
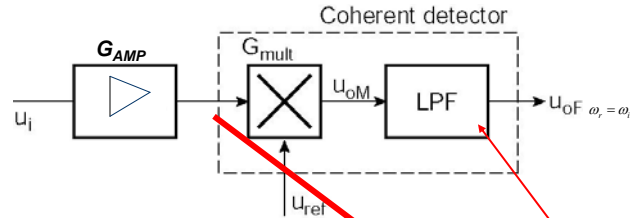
## Phase detection

Suppose  $U_i$  and  $U_{ref}$  have a phase difference:



$$u_{oM} = G_{AMP} G_{mult} [\hat{u}_i \sin(\omega_i t + \varphi) \hat{u}_r \sin(\omega_r t)]$$


$$u_{oM} = G_{AMP} G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} [\cos((\omega_r - \omega_i)t + \varphi) - \cos((\omega_r + \omega_i)t + \varphi)]$$

$$u_{oF} = G_{LPF} G_{AMP} G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} [\cos(\varphi)] = 0$$

This coherent detector is also **phase sensitive**.
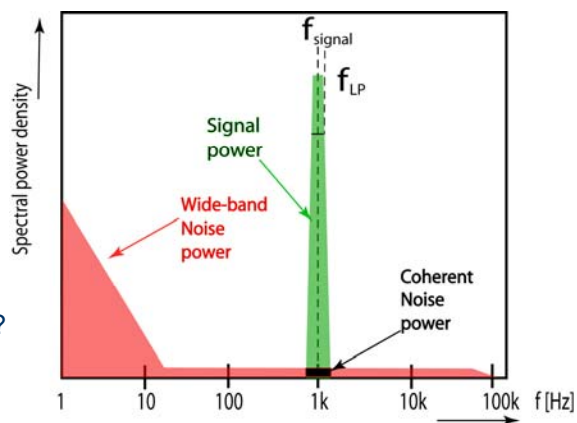
## Signal-to-noise ratio

What would be the S/N ratio of  
- an oscilloscope?  
- a coherent detector?




Some numbers:

What would be the detection limit of the coherent detector if the white noise spectral density = 10 nV/ $\sqrt{\text{Hz}}$  and  $f_{LP} = 1\text{Hz}$  ???



Linear operation of an analog multiplier circuit, working over a large range of input signals is difficult to realize in practice.

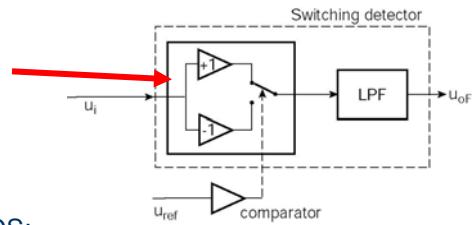A much simpler realization is a switching detector a.k.a. a **chopper**




Chopper realization in CMOS:

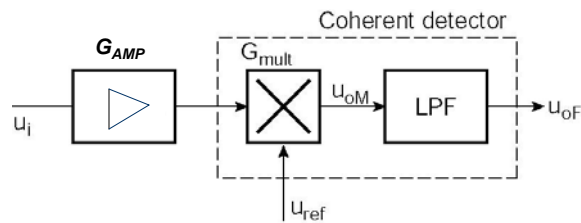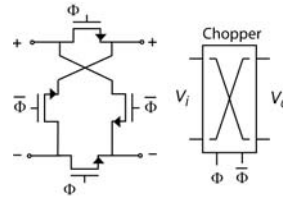Easy: just 4 transistors!  
Accurate: does not introduce offset  
But: switching spikes can cause problems (residual offset)




REMEMBER:

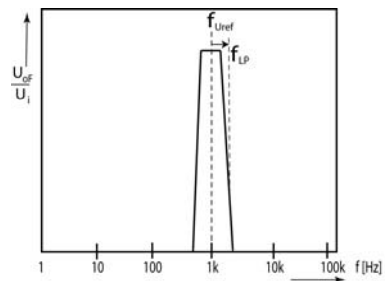- An ideal coherent detector is only sensitive to frequency components in a narrow band around a reference signal  $U_{ref}$ .
- The low-pass filter determines the signal bandwidth



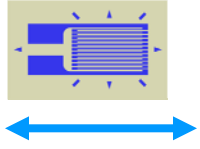So what happens if  $U_{ref}$  is a square wave ??



**R is typically 100-2000  $\Omega$**

**$\Delta R$  is typically  $10^{-1}$ -  $10^{-5}$   $\Omega$**


**Very small changes in resistance  
should be measured**





Wheatstone 1/2 bridge

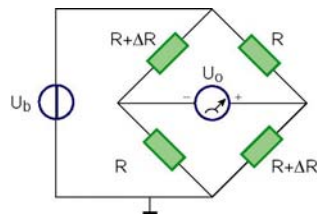Construction enables only stressed and non-stressed strain gauges



$$U_{o+} = \frac{R + \Delta R}{(R + \Delta R) + R} U_b = \frac{R + \Delta R}{2R + \Delta R} U_b$$


$$U_{o-} = \frac{R}{(R + \Delta R) + R} U_b = \frac{R}{2R + \Delta R} U_b$$

$$U_d = U_{o+} - U_{o-} = \frac{\Delta R}{2R + \Delta R} U_b$$

Non-linearity error is small if  $\Delta R \ll 2R$

$U_b$  can be an AC source of well-known frequency  
 $U_o$  is a very small AC signal ( typically a few  $\mu V$ )

with a high noise level !

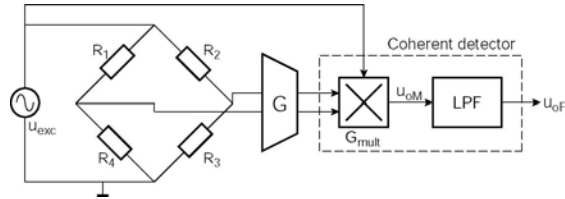


Design considerations:


What is the typical response time for this system used as a weighing scale ?

Frequency of  $u_{exc}$  ?

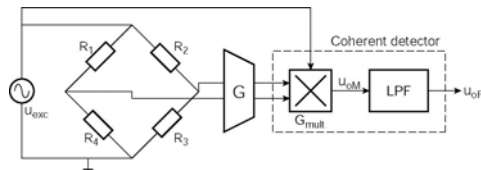What are the effects of offset in amplifier G



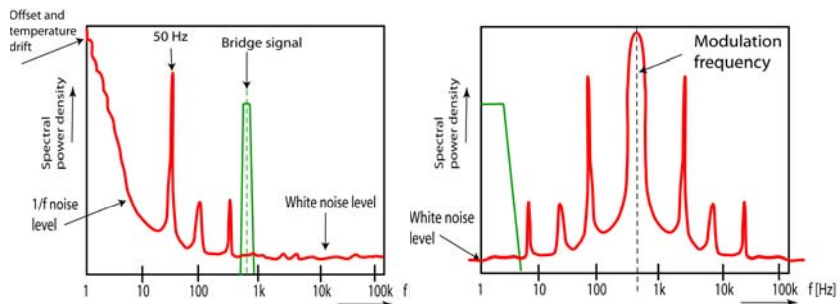Demodulation causes a shift in the frequency domain





**Some data:**

Strain gauges : 120 ohm, length 6mm  
Steel bar: area = 1cm<sup>2</sup>

1 kg gives:  $\Delta l = 2,86 \text{ nm}$

Resistance change:  $\Delta R = 120 \mu\Omega$

Relative change:  $\Delta R/R = 10^{-6}$




**Noise level:**

Force: 10N , or 1kg

Max force: 15 kN, or 1500 kg ( Steel bar limit )

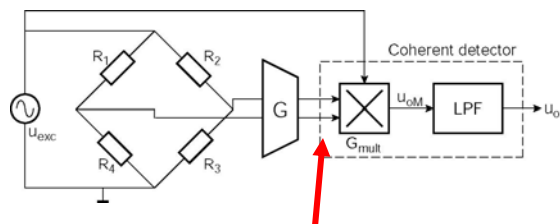
Dynamic range:  $1500/0.1 = 15 \cdot 10^3 = 84 \text{ dB}$



Important limitation of a coherent detector is the maximum allowable signal at the input of the multiplier.


( saturation and non-linearity will lead to unwanted effects such as harmonic sensitivity and self-detection as will be shown later )

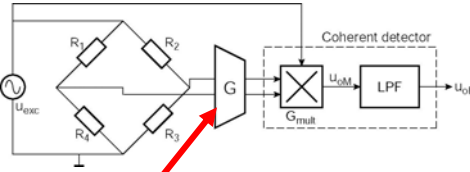Generally a maximum signal indicator is placed at the signal input of the multiplier to indicate overload situations



Use an AC amplifier

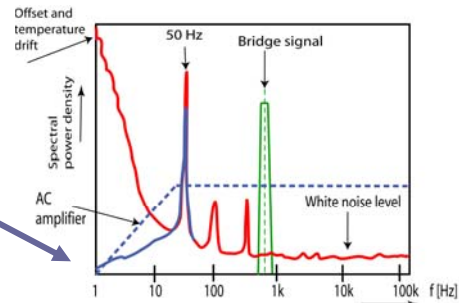Offset suppression  
reduces overload on  
multiplier




Signal-Noise ratio

=


Green area

Black area

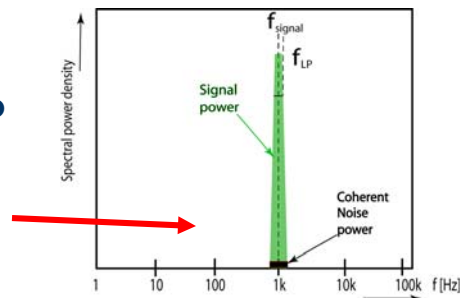

Other detection limits are due to:

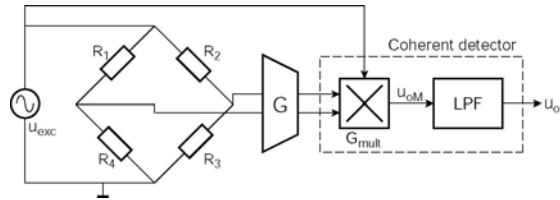- o Offsets in both input- and output channel
- o Non-linearities in the reference channel
- o Non-linearities in the input channel
- o Non-linearities at the output of the multiplier



Offset in the input AND reference channels are DC signals that are simply multiplied and pass through the low-pass filter, therefore:

$$U_{oF} = GG_{mult}G_{LPF}U_{excDC}U_{bridgeDC}$$

- o Non-linearities in the reference channel
- o Non-linearities in the input channel
- o Non-linearities at the output of the multiplier


In case of a second-order harmonic distortion only:

$$u_{oM} = G_{mult} [\hat{u}_r (\sin(\omega_r t) + \beta_2 \sin(2\omega_r t)) \times \hat{u}_i \sin(\omega_i t)] =$$

$$G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} [\cos((\omega_r - \omega_i)t) - \cos((\omega_r + \omega_i)t) + \beta_2 \cos((2\omega_r - \omega_i)t) - \beta_2 \cos((2\omega_r + \omega_i)t)]$$


So input components at  $\omega_i = 2\omega_r$  cause output!

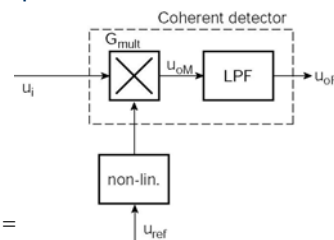Makes the coherent detector sensitive to SUPERHARMONICS in the input signal



- o Non-linearities in the reference channel
- o Non-linearities in the input channel
- o Non-linearities at the output of the multiplier

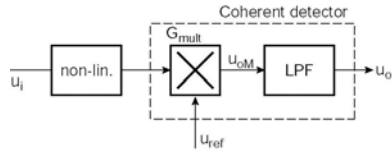In case of a third-order harmonic distortion only:



$$u_{oM} = G_{mult} [\hat{u}_i (\sin(\omega_i t) + \beta_1 \sin(3\omega_i t)) \times \hat{u}_r \sin(\omega_r t)] =$$


$$G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} [\cos((\omega_r - \omega_i)t) - \cos((\omega_r + \omega_i)t) + \beta_1 \cos((3\omega_i - \omega_r)t) - \beta_1 \cos((3\omega_i + \omega_r)t)]$$

This term generates output if  $\omega_i = \omega_r/3$

Makes the coherent detector sensitive to SUBHARMONICS in the input signal (and also to noise in these bands !)

- o Non-linearities in the reference channel
- o Non-linearities in the input channel
- o Non-linearities at the output of the multiplier

In case of a quadratic distortion only:

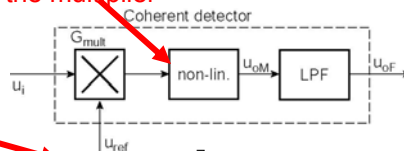

$$u_{oM} = G_{mult} \hat{u}_r \hat{u}_i \left[ (\cos(\omega_r t) \times \cos(\omega_i t)) + \delta_2 \hat{u}_r \hat{u}_i (\cos(\omega_r t) \times \cos(\omega_i t))^2 \right] =$$


$$G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} \left[ \cos((\omega_r \pm \omega_i)t) + \frac{\delta_2 \hat{u}_r \hat{u}_i}{2} (1 + \cos(2\omega_r t))(1 + \cos(2\omega_i t)) \right] =$$

$$G_{mult} \frac{\hat{u}_r \hat{u}_i}{2} \left[ \cos((\omega_r \pm \omega_i)t) + \frac{\delta_2 \hat{u}_r \hat{u}_i}{2} \times \left( 1 + \cos(2\omega_r t) + \cos(2\omega_i t) + \frac{1}{2} (\cos(2(\omega_r \pm \omega_i)t)) \right) \right]$$

So components at  $\omega_i = \omega_r$  cause output

Self detection

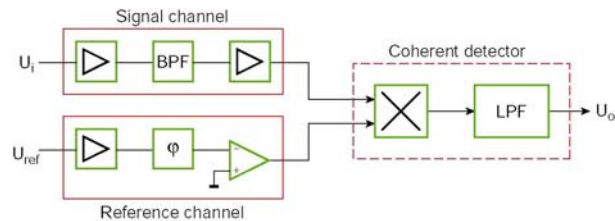A lock-in amplifier is a coherent detector with all the extra features required of a general-purpose laboratory instrument.



**Source: LED modulated with a sine wave**


**Detector: Photodiode**

**Instrument: Analog lock-in amplifier (PAR 186)**

**Interference:**

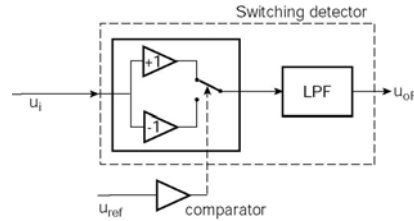**Ambient light, DC (offset), 50 Hz mains (lamp)**

Simplifying multiplier at the expense of super-harmonic sensitivity



Use Fourier series of square wave signal,  $S(t)$ :


$$U_{oM} = \hat{u}_i \cos(\omega t + \varphi) [S(t)] =$$

$$\hat{u}_i \cos(\omega t + \varphi) \left( \frac{4}{\pi} \left( \cos(\omega t) - \frac{\cos(3\omega t)}{3} + \frac{\cos(5\omega t)}{5} - \dots \right) \right) =$$

$$\frac{2\hat{u}_i}{\pi} \left( \cos(\varphi) + \cos(2\omega t + \varphi) - \frac{\cos(2\omega t + \varphi)}{3} - \frac{\cos(4\omega t + \varphi)}{3} + \dots \right)$$

$$U_{oF} = \frac{2\hat{u}_i}{\pi} \cos(\theta) \quad \text{Similar transfer function as multiplier detector (apart from factor } 2/\pi \text{ instead of } 1/2).$$

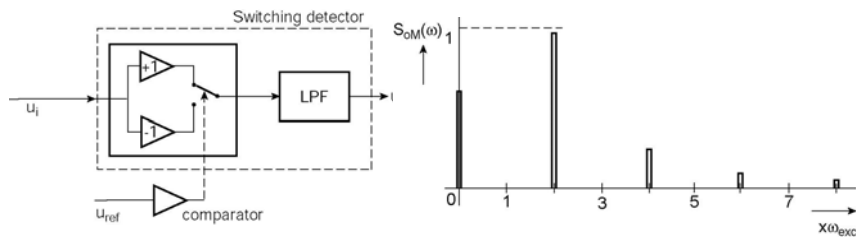Simplifying multiplier at the expense of a slight decrease in SNR




$$u_{n,SD}^2 = N_o 2f_{LPF} + \frac{N_o 2f_{LDF}}{(-3)^2} + \frac{N_o 2f_{LDF}}{5^2} + \frac{N_o 2f_{LDF}}{(-7)^2} + \dots =$$

$$N_o 2f_{LDF} \left[ 1 + \left(\frac{1}{3}\right)^2 + \left(\frac{1}{5}\right)^2 + \left(\frac{1}{7}\right)^2 + \dots \right] = N_o 2f_{LDF} \sum_{n=0}^{\infty} \left(\frac{1}{2n+1}\right)^2 = \frac{\pi^2}{8} N_o 2f_{LDF}$$

Increase of noise due to super-harmonic sensitivity by a factor  $\pi^2/8$ .

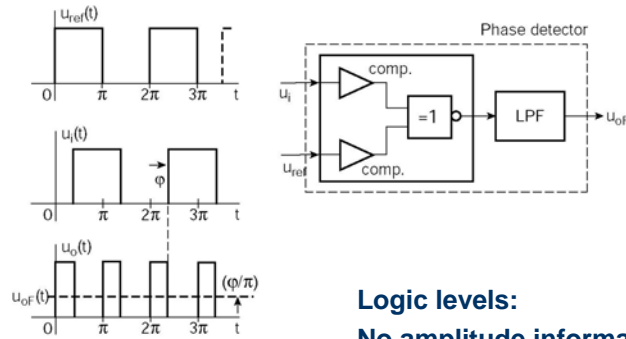
Further simplification of multiplier at the expense of super- and sub-harmonic sensitivity



Logic levels:  
No amplitude information

Is often used in Phase Locked Loops (PLL).

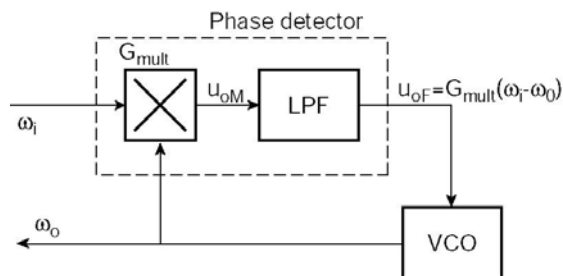
The excitation frequency of remote sensors is not always directly available, but can be retrieved from the sensor's output signal by a phase-locked loop (PLL).



The loop drives the VCO so as to minimize the error signal  $U_{oM}$   
As a result,  $\omega_i \sim \omega_o$  with a small loop-gain-dependent phase error

Analog functionality is replaced by digital signal processing (DSP)

⇒ Cost, Flexibility, User friendliness

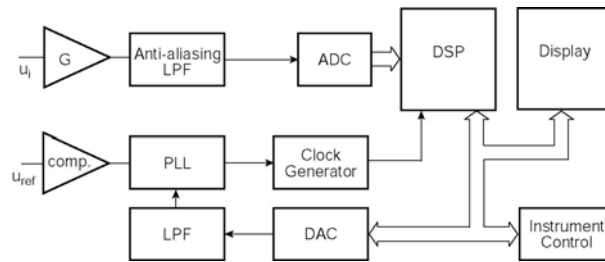

ADC and DSP are critical (frequency limiting) components

Digital lock-in amplifiers are becoming more and more economical and common in test-setups in the lab and in industry

Coherent detection is a powerful technique to accurately measure low-level periodic signals in the presence of high levels of noise and interference.

Both amplitude and phase can be measured

The signal frequency should be known (reference channel) or it should be possible to regenerate it with a PLL.

The operating frequency should be in a frequency band where disturbing signals and noise are low.

Distortion in the input- or reference channel can lead to harmonic sensitivity

Modern (digital) lock-in amplifiers can also measure the amplitude and phase of harmonic signals (2f, 3f, 4f etc. ) e.g. for the measurement of signal distortion.