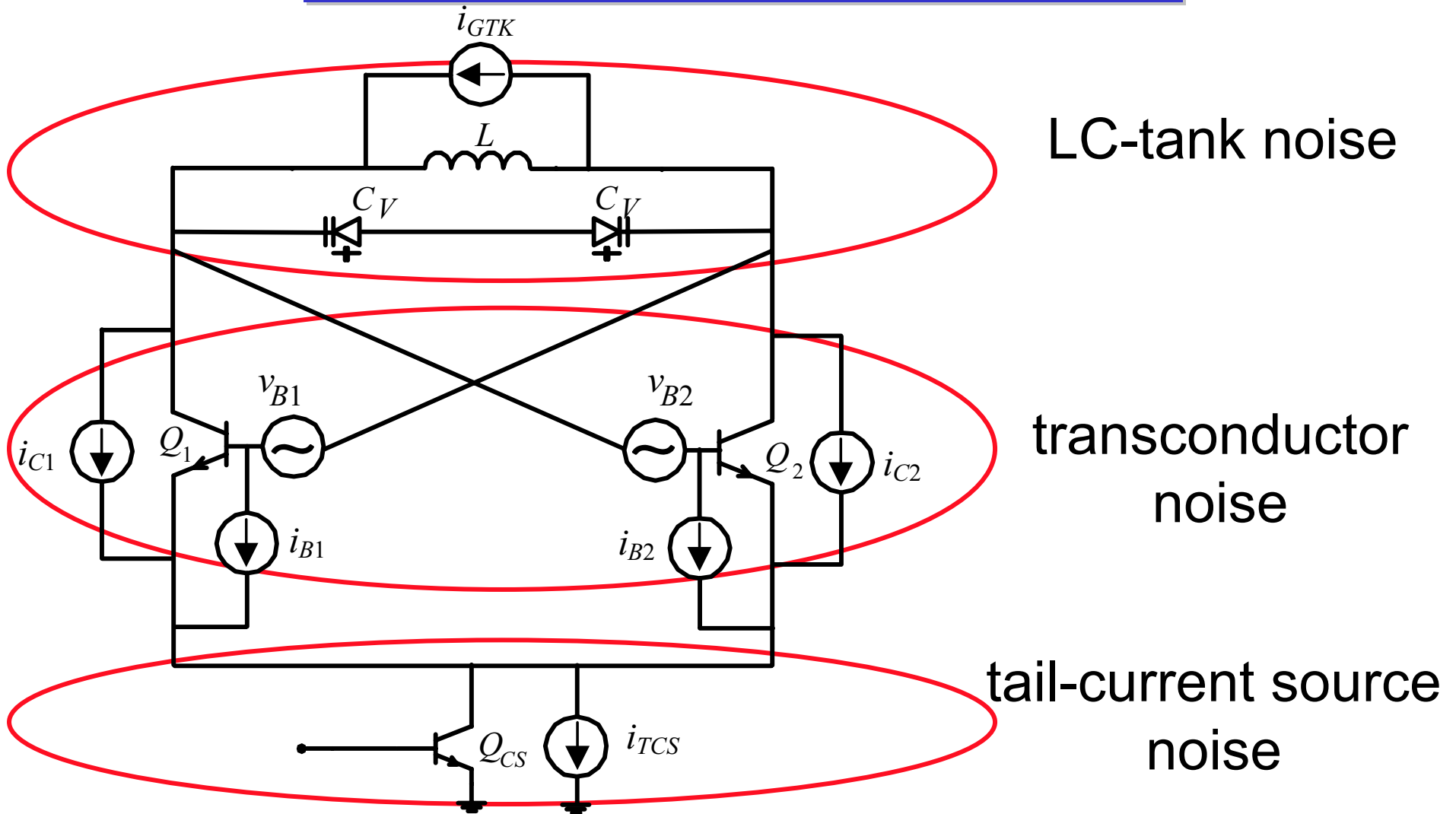


Spectral Analysis of Noise in Switching LC-Oscillators

Sub-Outline

- Duty Cycle of g_m -cell Small-Signal Gain
- Oscillation Condition
- LC-Tank Noise
- g_m -cell Noise
- Tail-Current Source Noise
- (Phase) Noise Factor – Bipolar VCO
- (Phase) Noise Factor – CMOS VCO
- Bipolar vs. CMOS VCO


Is it Indeed so Simple?




- noise from the transistors Q_1 and Q_2 is switched ON and OFF
- noise from current source Q_{CS} is modulated by oscillator switching

g_m -cell Transfer Function

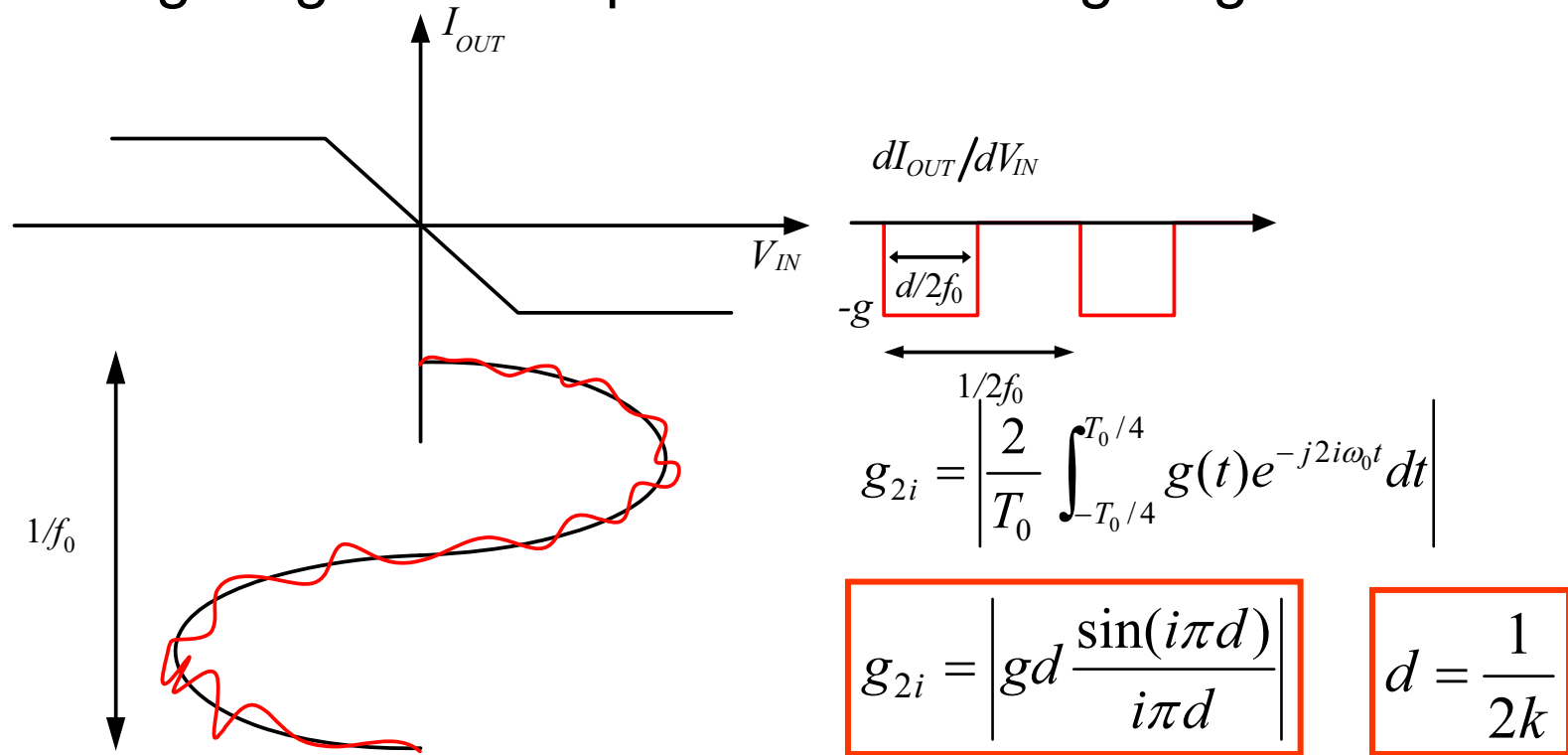- small-signal gain in the presence of a large signal



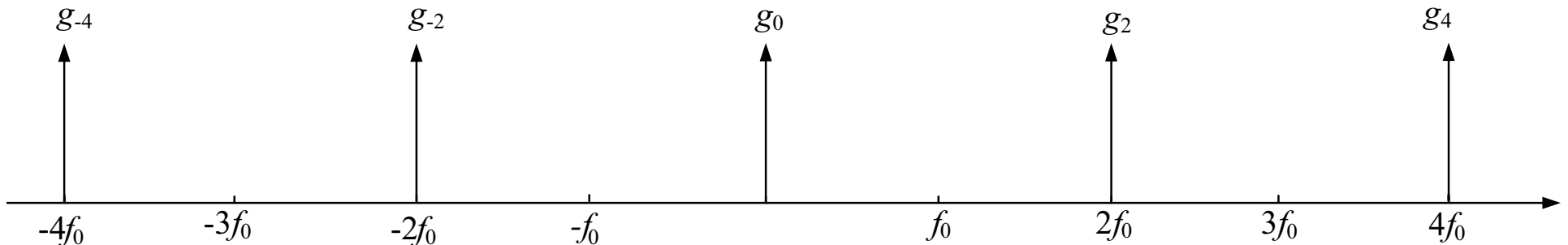- Fourier domain – (magnitude) complex harmonic components



LC-Tank Noise Contribution

- phase-modulating noise component:

$$i_{PM} = \frac{1}{2} \left[i_{N,O}(f_0 + \Delta) + i_{N,O}(-f_0 + \Delta) + i_{N,O}(-f_0 - \Delta) + i_{N,O}(f_0 - \Delta) \right]$$

$$i_{PM} = (g_0 + g_2)v_N(f_0 + \Delta) + (g_0 + g_2)v_N(f_0 - \Delta)$$

- phase-related noise power ($k \gg 1$, $g = g_0 = g_{\pm 2}$):

$$i_{PM}^2(R_{TK}) = (g_0 + g_2)^2 v_N^2(R_{TK})$$


- LC-tank noise transfer function:

$$g^2(R_{TK}) = (g_0 + g_2)^2 = G_{TK}^2$$


- LC-tank noise factor:

$$F(R_{TK}) = \frac{2i_{PM}^2(R_{TK})}{4KTG_{TK}} = \frac{2(g_0 + g_2)^2 v_N^2(R_{TK})}{4KTG_{TK}} = \frac{2G_{TK}^2 v_N^2(R_{TK})}{4KTG_{TK}} = \frac{4KTG_{TK}}{4KTG_{TK}} = 1$$

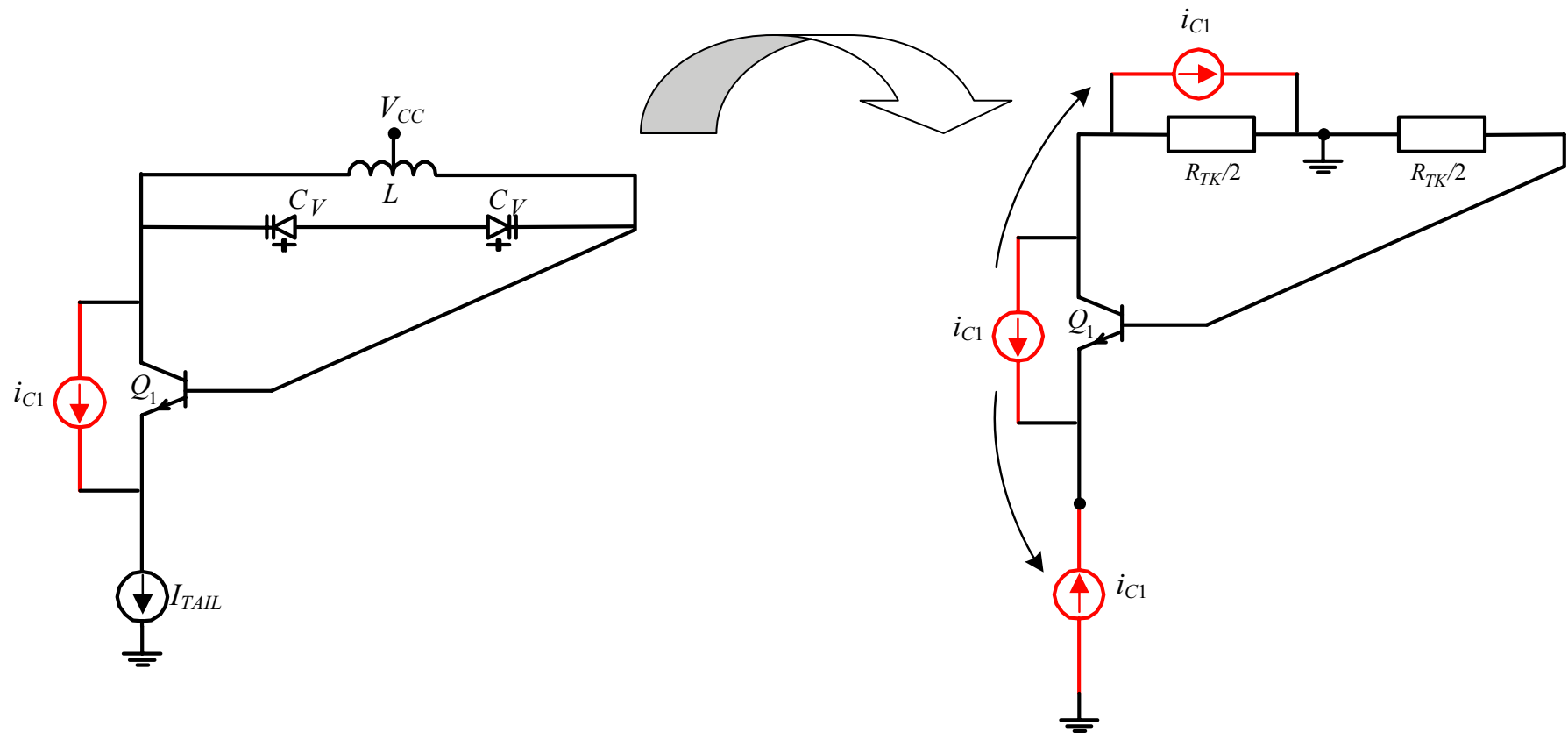
Collector-Current Noise Transfer Function in Limiting Region



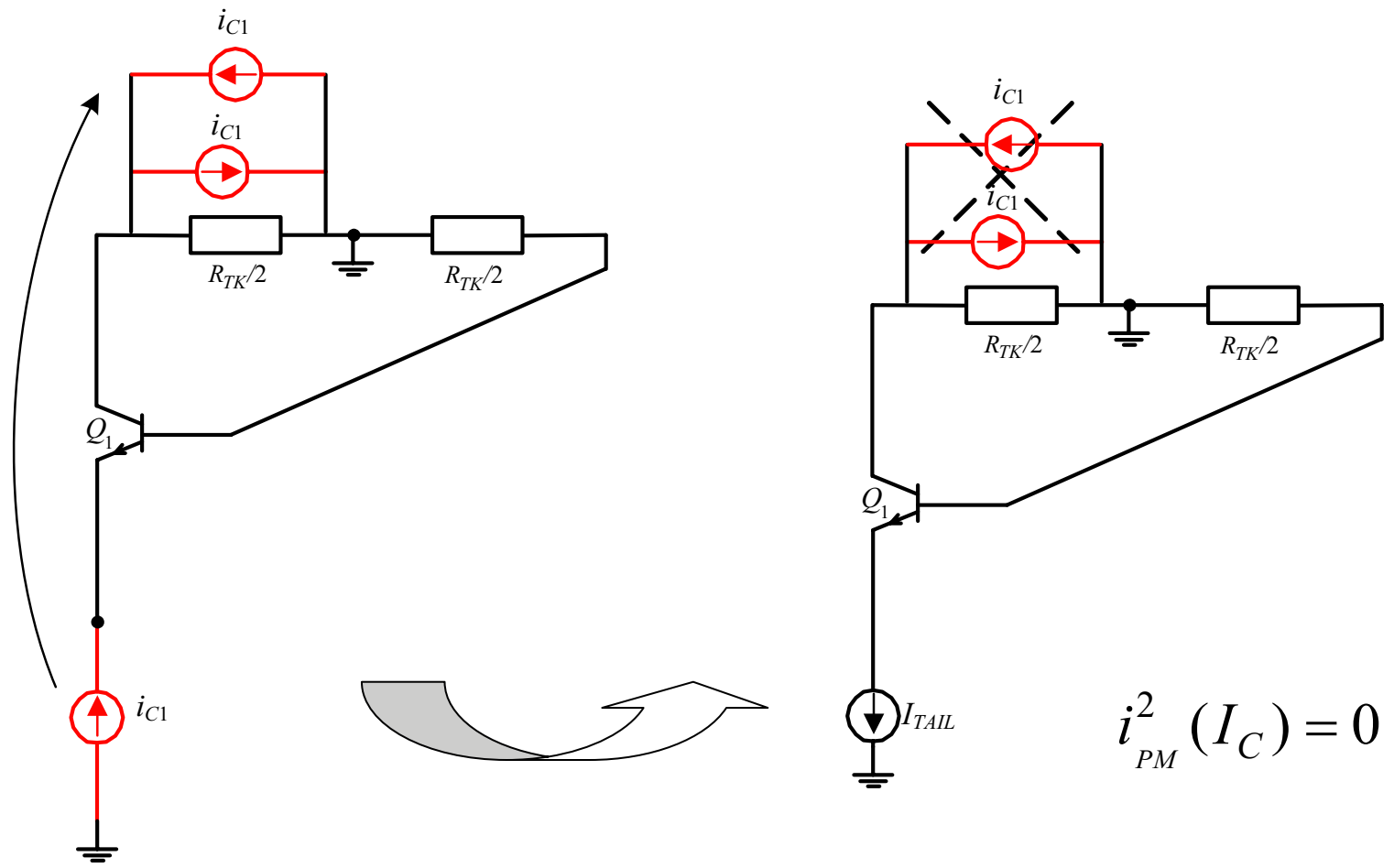
Collector-Current Noise Transfer Function in Limiting Region



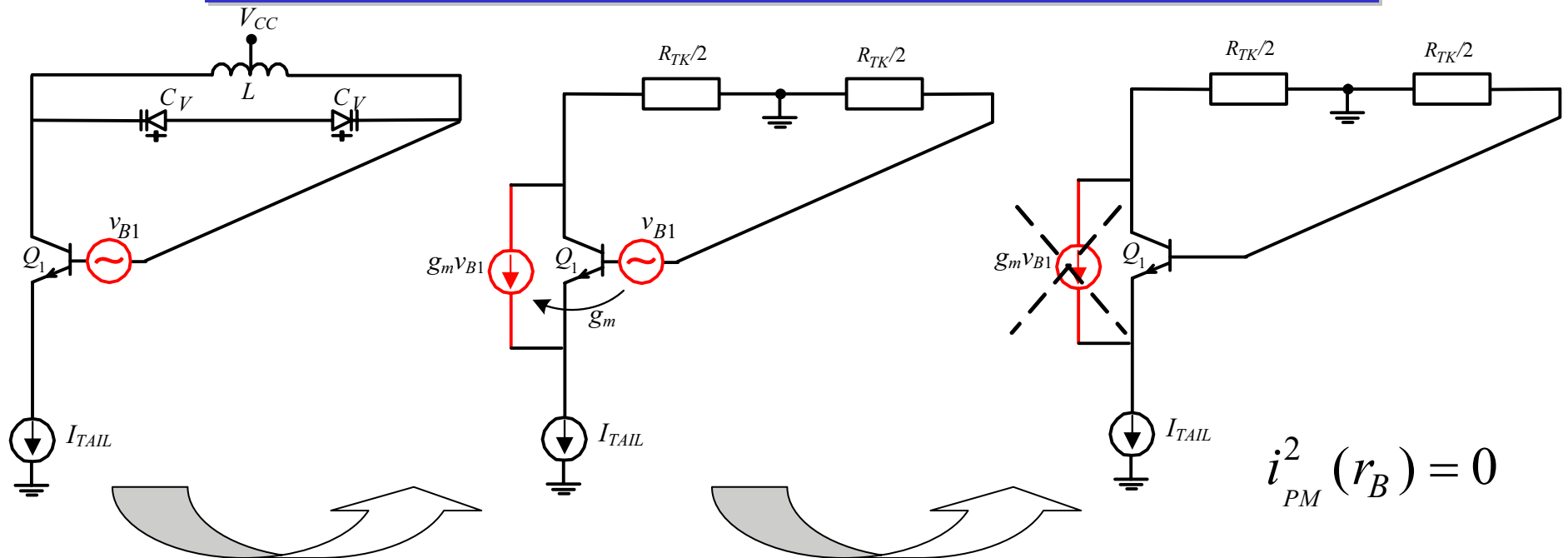Base-Resistance Noise Transfer Function in Limiting Region



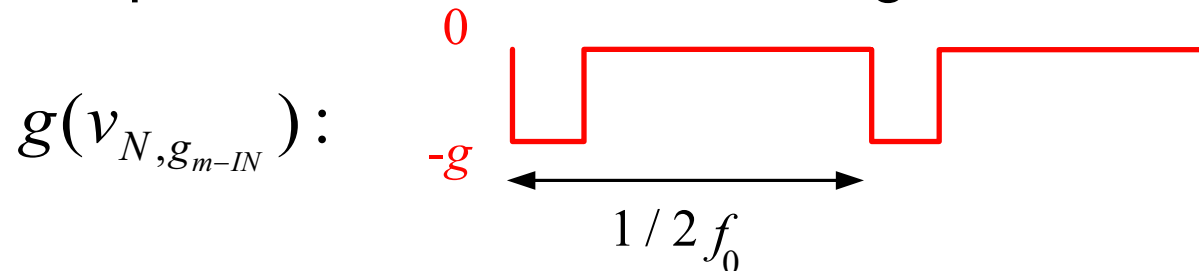- g_m -cell input-noise linear and limiting transfer function:



$$v_N(g_{m-IN}) = 2(v_N(r_B) + i_N(I_C) / g_m^2) = 4KT r_B + 2KT / g_m$$

g_m -Cell Noise Contributions

- phase-related noise power:

$$i_{PM}^2(g_{m-IN}) = \frac{1}{2d}(g_{2i-2} + g_{2i})^2 v_N^2(g_{m-IN}) = \frac{2g_{2i}^2}{d} v_N^2(g_{m-IN}) = 2dg^2 v_N^2(g_{m-IN})$$

- g_m -cell noise transfer function:

$$g^2(g_{m-IN}) = 2dg^2 = 2d\left(\frac{g_m}{2}\right)^2 = 2\frac{1}{2k}(kG_{TK})^2 = kG_{TK}^2$$

- g_m -cell noise factors:


$$F(2r_B) = \frac{2i_{PM}^2(2r_B)}{4KTG_{TK}} = \frac{2kG_{TK}^2 4KTr_B}{4KTG_{TK}} = 2kr_B G_{TK} = kc$$

$$F(2I_C) = \frac{2i_{PM}^2(2I_C)}{4KTG_{TK}} = \frac{2kG_{TK}^2 2KT / g_m}{4KTG_{TK}} = kG_{TK} / g_m = \frac{1}{2}$$


- input g_m -cell noise around odd multiples of the oscillation frequency is folded to the LC-tank noise around the oscillation frequency

Tail-Current Noise Transfer Function

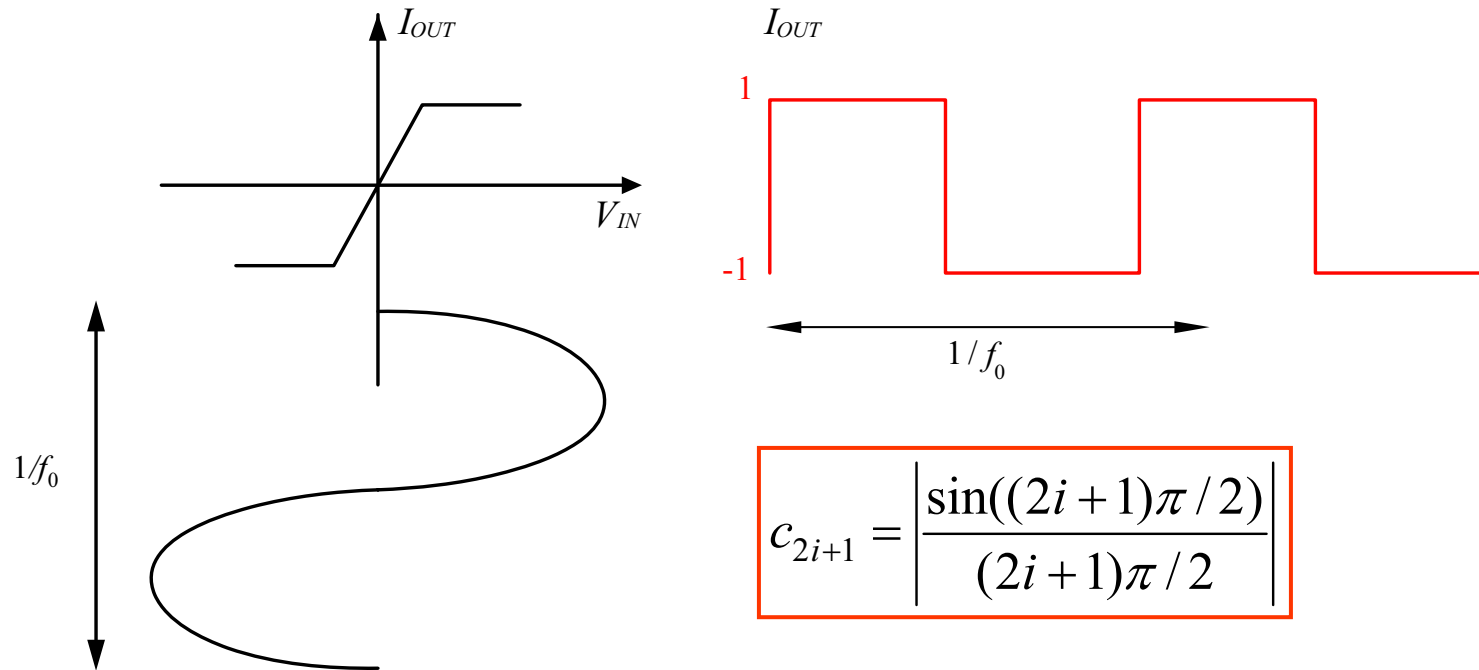- g_m -cell large-signal V-to-I transfer function



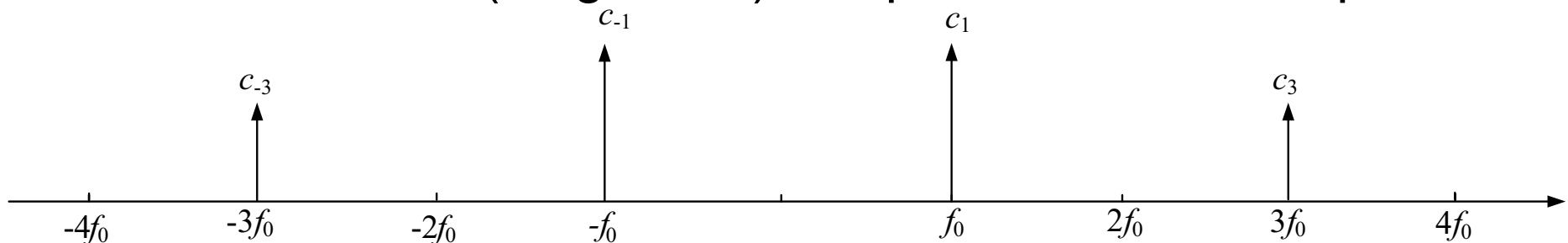- Fourier domain – (magnitude) complex harmonic components



TCS-Noise Contribution

- phase-related noise power:

$$i_{PM}^2(I_{TCS}) = \frac{i_{PM,DIFF}^2(I_{TCS})}{4} = \frac{1}{4} i_N^2(I_{TCS})$$

- TCS-noise transfer function:

$$g^2(I_{TCS}) = \frac{1}{4}$$

- TCS-noise factor:

$$\begin{aligned} F(I_{TCS}) &= \frac{2i_{PM}^2(I_{TCS})}{4KTG_{TK}} = \frac{KTg_m(1+2r_Bg_m)}{4KTG_{TK}} = \frac{KT2kG_{TK}(1+2kc)}{4KTG_{TK}} = \\ &= \frac{1}{2}k(1+2kc) = k\left(\frac{1}{2} + kc\right) = k\left(F(2I_C + 2I_B) + F(2r_B)\right) \end{aligned}$$

- TCS noise around even multiples of the oscillation frequency is folded to the LC-tank noise around the oscillation frequency

Switching-Oscillator Phase Noise

- Noise factor:

$$F = F(R_{TK}) + F(2I_C) + F(2I_B) + F(2r_B) + F(I_{TCS})$$

$$F = 1 + \frac{1}{2} + \frac{1}{2\beta} + kc + k\left(\frac{1}{2} + kc\right) \cong 1 + (1+k)\left(\frac{1}{2} + kc\right)$$

- Phase noise:

$$\mathcal{L} = \frac{\mathcal{L}(R_{TK}) + \mathcal{L}(2I_C) + \mathcal{L}(2I_B) + \mathcal{L}(2r_B) + \mathcal{L}(I_{TCS})}{(4\pi C_{TOT}\Delta)^2} = \frac{4KTG_{TK}F}{v_s^2 (4\pi C_{TOT}\Delta)^2}$$

$$\mathcal{L} = \frac{4KTG_{TK}}{(4\pi C_{TOT}\Delta)^2} \left(\frac{\pi}{8V_T}\right)^2 \frac{1 + (1+k)\left(\frac{1}{2} + kc\right)}{k^2}$$

Phase Noise Model of Bipolar Switching LC-Oscillators

$$F = 1 + \frac{1}{2} + kc + k\left(\frac{1}{2} + kc\right)$$

- **Constant phase-noise contributions**
 - LC-tank noise contribution ~ 1
 - g_m -cell current shot noise contribution $\sim \frac{1}{2}$
- **Loop-gain related contributions**
 - g_m -cell base-resistance noise contribution $\sim ck$
 - phase-noise contribution of the bias current source is k -times larger than the noise contribution of the g_m -cell $\sim k(\frac{1}{2} + ck)!$

Low/High-Performance VCO Designs

- high loop-gain, high quality LC-tank, BCS noise eliminated:

e.g., $k \gg 1 (=10)$, $c \ll 1 (\sim 0.01)$

$$\mathcal{L} \sim \frac{1 + \frac{1}{2} + kc}{k^2} = \frac{8}{5} \frac{1}{10} \frac{1}{10} \sim \frac{1}{k^2}$$

- high loop-gain, high quality LC-tank:

e.g., $k \gg 1 (=10)$, $c \ll 1 (\sim 0.01)$


$$\mathcal{L} \sim \frac{k(\frac{1}{2} + kc)}{k^2} = \frac{\frac{1}{2} + kc}{k} = \frac{3}{5} \frac{1}{10} \sim \frac{1}{k}$$

- low loop-gain, low quality LC-tank:

e.g., $k \sim 1 (=2)$, $c \sim 1 (\sim 0.5)$


$$\mathcal{L} \sim \frac{1 + (1+k)\frac{3}{2}}{k^2} = \frac{11}{8} \sim 1$$

Single/Double-Switch CMOS LC-VCOs

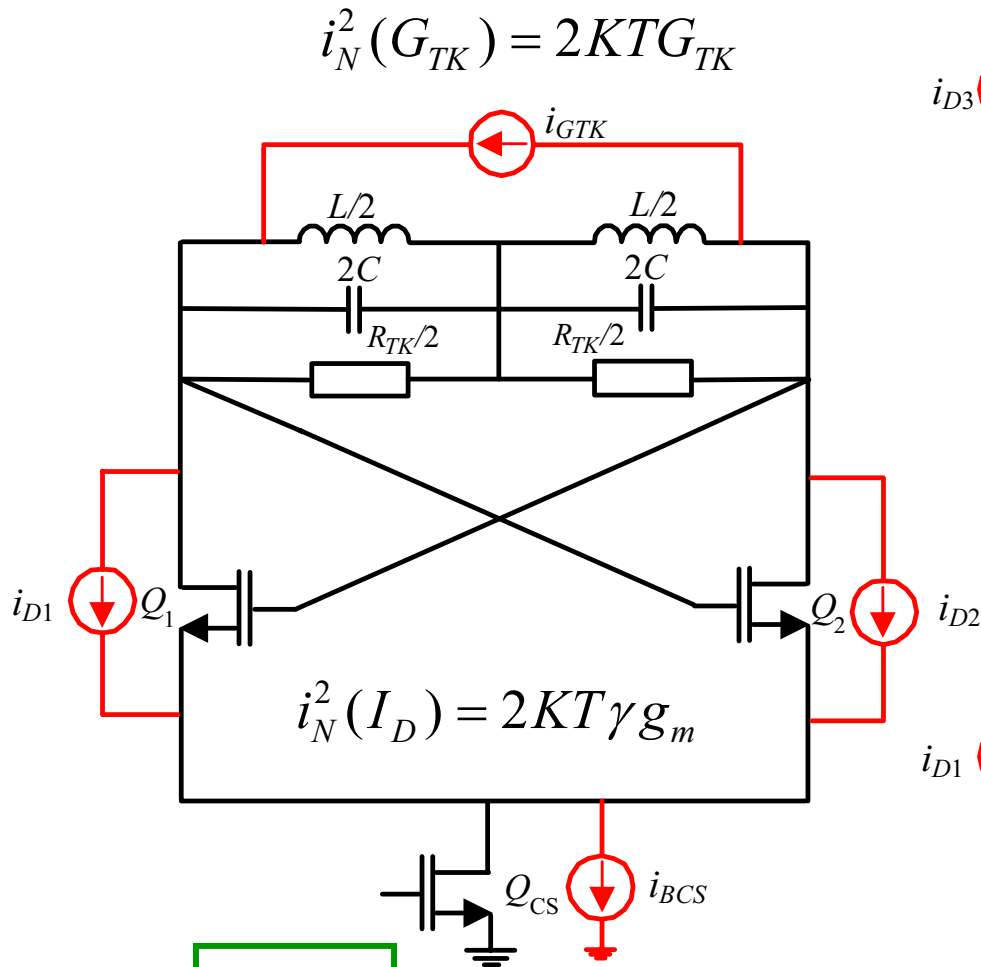

$$d = \frac{1}{2k}$$

$$i_N^2(I_{BCS}) = 2KT\gamma g_{m,CS}$$

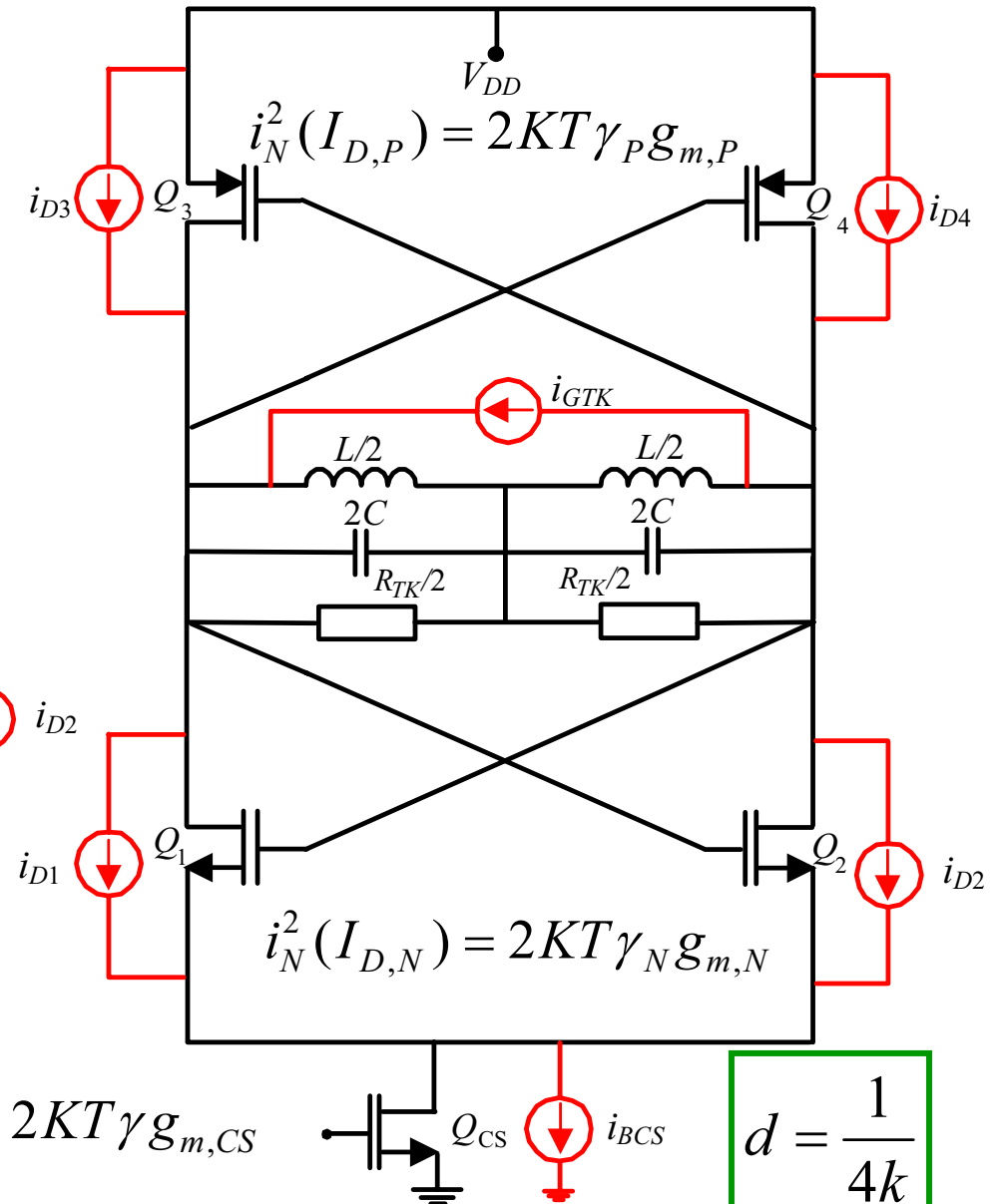

$$d = \frac{1}{4k}$$

Phase Noise Model of CMOS LC-Oscillators

- Noise factor ($\gamma_N = \gamma_P$, $g_{m,N} = g_{m,P}$, $g_{m,N,CS} = 2g_{m,N}$):

$$F_{SS} = F(R_{TK}) + F(2I_D) + F(I_{BCS}) \quad F_{DS} = F(R_{TK}) + F(4I_D) + F(I_{BCS})$$

$$F_{SS} = 1 + \gamma + k\gamma = 1 + (1+k)\gamma \quad F_{DS} = 1 + \gamma + 2k\gamma = 1 + (1+2k)\gamma$$

- Phase noise:

$$\mathcal{L} = \frac{\mathcal{L}(R_{TK}) + \mathcal{L}(2I_D) + \mathcal{L}(I_{BCS})}{(4\pi C_{TOT} \Delta)^2} = \frac{4KTG_{TK}F}{v_s^2 (4\pi C_{TOT} \Delta)^2}$$

$$\mathcal{L}_{SS} = \frac{4KTG_{TK}}{(4\pi C_{TOT} \Delta)^2} \frac{1 + (1+k)\gamma}{\left(\frac{2}{\pi} I_{TAIL} R_{TK}\right)^2} \quad \mathcal{L}_{DS} = \frac{4KTG_{TK}}{(4\pi C_{TOT} \Delta)^2} \frac{1 + (1+2k)\gamma}{\left(\frac{4}{\pi} I_{TAIL} R_{TK}\right)^2}$$

Phase Noise Model of CMOS LC-Oscillators

$$F = 1 + \gamma + \alpha k \gamma$$

- **Constant phase-noise contributions**
 - LC-tank noise contribution ~ 1
 - g_m -cell drain-current thermal noise contribution $\sim \gamma$
- **Loop-gain related contributions**
 - bias current source noise contribution $\sim k\gamma$

CMOS vs. Bipolar LC-Oscillators

- noise factors (for removed BCS noise):

$$F_{BIP} = 1 + \frac{1}{2} + kc$$

$$F_{CMOS} = 1 + \gamma$$

- bipolar VCO better for the same power consumption ($v_{s,BIP} = v_{s,CMOS}$)

$$\frac{3}{2} + kc < \frac{5}{3} \quad \Rightarrow$$

$$kr_B < \frac{R_{TK}}{12}$$

- e.g., $k=10$, $R_{TK}=1000\Omega$

$$r_B < \frac{1000}{120} = 8.4\Omega$$

- e.g., $k=10$, $R_{TK}=100\Omega$

$$r_B < \frac{100}{120} = 0.84\Omega$$

CMOS vs. Bipolar LC-Oscillators

- power consumption figure of merit:

$$FOM = 10 \log \left(\mathcal{L}(\Delta) \left(\frac{\Delta}{\omega_0} \right)^2 V_{CC} I_{CC} \right)$$

- $V_{CC}=1.8V$, $v_{s,BIP}=0.4V$, $v_{s,SS-CMOS}=1.2V$, ($3I_{CC,BIP}=I_{CC,SS-CMOS}$)

$$FOM_{BIP} = FOM_{SS-CMOS} + 4.8dB$$

- $V_{CC}=1.8V$, $v_{s,BIP}=0.4V$, $v_{s,DS-CMOS}=1.2V$, ($1.5I_{CC,BIP}=I_{CC,DS-CMOS}$)

$$FOM_{BIP} = FOM_{DS-CMOS} + 7.8dB$$

Phase-Noise Model Conclusions

- Parametric Phase-Noise Model
 - electrical circuit parameters (loop gain)
 - worst-case phase noise (bandwidth unlimited)
- Bipolar vs. CMOS LC-Oscillators
 - bipolar loop-gain related contributions
 - $V_{S,BIP} \sim k (\ll V_{CC}), V_{S,CMOS} \sim V_{CC}$
 - bipolar capacitive tapping for larger $v_{S,BIP}$, but also larger k -related noise contributions and power consumption

So Far

VCO design parameters	<i>Design requirement</i>
Oscillating frequency	2.1GHz
Tuning range	400MHz
Voltage swing	0.7V
Phase noise	-110dBc@1MHz
Supply voltage	3V
Power consumption	10mW

Technology parameters	<i>Values</i>
Technology	BiCMOS
Number of metals	4
Transit frequency	50GHz
MIM capacitors	available
Varactors	available

Suppression of Noise in Oscillator's Tail-Current Source


VCO Phase-Noise

$$PN = \frac{\text{noise power(LC - tank, - } g_m \text{ cell, current source)}}{\text{signal power } (\sim k^2)}$$

- TCS noise \gg LC-tank noise + g_m -cell noise
 - VCO noise power ~ 1 or $c \cdot k^2$
 - phase noise $\sim 1/k^2$ or *const*
- TCS noise suppressed
 - VCO noise power ~ 1 or $c \cdot k$
 - phase noise $\sim 1/k^2$ or $1/k$


Bias Noise Reduction Techniques

resistive
degeneration

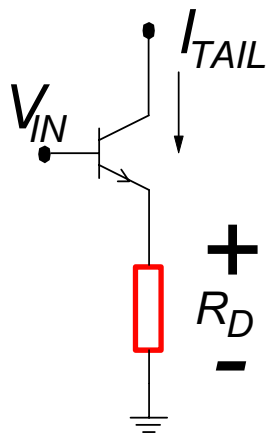


☹ high supply
required

inductive
degeneration

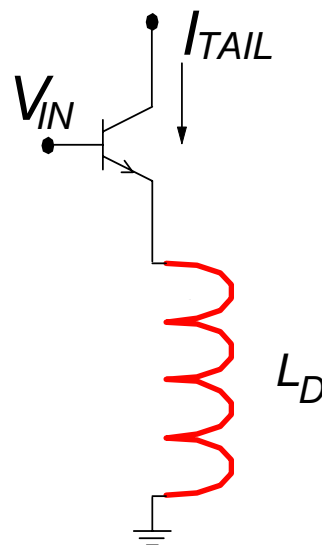



☹ large area if
integrated
☹ noise injection if
discrete

filtering?

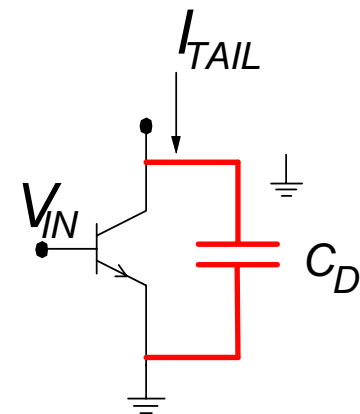



☹ transconductor
noise always ON
☹ reduced output
impedance

Capacitive Filtering

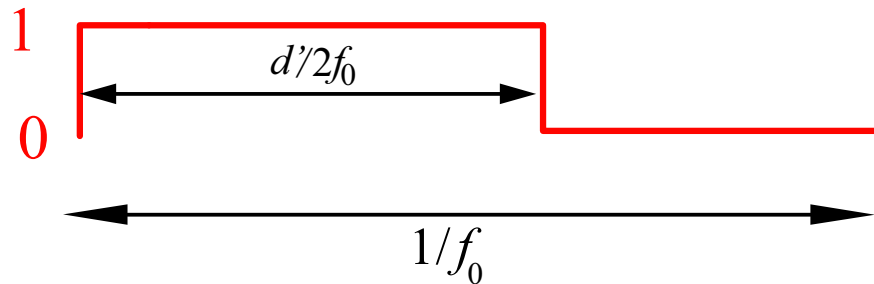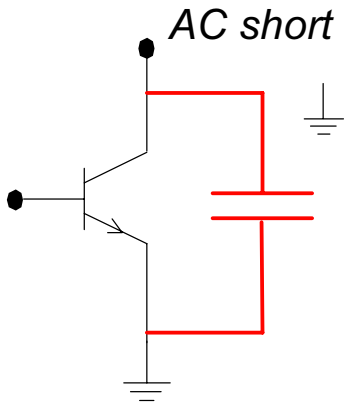

$$d' = \frac{1}{2}(1 + d)$$

$$F'(2I_C) \sim k \frac{n}{2}$$

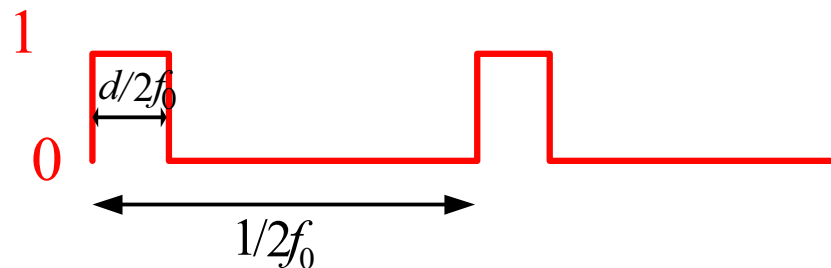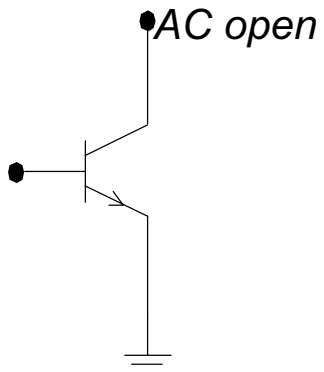


$$d = \frac{1}{2k}$$

$$F(2I_C) \sim \frac{n}{2}$$

- for $k=10$, $d=0.5\%$, $d'=50.25\%$, and $F' > F$

Resonant-Inductive Degeneration (RID)

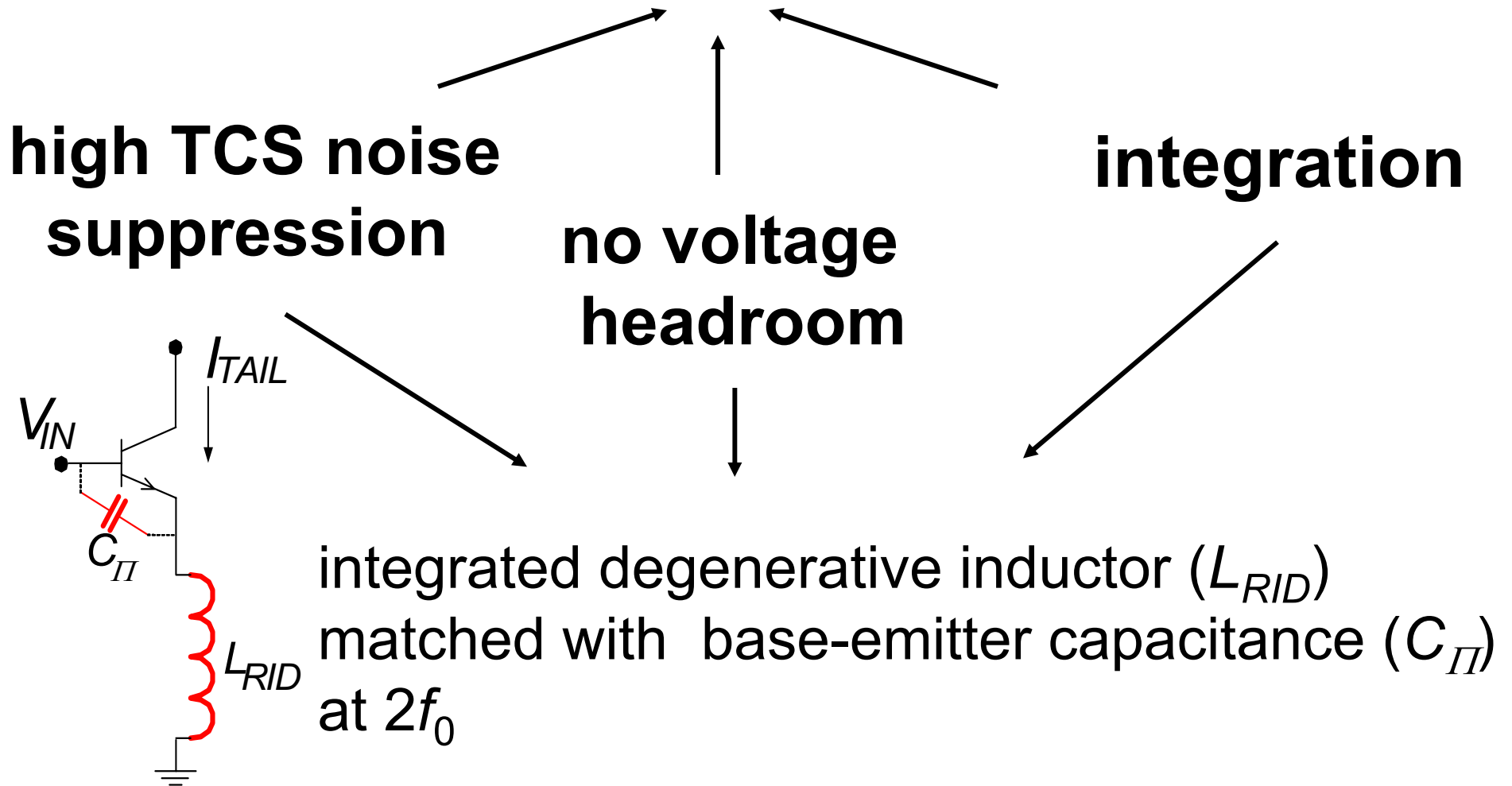

So Far

VCO design parameters	<i>Design requirement</i>
Oscillating frequency	2.1GHz
Tuning range	400MHz
Voltage swing	0.7V
Phase noise	-110dBc@1MHz
Supply voltage	3V
Power consumption	10mW

Technology parameters	<i>Values</i>
Technology	BiCMOS
Number of metals	4
Transit frequency	50GHz
MIM capacitors	available
Varactors	available