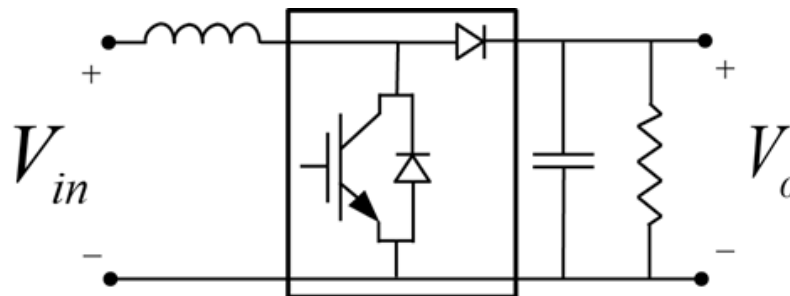


### Key equations for a boost converter

Now that you have an understanding of how the simple DC-DC boost converter works, we summarize the main equations for the converter here. These equations are for continuous conduction mode, where the current always flows through the inductor. Discontinuous conduction mode is out of the scope of this course.



$$V_o = V_{in} / (1-D)$$

$$T = 1/f$$

$$D = T_{on} / (T)$$

$$T = T_{on} + T_{off}$$

where

$V_o$  is the output voltage

$D$  is the duty cycle of the switch

$V_{in}$  is the input voltage

$f$  is the switching frequency of the semiconductor switch

$T$  is the time period of the semiconductor switch

$T_{on}$  is the ON time of the semiconductor switch

$T_{off}$  is the OFF time of the semiconductor switch



This course material is licensed under a Creative Commons Attribution-NonCommercial-ShareAlike 4.0 License.

## DC-DC converter: driving and regenerative braking

In a battery-powered electric vehicle, regenerative braking (also called regen) is the conversion of the vehicle's kinetic energy into chemical energy stored in the battery, where it can be used later to drive the vehicle. It is braking because it also serves to slow the vehicle. It is regenerative because the energy is recaptured in the battery where it can be used again.

A torque command is derived from the position of the throttle pedal. The motor controller converts this torque command into the appropriate 3-phase voltage and current waveforms to produce the commanded torque in the motor in the most efficient way. The torque command can be positive or negative. When the torque serves to slow the vehicle then energy is returned to the battery and presto - we have regenerative braking!

So a good proportion of the energy you lose by braking is returned to the batteries and can be reused when you start off again as shown in Figure 1. In practice, regenerative brakes take time to slow cars down and have power limitations based on the rated power of the motor, power electronics and battery. So, most vehicles that use them also have ordinary (friction) brakes working alongside. That's one reason why regenerative brakes doesn't save 100% of your braking energy.

In case of driving the vehicle forward, the opposite occurs and energy from the battery is used by the battery converter and motor drive to power the motor with a positive torque command.



## Buck and boost mode of operation for the battery DC-DC converter

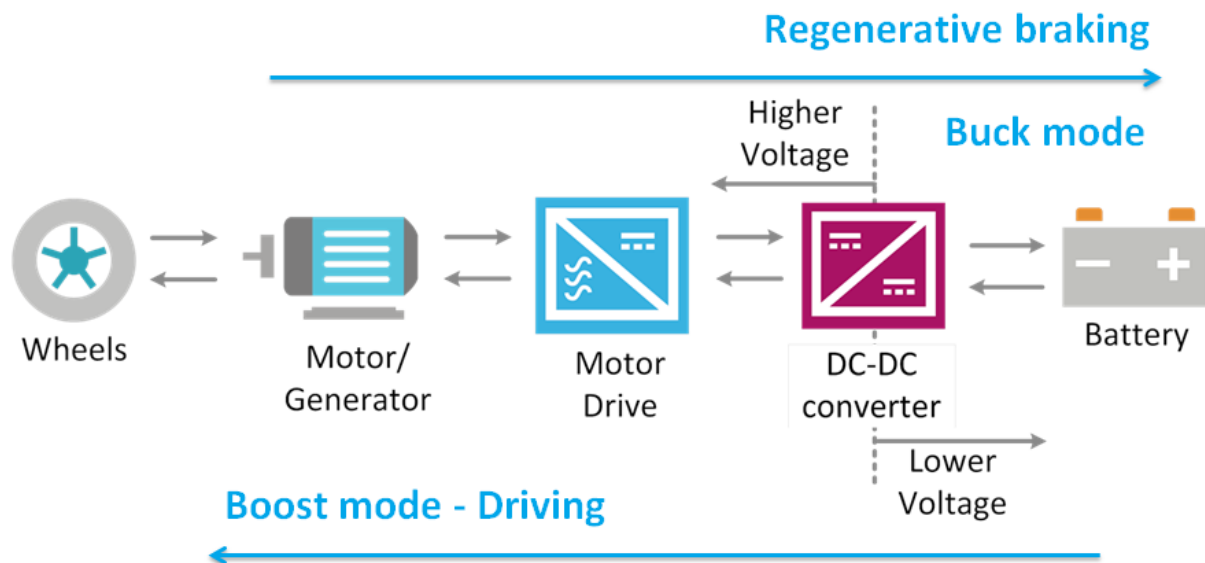


Figure 1

The most common power processing converter used for the battery converter of BEV is a buck and boost converter, shown in Figure 2. When recovering the kinetic energy from the vehicle, the device operates in buck mode, where the voltage level is decreased to a level that is within the safe voltage range of the battery as shown in Figure 1. When propelling the vehicle, the device operates in boost mode and the DC voltage is regulated to output a higher voltage level for the electric motor drive and motor. As already concluded, the DC-DC battery converter should work in two quadrants as a class C converter and the current must be able to reverse.



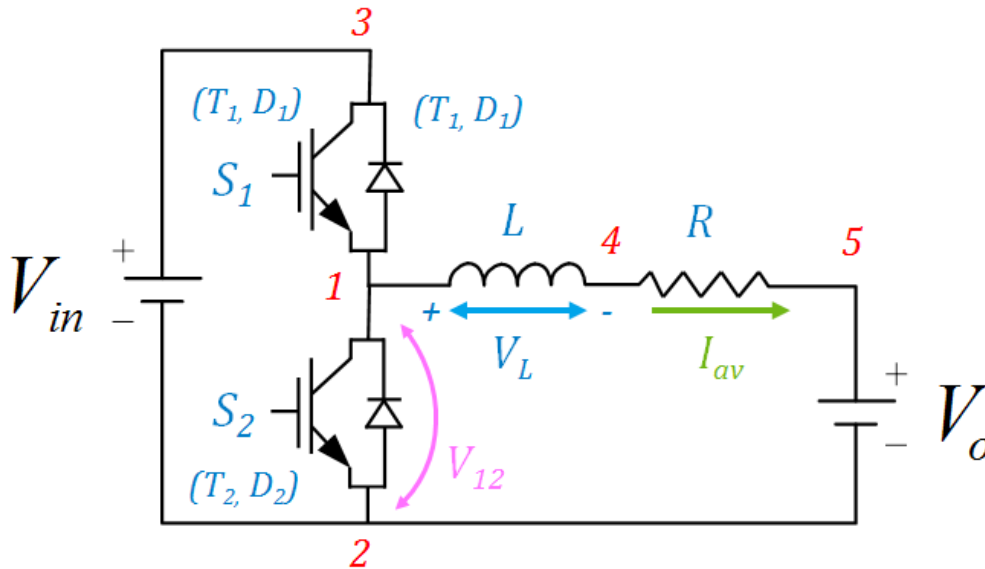


Figure 2

### Semiconductor switches

That is why the switches  $S_1$  and  $S_2$  must allow the bidirectional flow of current through them. But electronic switches (like the IGBT  $T_1$  and  $T_2$  shown in Figure 2) can inherently carry current in only one direction. Therefore, in order to get bidirectionality, diodes  $D_1$  and  $D_2$  have to be placed in antiparallel with the respective semiconductor switches in  $S_1$  and  $S_2$ . The switch contacts are shown with an arrowhead to indicate the allowed direction of current flow. For example, when current flows into terminal 1, it can continue on to terminal 2 either by way of diode  $D_1$  and source  $V_1$  or by way of  $T_2$ , provided  $T_2$  is closed. Similarly if current flows out of terminal 1, it can take the path through diode  $D_2$  or the path through  $T_1$  and  $V_1$ , provided that  $T_1$  is closed.



### Operation of buck and boost converter

Consider the buck and boost converter topology shown in the Figure 2 in which two switches  $S_1$  to  $S_2$  are connected across a dc voltage source  $V_{in}$ . The switches open and close alternately in such a way that when  $S_1$  is closed,  $S_2$  is open and vice versa. The time of one cycle is  $T$ , and  $S_1$  is closed for a period  $T_{on}$ . It follows that the duty cycle of  $S_1$  and  $S_2$  namely  $D_{S1}$  and  $D_{S2}$  can be given by

$$D_{S1} = T_{on}/T$$

$$D_{S2} = (1-D_{S1})$$

When  $S_1$  is closed, terminal 1 is at the level of point 3 and so the output voltage is  $V_{12} = V_{in}$  for a period  $T_{on}$  as shown in Figure 3. Then, when  $S_1$  is open,  $S_2$  is closed and so  $V_{12} = 0$  for a period  $T_{off}$ . The output voltage oscillates, therefore, between  $V_{in}$  and zero (Figure 3) and its average DC value  $V_{12(avg)}$  is given by

$$V_{12(avg)} = D_{S1} V_{in}$$

By varying  $D_{S1}$  from zero to 1, we can vary the magnitude of  $V_{12(avg)}$  from zero to  $V_{in}$ .



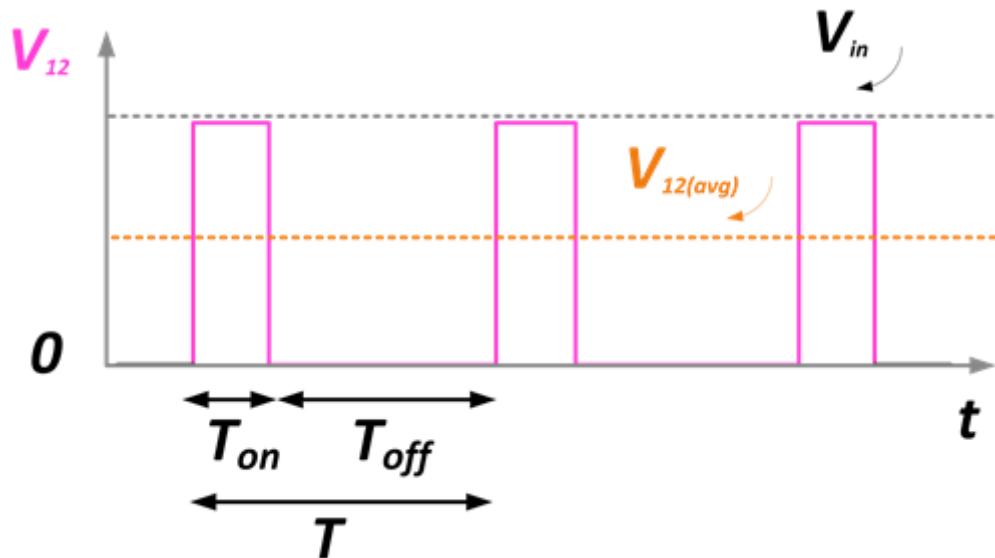


Figure 3

It is apparent that the circuit on the left-hand side of terminals 1, 2 is never open. For example, if current  $I_{av}$  happens to flow into terminal 1, it can find its way back to terminal 2 either via  $S_2$  (if  $S_2$  is closed) or via  $S_1$  and source  $V_{in}$  if  $S_2$  is open. Because one of the switches is always closed, it is evident that current  $I_{av}$  can always circulate, no matter what its direction happens to be. This is a crucially important feature of the converter. It is called a two-quadrant converter because current  $I_{av}$  can flow in either direction, but the polarity of the DC voltage  $V_{in}$  and hence the polarity of  $V_{12}$  remains fixed: Terminal 1 is always positive (+) with respect to terminal 2.

Suppose we want to transfer the power from terminals  $V_{12}$  to a load (in our case battery), whose DC voltage has a value  $V_0$  (Figure 2). Knowing that  $V_{12}$  is fluctuating while  $V_2$  is constant, it is essential to place a buffer between the two, otherwise



it will result in short-circuit currents. We could place a resistor between points 1 and 5, but that would involve  $I^2R$  losses which would reduce the efficiency of the converter. The best solution is to use an inductance  $L$  as shown in Figure 2. It has the advantage of opposing AC current flow while offering no opposition to DC. We assume that the load has a small internal resistance  $R$ . In reality there is a cable between the converter and battery, which also acts provides some resistance.

### Buck operation

Suppose that both the voltage source  $V_{in}$  and the duty cycle  $D_{S1}$  are fixed.

Consequently, the DC component  $V_{12(avg)}$  between points 1 and 2 is constant. If  $V_0$  is exactly equal to  $V_{12(avg)}$ , no DC current will flow and no DC power exchange will take place. At that point,

$$V_{12(avg)} = D_{S1} V_{in} = V_0$$

For no power flow,

$$D_{S1} = V_0 / V_{in}$$

But if  $V_0$  is less than  $V_{12(avg)}$ , a DC current  $I_{av}$  will flow from terminal 1 into battery of voltage  $V_0$  in Figure 2. Its magnitude is given by

$$I_{av} = (V_{12(avg)} - V_0) / R$$

$$P_0 = I_{av} V_0$$



Path of current during ON time of  $S_1$ :  $V_{in}, T_1, L, R, V_o$

Path of current during OFF time of  $S_1$ :  $D_2, L, R, V_o$

Power  $P_o$  equal to  $V_{12(avg)} I_{av}$  will, therefore, flow from terminals 1 toward the battery. This DC power can only come from the higher voltage source  $V_{in}$ . In this mode of operation, with  $V_o$  less than  $V_{12(avg)}$ , the converter acts like the step-down (buck) chopper.

### Boost operation

On the other hand, if  $V_o$  is greater than  $V_{12(avg)}$ , a DC current  $I_{av}$  will flow out of terminal 5 and into terminal 1 in Figure 2. Its magnitude is

$$I_{av} = (V_o - V_{12(avg)})/R$$

Path of current during ON time of  $S_2$ :  $V_o, R, L, T_2$

Path of current during OFF time of  $S_2$ :  $V_o, R, L, D_1, V_{in}$

Power now flows from the low-voltage battery side  $V_o$  to the higher voltage side  $V_{12(avg)}$  and subsequently to  $V_{in}$ . In this mode of operation, with  $V_o$  greater than  $V_{12(avg)}$ , the converter acts like a step-up (boost) chopper.

### Ripple in the inductor

While a perfect DC current is required for charging or discharging the battery, this is not the case in reality. This is because a current ripple  $\Delta I$  is present in the inductor current due to the energy storage in the inductor, as shown in Figure 4.





To determine the peak-to-peak ripple  $\Delta I$ , let us examine the situation when  $S_1$  is closed and  $S_2$  is open for the buck mode of operation (Figure 2). Assuming the current  $I_L$  is momentarily equal to its DC value of  $I_{av}$ , the voltage  $V_L$  across the inductor can be written as :

$$V_{L(on)} = V_{in} - V_o - I_{av}R$$

where  $I_{av}R$  is the voltage drop across the resistor. Since,  $V_{in} > V_o$ ,  $V_{L(on)}$  is positive and the voltage polarity across the inductor is as shown in Figure 2. Knowing that  $I_L$  is flowing into terminal 1 to terminal 4 and that terminal 1 is (+) with respect to terminal 4, it follows that  $I_L$  must be increasing. This is because the current through the inductor increases when the voltage across it is positive. The inductor accumulates volt-seconds and during the  $T_{on}$  that  $S_1$  is closed, the magnetic "charge" totals  $V_{L(on)}T_{on}$ . Therefore the current increases by an amount,

$$\Delta I = V_{L(on)}T_{on}/L$$

When  $S_1$  is open and  $S_2$  is closed, then the voltage across the inductor is negative (shown by the minus sign in the formula below) and the inductor current reduces,

$$V_{L(off)} = -V_o - I_{av}R$$

$$\Delta I = V_{L(off)}T_{off}/L$$

In steady state, the rise in inductor current in the ON state of  $S_1$  must be balanced



by the fall in inductor current during the off state of  $S_1$ . Hence, the actual inductor current  $I_L$  varies from  $(I_{av} - \Delta I/2)$  to  $(I_{av} + \Delta I/2)$  as shown in Figure 4 with an average value of  $I_{av}$ . In the ideal case,  $\Delta I = 0$  and this requires a large size of inductor as shown by the formula,  $\Delta I = V_{L(on)} T_{on} / L$ .

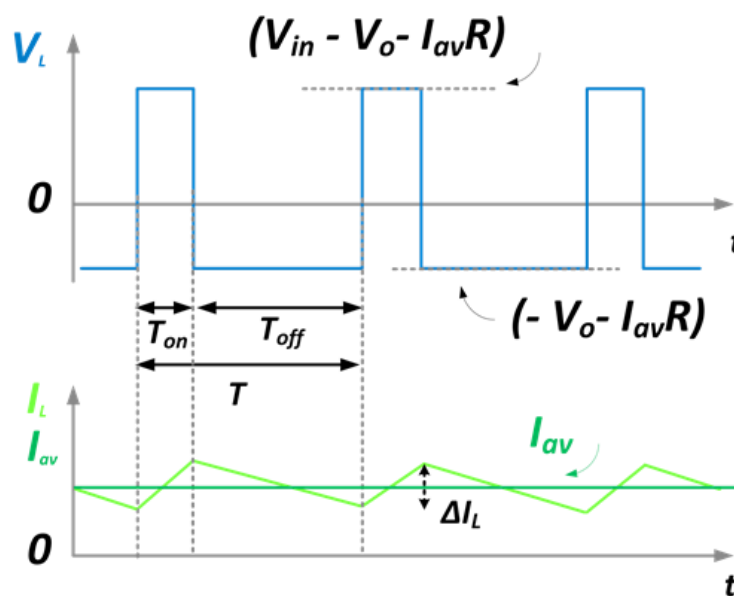


Figure 4: Buck mode of operation, where  $I_{av}$  is positive

## Overview of buck and boost mode

The table on the next page shows how the operation mode of the converter changes based on the duty cycle of  $S_1$ . The switching system of the buck and boost converter is therefore able to transfer DC power in both directions—from the high-voltage side  $V_{in}$  to the low voltage side  $V_o$  or vice versa. Again, because the current can reverse while the polarity of  $V_{12(avg)}$  remains the same, this buck/boost converter operates in two quadrants.



Mode	Duty cycle of $S_1$
No power flow	$D_{S1} = V_o/V_{in}$
Buck operation	$D_{S1} > V_o/V_{in}$
Boost operation	$D_{S1} < V_o/V_{in}$

To summarize the equations:

$$D_{S1} = T_{on}/T$$

$$T = T_{on} + T_{off}$$

$$D_{S2} = (1 - D_{S1})$$

$$T = 1/f$$

$$V_{12(avg)} = D_{S1} V_{in}$$

$$I_{av} = (V_{12(avg)} - V_o) / R$$

$$P_o = I_{av} V_o$$

$$\Delta I = V_{L(on)} T_{on} / L$$

$$V_{L(off)} = -V_o - I_{av} R$$

$$\Delta I = V_{L(off)} T_{off} / L$$

where

$V_o$  is the output voltage

$V_{in}$  is the input voltage

$D_{S1}$  is the duty cycle of the switch  $S_1$

$D_{S2}$  is the duty cycle of the switch  $S_2$

$f$  is the switching frequency of the semiconductor switch

$T$  is the time period of the semiconductor switch

$T_{on}$  is the ON time of the semiconductor switch



This course material is licensed under a Creative Commons Attribution-NonCommercial-ShareAlike 4.0 License.

$T_{off}$  is the OFF time of the semiconductor switch

$V_{12(avg)}$  is the average voltage across the switch  $S_2$

$I_{av}$  is the average current through the inductor, sign of  $I_{av}$  determines direction of power flow

$R$  is the resistance of the inductor

$P_o$  is the power delivered to the output voltage  $V_o$

## Electromagnetic compatibility (EMC)

Electromagnetic compatibility (EMC) defines an electrical systems' ability to remain neutral in the vicinity of other systems. In automotive systems, all electrical equipment must be able to function in close proximity to each other without producing emissions that directly or indirectly degrade the performance of other equipment. Modern vehicles have numerous electronic systems, including electronic ignition, electronic fuel injection, ABS, airbags, radio, car phone and navigation systems. The introduction of high voltage electric machines and high frequency switching controllers will raise further EMC problems for vehicle manufacturers.



This course material is licensed under a Creative Commons Attribution-NonCommercial-ShareAlike 4.0 License.